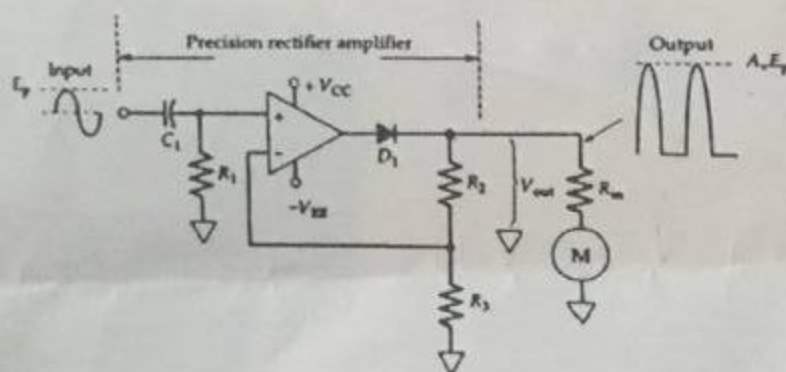





Course:	Instrumentation & Measurements	Course Code:	EE220
Program:	BS (Electrical Engineering)	Semester:	Fall 2017
Duration:	60 Minutes	Total Marks:	30
Paper Date:	4-Nov-17	Weight	15%
Section:	EE	Page(s):	1
Exam:	Midterm-2	Roll No:	L14-4435

Instruction/Notes: Solve All Questions

- Q.1a** A 6-bit R-2R DAC has $R_F = R = 4 \text{ k}\Omega$ and $V_{ref} = 8 \text{ V}$. Determine the lowest current level in the circuit, and calculate the output voltage for MSB. Assume ideal OpAmp. [5]
- Q.1b** A 64 mV level is to be converted into an 10-bit code. Calculate the resolution of the conversion, and analog levels represented by the MSB and LSB, and determine the analog level represented by 111111110. [5]
- Q.2a** The ac electronic voltmeter as shown in the following circuit uses the following components: $R_1 = 22 \text{ k}\Omega$, $R_2 = 2.25 \text{ k}\Omega$, $R_3 = 6.8 \text{ k}\Omega$, and $R_S + R_m = 1 \text{ k}\Omega$. The meter gives FSD for 300 μA . Calculate the rms input voltage for meter FSD and for 0.5 FSD. [5]



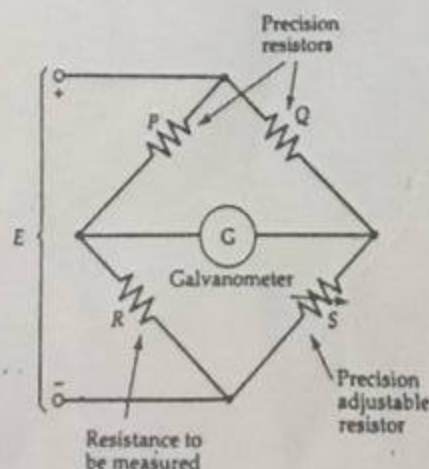- Q.2b** A frequency meter measuring the ratio of two frequencies display 1212 when the pulses of the unknown frequency (f_2) are counted over 1000 cycles of the known frequency (f_1). If f_1 is 33.35 kHz, determine f_2 . [5]
- Q.3a** A Wheatstone bridge as shown below has $P = 1 \text{ k}\Omega$, $Q = (100 \Omega, 1 \text{ k}\Omega, \text{ or } 100 \text{ k}\Omega)$, and S is adjustable from 1 k Ω to 5 k Ω . Determine the range of resistance that can be measured. [5]



- 3b** When a 10 kV supply is used for measuring insulation resistance of a metal-sheathed electrical cable, the measured current is 4.3 μA without the use of the guard wire. When a guard wire is used, the current is 3.3 μA . Calculate the combined volume and surface leakage resistance of the cable. Also, determine the separate volume and surface leakage resistances. [5]

National University of Computer and Emerging Sciences, Lahore Campus




Course:	Instrumentation & Measurements	Course Code:	EE220
Program:	BS (Electrical Engineering)	Semester:	Spring 2018
Duration:	3 Hours	Total Marks:	100
Paper Date:	21-May-2018	Weight	50%
Section:	EE	Page(s):	2
Exam:	Final	Roll No:	


Instruction/Notes: Solve All Questions

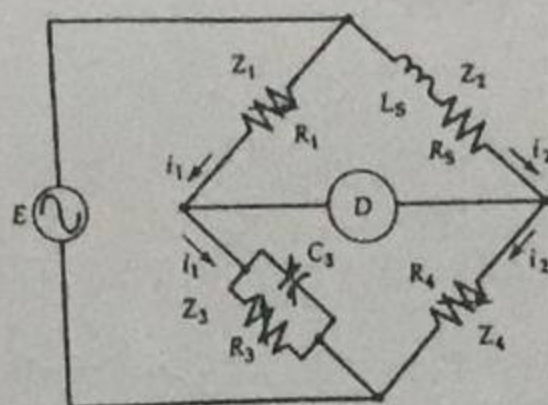- Q.1a A 300 Ω , 75 cm length of nickel wire which is bounded to a steel girder has its resistance change by 0.9 Ω when the girder is under compression. If the wire has a gauge factor of 3, calculate the change in the wire length. [CLO 6] [10]
- Q.1b When its total air gap is 0.33 mm, a variable reluctance transducer has 0.35 mH inductance. The inductance decreases to 0.3 mH when the target is moved further from the core. Calculate the target movement. [CLO 6] [10]
- Q.2a The distance between plates of a capacitive transducer increases from 0.59 mm to 0.82 mm. Determine the corresponding percentage change in capacitance.

$$C - \Delta C = \frac{\epsilon_0 \epsilon_r A}{d + \Delta d}$$
 [CLO 6] [10]
- Q.2b A resistance thermometer has a 100 Ω resistance and a temperature coefficient of 0.0037 at 20 $^{\circ}\text{C}$. Calculate its resistance at 75 $^{\circ}\text{C}$, and determine the temperature when its resistance is 150 Ω . [CLO 6] [10]
- Q.3a A Maxwell bridge with a 10 kHz supply frequency uses a 0.1 μF capacitor for C_3 and a 100 Ω standard resistor for R_1 . Resistors R_3 and R_4 can be adjusted from 100 Ω to 1 k Ω . Calculate the range of inductances and Q factors that can be measured on the bridge. [PLO 1][CLO 5] [10]



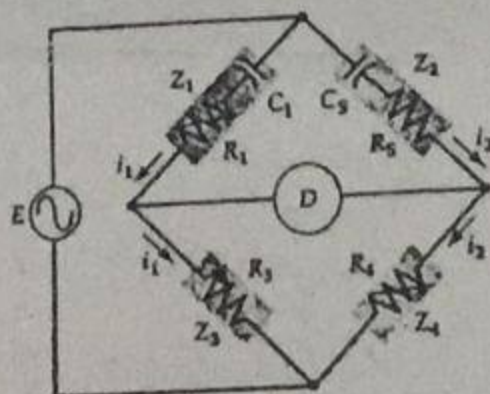- Q.3b When investigating an unknown capacitor, a series RC bridge as shown below has the following components at balance: $C_1 = 0.5 \mu\text{F}$, $R_1 = 5.5 \Omega$, $R_3 = 1.25 \text{ k}\Omega$, and $R_4 = 2.7 \text{ k}\Omega$. If a 3.9 Ω resistor is included in series with C_s , determine the capacitance C_s and series-resistive component of C_s . [PLO 1][CLO 5] [10]





Course:
Program:
Duration:
Paper Date:
Section:
Exam:

Instrumentation & Measurements
BS (Electrical Engineering)
60 Minutes
20-Sep-17
EE
Midterm-1

Course Code:
Semester:
Total Marks:
Weight
Page(s):
Roll No:


EE 220
Fall 2017
30
15%
1

Instruction/Notes:

Solve All Questions. Attempt all parts of a question together.


L-14-4435

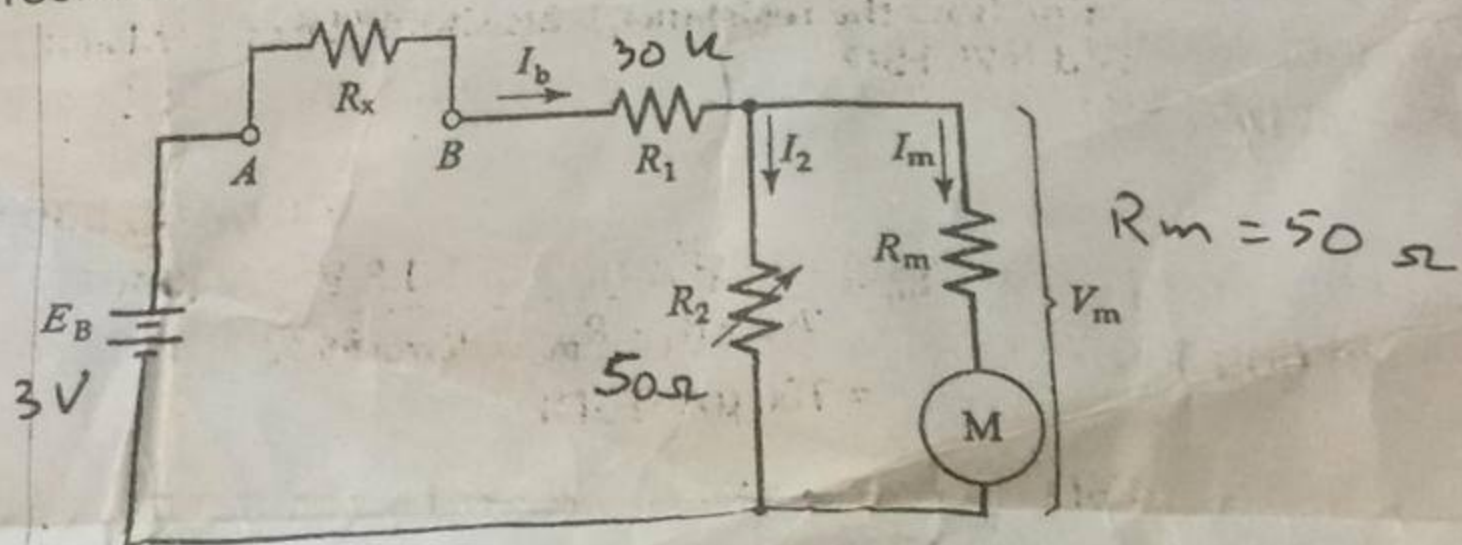- Q.1 a. Two series connected resistors are specified as $R_1 = 1.8 \text{ k}\Omega \pm 5\%$ and $R_2 = 4.7 \text{ k}\Omega \pm 10\%$ at 25°C . If each has a $200 \text{ ppm}/^\circ\text{C}$ temperature coefficient, calculate the maximum and minimum resistance of the two at 60°C . [5]
- b. A $10 \text{ k}\Omega$ potentiometer with a 20Ω resolution is used as a voltage divider. If the potentiometer supply is 12 V , determine the precision of the output voltage. [5]
- Q.2 a. An ohmmeter is made up of the following components: supply voltage $E_B = 3 \text{ V}$, series resistor $R_1 = 30 \text{ k}\Omega$, meter shunt resistor $R_2 = 50 \Omega$, and meter resistance $R_m = 50 \Omega$. Determine the resistance measured at 0.25, 0.5, and 0.75 FSD. [5]



- b. A PMMC instrument with a 750Ω coil resistance gives FSD with a $500 \mu\text{A}$ coil current. Determine the required shunt resistance to convert the instrument into a dc ammeter with an FSD of (a) 50 mA and (b) 30 mA . [5]

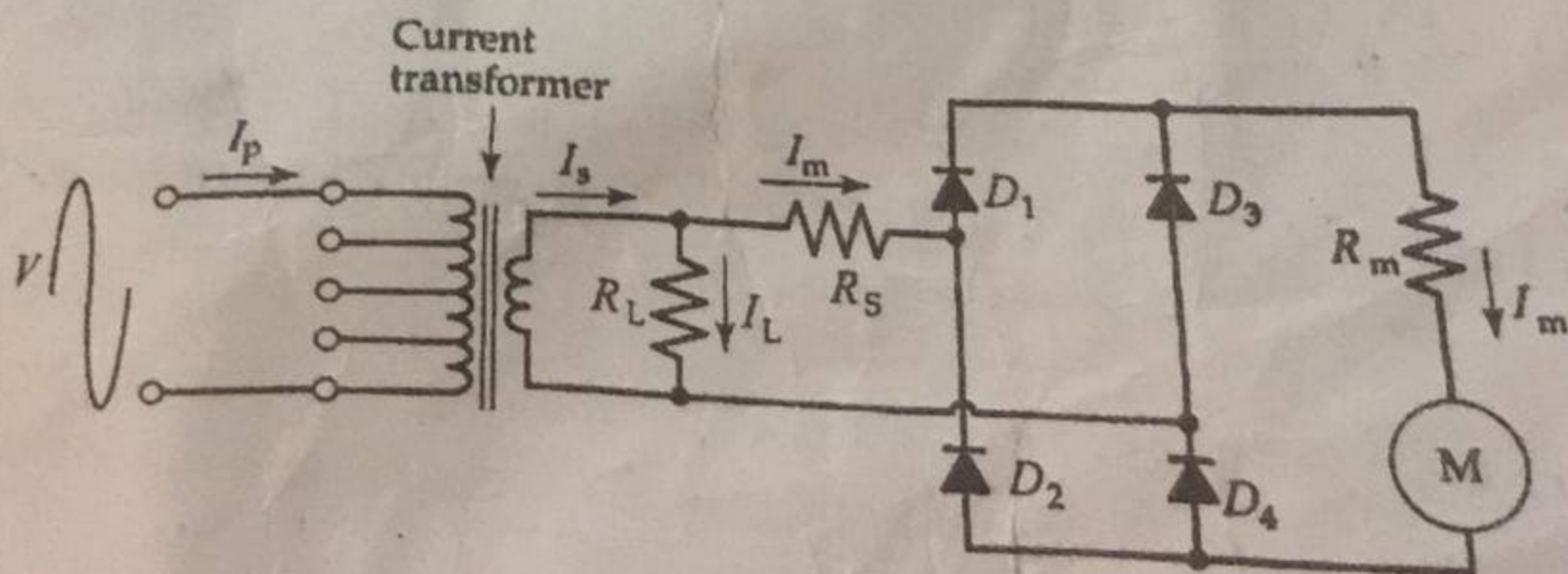- Q.3 A rectifier ammeter is to indicate full scale for a 1 A rms current. The PMMC instrument used has $500 \mu\text{A}$ FSD and a 1200Ω coil resistance. The current transformer turns ratio is $N_s = 7000$ and $N_p = 10$. Silicon diodes are used and the meter series resistance is $R_s \text{ k}\Omega$. Determine the required secondary shunt resistance value R_L .



National University of Computer and Emerging Sciences, Lahore Campus




Course: Instrumentation & Measurements
Program: BS (Electrical Engineering)
Duration: 60 Minutes
Paper Date: 4-Nov-17
Section: EE
Exam: Midterm-2

Course Code: EE220
Semester: Fall 2017
Total Marks: 30
Weight: 15%
Page(s): 1
Roll No:


414-4435

Instruction/Notes: Solve All Questions

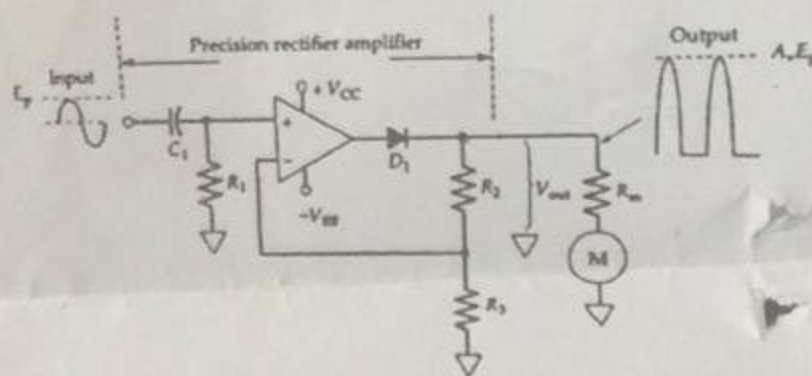- Q.1a** A 6-bit R-2R DAC has $R_F = R = 4 \text{ k}\Omega$ and $V_{\text{ref}} = 8 \text{ V}$. Determine the lowest current level in the circuit, and calculate the output voltage for MSB. Assume ideal OpAmp. [5]
- Q.1b** A 64 mV level is to be converted into an 10-bit code. Calculate the resolution of the conversion, and analog levels represented by the MSB and LSB, and determine the analog level represented by 111111110. [5]
- Q.2a** The ac electronic voltmeter as shown in the following circuit uses the following components: $R_1 = 22 \text{ k}\Omega$, $R_2 = 2.25 \text{ k}\Omega$, $R_3 = 6.8 \text{ k}\Omega$, and $R_S + R_m = 1 \text{ k}\Omega$. The meter gives FSD for 300 μA . Calculate the rms input voltage for meter FSD and for 0.5 FSD. [5]



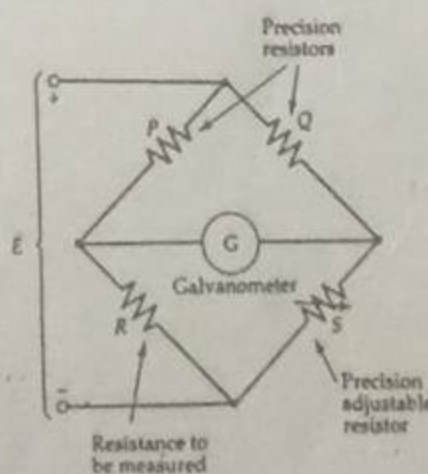- Q.2b** A frequency meter measuring the ratio of two frequencies display 1212 when the pulses of the unknown frequency (f_2) are counted over 1000 cycles of the known frequency (f_1). If f_1 is 33.35 kHz, determine f_2 . [5]
- Q.3a** A Wheatstone bridge as shown below has $P = 1 \text{ k}\Omega$, $Q = (100 \Omega, 1 \text{ k}\Omega, \text{ or } 100 \text{ k}\Omega)$, and S is adjustable from 1 k Ω to 5 k Ω . Determine the range of resistance that can be measured. [5]



- Q.3b** When a 10 kV supply is used for measuring insulation resistance of a metal-sheathed electrical cable, the measured current is 4.3 μA without the use of the guard wire. When a guard wire is used, the current is 3.3 μA . Calculate the combined volume and surface leakage resistance of the cable. Also, determine the separate volume and surface leakage resistances. [5]

National University of Computer and Emerging Sciences, Lahore Campus
 Quiz 1, Instrumentation & Measurements EE, Fall 2017, Sep 7, 2017
 Max Marks = 20, Time Allowed 15 minutes

Name: Hadia Hassan

Roll #: L14.4435

Q.1 Three resistors connected in series have the following values:
 (5.6 kΩ ± 5%), (8.2 kΩ ± 6%), (6.8 kΩ ± 5%).

Calculate the total resistance, the maximum absolute error, and the maximum relative error.

$$R_T = R_1 + R_2 + R_3 = (5.6 \text{ k}\Omega \pm 5\%) + (8.2 \text{ k}\Omega \pm 6\%) + (6.8 \text{ k}\Omega \pm 5\%)$$

$$R_1 = 5.6 \text{ k}\Omega \pm 0.28, R_2 = 8.2 \text{ k}\Omega \pm 0.492$$

$$R_3 = 6.8 \text{ k}\Omega \pm 0.34$$

$$R_T = (5.6 \text{ k}\Omega + 8.2 \text{ k}\Omega + 6.8 \text{ k}\Omega) \pm (0.28 + 0.492 + 0.34)$$

$$R_T = 20.6 \text{ k}\Omega \pm 1.112$$

$$R = 20.6 \pm (16\%)$$

Relative Resistance

$$R_1 = \frac{5.88}{5.6} \times 100 = 105\%, R_2 = \frac{8.692}{8.2} \times 100 = 106\%, R_3 = 105\%$$

$$\text{Relative Resistance} = 105\% + 106\% + 105\% = 316\%$$

Q.2 A dc ammeter is constructed of 5.01 Ω resistance in parallel with a PMMC instrument. If the instrument has a 2.0 kΩ coil resistance and 100 μA FSD, determined measured current at FSD.

$$R_m = 5.01 \Omega$$

$$V_m = I_m R_m$$

$$V_m = \frac{2 \text{ k}\Omega}{5.01} \times 100 \mu\text{A} = 0.501 \text{ mV}$$

$$I_m = 2000 \mu\text{A}$$

$$\text{Measured Current} = \frac{V_m}{R_m} - I$$

Q.1 A digital frequency meter displays a count of 156. The time base has a 2 MHz clock generator frequency-divided by four decade counters and one flip-flop. Calculate the gate time and the measured frequency. Determine the count that would be displayed if the flip-flop is removed from the time base.

Q.2 The LSB for an analog voltage converted in to a 16-bit digital code is $1 \mu\text{V}$. Calculate the analog equivalent for the MSB and for full scale.

$$V_m = \text{LSB} \times 2^n = 1 \text{ mV} \times 2^{16} = 0.0655 \text{ V}$$

$$\text{MSB} = \frac{V_m}{2} = \frac{0.0655}{2} = 0.03275 \text{ V}$$

$$\text{MSB} = 2^{n-1} \times \text{LSB} = 2^{15} \times 1 \text{ mV} = 0.0327 \text{ V}$$

$$V_{\text{FSR}} = V_m - \text{LSB} = 0.0655 - 1 \times 10^{-6} = 0.0654 \text{ V}$$

$V_{\text{MSB}} = 32.768 \text{ mV}$
 65.535 mV

Q.3 A frequency meter with an accuracy of $\pm 1 \text{ LSD} \pm (1 \times 10^{-5})$ is used to measure frequencies of 30 Hz, 30 MHz, and 300 MHz. Calculate percentage error in each measurement.


$$31 + 1 \times 10^{-5} = 31.00001$$

$$31 - 1 \times 10^{-5} = 30.99999$$

$$\Delta f = 31.00001 - 30.99999 = 2 \times 10^{-5}$$

$$= \frac{\Delta f \times 30}{100} = 6 \times 10^{-4}$$

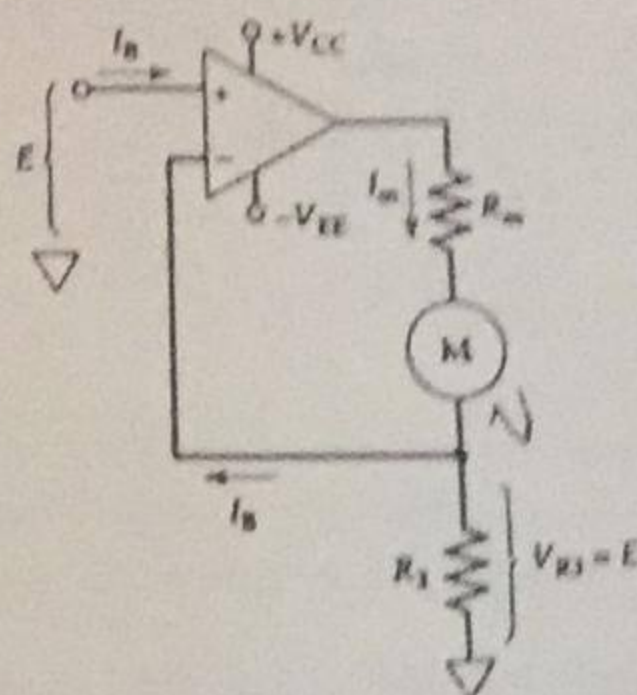- Q.4a The following voltage-to-current converter circuit uses $37.5 \mu\text{A}$ (FSD) deflection meter with $R_m = 900 \Omega$. If $R_3 = 80 \text{ k}\Omega$, determine the input voltage level to give FSD and 0.5 FSD. [PLO 1] [CLO 3] [10]




Handwritten notes for Q.4a:

$$I_m = I_B + I_{R_3}$$

$$I_m = I_B + \frac{V_{R_3}}{R_3} = I_B + \frac{E}{80 \text{ k}\Omega}$$

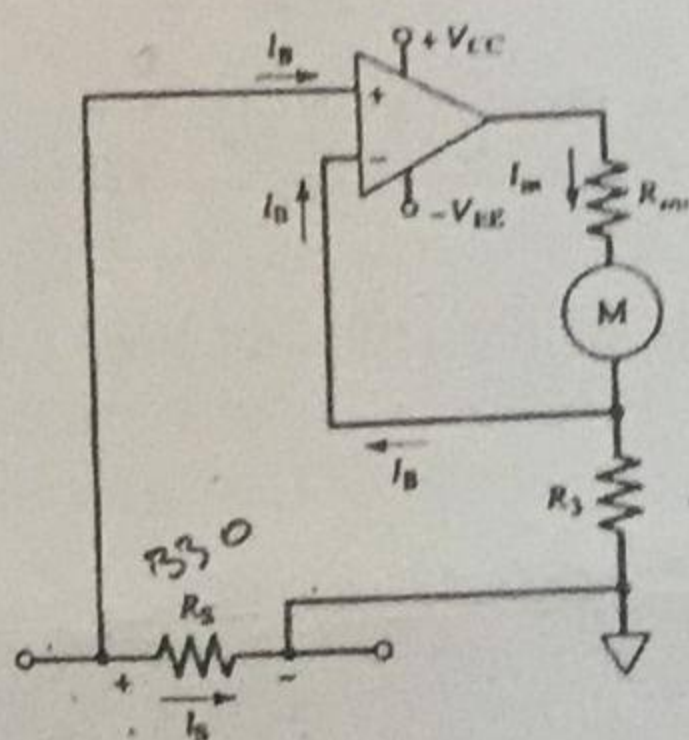- Q.4b A $200 \mu\text{A}$ current is to be measured by the type of the circuit shown below. The shunt resistor is 330Ω , and 1 mA (FSD) PMMC meter with 900Ω coil resistance is to be used. Determine a suitable resistance for R_3 to give FSD on the meter and calculate the maximum output voltage of the operational amplifier. [PLO 1] [CLO 3] [10]



Handwritten notes for Q.4b:

$$\frac{V_m - V_{R_3}}{R_3} = I_{R_3}$$

$$V_m = I_{R_3} R_3$$

$$V_m = I R$$

- Q.5a A dc ammeter is constructed of a 133.3Ω resistance in parallel with a PMMC instrument. If the instrument has a $1.2 \text{ k}\Omega$ coil resistance and $30 \mu\text{A}$ FSD, determine the measured current at FSD, 0.5 FSD, and 0.33 FSD. [CLO 2] [10]
- Q.5b Two resistors $R_1 = 70 \text{ k}\Omega$ and $R_2 = 50 \text{ k}\Omega$, are connected in series across a 12 V supply. A voltmeter on a 5 V range is connected to measure the voltage across R_2 . Calculate V_{R_2} (a) with the voltmeter disconnected, (b) with a voltmeter having a sensitivity of $20 \text{ k}\Omega/\text{V}$, and (c) with a voltmeter that has a sensitivity of $200 \text{ k}\Omega/\text{V}$. [CLO 2] [10]

Handwritten notes for Q.5b:

$$12 \text{ V} \times 20 \text{ k}\Omega$$