



Experiment #09

Owais Rao

22L-7638



BEE-3A2

Exercise 01:

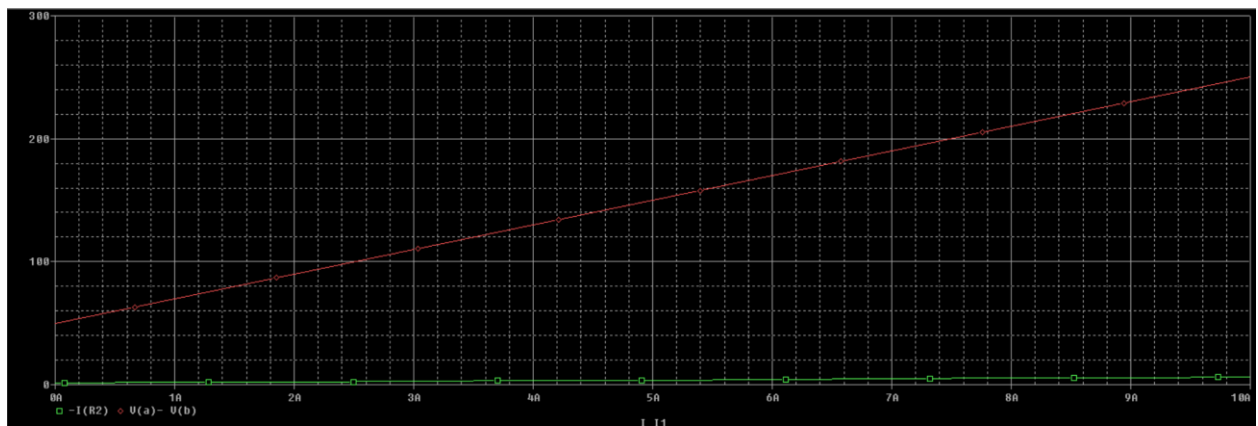
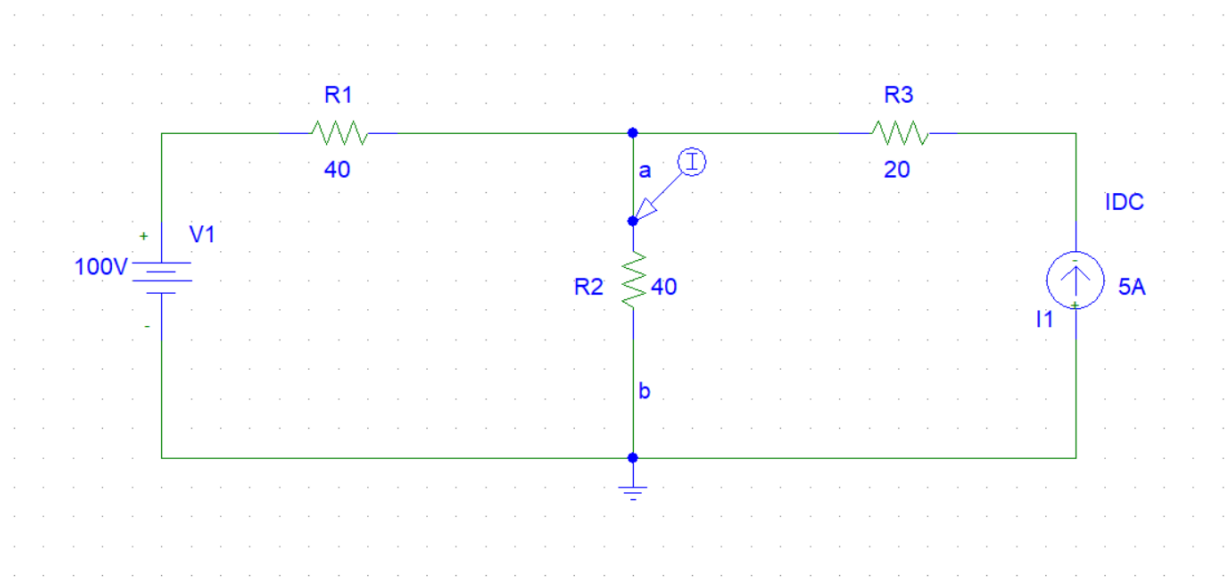


Exercise 02:


Capacitor:-

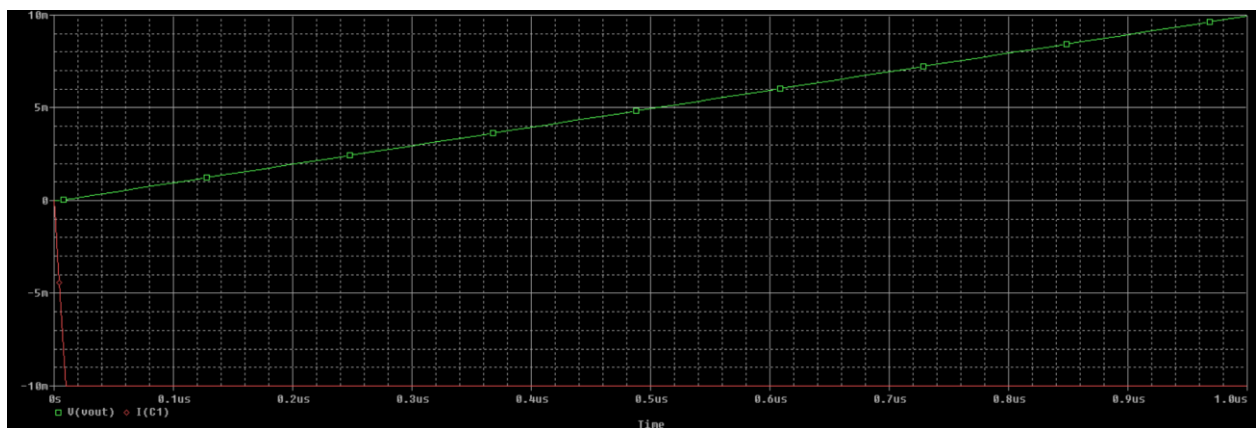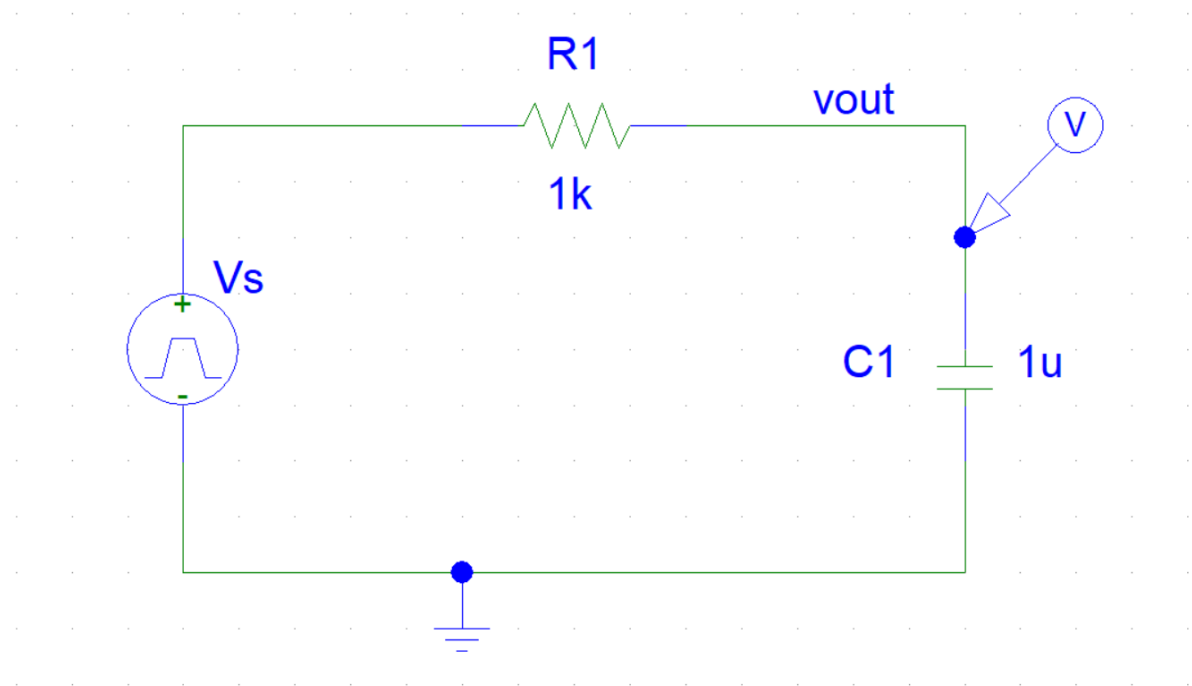

Inductor:-

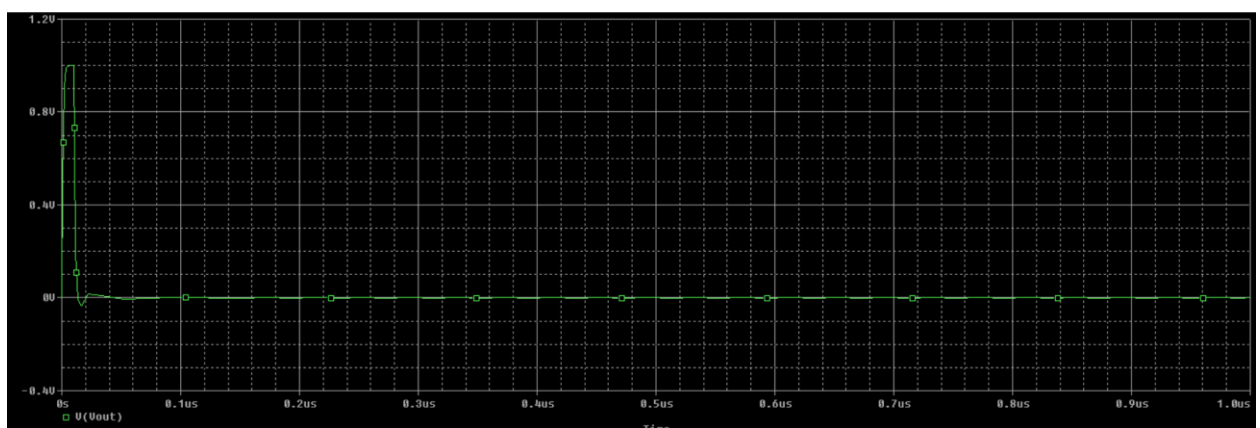
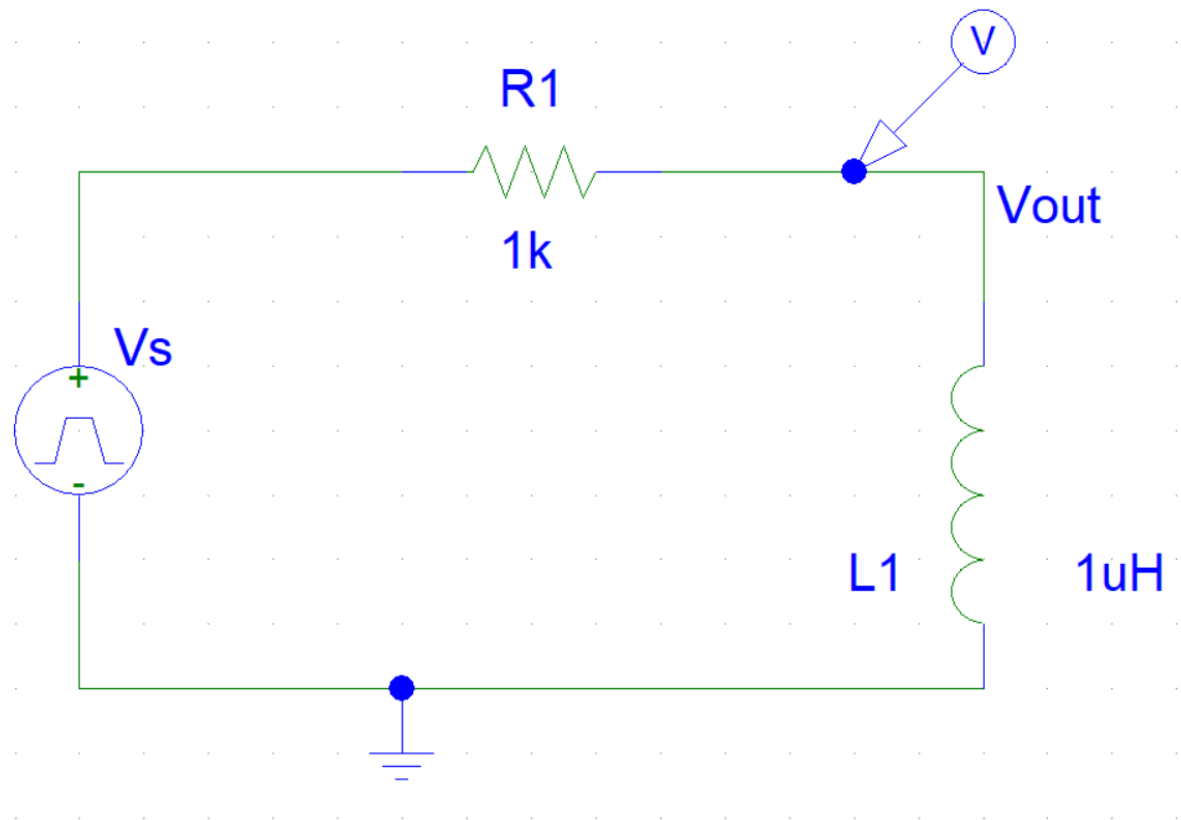


Exercise 03:

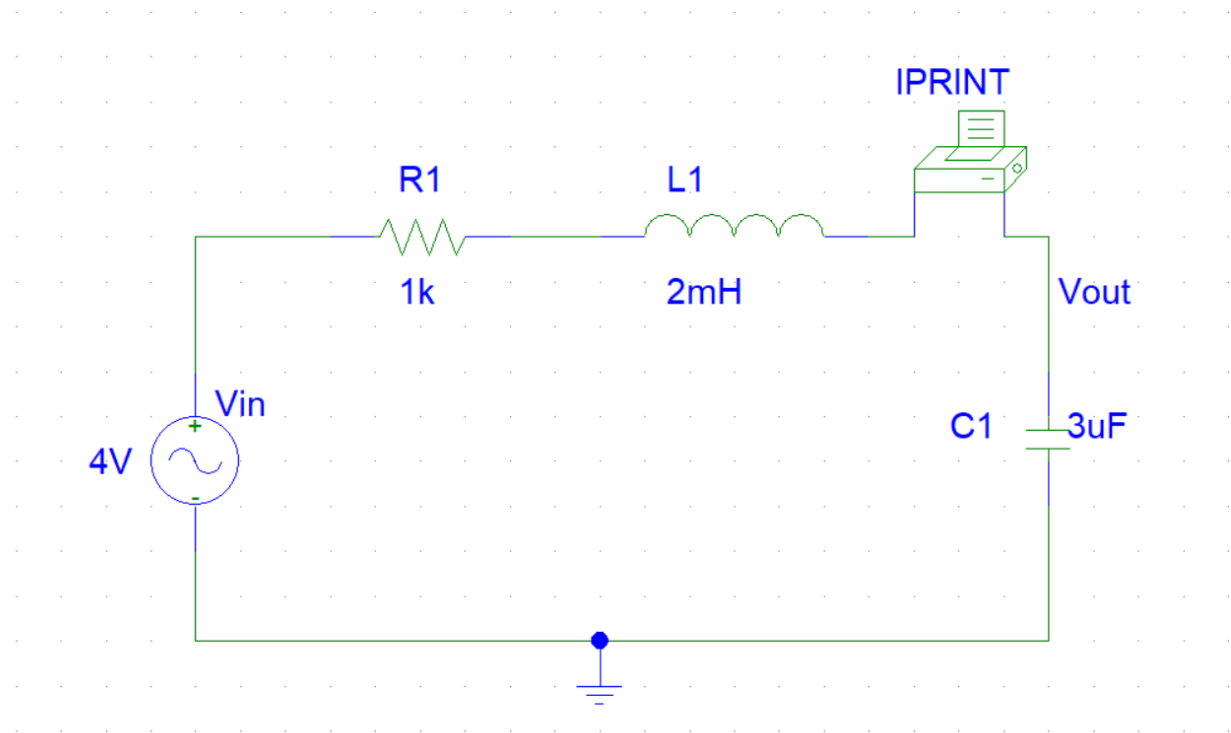

FREQ	IM(V_PRINT4)	IP(V_PRINT4)
5.000E+01	2.744E-03	4.668E+01

Exercise 04:

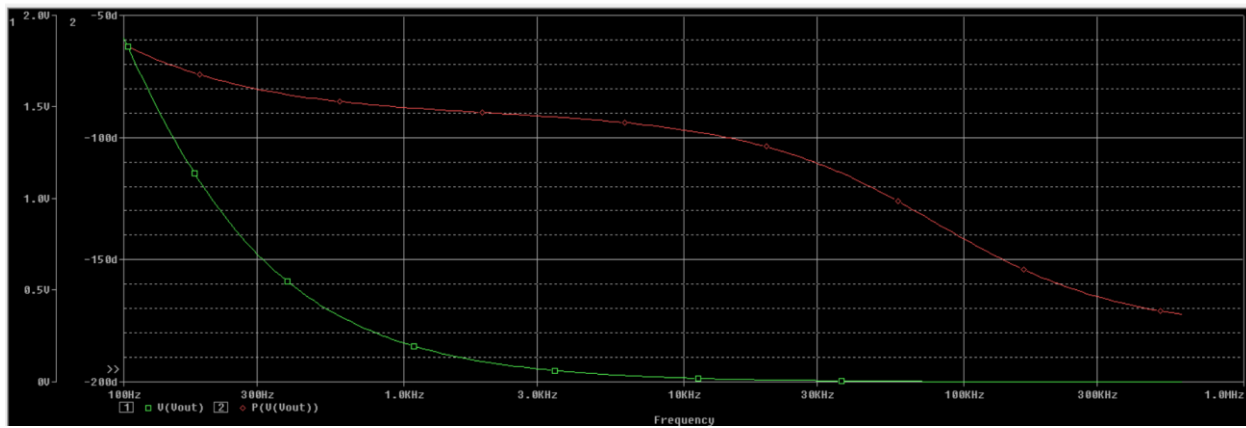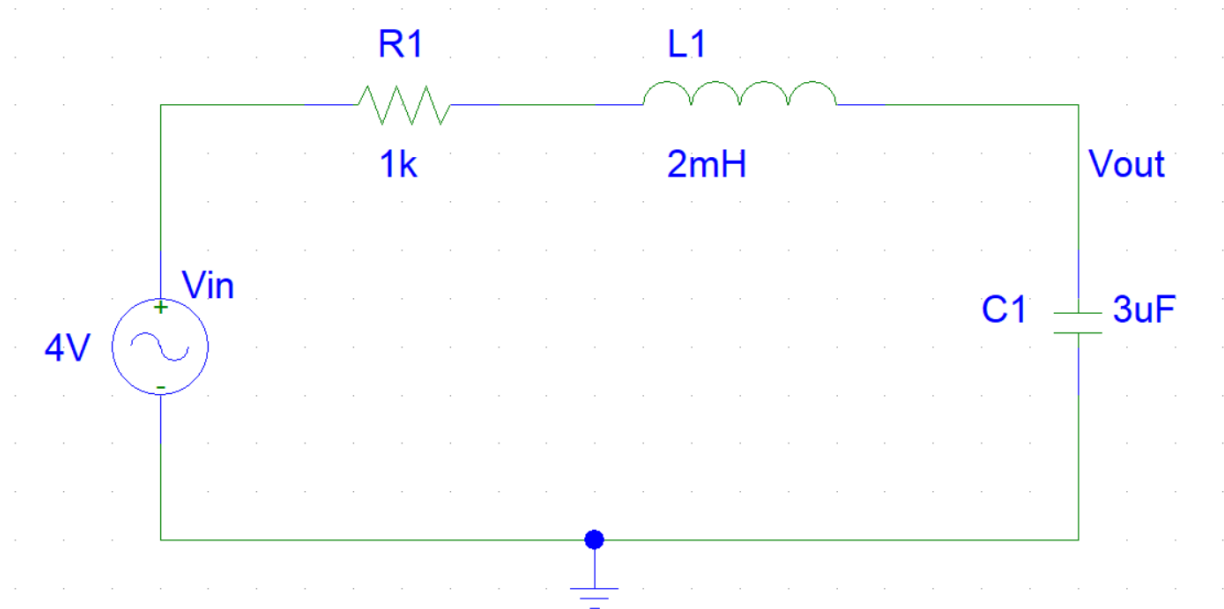

Post Lab:

