

Electronic Circuit Design (EE2001)

Sessional-II Exam

Date: November 5th 2024

Course Instructor

Dr. Omer Saleem

Total Time (Hrs): 1

Total Marks: 30

Total Questions: 3

Roll No


Section

Student Signature

Do not write below this line

CLO # 3: Appraise the limitations of real op-amp circuits.

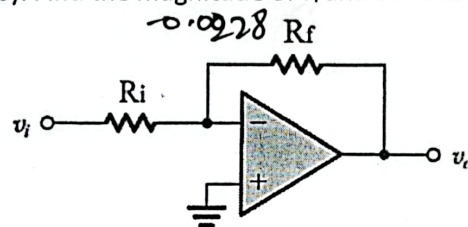
Q1: An imperfect op-amp is connected as shown below, with a $R_i = 100 \text{ k}\Omega$ and $R_f = 10.0 \text{ M}\Omega$. The output voltage is found to be $+9.35 \text{ V}$ when a non-zero DC input voltage v_i is applied, and $+7.10 \text{ V}$ when the input is grounded (i.e. $v_i = 0$). Find the magnitude of v_i and the offset voltage V_{offset} . [10 marks]



CLO # 4: Design wave-form generation circuits.

Q2: Refer to the following bistable multivibrator circuit. [10 marks]

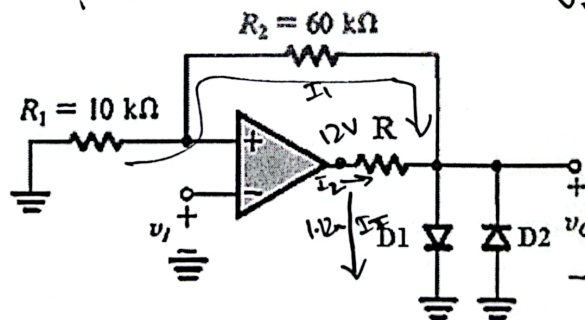- a) Sketch and label the transfer characteristics of v_o-v_i . The diodes are assumed to have a constant 0.7 V drop when conducting, and the immediate output of the op-amp saturates at $\pm 12 \text{ V}$.
- b) Find the value of R , such that the maximum diode current in $D1$ is 1.12 mA when the op-amp output is saturated at $+12 \text{ V}$.



$$I_T = I_1 + I_2$$

$$1.12 \text{ mA} = \frac{0 - V_o}{70 \text{ k}\Omega} + \frac{12 - V_o}{R}$$

$$1.12 \text{ mA} + \frac{V_o}{70 \text{ k}\Omega} = \frac{12 - V_o}{R}$$

$$R = \frac{12 - V_o}{1.12 \text{ mA} + \frac{V_o}{70 \text{ k}\Omega}}$$

$$= \frac{12 - 11.3}{1.12 \text{ mA} + \frac{11.3}{70 \text{ k}\Omega}}$$

CLO # 4: Design wave-form generation circuits.

Q3: Design a Wien-Bridge oscillator that generates a sine wave of frequency 9.95 kHz . [10 marks]

a) Draw the circuit schematic.

b) Find the values of all circuit components, using a minimum resistance of $150 \text{ k}\Omega$ in the circuit.

$$i = i_2 + i_1$$