

Date: 15/10

CHAPTER

SIGNAL GENERATOR

SINE WAVE GENERATOR (OSCILLATOR)

OSCILLATORS:


everything having oscillator bi-directional signal

Oscillators generate a finite output signal by using an amplifier followed by a "frequency selective circuit" connected in the feedback loop with NO input signal

freq. selective circuit
⇒ filter

NEGATIVE FEEDBACK LOOP

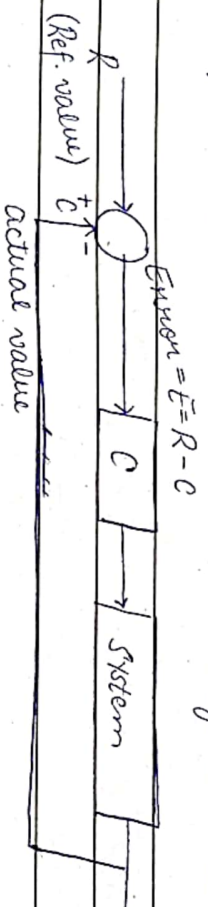(it is preferred because error converges to zero - stable system)



REF TEMP. (R)	ACTUAL TEMP. (C)	ERROR (E)
25	30	-5
25	27	-2
25	22	+3
25	26	-1
25	24.5	+0.5
25	25.2	-0.2
25	25	0
25	25	0



Date: 15/10




error converging to zero

POSITIVE FEEDBACK SYSTEM




REF. (R)	ACTUAL TEMP. (C)	ERROR (E=R+C)
25	30	+55
25	35	+60
		∞

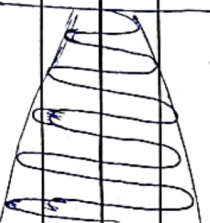

(exponentially increasing)
error diverging - unstable system

SINUSOIDAL OSCILLATOR:

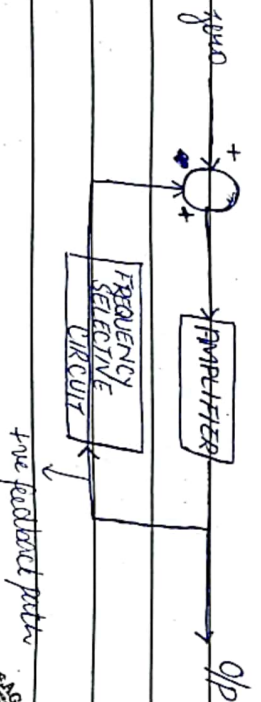

Date: _____

SUPPOSE:

$$N_i = x_s$$

x_s — maximum of infinite sinusoidal frequency.

$$M_f \sin(\omega t)$$

$$x_s = M_1 \sin(\omega t) + M_2 \sin(2\omega t) + M_3 \sin(3\omega t) + \dots + M_n \sin(n\omega t)$$

* magnitude of $M_1, M_2, M_3, \dots, M_n$ — is extremely small of the order 10^{-30}


amplifier's gain $-A$, freq. selective circuit $-\beta$

$$Q/P = \text{finite signal} = x_F$$

(Sum) $\rightarrow$ (amp) $\rightarrow$ (freq.)

$$I - x_s + 0 \rightarrow Ax_s \rightarrow Ax_F \beta$$
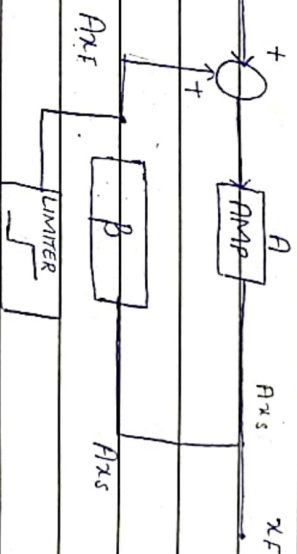
$$II - x_s + A\beta x_F \rightarrow Ax_s + A^2\beta x_F \rightarrow A^2\beta x_F$$




$$III - x_s + A^2\beta x_F \rightarrow Ax_s + A^3\beta x_F \rightarrow A^3\beta x_F$$

$$\therefore A = 10^5, \beta = 1$$

$$IV - x_s + A^3\beta x_F \rightarrow Ax_s + A^4\beta x_F \rightarrow A^4\beta x_F$$

$$A/\beta \cdot A^{n-1} \rightarrow Ax_s + A^n \beta x_F \rightarrow A^n \beta x_F$$


after limiter

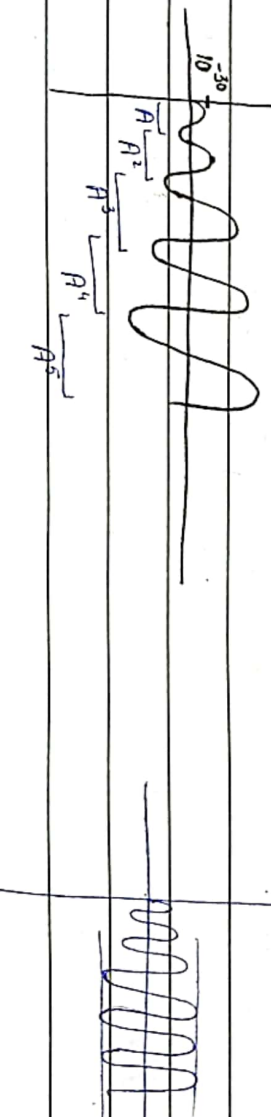

Date: _____

Thermal noise of the resistor is used

MATHEMATICALLY:

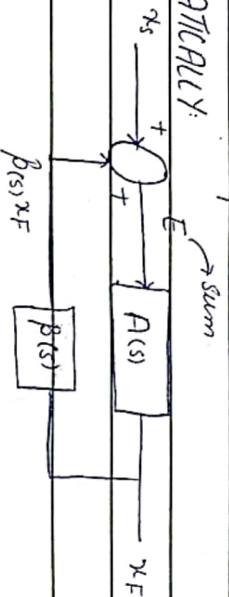

$$E = X_s + \beta(s) X_F \quad (i)$$

$$X_F = A(s) E \quad (ii)$$

Put (i) in (ii)

$$X_F = A(s) (X_s + \beta(s) X_F)$$

$$X_F \neq (1 - A(s)\beta(s)) X_F = A(s) \times X_s$$

$X_F = A(s)$	
X_s	$1 - A(s)\beta(s)$

When ~~at~~ NO I/P is connected

$$X_F = X_F \quad \div \infty$$

$$X_s = 0$$

$$A(s) = \infty$$

$$1 - A(s)\beta(s)$$

(when denominator = 0)

$$\Rightarrow 1 - A(s)\beta(s) = 0$$

$$A(s)\beta(s) = 1$$

(BARK HAUSMAN'S CRITERIA)

$$\therefore A(\omega_0)\beta(\omega_0) = 1$$

$$\omega_0 = 2\pi f$$



Date: _____


So, if we apply zero input, the output would be a finite signal of frequency (f_0) if and only if $A(\omega_0)B(\omega_0) = 1$; $\omega_0 = 2\pi f$ holds at the frequency (f_0)

Wien-Bridge Oscillator:



17/10

Wien-Bridge Oscillator

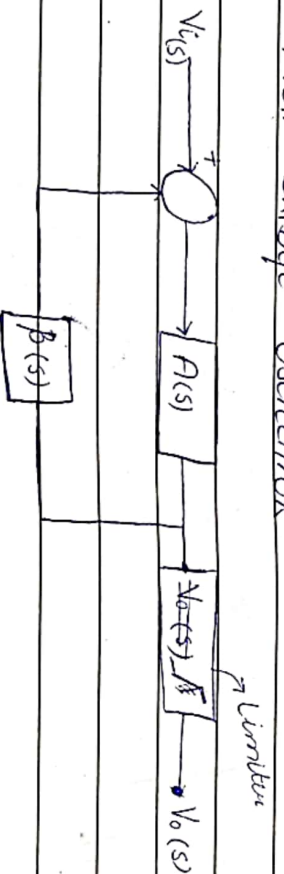

Barkhausen Criteria:

To get a finite sine signal at $f = f_0$


$$A(\omega_0)B(\omega_0) = 1$$




Date: _____

circuit when limiter is not connected (as previous)

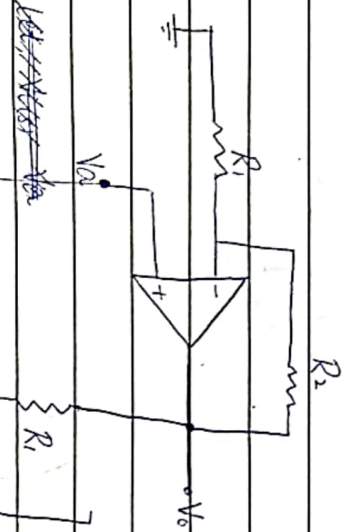(-ve feedback (o/p connected to))
-ve terminal



let, $V_c(s) = V_a$

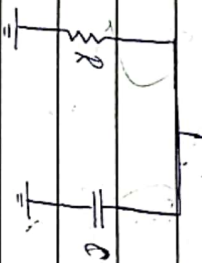


$\Rightarrow$



Remove 'Vo' & 'Vc' after joining
names

OR

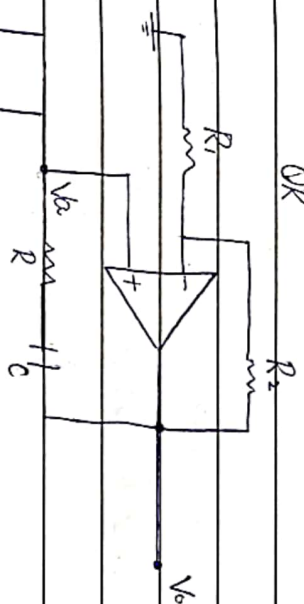

$$V_o(s) = \left(1 + \frac{R_2}{R_1}\right) V_a(s)$$



$$\frac{V_o(s)}{V_a(s)} = \left(1 + \frac{R_2}{R_1}\right)$$

$$V_o(s) = A(s) V_a(s)$$


$$\therefore A(s) = 1 + \frac{R_2}{R_1}$$



Date: _____

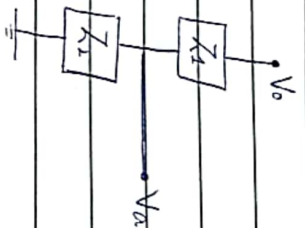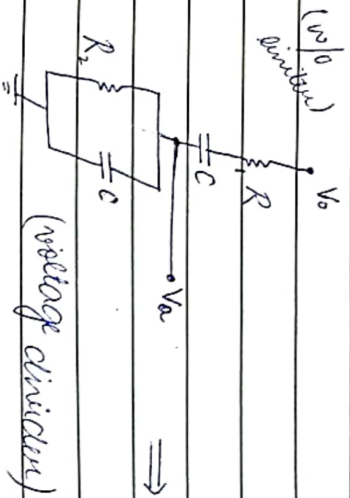
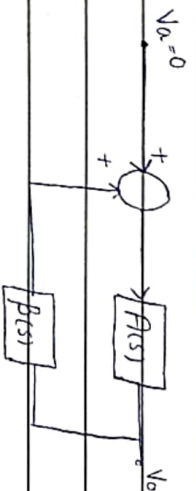
$$\begin{aligned} \beta(s) &= \frac{Z_2}{Z_1 + Z_2} \\ &= \frac{R_2 \parallel (1/sC)}{(R_1 + \frac{1}{sC}) + (R_2 \parallel \frac{1}{sC})} \end{aligned}$$



$$\begin{aligned} &= \frac{1 + \cancel{(R_2/R_1)}}{3 + (RC)s + \frac{1}{(RC)s}} \\ \therefore A(s) &= \frac{1 + R_2}{R_1} \end{aligned}$$

* $A(s) \beta(s) = 1$, $\therefore$

$$A(s) \beta(s) = \frac{1 + (R_2/R_1)}{3 + (RC)s + 1/(RC)s}$$

Put $s = j\omega$

$$A(j\omega) \beta(j\omega) = \frac{1 + (R_2/R_1)}{3 + j(RC\omega) + \frac{1}{j(RC\omega)}}$$



Date: _____

$$= 1 + (R_2/R_1)$$
$$3 + j(RC\omega - \frac{1}{RC\omega})$$

BARK HOUSAN CRITERIA To get a 'REAL' time wave of freq. f_0 ,
 $A(\omega)B(\omega) = 1$ at $f = f_0$

$$A(\omega_0)B(\omega_0) = 1 + (R_2/R_1)$$
$$3 + j(RC\omega_0 - \frac{1}{RC\omega_0})$$

If we make this imaginary part = 0, then this whole thing becomes REAL.

TO MAKE SYSTEM REAL:

$$RC\omega_0 - \frac{1}{RC\omega_0} = 0$$

$$RC\omega_0$$

$$RC\omega_0 = 1$$

$$2\pi f_0 = \omega_0$$

$$RC\omega_0$$

$$\omega_0^2 = 1$$

$$\Rightarrow$$

$$\boxed{\omega_0 = 1 \over RC}$$

(filter design)

FOR $R_1 \neq R_2$

$$A(\omega_0)B(\omega_0) = 1$$

$$1 + (R_2/R_1)$$

$$= 1$$

$\therefore$ at $\omega_0 = 1$

$$3 + j(RC\omega_0 - \frac{1}{RC\omega_0})$$

$$RC$$

$$1 + (R_2/R_1) = 1$$

$$3$$



Date: _____

$$1 + \frac{R_2}{R_1} = 3$$

$$\frac{R_2}{R_1} = 2$$

$$\left[\frac{R_2}{R_1} \gg 2 \right]$$

Assume, $R_1 = 100k$

$$R_2 = 200k$$

* FILTER:

$$\omega_0 = 1/RC$$


$$\omega_0 = 2\pi f_0$$

$f_0 \Rightarrow$ given

$\Rightarrow R_2 = 201k\Omega$
should be greater (practical)


AMP:

$$R_2/R_1 \gg 2$$

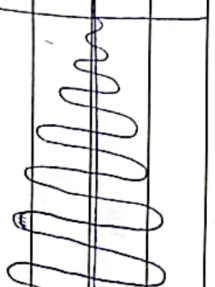

(w/o limiter)

LIMITER CIRCUIT OF AMPLITUDE CONTROL:

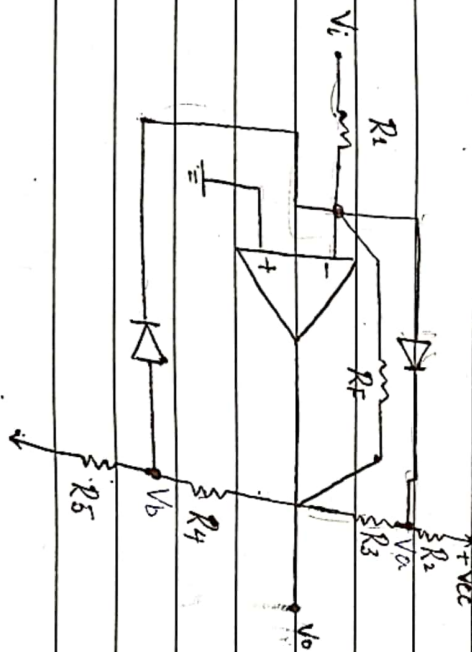

FOR +VE HALF CYCLE

• V_i is very small (close to zero) but +ve.

$$V_o = -\left(\frac{R_F}{R_1}\right) \times V_i \quad (\text{inverting amplifier})$$



Date: _____

• V_o is also very small and -ve ≈ -0.01

* $V_{ANODE} > V_{CATHODE}$

(short circuit) $\rightarrow$ forward

*

V_{ANODE}

$V_{CATHODE}$

[$V_{ANODE} < V_{CATHODE}$ (open circuit) — reverse biased]

• V_i will gradually increase

• V_o will move $\uparrow$ more & more -ve (decrease) ($\uparrow$)


$$\Rightarrow V_o = - \left(\frac{R_F}{R_1} \right) \times V_i$$

• V_A will continue to decrease in magnitude

• Until $V_A = -0.7V \rightarrow$ at this point 'Diode turns on'

• It brings R_3 in parallel with R_F
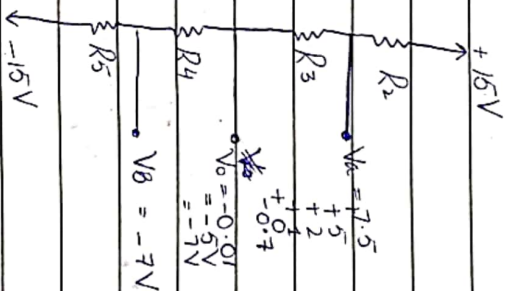
$$V_o = - \left(\frac{R_3 \parallel R_F}{R_1} \right) \times V_i$$



Diode turns on

gain

increases

gain

decreases

$\downarrow$ due to limiter

$$* \frac{R_F}{R_1} \gg \frac{R_3 \parallel R_F}{R_1}$$



$$G_1 \gg G_2$$




Date: _____

FOR -VE CYCLE:

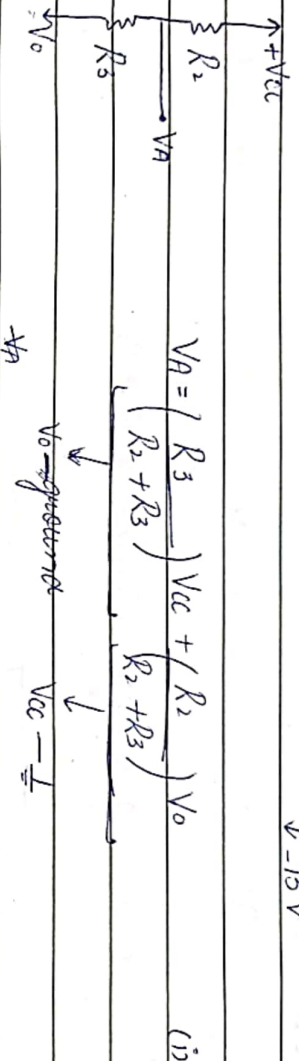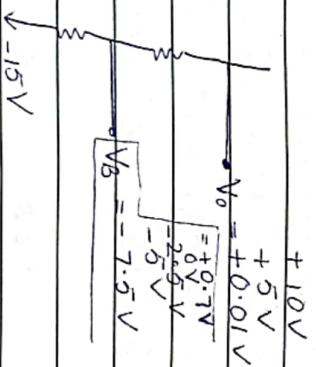- V_i becomes more 'ne'
- V_o becomes more 'ne'
- V_B becomes less 'ne'
- $V_o = -\left(\frac{R_1 \parallel R_4}{R_2}\right) \times V_i$ (diode short)



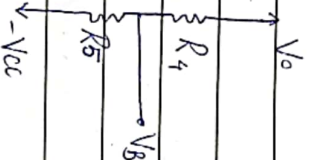
$$V_B = \left(\frac{R_4}{R_4 + R_5} \right) (-V_{cc}) + \left(\frac{R_5}{R_4 + R_5} \right) \times V_o \quad (ii)$$



TRANSFER CHARACTERISTICS

for (i) $V_A = -V_D$, $V_o = L_-$
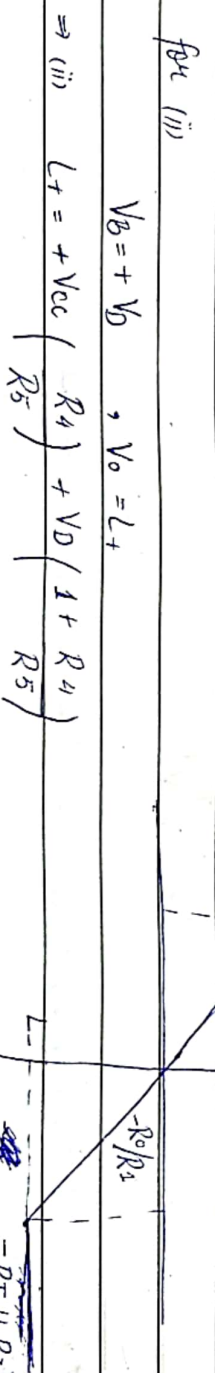
$$\Rightarrow (i) \quad L_- = -V_{cc} \times \frac{R_3}{R_2} - V_D \left(1 + \frac{R_3}{R_2} \right) - \frac{R_1 \parallel R_4}{R_2} \times V_o$$



R_1



Date: 22/10


MULTI-VIBRATOR CCT's FOR SIGNAL GENERATION

used to generate sq. wave

- Bistable MVB (2 stable states)
- Monostable MVB (1 stable state) (used in alarms)
- Astable MVB (No stable state)

→ BISTABLE MVB:

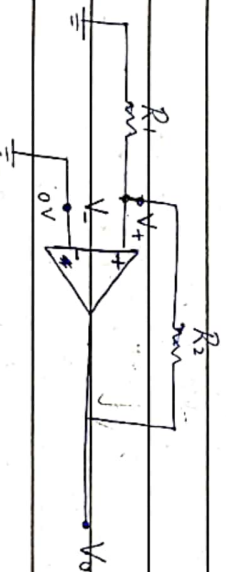- Bistability: DC amplifier in +ve feedback loop (no filter)
- * Open loop gain: $AB > 1$
- Feedback contains a voltage divider of R_1 & R_2



$$V_- = 0V$$

- No external input voltage
- Electrical noise in ckt introduces a small +ve voltage at V_+

Hence,

$$V_o^+ = A(V_+ - V_-)$$

$$\Rightarrow V_o^+ > 0$$

V_o^+ ① → 1st situation

$$\text{O/P is fed back at } V_+ = \left(\frac{R_1}{R_1 + R_2} \right) V_o^+$$


$$V_+ = \beta V_o^+$$

* Disturbance happens in pico sec. $\Rightarrow V_o$ - increases




Date: _____

TRANSFER CHARACTERISTICS OF BISTABLE MVB

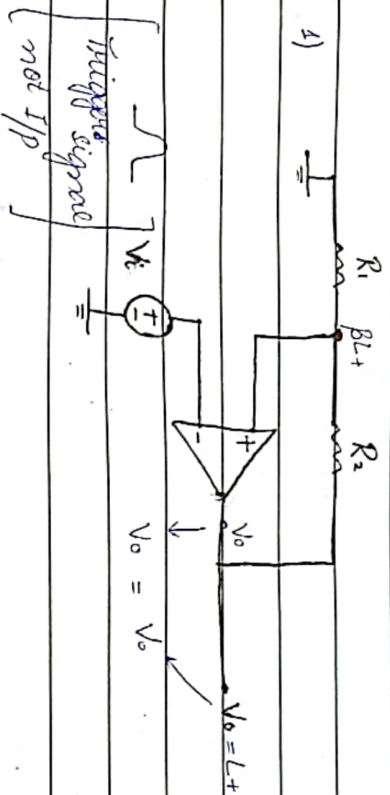

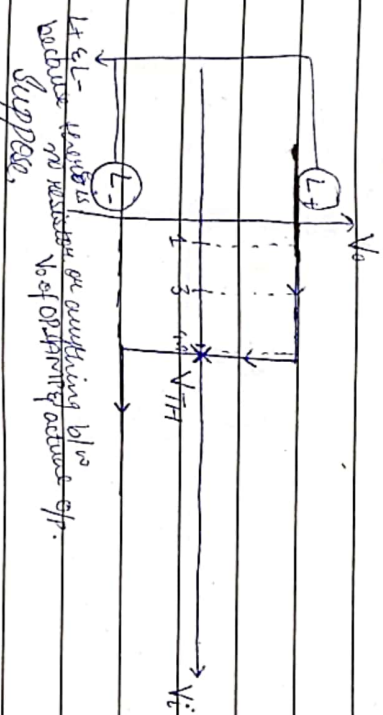
$$\begin{aligned} L_+ &= 10V \\ \beta &= 0.5 \\ \beta L_+ &= 5V \\ V_+ &= \frac{R_1}{R_1 + R_2} \times V_o \end{aligned}$$




(Fig #1)

$$V_o = L_+ ; \quad V_+ = \left(\frac{R_1}{R_1 + R_2} \right) L_+ = \beta L_+$$

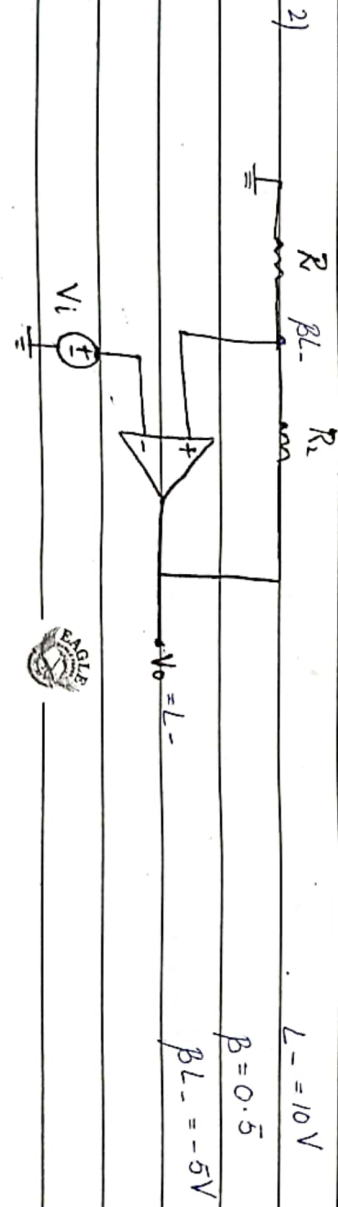- $V_+ = \beta L_+$
- $V_- = V_i$
- AMP: $V_o = A(L_+ - L_-)$ ($V_i \gg \beta L_+$)
- initially, $V_- = 0V$
- We start increasing V_i gradually



Date: _____

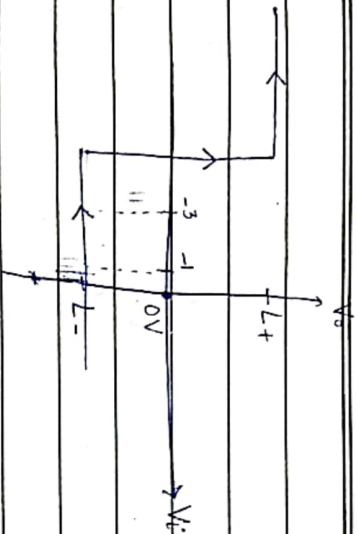

(Fig #2)

Suppose, $V_o = L^-$; $V_{i+} = \frac{R_1}{R_1 + R_2} \times L^- = \beta L^-$

• $V_+ = +\beta L^-$


• $V_- = V_i = 0$

• AMP ; $V_o = A(V_+ - V_-)$ ($V_i \leq \beta L^-$)

• initially, $V_i = 0V$

• we start decrease V_i gradually

Combine Fig #1 & fig #2

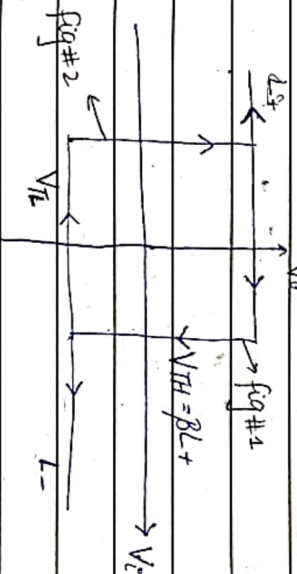

(hysteresis comparator)

$V_{TH} = \beta L^+$ (high to low)

$V_{TH} = \beta L^-$ (low to high)

★ inverting bistable MVB

or

hysteresis comparator

★ $V_{TH} = \frac{R_1}{R_1 + R_2} \times L^+$

★ $V_{TL} = \frac{R_1}{R_1 + R_2} \times L^-$






Date: _____

* if trigger (V_i) $> V_{L+}$ — V_o goes from $L+$ to $L-$
 if trigger (V_i) $< V_{L-}$ — V_o goes from $L-$ to $L+$

We can have noise at ~~ripple~~ noise near switching
 Hysteresis counteracts:
 helps to eliminate the ripples near the crossing of the signal
 wave form.

INVERTING BISTABLE MULT

24/10 NON-INVERTING BISTABLE MULT

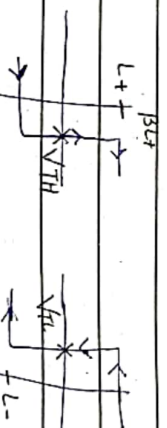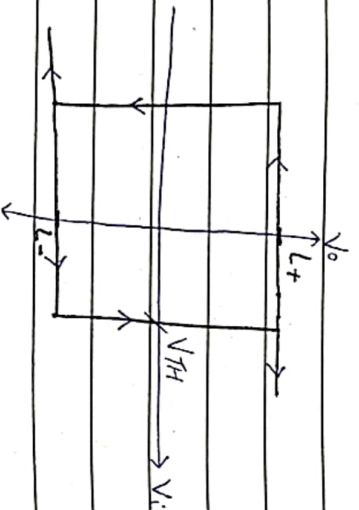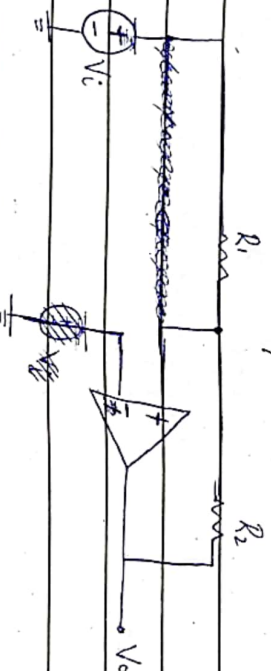

$$V_{TH} = \frac{V_i \xrightarrow{\text{ground}} \left(\frac{R_1}{R_1 + R_2} \right) \times V_o + \left(\frac{R_2}{R_1 + R_2} \right) \times V_i}{V_i \xrightarrow{\text{ground}}}$$



$$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) \times L-$$

$$V_{TL} = - \left(\frac{R_1}{R_1 + R_2} \right) \times L+$$



Date: _____

Q. (Non-inverting)

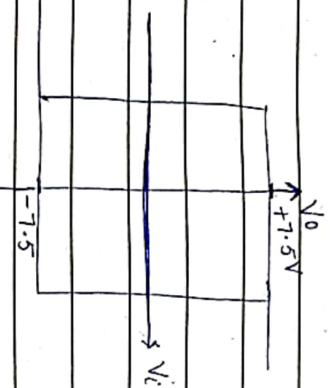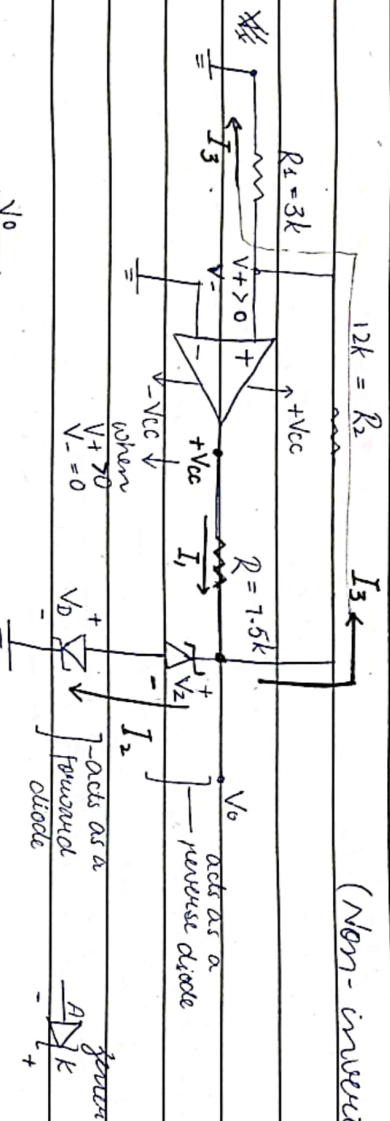

→ forward current in Zener :
it acts like an ordinary diode
 $V_{AK} = 0$
anode → cathode

→ reverse current:


it acts like a Zener diode

Let $V_Z = 6.8\text{V}$, $V_D = 0.7\text{V}$ (given) $V = V_Z$

$V_O = V_{DZ} + V_D$
 $= 6.8 + 0.7$
for $V_+ > 0$

$V_O = 7.5\text{V}$ (L+)
for $V_- = 0$

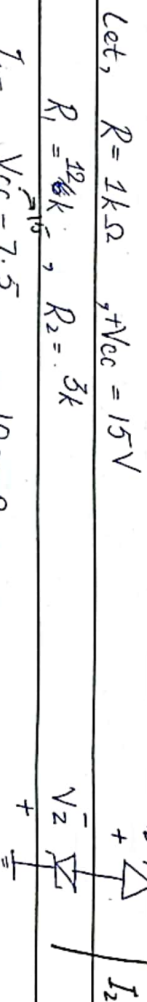$0 - V_O = V_Z + V_D$ for $V_+ < 0$
 $-V_O = 6.8 + 0.7$
 $V_O = -7.5\text{V}$ (L-)
for $V_+ = 0$
(direction of current changes)



Let, $R = 1\text{k}\Omega$, $V_{CC} = 15\text{V}$
 $R_1 = 10\text{k}$, $R_2 = 3\text{k}$
 $I_Z = V_{CC} - 7.5 = 10\text{mA}$
 7.5k

$I_3 = 7.5 - 0 = 0.5\text{mA}$
 12k , $R_2 + 3\text{k}$
 R_2 , R_1



Date: _____

$$I_3 = I_3 - I_1$$

$$= 0.5 \text{ mA}$$


$$V_+ = \frac{R_1}{R_1 + R_3} \times V_0$$

$$= \frac{3k}{3k + 15k} \times -7.5$$

$$V_+ = -1.25 \text{ V}$$




ASTABLE NNB (using inverting bistable config)

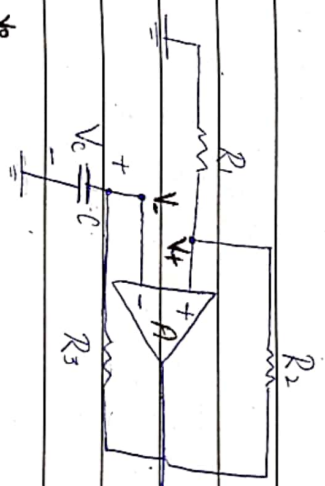- No stable state
- keeps toggling between $L+$ & $L-$
- Used to generate sq. wave & rect. waves.
- Uses bistable NNB circuit with RC circuit in $-ve$ feedback.



$$V_0 = A(V_+ - V_-)$$

$$V_- = V_c$$

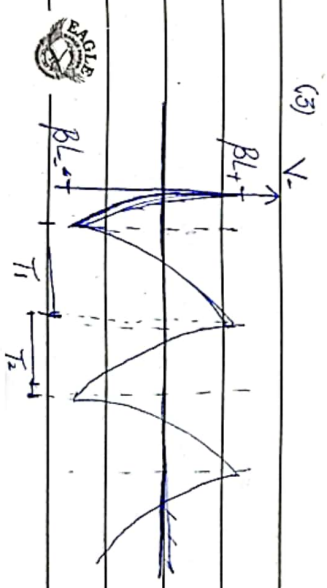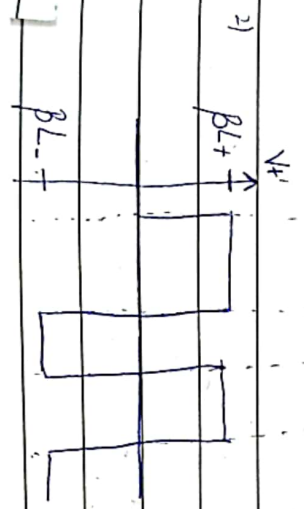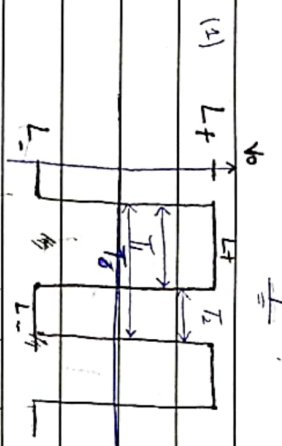

Date: _____

Initially:

$$V_0 = L_+, \quad V_+ = \beta L_+$$

- V_c will start rising exponentially.
- V_- will start rising exponentially.
- Because $V_0 = L_+$ is fixed, V_+ is also ~~was fixed~~ ~~constant~~ fixed.
- $V_0 = A (V_+ - V_-)$

TIME PERIOD:

$$V_c(t) = V_c(\infty) - (V_c(\infty) - V_c(0)) e^{-t/\tau_c}$$

for T_1 : $V_c(0) = \beta L_-$

$$V_c(\infty) = L_+$$

at $t = T_1$, $V_c(t) = \beta L_+$

$$\beta L_+ = L_+ - (L_+ - \beta L_-) e^{-T_1/\tau_c}$$

$$\ln \left(\frac{\beta L_+ - L_+}{-(L_+ - \beta L_-)} \right) = \ln \left(\frac{-T_1}{\tau_c} \right)$$

$$* \quad T_1 = \tau_c \ln \left(\frac{1 - \beta(L_-/L_+)}{1 - \beta} \right)$$

For symmetry power supplies: $L_+ = -L_-$

$$* \quad T_1 = \tau_c \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$

for T_2 :

$$V_c(0) = \beta L_+$$

$$V_c(\infty) = L_-$$

at $t = T_2$, $V_c(t) = \beta L_-$




Date: _____

$$B_L = L_- - (L_- - B_L) e^{-T_2/RC}$$

$$* T_2 = RC \ln \left(\frac{1 - B}{1 - B_L} \right)$$

$$* T_2 = RC \ln \left(\frac{1 + B}{1 - B} \right)$$

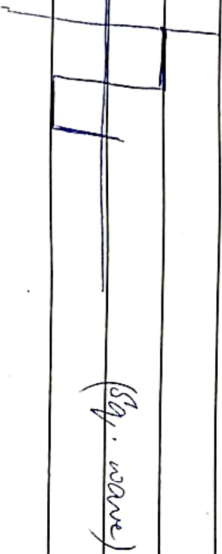
* for symmetrical power supplies $T_1 = T_2$



$$* B = \frac{R_1 + R_2}{R_1 + R_2}$$



$$* T = T_1 + T_2$$

To get a triangular wave:


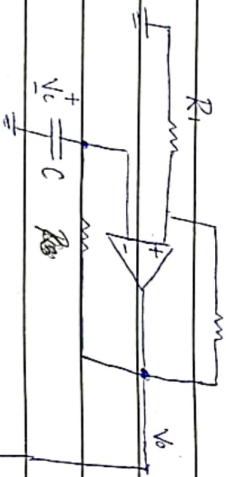


$$V_T = \frac{-1}{RC} \int V_o dt$$

assume, $V_o = 10$

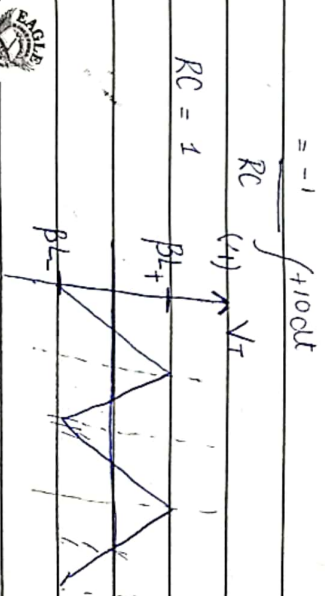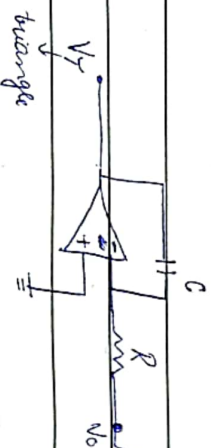

Date: _____

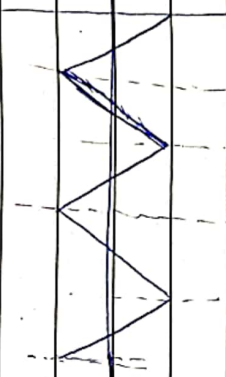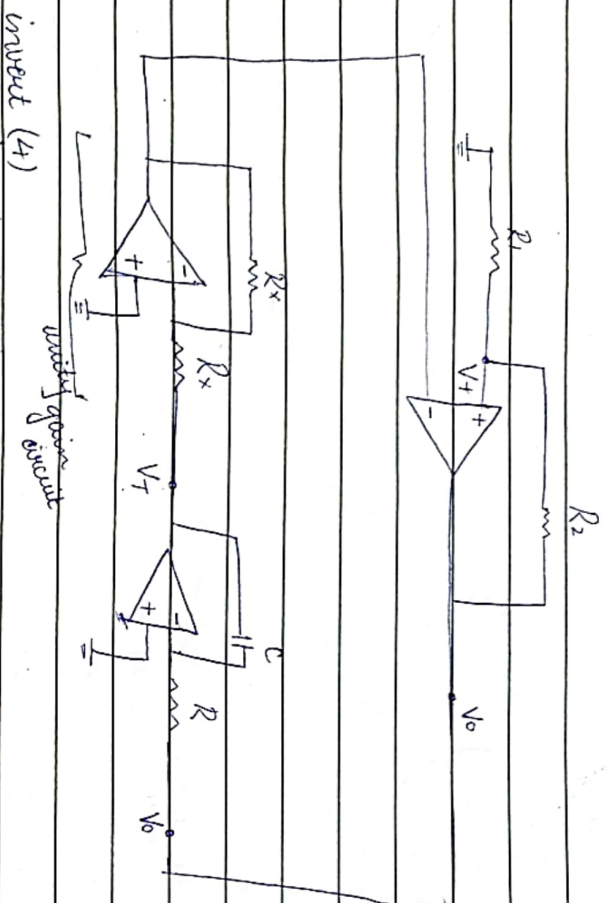

Function generator (Sq. + Δ wave ...)

for sym. power supplies: $L_+ = -L_-$

$$T_1 = RC \ln \left(\frac{V_{IH} - V_{TL}}{L_+} \right)$$

$$T_2 = RC \ln \left(\frac{V_{TH} - V_{TL}}{-L_-} \right)$$


$$\therefore V_{TH} = \beta L_+$$

$$\therefore V_{TL} = \beta L_-$$



Date: 31/10

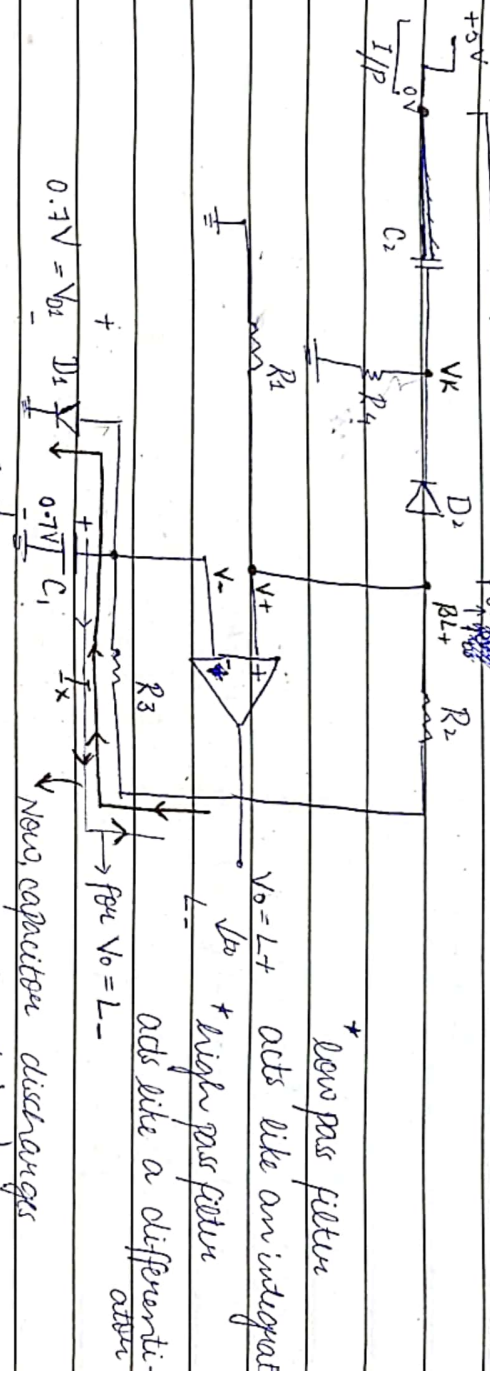MONOSTABLE MVB (Pulse generator) Triggering circuit



$V_0 = L+$, $V_+ = BL+$ (capacitor is charged at 0.7V at $L+$)
 $\beta = 0.1$
 $L+ = 12V$
 $BL+ = 1.2V$

Because $V_K > BL+$ ($\therefore 5V$)
 $\Rightarrow D_2$ is reverse biased (open circuit)

For I_x flows, D_1 is forward biased (forward circuit)
 $\Rightarrow D_1$ is short circuit

$$V_0 = A(V_+ - V_-)$$

$$= A(\beta L+ - 0.7)$$


When apply a trigger; $V_K = 0V$
 $\Rightarrow D_2$ becomes forward biased (short circuit)

D_2 is short circuit, 0V at V_K will travel ahead & force itself at V_+

$$V_0 = A(V_+ - V_-)$$

$$= A(\beta L+ - 0.7)$$

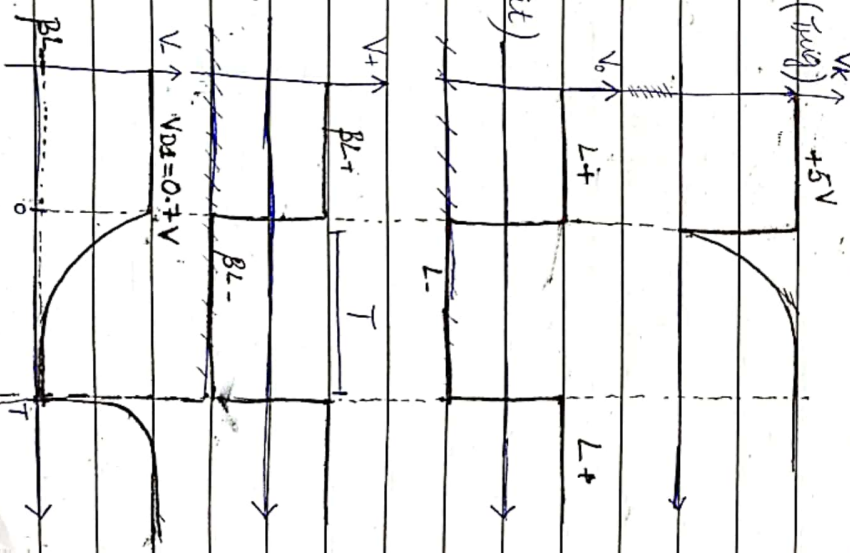In this duration, V_K becomes +ve again
 $\Rightarrow D_2$ is again open



Date: _____

$$V_o = A(V_+ - V_-)$$

$$= A(\beta L_- - V_-)$$

$$-1.2 - (-1.2001)$$

~~$y(t) = y_{ss}$~~
TIME PERIOD:

$$V_c(t) = V_c(\infty) - (V_c(\infty) - V_c(0))e^{-t/R_3C_1}$$


$$V_c(0) = V_{D1} \quad \text{at } t = T \quad ; \quad V_c(T) = \beta L_-$$

$$V_c(\infty) = L_-$$


$$\beta L_- = L_- - (L_- - V_{D1})e^{-T/R_3C_1}$$

$$\Rightarrow T = R_3C_1 \ln\left(\frac{V_{D1} - L_-}{\beta L_- - L_-}\right)$$

7/11 555 TIMER CIRCUIT:

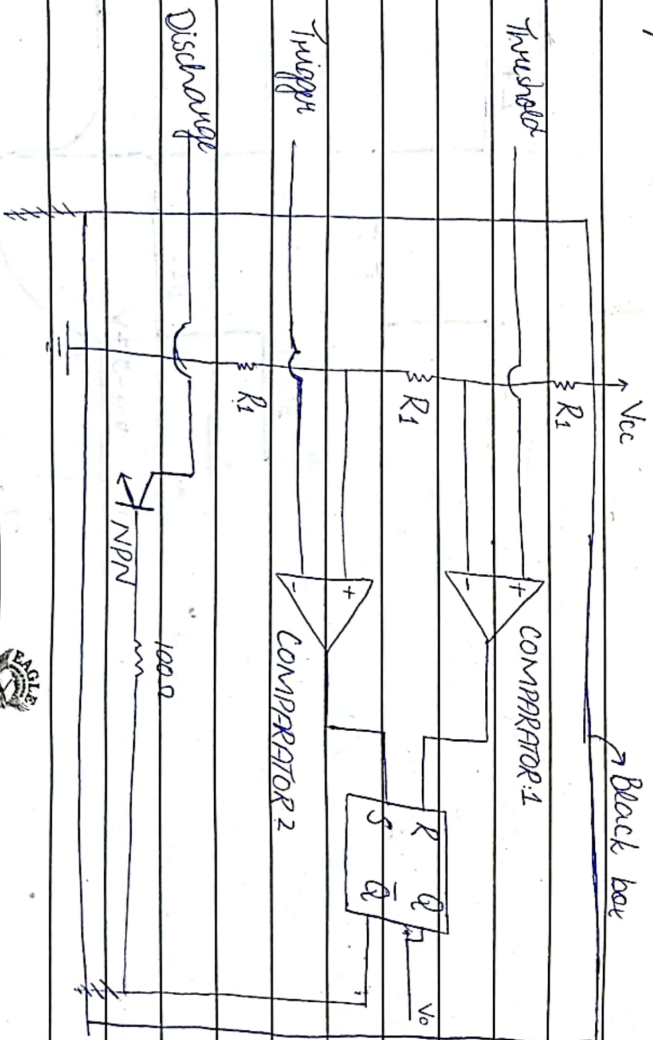


COMPARATOR:

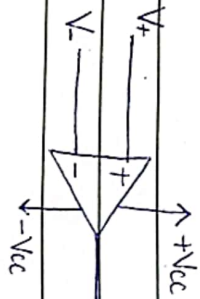

$$V_+ > V_- \Rightarrow V_0 = +V_{cc}$$

$$V_+ < V_- \Rightarrow V_0 = GND$$

Date: _____

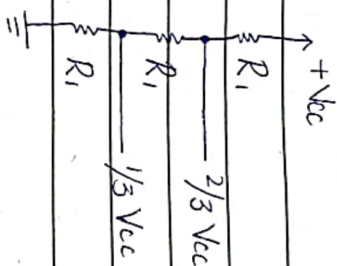


R	S	Q	$\bar{Q}$
0	0	Previous state	
0	1	1	0 (Set)
1	0	0	1 (Reset)
1	1	undefined	

R	Q
S	$\bar{Q}$

R S flip flop


when $\bar{Q} = 0$ NPN open (off)
 when $\bar{Q} = 1$ NPN short (ON)

555 TIMER CIRCUIT AS A MONOSTABLE MVB

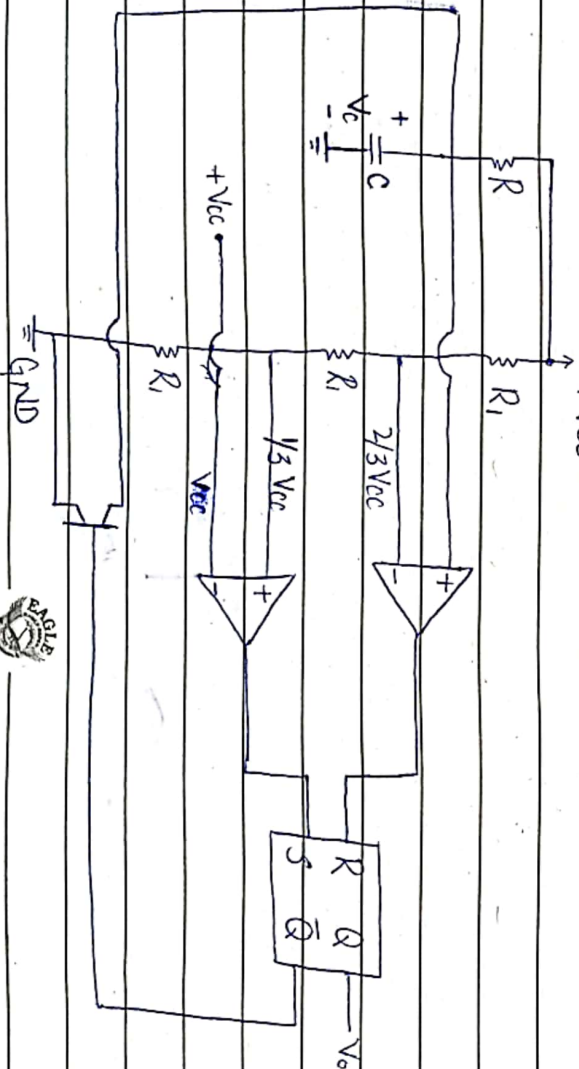

Date: _____

Tripper (T_R)


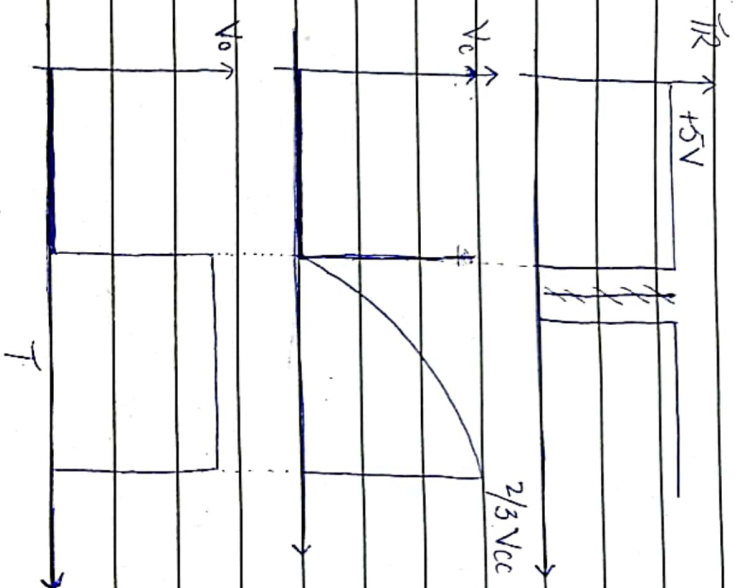


* $T = 0.1 \text{ s}$
 $T = 1.1 RC$




Date: 12/11

ASTABLE MVB USING 555 TIMER

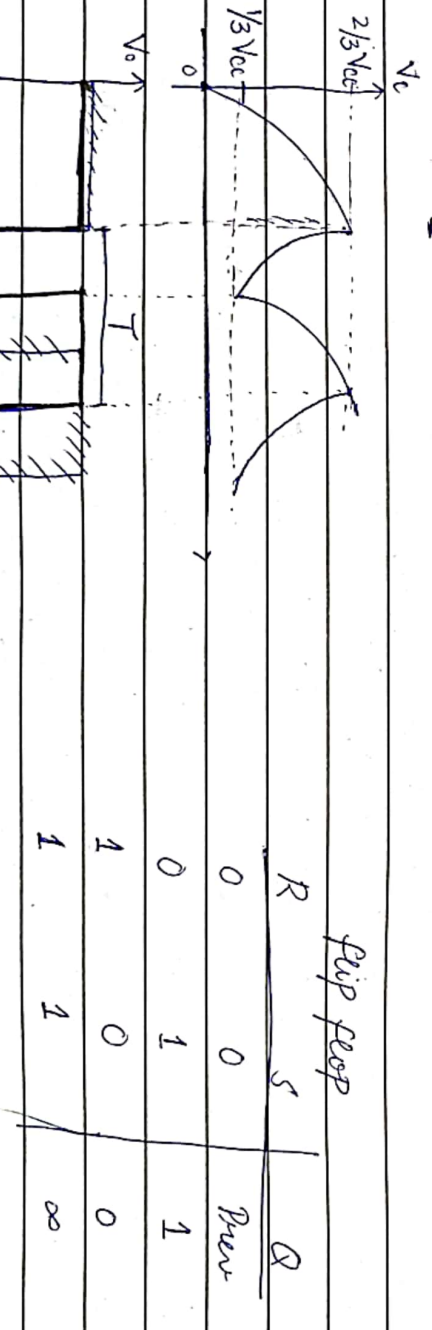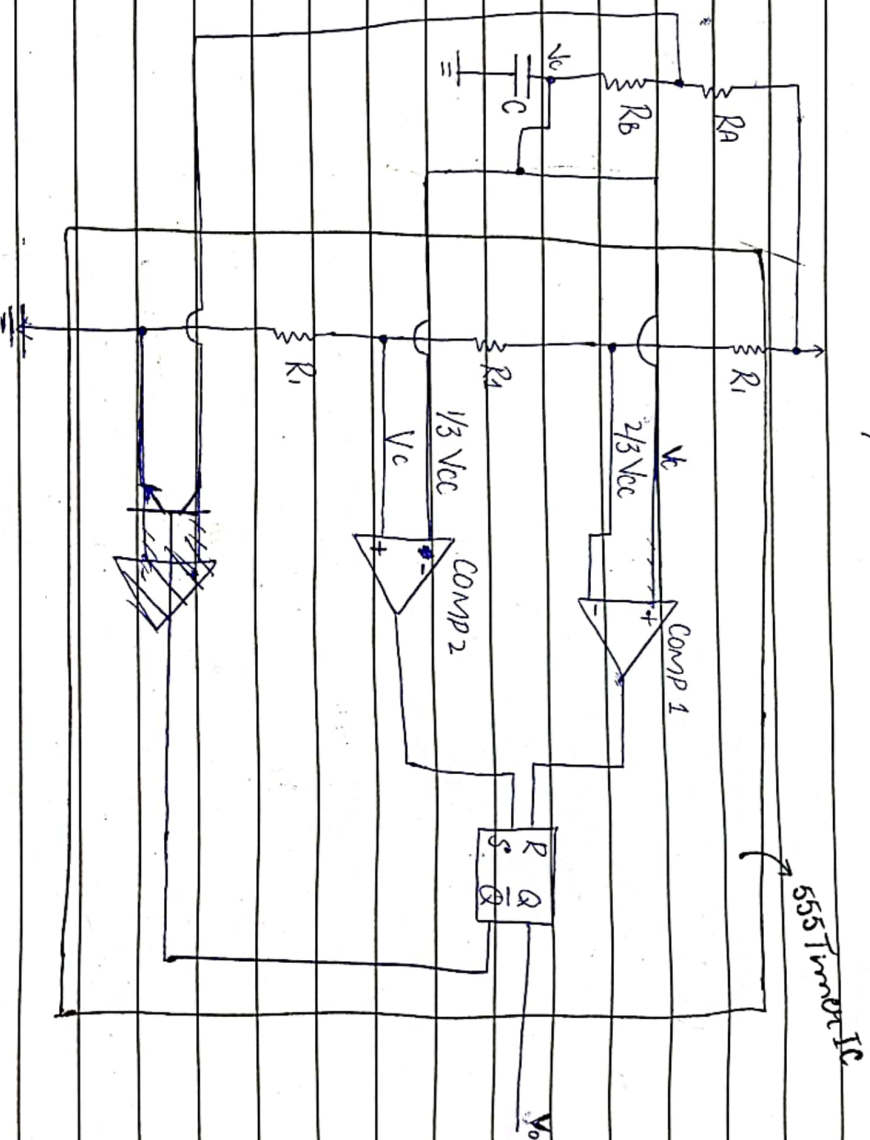

$$T_c = (R_A + R_B)C$$

$$T_{c1} = R_B \times C$$

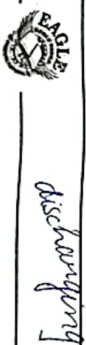

Date: _____

$$V_c(t) = V_c(\infty) - (V_c(\infty) - V_c(0)) e^{-t/RC}$$


FOR CHARGING $V_c(\infty) = V_{cc}$

$$V_c(0) = \text{initial value}$$

at $t = T_H$

$$\Rightarrow V_c = 2/3 V_{cc}$$
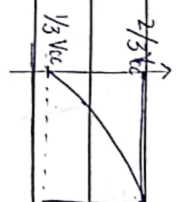
$$2/3 V_{cc} = V_{cc} - (V_{cc} - 1/3 V_{cc}) e^{-T_H / (R_A + R_B)C}$$



$$T_H = \ln 2 (R_A + R_B)C$$

FOR DISCHARGING

$$V_c(\infty) = 0$$


$$V_c(0) = 2/3 V_{cc}$$

at $t = T_L$

$$\Rightarrow V_c = 1/3 V_{cc}$$

$$-1/3 V_{cc} = 0 - (0 - 2/3 V_{cc}) e^{-T_L / R_B C}$$
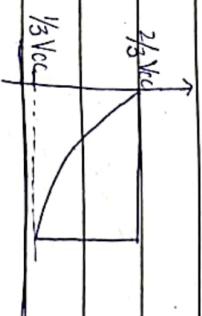
$$\Rightarrow 1/3 V_{cc} = 0 - (0 - 2/3 V_{cc}) e^{-T_L / R_B C}$$



$$T_L = \ln 2 (R_B)C$$

$$T = T_H + T_L$$

$$T = \ln 2 (R_A + 2R_B)C$$

$$D = T_H / (T_H + T_L) = T_H / T$$

$$D = \frac{R_A + R_B}{R_A + 2R_B}$$

(duty cycle)

$D \geq 51\%$
(max)




Date: _____

DUTY CYCLE:

OR ratio
The percentage of the total time period for which the signal is logic high OR logic '1'.

EXAMPLE:

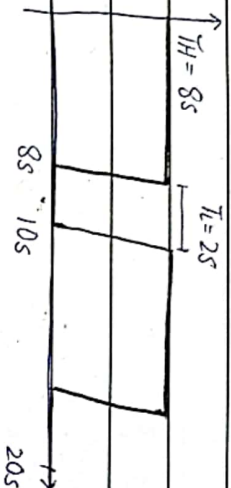

$$D = \frac{8}{10} = 0.8 \quad (80\%)$$

$$* D = \frac{T_H}{T_H + T_L} \times 100\%$$

DRAINBACKS

- $T_H \neq T_L$ (never)

In current settings, T_H can never be equal to T_L . So, you can't achieve a square wave and a 50% duty cycle.

FOR 50% DUTY CYCLE:

$$T_H = \ln 2 (R_A) C$$

$$T_L = \ln 2 (R_B) C$$

$$T = T_H + T_L$$


$$= \ln 2 (R_A + R_B) C$$

$$D = \frac{T_H}{T_H + T_L} = \frac{T_H}{T}$$

$$= R_A$$

$$R_A + R_B$$

$$\therefore R_A = R_B$$

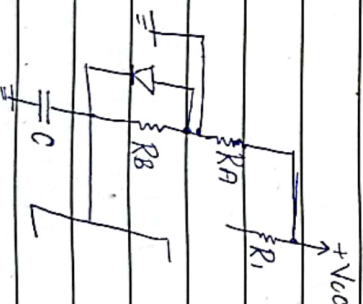

Date: 14/11

FOR DUTY CYCLE 750%

$$T_1 = \ln 2 (R_A + R_B) C$$

$$T_2 = \ln 2 (R_B) C$$

$$T = \ln 2 (R_A + 2R_B) C$$

$$f = 1/T$$

$$D = \frac{R_A + R_B}{R_A + 2R_B}$$

$$R_A + 2R_B$$

FOR DUTY CYCLE $\leq 50\%$

$$T_1 = \ln 2 (R_A) C$$


$$T_2 = \ln 2 (R_B) C$$

$$T = \ln 2 (R_A + R_B) C$$

$$f = 1/T$$

$$D = R_A$$

$$R_A + R_B$$

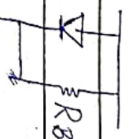

Q. Use 1mF capacitor in a 555 timer circuit, find the value of R that generates a pulse of 10 μ s.

$$T = (\ln 3) RC$$

$$10^{-4} = (\ln 3) R$$

$$(\ln 3) (10^{-4})$$


$$R = 9.1 k\Omega$$

Q. Design ² different ~~at least~~ circuits that can generate sq. wave. (50% duty cycle)



Date: _____


1)

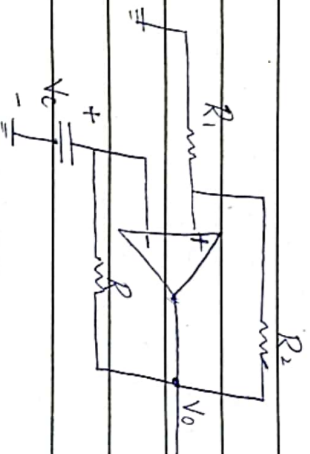

$$T = RC \ln \left(\frac{1+\beta}{1-\beta} \right)$$

$$L+ = -L-$$

2)

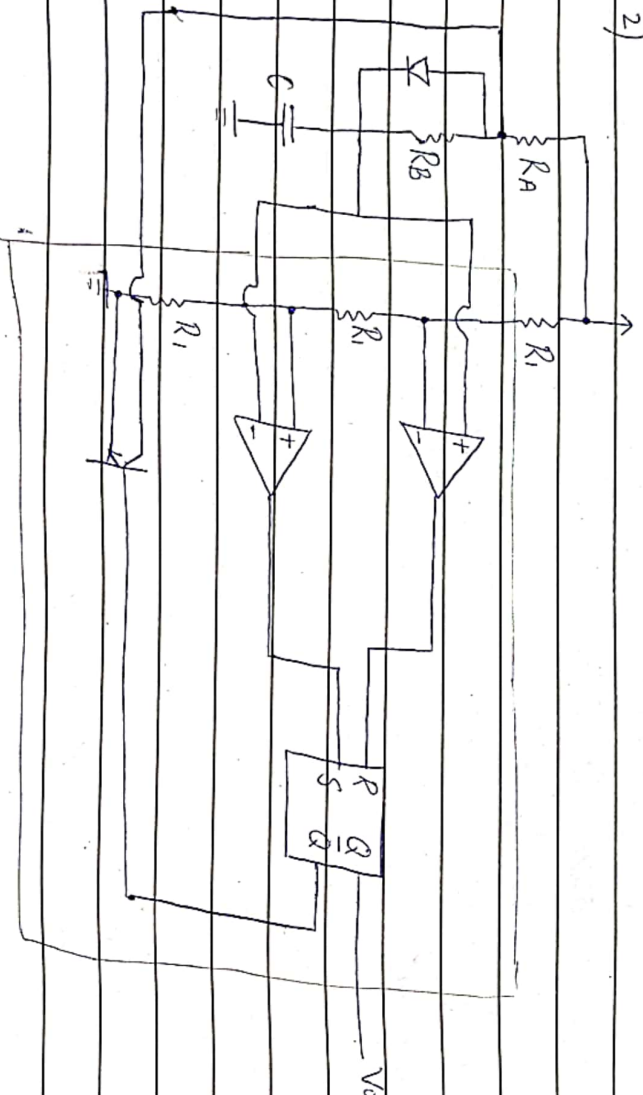

Q. Use a 680pF capacitor, design a circuit using 555 timer that generates a rectangular signal of 75% duty cycle & 50kHz frequency find R_A & R_B .

→ A stable MVB using 555 timer

$$T = \frac{1}{f} = \frac{1}{50k} = 20\mu s$$



Date: _____

$$D = R_A + R_B$$

$$\therefore 75\% = 0.75 = \frac{34}{44}$$

$$R_A + 2R_B$$

$$\frac{3}{4} = \frac{R_A + R_B}{R_A + 2R_B}$$

$$4$$

$$4R_A + 4R_B = 3R_A + 3R_B$$

$$R_A = 2R_B$$

(i)

$$T = \ln 2 (R_A + 2R_B) C$$

$$20\mu = \ln 2 (R_A + 2R_B) (680\mu)$$

$$R_A + 2R_B = 20\mu$$

$$(\ln 2) (680\mu)$$

$$R_A + 2R_B = 42.432k$$

$$\rightarrow (i) \quad R_A + R_A = 42.432k$$

$$2R_A = 42.432k$$

$$R_A = 21.216k$$

$$\rightarrow (i) \quad \frac{R_A}{2} = R_B \Rightarrow \frac{21.216k}{2} = R_B$$

$$R_B = 10.5k\Omega$$

Q. Use a 555 timer to generate a 50% duty cycle square wave signal of 10k Hz using a capacitor of 4nF.

$$f = \frac{1}{T}$$

$$T = \frac{1}{f} = \frac{1}{10k} = 0.1\mu s \quad 100\mu s$$



Date: _____

$$0.5 = R_A$$

$$R_A + R_B$$

$$0.5R_A + 0.5R_B = R_A$$

$$\cancel{0.5R_A} + 0.5R_B = \cancel{0.5R_A} \quad (i) \quad \Rightarrow R_B = +0.5R_A$$

$$0.5$$

$$T = \ln 2 (R_A + R_B) C$$

$$100 \mu s = R_A + R_B$$

$$(\ln 2)(14)$$

$$R_A + R_B = 144.26 \Omega$$

(iii)

$$R_A = 144.26 \Omega - R_B$$

$$R_A = 144.26 \Omega - (+R_A)$$



$$\cancel{R_A} = 144.26 \Omega - \cancel{R_A} \Rightarrow 2R_A = 144.26 \Omega$$

$$R_A = 72.13 \Omega$$

$$R_B = 144.26 - 72.13$$

$$R_B = 72.13 \Omega$$

ORDINARY HALF-WAVE RECTIFIER:

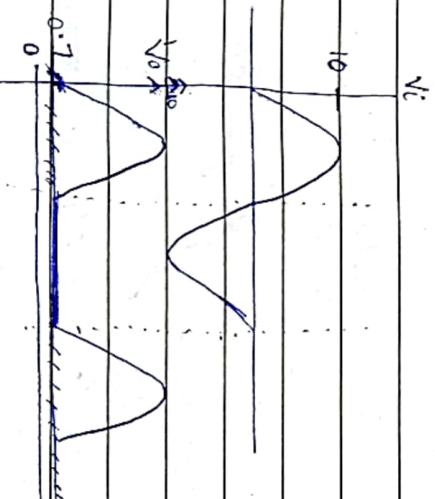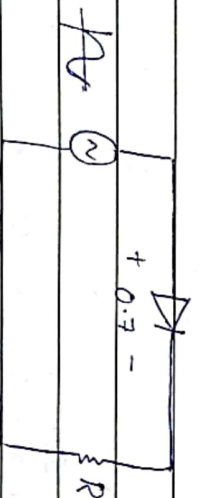

PRECISION HALF-WAVE RECTIFIER:

Date: _____


SUPER-DIODE:

Diode as comparator





$$V_+ > V_- \Rightarrow V_o = L_+$$

$$V_+ < V_- \Rightarrow V_o = L_-$$

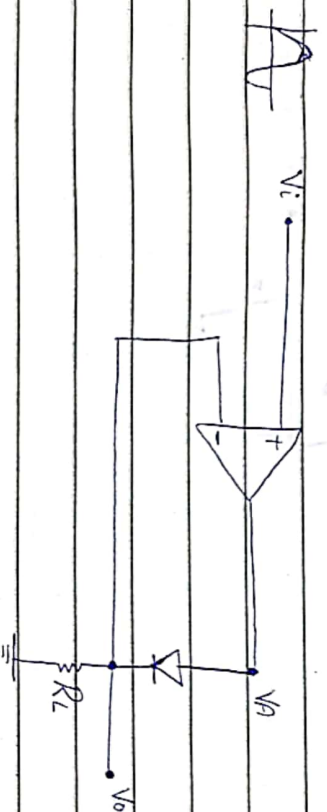

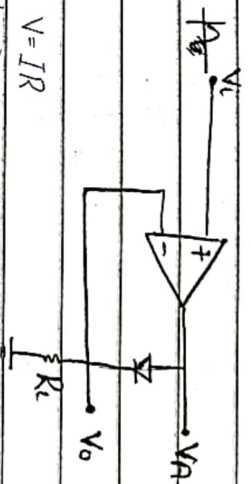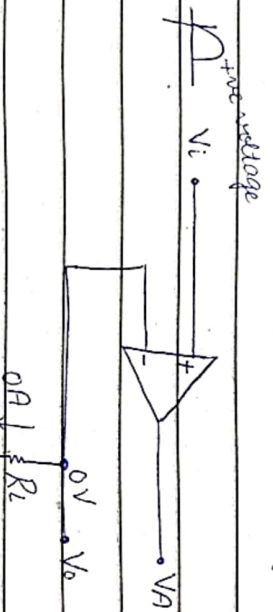→ During the +ve half cycle ($V_i > 0$)
 For a moment, ignore that diode is existing.



forward bias $\Rightarrow$ short circuit
 $\Rightarrow V_i = V_o$

$$V_+ = +ve$$

$$V_- = 0$$

$$V_A = A(V_+ - V_-)$$

$$V_A = L_+$$

$$\Rightarrow V_i = V_o$$

→ DURING THE -ve HALF CYCLE ($V_i < 0$)



Date: _____


$$V_A = -v_e$$

$$V_s = 0$$

$$V_A = A(V_+ - V_-)$$

$$= A(-v_e - 0) \Rightarrow -v_e$$




$$\Rightarrow \boxed{V_o = 0V}$$

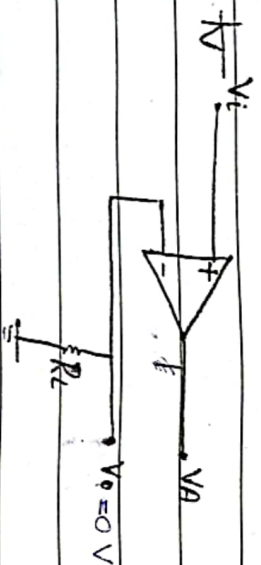

diode reverse biased
→ open circuit

19/11

ACTUAL CIRCUIT

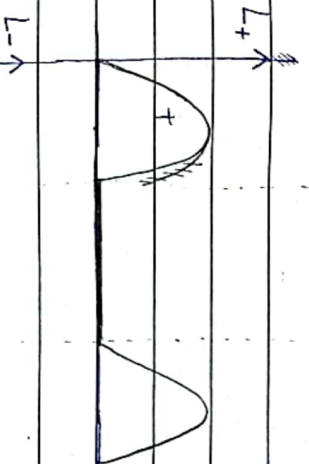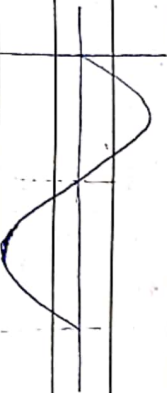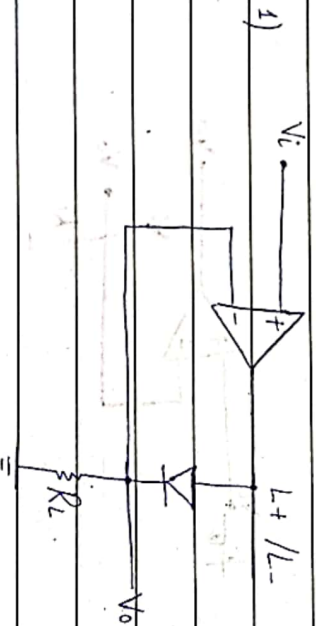



when short circuit

Plot


when open circuit



Date: _____

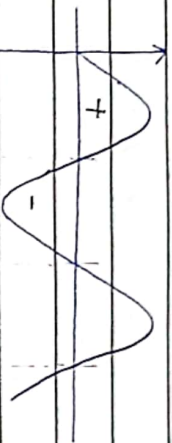
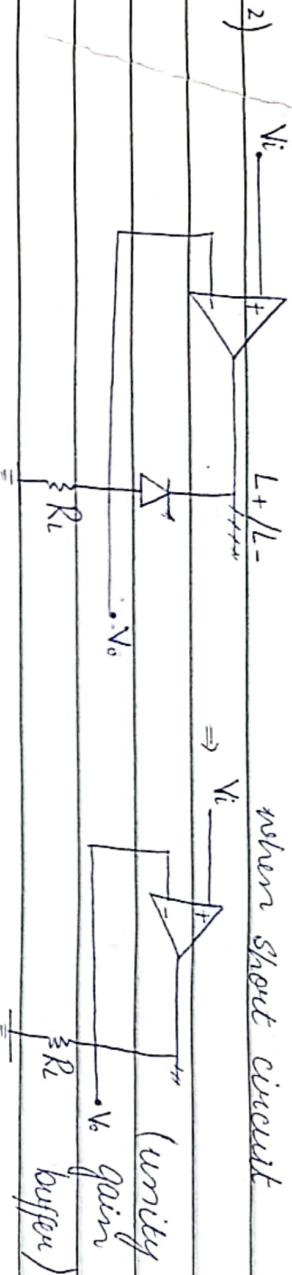


when open circuit

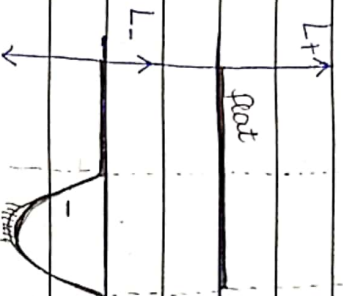

when short circuit
(unity gain buffer)

IMPROVED CIRCUIT:

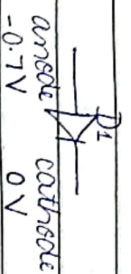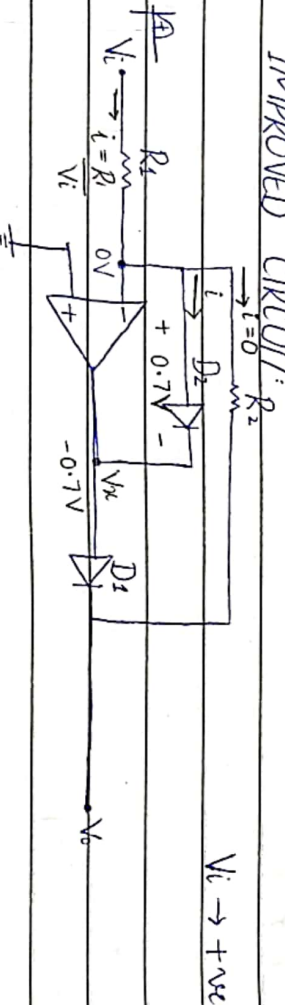


FOR POSITIVE HALF CYCLE:

- D_2 is forward biased (short circuit) $\Rightarrow$ open circuit $V_o < V_{ref}$
- 'i' passes through D_2 .
- D_2 will be reverse biased (open circuit)



Date: _____


$V_i \rightarrow -ve$

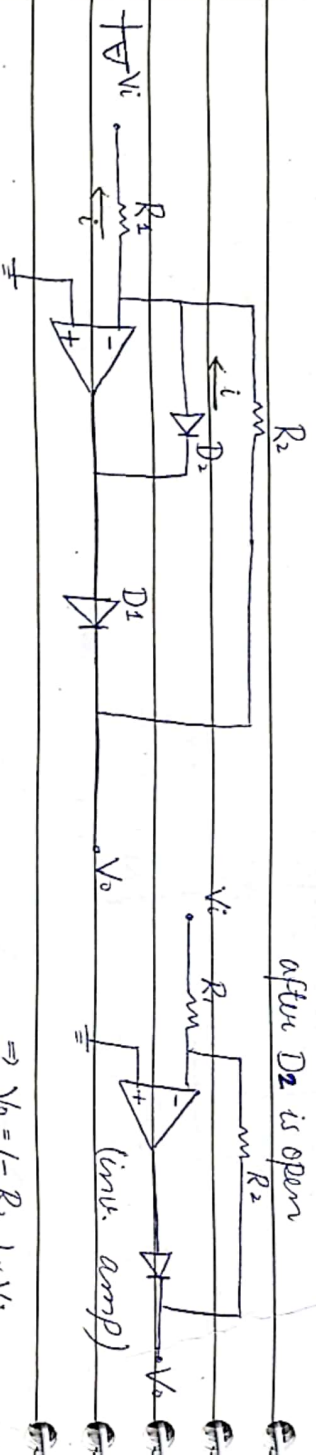



$$\Rightarrow V_o = \left(-\frac{R_2}{R_1} \right) \times V_i$$

FOR NEGATIVE HALF CYCLE

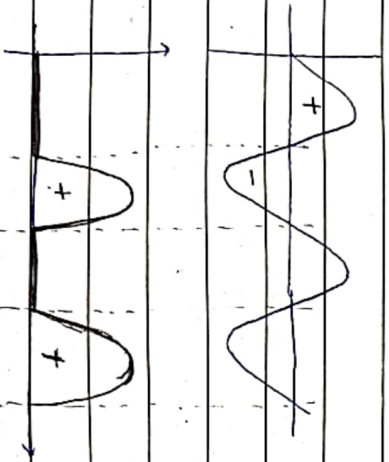- D_2 is open circuit
- $'i'$ passes through D_1
- D_1 is forward biased (open circuit)




FOR REVERSE DIODES

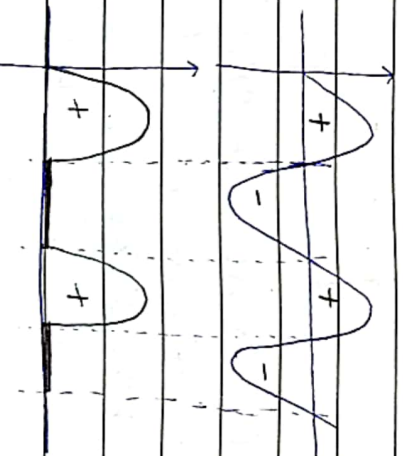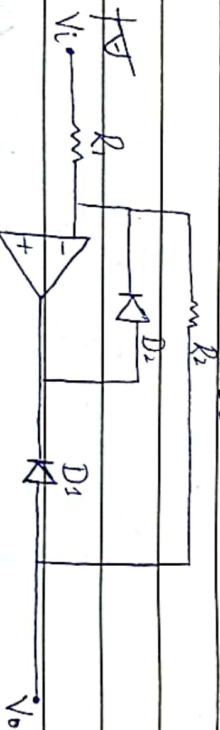

Date: _____

AC VOLTMETER

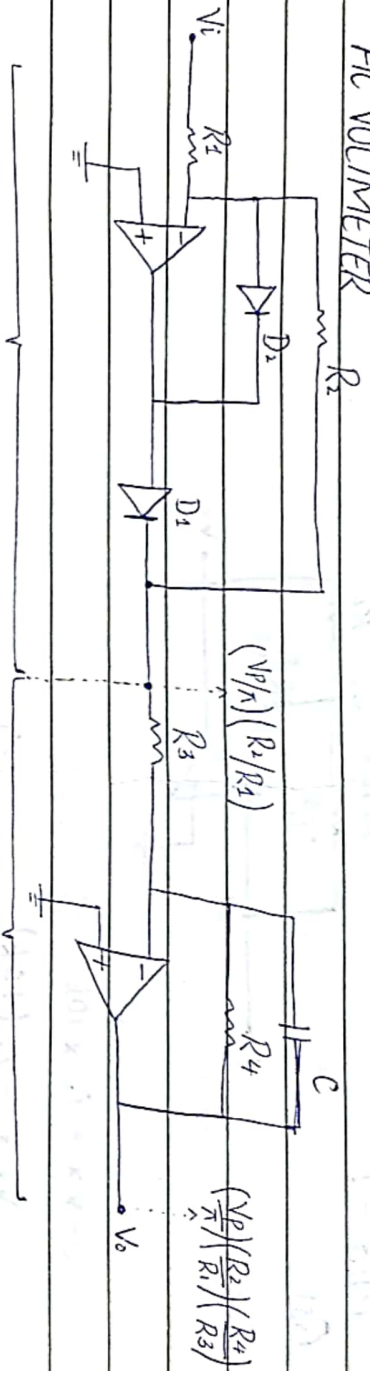

Precision rectifier

$$DC \text{ gain} = R_2/R_1$$

Low pass filter

$$DC \text{ gain} = R_4/R_3$$


$$\text{Average value} = \frac{V_p}{\pi}$$

odd harmonics
→ high freq. noise

before LPF



→ after LPF

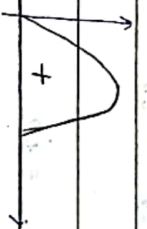

LPF is used to remove noise

$$* V_o, \text{avg} = \frac{V_p}{\pi} \times \frac{R_4}{R_3} \times \frac{R_2}{R_1}$$

$$\therefore V_o, \text{avg} \propto V_p$$

$$* \omega_0 = \frac{1}{CR_4}$$

filter design:

cut off frequency.

$$\omega = \frac{1}{CR_4}$$

$$f = \frac{1}{2\pi CR_4}$$

$$* V_p = \left(\frac{\pi V_o, \text{avg}}{R_2} \right) \left(\frac{R_1}{R_4} \right) \left(\frac{R_3}{R_4} \right)$$

∴ V_o, avg - given




AC VOLTMETER

Date: 19/11

Q. Design an AC voltmeter for a 10Hz input signal. It is calibrated for a sine wave signal to provide a $+10\text{V}$ output for input of 1.0V_{rms} . The R_{in} must as high as possible, keeping the gain of AC rectifier part to unity. The largest resistor available is $1\text{M}\Omega$

Sol.

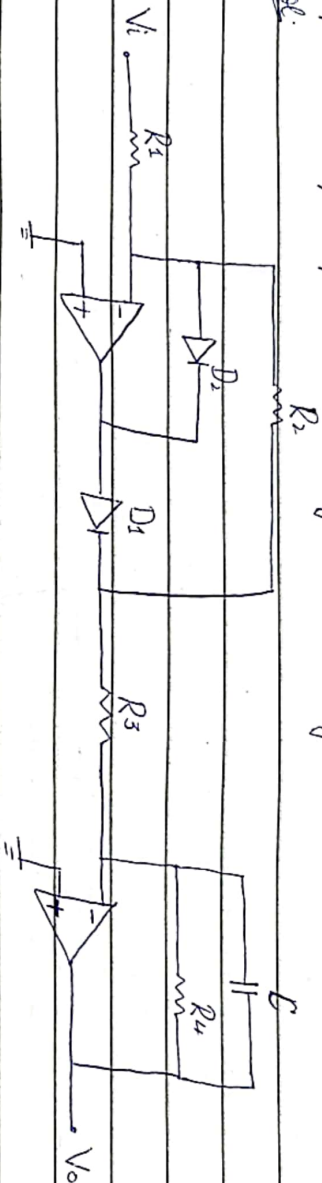

AC rectifier gain is unity $\Rightarrow \frac{R_2}{R_1} = 1.0$

input resistor must be as large $\Rightarrow R_1 = 1.0\text{M}\Omega$
 $\therefore R_2 = 1.0\text{M}\Omega$

$$V_{\text{in}} = 1.0\text{V}_{\text{rms}}$$

$$V_o = (1.0)(\sqrt{2}) \Rightarrow V_p = V_{\text{rms}} \times \sqrt{2}$$

$$V_o = V_p \times \frac{R_2}{R_1} \times \frac{R_4}{R_3}$$

$$+10 = \frac{\sqrt{2}}{\pi} \left(\frac{1}{R_3} \right) \left(\frac{R_4}{R_4} \right)$$

* if R_3 is $1\text{M}\Omega$ then R_4 would become $1\text{M}\Omega$.
 larger than $1\text{M}\Omega$.

Highest is $10\text{M}\Omega \Rightarrow$ let $R_4 = 1.0\text{M}\Omega$

So, that R_3 is lesser than R_4

$$10 = \frac{\sqrt{2}}{\pi} \left(\frac{1}{R_3} \right) \left(\frac{1 \times 10^6}{R_3} \right)$$

$$R_3 = 45\text{k}\Omega$$

$$\omega = 1/CR_4$$

$$f = 1/2\pi CR_4$$


$$10 = 1/2\pi C(10^6)$$

$$C = 15.9\text{nF}$$




Date: 21/11


PRECISION FULL WAVE RECTIFIER

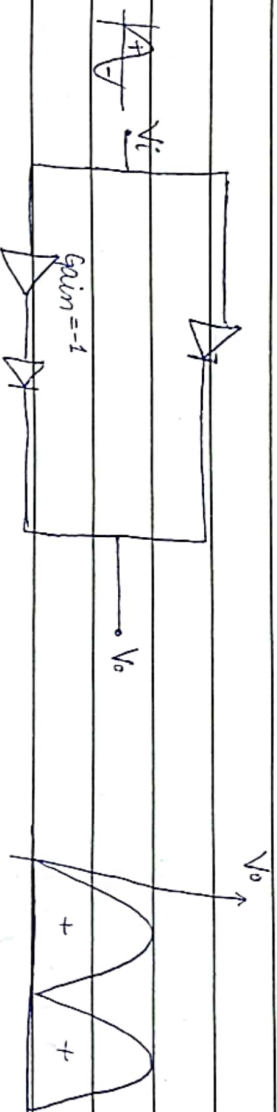

Full-wave rectifier

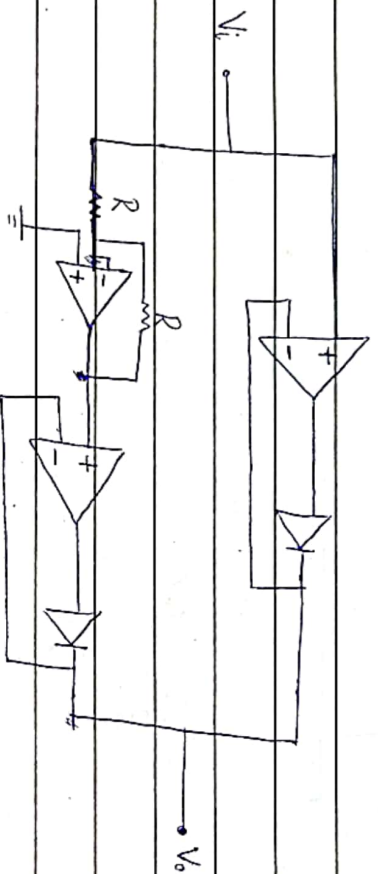

↓


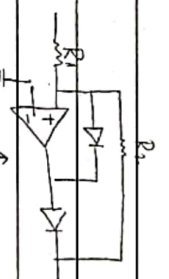


use improved circuit for

-ve half cycle.

and super diode for

+ve half cycle.

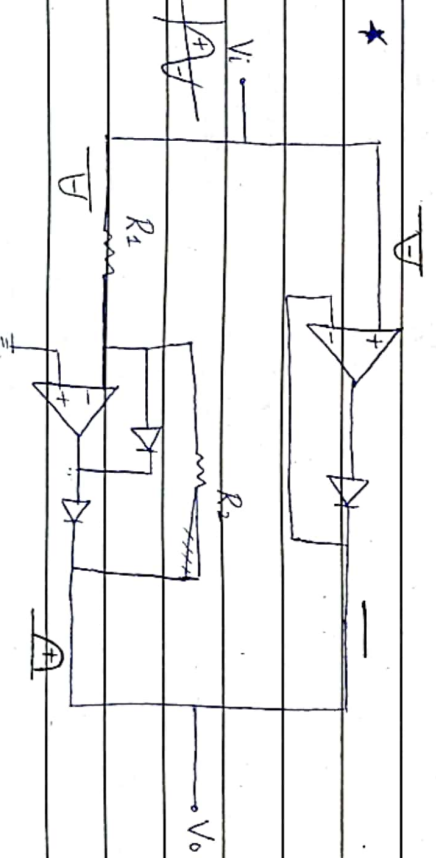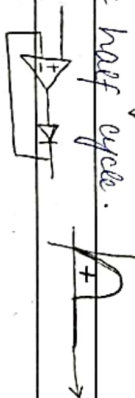


(precision full-wave rectifier)




Date: _____

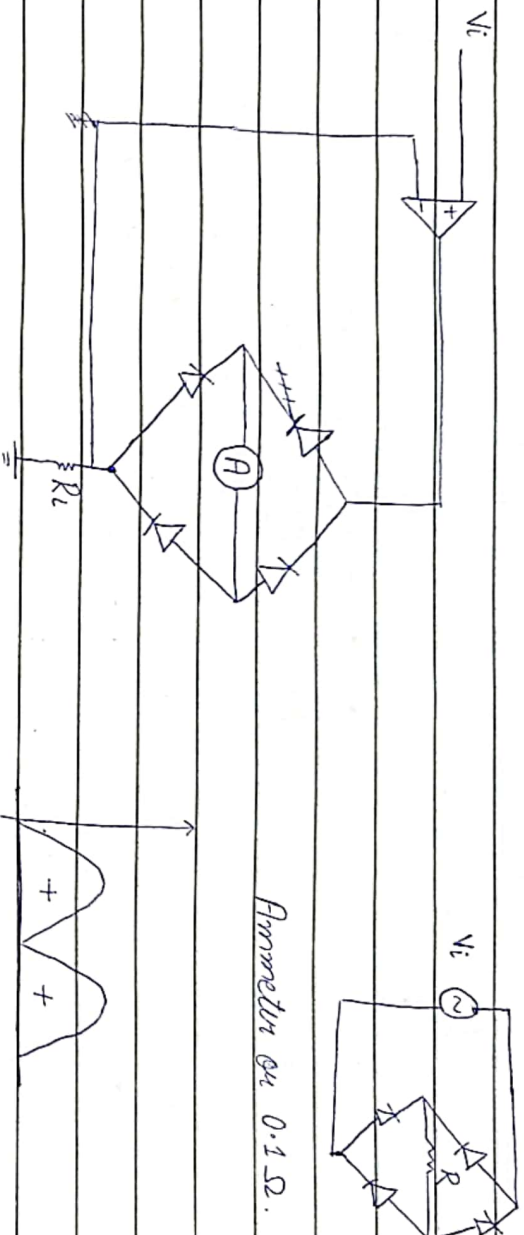full wave rectifier using BRIDGE (INPA) bridge





PEAK RECTIFIER

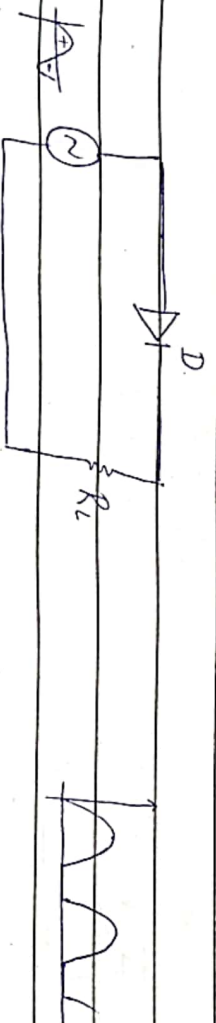

(Half wave)




PRECISION IN PEAK RECTIFIER

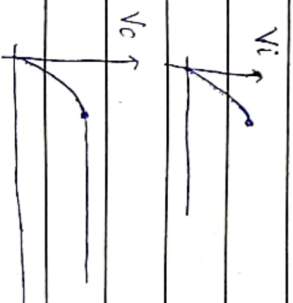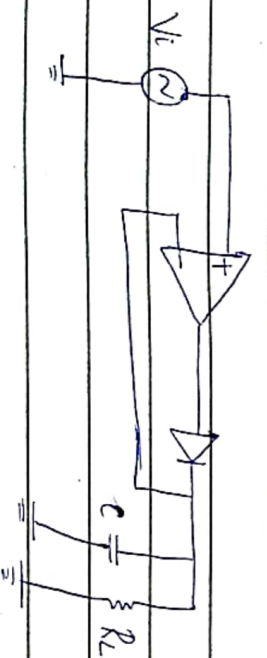


Date: _____


BUFFERED PRECISION RECTIFIER

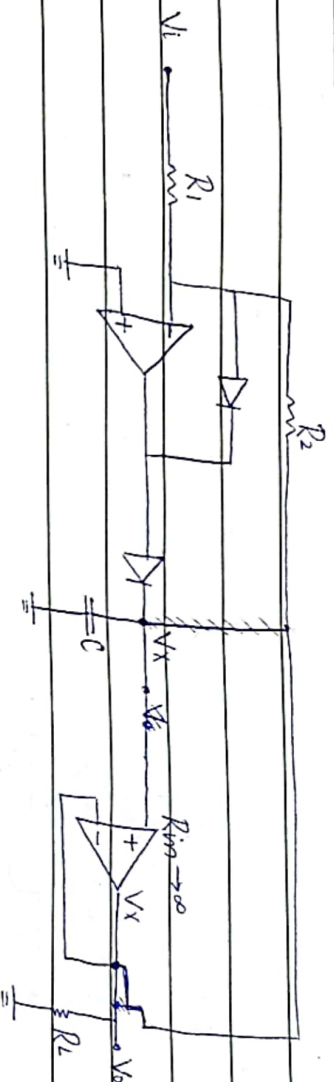

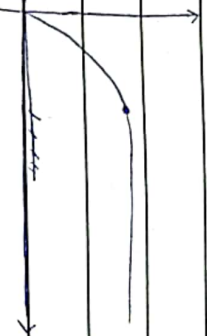* feedback loop is closed
where R_L is connected.




CLAMPER

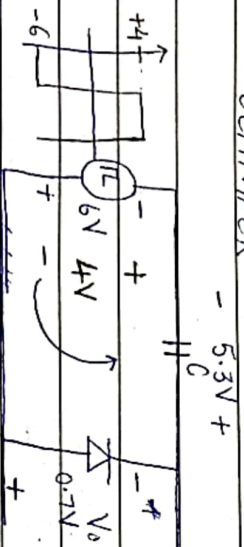


for $-6V$

for $+4V$

overall

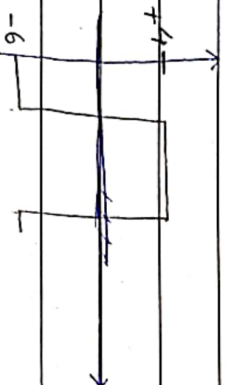

$$10 - 0.7 = 9.3V$$

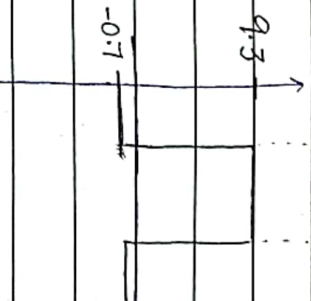

Date: _____

PRECISION CLAMPER

