

Electric Circuit Design (ECD)


Date

DAY-1

- 1) Amplification (o/p is greater than i/p)
- 2) Switching (BJT)
- 3) Buffering (o/p = i/p)
- * 4) Isolation
- 5) Filtering (LP & HP)
- 6) Math operations


$$Z = \frac{200V}{nV}$$

$$= 200V$$

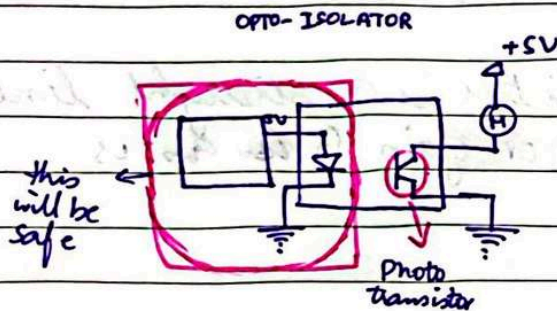


Signal Amplification:

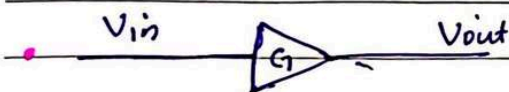- Most practical sensors generate o/p of mV, ~~AV~~, μV , mA, μA .
- Since the signal are very weak, they need to be amplified.



$$V_{out} = G \times V_{in}$$

$$\frac{V_{out}}{V_{in}} = G$$

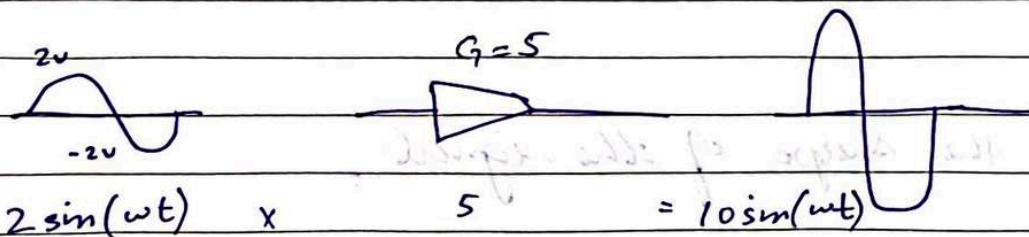

Date

I-VAD


Types of Amplifiers :-

- 1) linear
- 2) Non linear

Linear ::




$$\frac{V_{out}}{V_{in}} = 5$$

$$V_{out} = 5 V_{in}$$

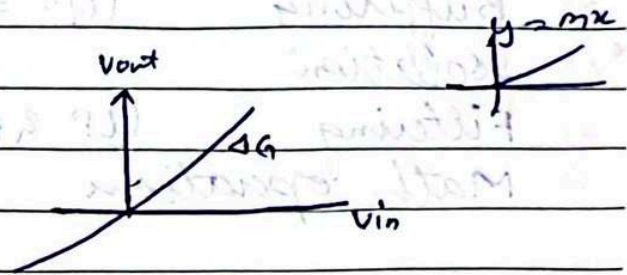

V_{out} vs V_{in} transfer characteristics is a straight line — hence it is a linear amplifier or gain G is constant.

Non-linear ::

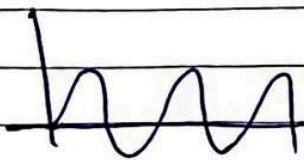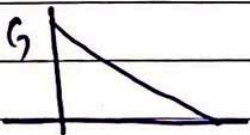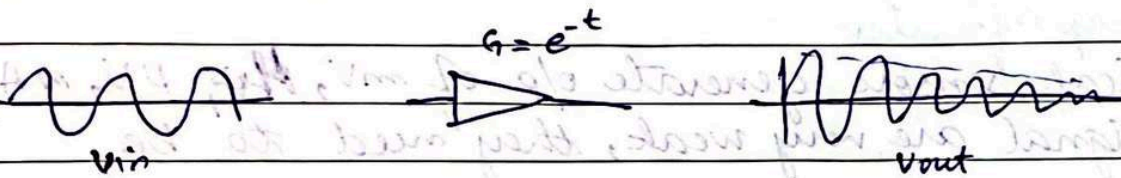

it changes the shape of the signal.

Date

Signal Amplification :-

$$\text{Voltage Amplifier} = \frac{V_{out}}{V_{in}} = A_v \quad (V/V)$$

$$\text{Current AMP} = \frac{I_{out}}{I_{in}} = A_i \quad (A/A)$$

$$\begin{aligned} \text{Power AMP} &= \frac{P_{out}}{P_{in}} = \frac{V_{out} I_{out}}{V_{in} I_{in}} = \left(\frac{V_{out}}{V_{in}} \right) \left(\frac{I_{out}}{I_{in}} \right) = A_v A_i \\ &= A = \left(\frac{W}{W} \right) \end{aligned}$$

DAY-2

Amplification Gains (in dB's)

voltage gain

$$A_v = \frac{V_o}{V_i} \quad (V/V)$$

$$\begin{aligned} A_v(\text{dB}) &= 20 \log |A_v| \\ &= 20 \log |V_o/V_i| \text{ dB} \end{aligned}$$


current gain

$$A_i = \frac{I_o}{I_i} \quad A/A$$

$$\begin{aligned} A_i(\text{dB}) &= 20 \log |A_i| \\ &= 20 \log \left| \frac{I_o}{I_i} \right| \text{ dB} \end{aligned}$$

Power gain :-

$$\begin{aligned} &20 \log |A_v| \\ &20 \log \left| \frac{V_o}{V_i} \right| \end{aligned}$$

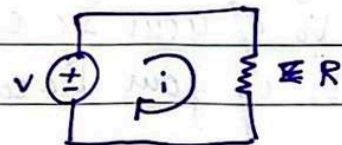

Date

$$= 10 \log \left| \frac{V_o}{V_i} \right|^2$$

$$= 10 \log \left(\frac{V_o^2}{V_i^2} \right)$$

$$= 10 \log \left| \frac{V_o^2/R}{V_i^2/R} \right|$$

$$= 10 \log \left| \frac{P_o}{P_i} \right| \text{ dB}$$

$$A_p = \frac{P_o}{P_i}$$

w/w

$$A_p (\text{dB}) = 10 \log \left| \frac{P_o}{P_i} \right|$$


s-VAD

$$A_v = \frac{V_o}{V_i} < 0 \quad (\text{meaning?}) \quad \text{It means that it is inverted.}$$

$$A_v (\text{dB}) = 20 \log \left| \frac{V_o}{V_i} \right| < 0 \quad (\text{meaning?}) \quad \text{It has been attenuated (lessen the value)}$$

Amplifier Power Supplies & Saturation :-

Max limit of V_{cc}

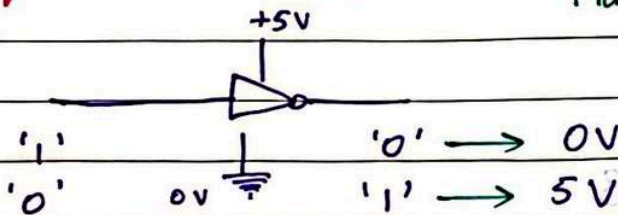

Note:- Logic '1' = $+V_{cc}$ and Logic '0' = ground

Max V_o of your I_c ckt = $+V_{cc}$

Min V_o of your I_c ckt = $-V_{cc}$



Date _____

Ideal Transfer characteristics :-




$$G = \frac{V_o}{V_i} = 5 \quad \left(\begin{array}{l} V_o = 5 V_i \\ y = mx \end{array} \right)$$

$$\pm V_{CC} = \pm 15V$$

$$V_i = 3 \sin(\omega t)$$

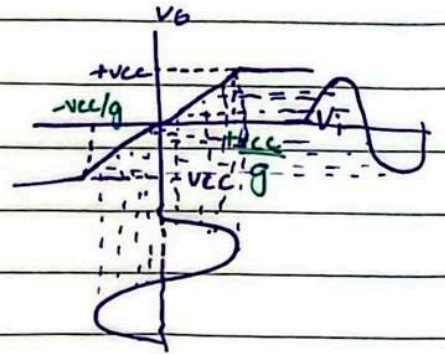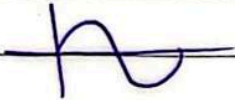

Practical Transfer characteristics :-

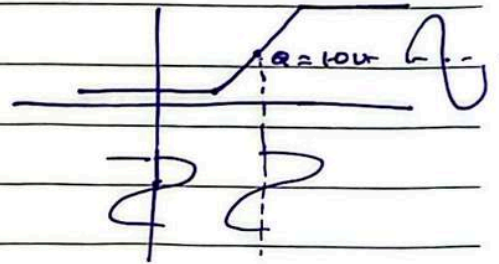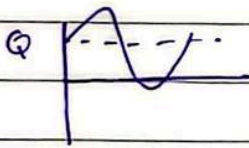
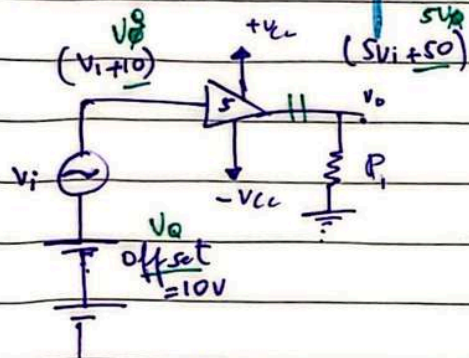


$\therefore$ capacitor blocks DC





$\therefore$ // allows AC

$$V_{CC} = \pm 15V$$

$$V_i = 3 \sin(\omega t)$$

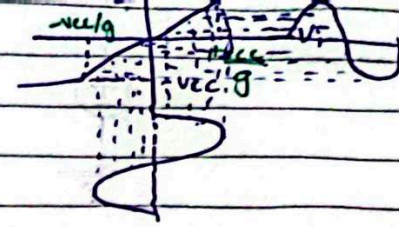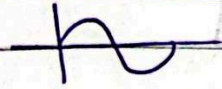

Practical Transfer characteristics :-

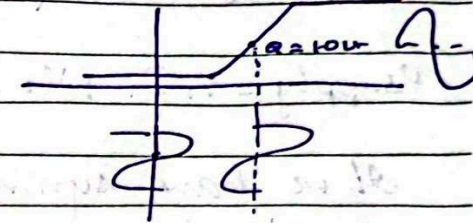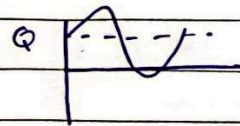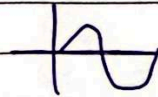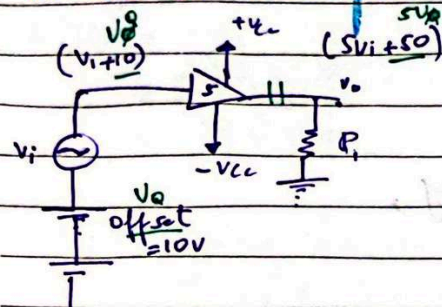


∴ capacitor blocks DC
∴ " allows AC

DAY - 3

QUESTION -

Consider an amplifier operating at $\pm 10V$ power supplies. It is fed sine voltage. Example 1.1.

Date

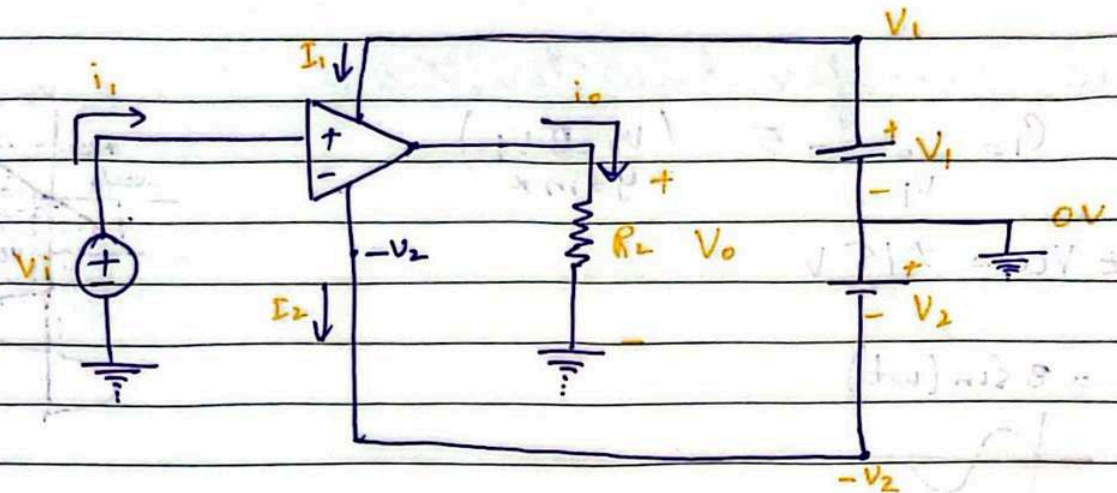

$$P_i = V_i i_i \quad (\text{input})$$

$$P_o = V_o i_o \quad (\text{output})$$

$$P_{\text{supply}} = V_1 I_1 + V_2 I_2 = 2 V_1 I_1$$

If we have symmetrical power supply,
 $V_1 = V_2$
 $I_1 = I_2$

$$i/p = o/p$$

$$P_i + P_{\text{supply}} = P_o + P_{\text{loss}}$$

$$P_{\text{loss}} = P_i + P_{\text{supply}} - P_o$$

$$\eta = \frac{P_o}{P_i + P_{\text{supply}}} \times 100\%$$

E-1AD

Solution of previous Question:

$$V_i = 1 \text{ V}_p \Rightarrow 1/\sqrt{2} \quad V_o = 9 \text{ V}_p = 9/\sqrt{2}$$

$$R_L = 1 \text{ k}\Omega$$

$$V = I R$$

Date

$$i_o = \frac{V_o}{R_o} \Rightarrow \frac{9/\sqrt{2}}{1k} \Rightarrow 6.3 \text{ mA}$$

$$i_i = 0.1 \text{ mA} / \sqrt{2} = 0.0707 \text{ mA}$$

$$a) A_v = \frac{V_o}{V_i} = \frac{9}{1/\sqrt{2}} = 9\sqrt{2} \Rightarrow 20 \log(9) = 19.08 \text{ dB}$$

$$b) A_i = \frac{I_o}{I_i} = \frac{6.3 \text{ mA}}{0.07 \text{ mA}} = 90 \Rightarrow 20 \log(90) = 39.08 \text{ dB}$$

$$c) P_i = V_i I_i \\ = (1/\sqrt{2})(0.1 \text{ mA} / \sqrt{2}) \\ = 0.05 \text{ mW}$$

$$P_o = V_{o, \text{rms}} I_{o, \text{rms}} \\ = \left(\frac{9}{\sqrt{2}} \right) (6.3 \text{ mA}) \\ = 40.5 \text{ mW}$$

$$A_p = \frac{P_o}{P_i} = \frac{40.5 \text{ mW}}{0.05 \text{ mW}} = 810 \text{ W/W} \quad \text{or} \quad A_p = A_v A_i \\ \Rightarrow 10 \log(810) = 29.08 \text{ dB}$$

$$P_{\text{supply}} = 2 \times 10 \times 9.3 \text{ m} \\ = 190 \text{ mW}$$

$$P_{\text{loss}} = P_{\text{supply}} + P_i - P_o \\ = 190 \text{ m} + 0.05 \text{ m} - 40.5 \text{ m} \\ = 149.55 \text{ mW}$$

Date



$$\eta = \frac{40.5 \text{ m}}{190 + 0.05} \times 100$$
$$= 21.3\%$$

Note :-

- Always convert units of A_v , A_i & A_p into dB.
- Use the correct method to find A_p and recheck your answer by using the formula $A_p = A_v A_i$.
- Convert AC voltages and currents to DC or rms.

Circuit Model For Amplifiers :-

1. Voltage Amplifier :-

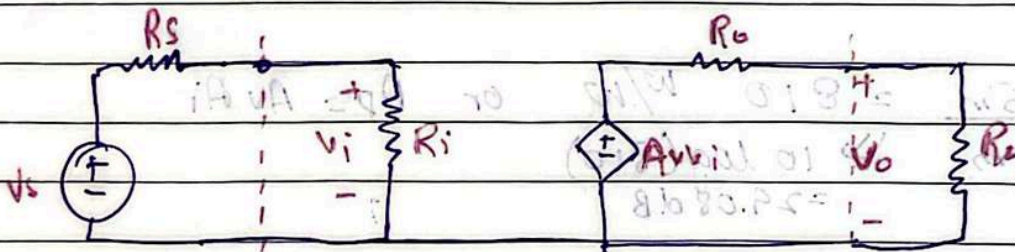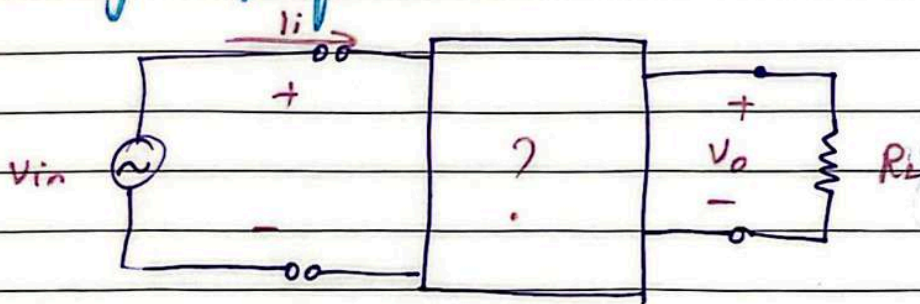

R_i accounts for the fact that amplifier draws a finite input current from the input voltage source.

$$R_s \ll R_i$$

ideally $R_i \rightarrow \infty$

Date

N-VAC

$$R_o \lll R_L$$

Ideally $R_o = 0$

Finding expressions :-



$$V_i = \left(\frac{R_i}{R_i + R_s} \right) V_s \rightarrow \textcircled{1}$$

$$V_o = \left(\frac{R_L}{R_o + R_L} \right) A_{v_o} V_i \rightarrow \textcircled{2}$$

$$V_o = A_{v_o} \left(\frac{R_L}{R_o + R_L} \right) \left(\frac{R_i}{R_i + R_s} \right) V_s$$

$$\boxed{G = \frac{V_o}{V_s} = A_{v_o} \left(\frac{R_L}{R_L + R_o} \right) \left(\frac{R_i}{R_i + R_s} \right)}$$

Loading Effect :-

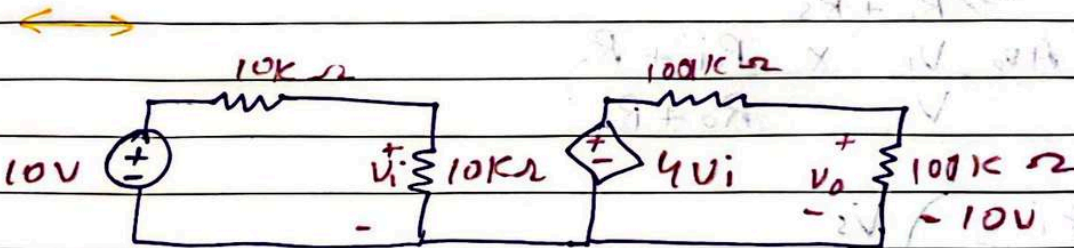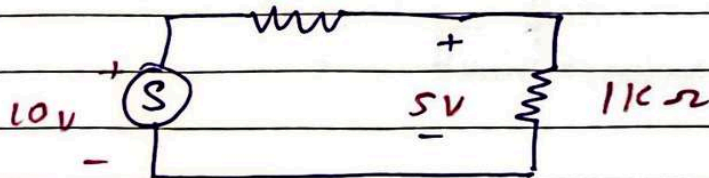


$$\frac{V_o}{V_s} = 4 \left(\frac{100k}{100k + 100k} \right) \left(\frac{10k}{10k + 10k} \right)$$
$$= 4 (0.5)(0.5)$$

$$\frac{V_o}{V_s} = 1 \Rightarrow V_o = V_s = 10V$$

Date

DAY-4

Voltage Amplifier :-

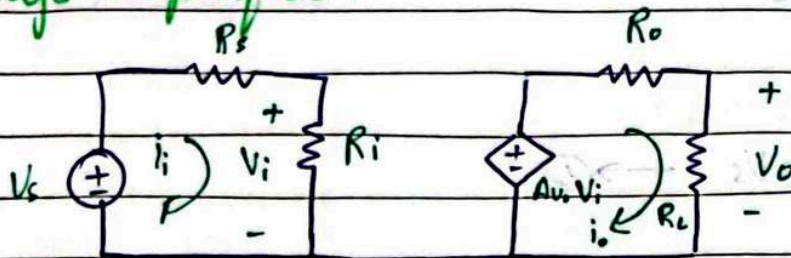

$$G = \frac{V_o}{V_s} = A_v \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{R_L}{R_o + R_L} \right)$$

Current Gain :-

$$\frac{i_o}{i_i} = ?$$

$$i_o = \frac{A_v V_i}{R_o + R_L}$$

$$i_i = \frac{V_s}{R_i + R_s}$$

$$\frac{i_o}{i_i} = \frac{A_v V_i / (R_o + R_L)}{V_s / (R_i + R_s)}$$

$$\frac{i_o}{i_i} = A_v \frac{V_i}{V_s} \times \frac{R_i + R_s}{R_o + R_L} \rightarrow \textcircled{1}$$

Now

$$V_i = \left(\frac{R_i}{R_i + R_s} \right) V_s$$

$$\frac{V_i}{V_s} = \frac{R_i}{R_i + R_s}$$

putting in ①

Date

$$= A_{V_o} \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{R_i + R_s}{R_o + R_L} \right)$$

$$\frac{i_o}{i_i} = A_{V_o} \left(\frac{R_i}{R_o + R_L} \right) \quad (\text{Sir does not like this method.})$$

Preferable Method:-

$$G = \frac{V_o}{V_s} = A_{V_o} \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{R_L}{R_o + R_L} \right) \quad (V/V)$$

$$\frac{i_o}{i_i} = \frac{V_o/R_L}{V_s/R_s + R_i} \quad (\text{using ohm's law})$$

$$= \left(\frac{V_o}{V_s} \right) \left(\frac{R_s + R_i}{R_L} \right)$$

$$= A_{V_o} \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{R_L}{R_o + R_L} \right) \left(\frac{R_s + R_i}{R_L} \right)$$

$$\frac{i_o}{i_i} = A_{V_o} \left(\frac{R_i}{R_o + R_L} \right) \quad (A/A)$$

Now finding V_o/i_i ?

$$\frac{V_o}{i_i} = \frac{V_o}{V_s/R_i + R_s} = \left(\frac{V_o}{V_s} \right) (R_i + R_s) \quad (V/A)$$

$$\frac{i_o}{V_s} = \frac{A_{V_o} V_o/R_L}{V_s} = \left(\frac{V_o}{V_s} \right) \left(\frac{1}{R_L} \right) \quad (A/V)$$

~~Cascade~~

Cascade Amplifier..


On the next page

Date

stage 1

stage 2

stage 3

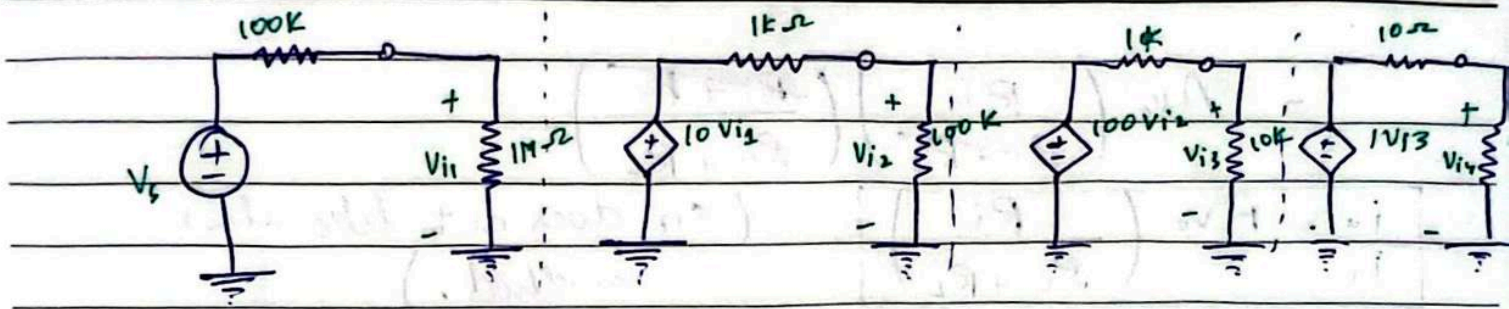

$$\frac{V_o}{V_{i3}} = \frac{100}{110} \Rightarrow 0.909 \quad (\text{V/V})$$

$$\frac{V_{i3}}{V_{i2}} = 100 \left(\frac{10k}{1k + 10k} \right) \Rightarrow 90.909 \quad (\text{V/V})$$

$$\frac{V_{i2}}{V_{i1}} = 10 \left(\frac{100k}{101k} \right) \Rightarrow 9.900 \quad (\text{V/V})$$

$$\frac{V_{i1}}{V_s} = \frac{1M}{1.1M} \Rightarrow 0.9090$$

$$\frac{V_o}{V_s} = \frac{V_o}{V_{i3}} \times \frac{V_{i3}}{V_{i2}} \times \frac{V_{i2}}{V_{i1}} \times \frac{V_{i1}}{V_s}$$

$$\frac{V_o}{V_s} = 743.6 \quad (\text{V/V}) \quad \text{or} \quad 57.4 \text{ dB}$$

$$\frac{V_o}{V_{i1}} = \frac{V_o}{V_{i3}} \times \frac{V_{i3}}{V_{i2}} \times \frac{V_{i2}}{V_{i1}}$$

$$\frac{V_o}{V_{i1}} = 818.0 \quad (\text{V/V}) \quad \text{or} \quad 58.25 \text{ dB}$$

$$\frac{i_o}{i_{i1}} = \frac{V_o/R_L}{V_{i1}/R_{i1}}$$

$$= \left(\frac{V_o}{V_{i1}} \right) \left(\frac{R_{i1}}{R_L} \right)$$

Date

$$= (818.0) \left(\frac{1M}{100} \right)$$

$$= 818 \times 10^4 \quad (A/A) \quad \text{or} \quad 138.25 \text{ dB}$$

$$A_p = A_v A_i$$

$$= \left(\frac{V_o}{V_{i_1}} \right) \left(\frac{i_o}{i_{i_1}} \right)$$


$$= 6.69 \times 10^9$$

$$= 6.69 \text{ GW} \quad \text{or} \quad 98.25 \text{ dB}$$

Four Amplifier Models:


- 1- Voltage Amplifier
- 2- Current Amplifier
- 3- Trans-Resistance
- 4- Trans-conductance

Voltage Amplifier:

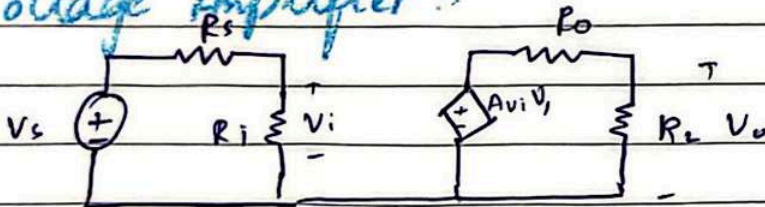

$$\frac{V_o}{V_s} = A_{v_o} \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{R_L}{R_o + R_L} \right)$$

Current Amplifier:

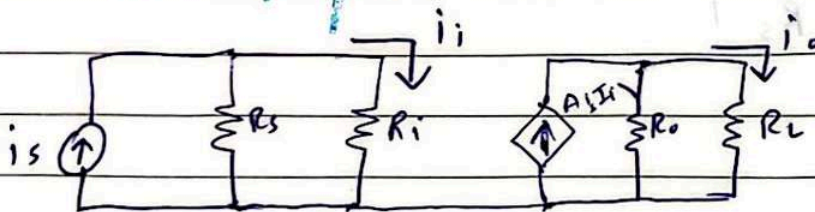

Date

$$i_i = \left(\frac{R_s}{R_s + R_i} \right) i_s$$

$$i_o = \left(\frac{R_o}{R_o + R_L} \right) A i_s i_i$$

$$\frac{i_o}{i_i} = A i_s \left(\frac{R_o}{R_o + R_L} \right) \left(\frac{R_s}{R_s + R_i} \right)$$


$$V_o = i_o R_L$$

$$V_i = i_s (R_i \parallel R_s)$$

$$\frac{V_o}{V_i} = \left(\frac{i_o}{i_s} \right) \left(\frac{R_L (R_i + R_s)}{R_i R_s} \right)$$

Trans-Resistance Amplifier :-

V_o / I_s

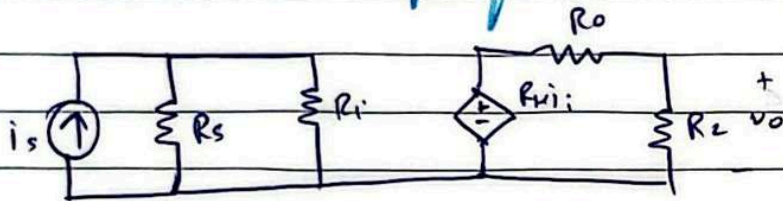

input current
output voltage

$$\frac{V_o}{I_s}$$


$$V_o = \left(\frac{R_L}{R_L + R_o} \right) R_m i_i$$

$$i_i = \left(\frac{R_s}{R_i + R_s} \right) i_s$$

$$\frac{V_o}{i_s} = R_m \left(\frac{R_L}{R_o + R_L} \right) \left(\frac{R_s}{R_i + R_s} \right)$$

Date

Trans-conductance Amp :- I_o/V_s

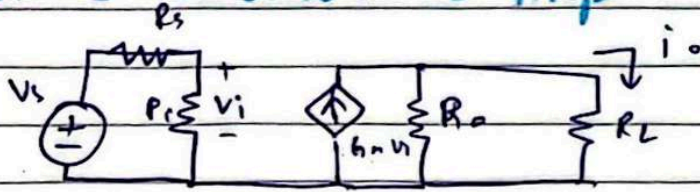


$$I_o = \left(\frac{R_o}{R_o + R_L} \right) g_m V_i$$

$$V_i = \left(\frac{R_i}{R_s + R_i} \right) V_s$$

$$\frac{I_o}{V_i} = g_m \left(\frac{R_o}{R_o + R_L} \right) \left(\frac{R_i}{R_s + R_i} \right)$$

Date

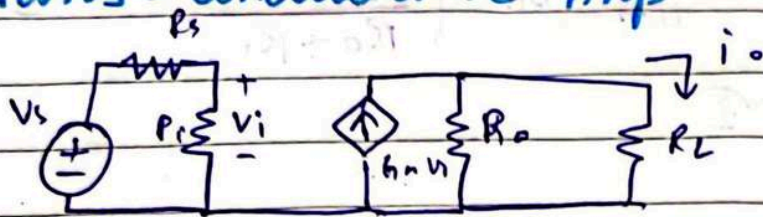Trans - conductance Amp $\therefore i_o/v_s$




$$i_o = \left(\frac{R_o}{R_o + R_L} \right) g_m V_i$$

$$V_i = \left(\frac{R_i}{R_s + R_i} \right) V_s$$

$$\frac{i_o}{V_i} = g_m \left(\frac{R_o}{R_o + R_L} \right) \left(\frac{R_i}{R_s + R_i} \right)$$

DAY-5

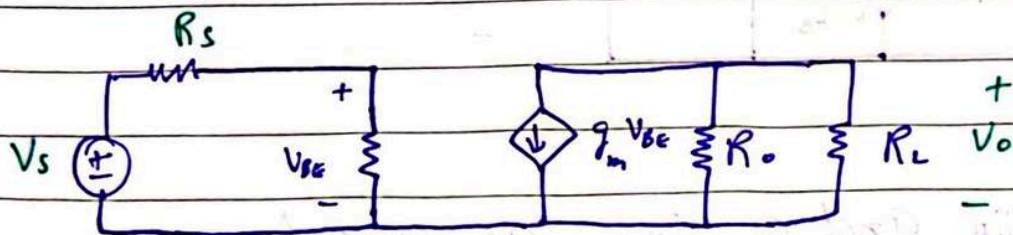BJT Model $\therefore$ (Transconductance Amp)



$$R_s = 5K\Omega$$

$$R_{\pi} = 2.5K\Omega$$

$$g_m = 40m \text{ (A/V)}$$

$$R_o = 100K\Omega$$

$$R_L = 5K\Omega$$

$$\frac{V_o}{V_s} = ?$$

Sol:-

Applying ohm's law to second part of circuit.

Date

$$V_o = -g_m V_{BE} (R_o \parallel R_L) = -g_m V_{BE} \left(\frac{R_o R_L}{R_o + R_L} \right) \rightarrow \textcircled{1}$$

$$V_{BE} = \left(\frac{r_\pi}{r_\pi + R_s} \right) V_s \rightarrow \textcircled{2}$$

Substitute $\textcircled{2}$ in $\textcircled{1}$

$$V_o = -g_m \left(\frac{r_\pi}{r_\pi + R_s} \right) V_s \left(\frac{R_o R_L}{R_o + R_L} \right)$$


$$\frac{V_o}{V_s} = -g_m \left(\frac{r_\pi}{r_\pi + R_s} \right) \left(\frac{R_o R_L}{R_o + R_L} \right)$$

putting the values

$$\frac{V_o}{V_s} = -63.5 \text{ V/V}$$

2-VAC

BJT Model: (current Amp)

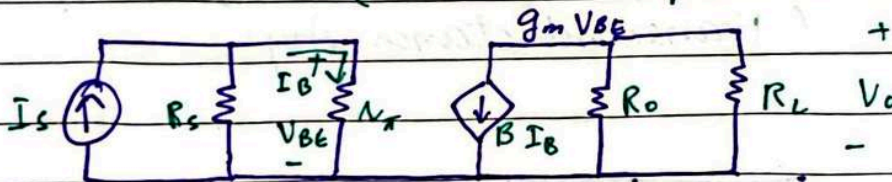

Sol.


Considering $B I_B$ and $g_m V_{BE}$ are equal

$$g_m V_{BE} = B I_B$$


$$B = g_m \left(\frac{V_{BE}}{I_B} \right) \Rightarrow g_m (r_\pi)$$

HOME TASK:- Find $\frac{I_o}{V_s}$ for T.C.A

QUESTION :-

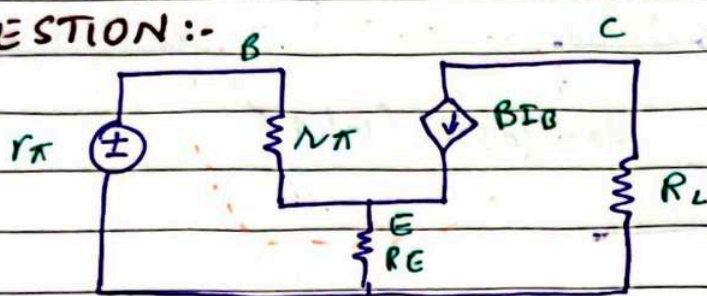

(Actual circuit)

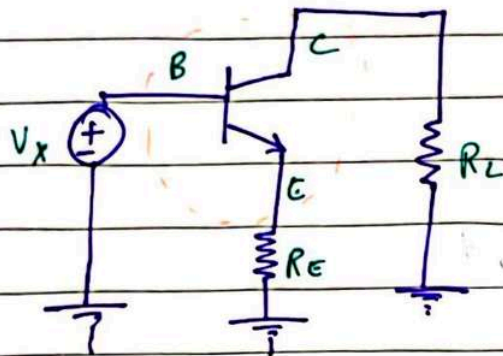

(Explained circuit)

Find internal resistance of this amplifier

Sol :-

$$\frac{V_x}{i_x} = R_{in}$$

$$V_x = V_i + V_o$$

$$= I_B r_\pi + (I_B + \beta I_B) R_E$$

$$= I_B (r_\pi + (1 + \beta) R_E)$$

$$\frac{V_x}{I_B} = r_\pi + (1 + \beta) R_E$$

$$i_x = I_B$$


$$\frac{V_x}{I_x} = r_\pi + (1 + \beta) R_E = R_{in}$$

Frequency Response of Amplifiers :-

NEXT PAGE (👉)

Date

$$V_i = V_i \sin(\omega t)$$



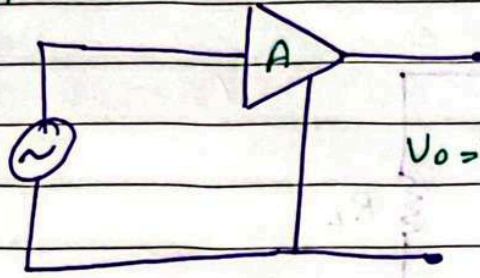


$$V_o = V_o \sin(\omega t + \phi)$$

Four Axioms:-

- Frequency is constant
- Shape of waveform is constant
- Amplitude is changing
- Phase angle is changing

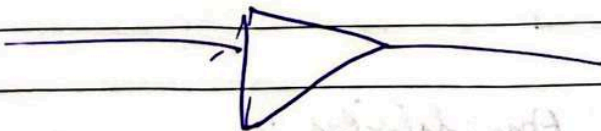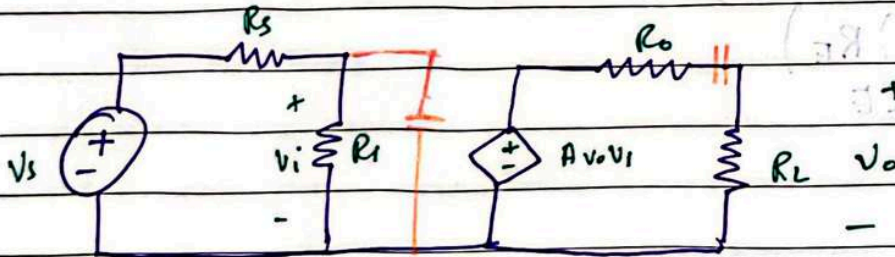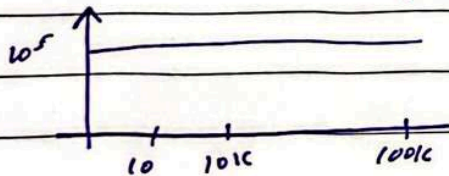Magnitude / gain of an "ideal" voltage Amp.




Mag. / gain of a real Voltage Amp:-


DAY-2

Single Time Constant Circuits:-

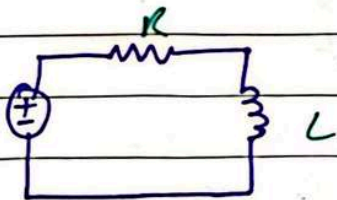Those circuits that have only one time constant



$$\tau = LR$$

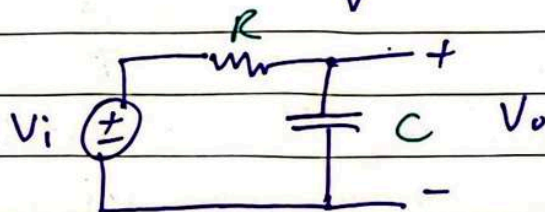


$$\tau = RC$$

$$X_C = \frac{1}{j\omega C}$$


(using this circuit)

$$\omega = 0 ; X_C \rightarrow \infty ; V_o = V_i$$

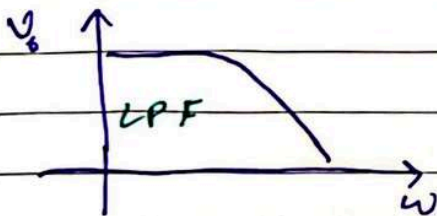
$$\omega = \infty ; X_C \rightarrow 0 ; V_o = 0$$





Changing the circuit

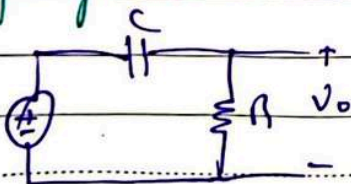

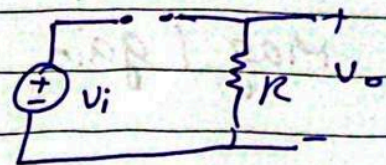$\omega \rightarrow 0$; $X_C \rightarrow \infty$; $V_o = 0$ (small)





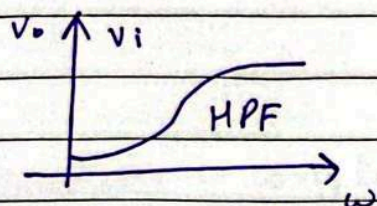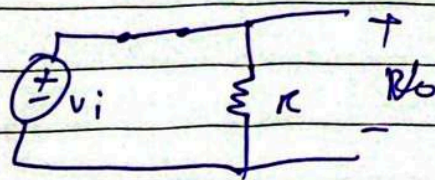$\omega = \infty$, $X_C \rightarrow 0$; $V_o = V_i$



DAY-6 (chapter 5)

Operational Amplifier :-

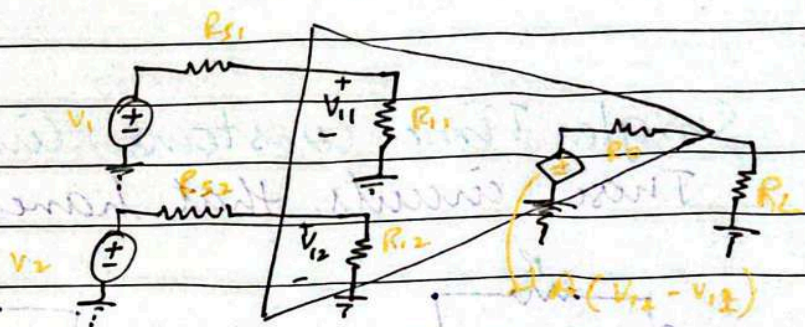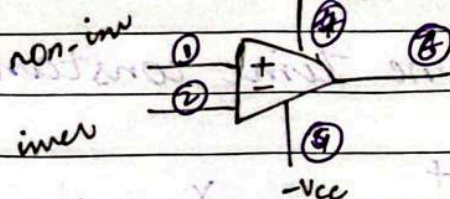

- a) An operational amplifier is used as a voltage amp. and is used to amplify the difference between inv. & non-inv voltage input (V_1 & V_2)

$$V_o = A (V_2 - V_1)$$

- b) Input current from signal V_1 & V_2 is **Zero**.
OP-AMP does not draw any current from V_1 & V_2 .

$$R_{i1} \rightarrow \infty$$

$$R_{i2} \rightarrow \infty$$

- c) $R_o = 0$

- Common mode rejection is ideally zero but practically it is non-zero.

$$V_o = A(V_2 - V_1) \Rightarrow A_o = \frac{V_o}{V_2 - V_1}$$

$$A_{cm} = \frac{V_o}{V_i} \rightarrow 0$$


$$CMRR = 20 \log \left| \frac{A_D}{A_{cm}} \right| \rightarrow \infty$$

d) C_i & C_o ^{DC} coupled

e) $CMRR \rightarrow \infty$
(Ideally)

f) $A \rightarrow \infty$
(Ideally)
 $A \rightarrow \omega^s \text{ V/V}$
(Practical)

g) Infinite bandwidth

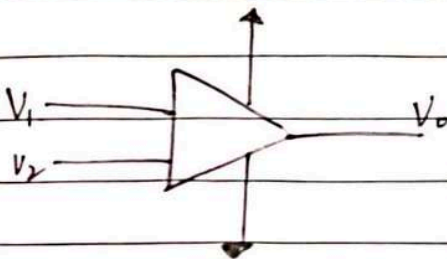

OP-AMP two way:-

- 1) Open-loop $\times$ Can only be used
- 2) Closed loop $\checkmark$

Date

If $V_1 = 1$ & $V_2 = 2$

$$V_o = A(V_2 - V_1) \\ = 10^5(2 - 1) \\ = 10^5 V \Rightarrow 5V$$

If $V_1 = 2$ & $V_2 = 1$

$$V_o = A(V_2 - V_1) \\ = A(1 - 2) \\ = -10^5 V \Rightarrow 0V$$

Simply


$$V_+ > V_- : V_o = +V_{cc}$$

$$V_- > V_+ : V_o = -V_{cc}$$

* In Open loop configuration an OP-AMP can only be used as comparator and you cannot adjust the gain as per your choice

* In closed loop design becomes more flexible and you can change the gain as per your choice.

INVERTING AMPLIFIER:-

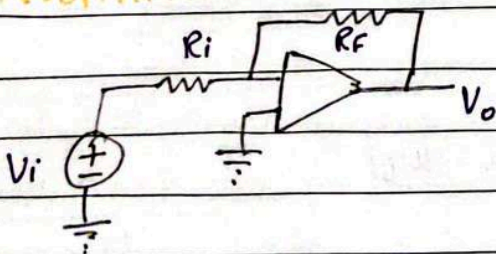

Case 1:- (A $\rightarrow\infty$)

$$V_o = A(V_+ - V_-)$$

Date

$$V_+ - V_- = \frac{V_o}{A}$$

$$A \rightarrow \infty, \frac{V_o}{A} \rightarrow 0$$

$$V_+ - V_- = 0$$

$$V_+ = V_- \quad (\text{Virtual Short Circuit})$$

Note: If the loop is closed, $V_+ = V_-$
(Ohm's Law)

$$V_+ = 0V$$

$$V_- = 0V$$

$$I_i = \frac{V_i - 0}{R_i} = \frac{V_i}{R_i} \rightarrow \textcircled{1}$$

$\therefore$ Current flows from higher to lower potential

$$0 - V_o = I_i R_f$$

$$V_o = -I_i R_f \rightarrow \textcircled{2}$$

Substitute $\textcircled{2}$ in $\textcircled{1}$

$$V_o = -\left(\frac{V_i}{R_i}\right) R_f$$

$$\frac{V_o}{V_i} = -\left(\frac{R_f}{R_i}\right) = G$$

(Node Voltage)

$$\frac{0 - V_i}{R_i} + \frac{0 - V_o}{R_f} = 0$$

$$-\frac{V_i}{R_i} - \frac{V_o}{R_f} = 0$$

$$\frac{V_o}{R_f} = -\frac{V_i}{R_i}$$

Date

$$\frac{V_o}{V_i} = -\frac{R_F}{R_i}$$

Case 2:- ($A \rightarrow \text{Finite}$)

$$V_o = A(V_+ - V_-)$$

$$V_+ - V_- = \frac{V_o}{A}$$

$A \rightarrow \text{finite}$

$$V_- = V_+ - \frac{V_o}{A}$$

$$V_+ = 0$$

$$V_- = -\frac{V_o}{A}$$

$$\frac{-V_o/A - V_i}{R_i} + \frac{-V_o/A - V_o}{R_F} = 0$$

$$\frac{-V_o}{AR_i} - \frac{V_i}{R_i} - \frac{V_o}{AR_F} - \frac{V_o}{R_F} = 0$$

$$\frac{-V_o}{AR_i} - \frac{V_o}{AR_F} - \frac{V_o}{R_F} = \frac{V_i}{R_i}$$

$$V_o \left(\frac{1}{AR_i} + \frac{1}{AR_F} + \frac{1}{R_F} \right) = -\frac{V_i}{R_i}$$

$$V_o \left(\frac{1}{A} \left(\frac{1}{R_i} + \frac{1}{R_F} \right) + \frac{1}{R_F} \right) = -\frac{V_i}{R_i}$$

Multiply ' R_F ' on both sides of eq

$$V_o \left(\frac{1}{A} \left(\frac{R_F}{R_i} + 1 \right) + 1 \right) = \left(-\frac{R_F}{R_i} \right) V_i$$


$$\frac{V_o}{V_i} = \frac{-R_F/R_i}{1 + \frac{1}{A} \left(1 + \frac{R_F}{R_i} \right)} = G$$

$$\frac{V_o}{V_i} = \frac{-R_F/R_i}{1 + \frac{1}{A} \left(1 + \frac{R_F}{R_i} \right)}$$

Date

DAY-7

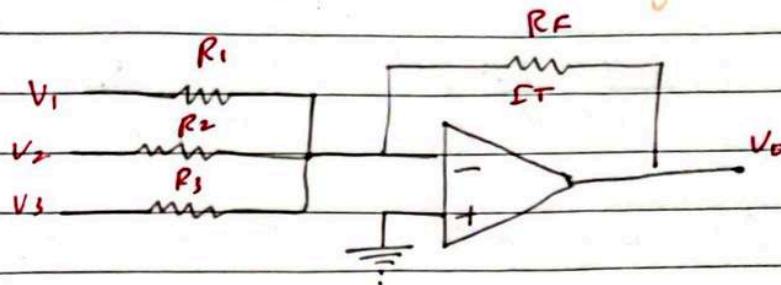Implementing Addition of multiple signals (Weighted Summing Amplifier)



$$I_1 = \frac{V_1}{R_1}, \quad I_2 = \frac{V_2}{R_2}, \quad I_3 = \frac{V_3}{R_3}$$

$$I_T = I_1 + I_2 + I_3$$

$$I_T = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \rightarrow \textcircled{1}$$

$$0 - V_0 = I_T R_F$$

$$V_0 = -I_T R_F \rightarrow \textcircled{2}$$

Substitute $\textcircled{2}$ in $\textcircled{1}$

$$V_0 = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$\therefore V_0 = - \left(\left[\frac{R_F}{R_1} \right] V_1 + \left[\frac{R_F}{R_2} \right] V_2 + \left[\frac{R_F}{R_3} \right] V_3 \right)$$


$$V_0 = - (2V_1 + 3V_2 + 6V_3)$$

$$R_F = R_1 = R_2 = R_3 = 10K$$

$$V_0 = - (V_1 + V_2 + V_3)$$

$$V_0 = -V_1 - V_2 - V_3$$

Bss samhaya tha

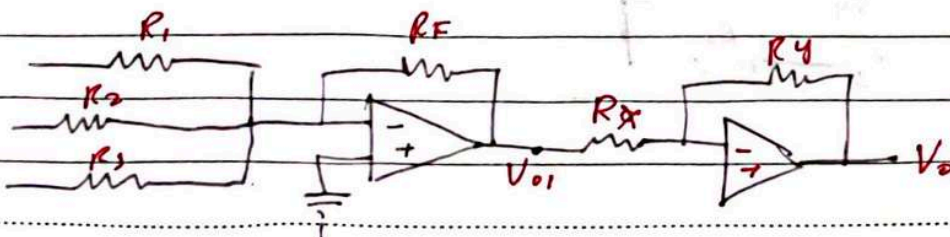

Date

F-VAD

$$V_{O1} = - \left[\left(\frac{R_F}{R_1} \right) V_1 + \left(\frac{R_F}{R_2} \right) V_2 + \left(\frac{R_F}{R_3} \right) V_3 \right]$$

$$V_O = - \left(\frac{R_y}{R_x} \right) V_{O1}$$

$$= + \left(\frac{R_y}{R_x} \right) \left(\frac{R_F}{R_1} \right) V_1 + \left(\frac{R_y}{R_x} \right) \left(\frac{R_F}{R_2} \right) V_2 + \left(\frac{R_y}{R_x} \right) \left(\frac{R_F}{R_3} \right) V_3$$


→ If you want to have a +ve gain, add two op-amps.

→ If you want a simpler expression, make $R_y = R_x$.

Implementing Addition / Subtraction circuit ::

→ In case of addition & subtraction, we will use a two stage amplifier design. All those voltages that have to be added will be applied at inverting terminal of stage 1. All those inputs that have to be subtracted will be applied at inverting terminal of 2nd op-amp.
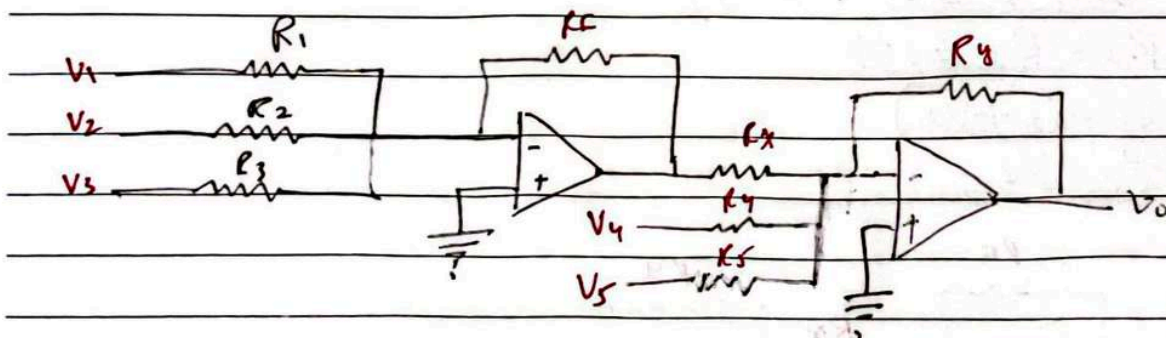
$$V_O = \alpha V_1 + \beta V_2 + \gamma V_3 - \epsilon V_4 - \phi V_5$$



Date

$$V_{o1} = - \left(\frac{R_F}{R_1} \right) V_1 - \left(\frac{R_F}{R_2} \right) V_2 - \left(\frac{R_F}{R_3} \right) V_3 \rightarrow \textcircled{1}$$

$$V_o = - \left(\frac{R_y}{R_n} \right) V_{o1} - \left(\frac{R_y}{R_4} \right) V_4 - \left(\frac{R_y}{R_5} \right) V_5 \rightarrow \textcircled{2}$$

put ① in ②

$$V_o = - \left(\frac{R_y}{R_n} \right) \left[- \left(\frac{R_F}{R_1} \right) V_1 - \left(\frac{R_F}{R_2} \right) V_2 - \left(\frac{R_F}{R_3} \right) V_3 \right] - \left(\frac{R_y}{R_4} \right) V_4 - \left(\frac{R_y}{R_5} \right) V_5$$


$$= \left(\frac{R_y R_F}{R_n R_1} \right) V_1 + \left(\frac{R_y R_F}{R_n R_2} \right) V_2 + \left(\frac{R_y R_F}{R_n R_3} \right) V_3 - \left(\frac{R_y}{R_4} \right) V_4 - \left(\frac{R_y}{R_5} \right) V_5$$

$$\propto V_1 + B V_2 + 8 V_3 - 6 V_4 - 4 V_5$$

Design a circuit that performs this equation.

$$V_o = 2 V_1 + 8 V_2 - 5 V_3 - 6 V_4 - 4 V_5$$

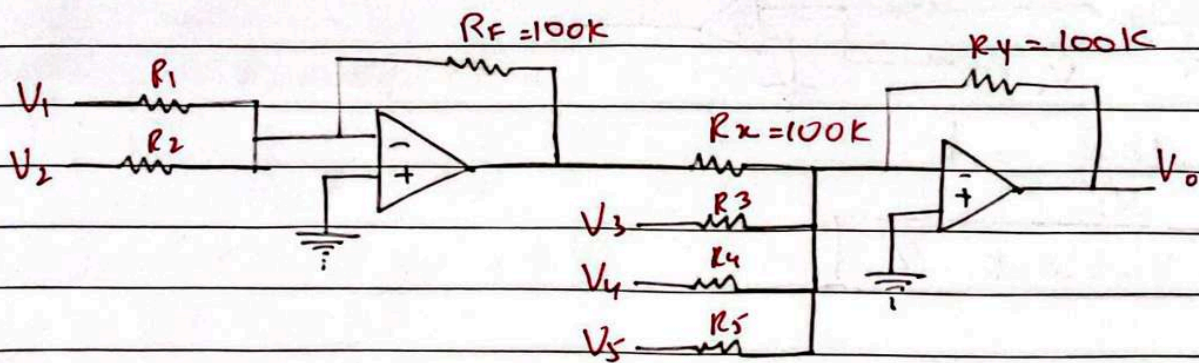You are required to use only 100 kΩ on the feedback.



$$V_o = \left(\frac{R_y R_F}{R_n R_1} \right) V_1 + \left(\frac{R_y R_F}{R_n R_2} \right) V_2 - \left(\frac{R_y}{R_3} \right) V_3 - \left(\frac{R_y}{R_4} \right) V_4 - \left(\frac{R_y}{R_5} \right) V_5$$

$$\frac{R_y}{R_5} = 4 \Rightarrow \frac{100k}{R_5} = 4 \Rightarrow R_5 = 25k \Omega$$

Date

$$\frac{R_y}{R_u} = 6 \Rightarrow \frac{100k}{R_u} = 6 \Rightarrow R_u = 16.66k \Omega$$

$$\frac{R_y}{R_s} = 5 \Rightarrow \frac{100k}{R_s} = 5 \Rightarrow R_s = 20k \Omega$$

$$\frac{R_y}{R_u} \cdot \frac{R_F}{R_2} = 8$$


$$\frac{100k}{100k} \cdot \frac{100k}{R_2} = 8$$

$$R_2 = 12.5k \Omega$$

$$\frac{R_y}{R_u} \cdot \frac{R_F}{R_1} = 2$$

$$\frac{100k}{100k} \cdot \frac{100k}{R_1} = 2$$

$$R_1 = 50k \Omega$$

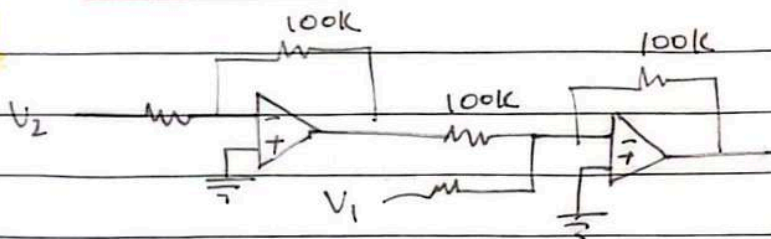

$$(V_0 = V_2 - V_1)$$

∴ Difference amplifier

$$\frac{100k}{100k} \cdot \frac{100k}{V_2} = 1$$


$$V_2 = 100k \Omega$$

$$\frac{100k}{V_1} = 1$$

$$V_1 = 100k$$

Date

NON-INVERTING AMP.

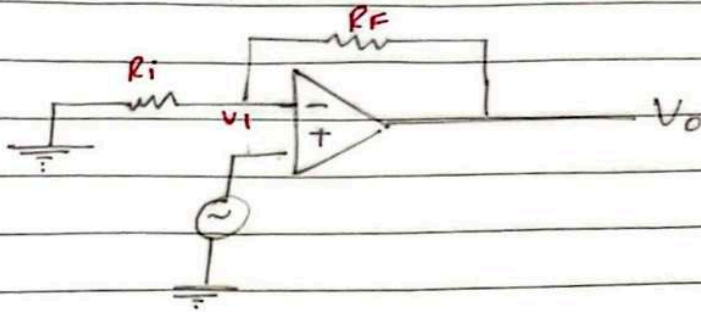

($A \rightarrow \infty$)

$$V_o = A (V_+ - V_-)$$

$$\frac{V_o}{A} = V_+ - V_-$$

$$V_+ - V_- = 0$$

$$V_+ = V_-$$

Case 1:-

$$0 + \frac{V_i - 0}{R_i} + \frac{V_i - V_o}{R_f} = 0$$

$$\frac{V_i}{R_i} + \frac{V_i}{R_f} = \frac{V_o}{R_f}$$

$$V_i \left(\frac{1}{R_i} + \frac{1}{R_f} \right) = \frac{V_o}{R_f}$$

$$V_o = \left(\frac{R_f}{R_i} + \frac{R_f}{R_f} \right) V_i$$

$$\boxed{\frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}}$$

Case 2:-

$$I_1 = \frac{V_i - 0}{R_i} = \frac{V_i}{R_i}$$

Date

$$= \frac{V_o - V_i}{R_F} = I_i$$

$$\frac{V_o}{R_F} - \frac{V_i}{R_F} = \frac{V_i}{R_i}$$

$$\frac{V_o}{R_F} = \frac{V_i}{R_i} + \frac{V_i}{R_F}$$

$$\boxed{\frac{V_o}{V_i} = 1 + \frac{R_F}{R_i}}$$

A → Finite

$$V_o = A (V_+ - V_-)$$

$$V_+ - V_- = \frac{V_o}{A}$$

$$V_- = V_+ - \frac{V_o}{A}$$

Case 1:-

$$V_+ = V_i$$

$$V_- = V_i - \frac{V_o}{A}$$

$$I_i = \frac{V_i - \frac{V_o}{A} - 0}{R_i}$$

$$I_i = \frac{V_i}{R_i} - \frac{V_o}{A R_i}$$

$$V_o - \left(\frac{V_i - \frac{V_o}{A}}{A} \right) = I_i R_F$$

$$\frac{V_o - V_i + \frac{V_o}{A}}{A} = R_F \left(\frac{V_i}{R_i} - \frac{V_o}{A R_i} \right)$$

$$\frac{V_o - V_i + \frac{V_o}{A}}{A} = \left(\frac{R_F}{R_i} \right) V_i - \left(\frac{R_F}{R_i} \right) \left(\frac{V_o}{A} \right)$$


Date

$$\frac{V_o + \frac{V_o}{A}}{1} + \left(\frac{R_F}{R_i} \right) \left(\frac{V_o}{A} \right) = V_i + \left(\frac{R_F}{R_i} \right) V_i$$

$$V_o \left(1 + \frac{1}{A} \left(1 + \frac{R_F}{R_i} \right) \right) = V_i \left(1 + \frac{R_F}{R_i} \right)$$

$$\frac{V_o}{V_i} = \frac{1 + R_F/R_i}{1 + 1/A (1 + R_F/R_i)}$$

Unity Gain Buffer (Voltage Follower) :-

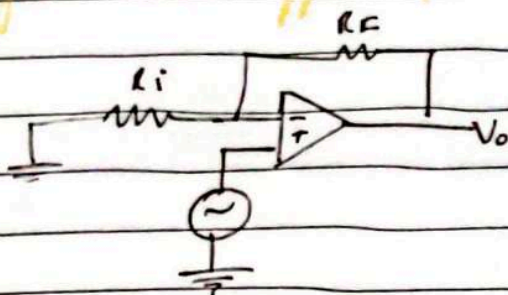


$$\frac{V_o}{V_i} = 1 + \frac{R_F}{R_i}$$

$$R_F = 0 \Rightarrow \frac{V_o}{V_i} = 1$$

(short circuit)

$$R_i = \infty \Rightarrow \frac{V_o}{V_i} = 1$$

(open circuit)

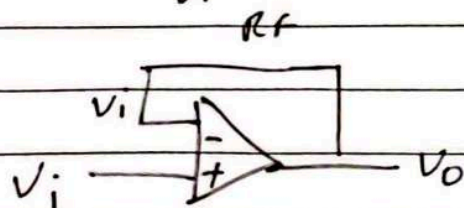

$$V_o = A(V_+ - V_-)$$

$$V_+ - V_- = \frac{V_o}{A}$$

$$A \rightarrow \infty$$

$$V_+ - V_- = \frac{V_o}{\infty}$$

Date

$$V_+ - V_- = 0$$

$$V_+ = V_-$$


$$V_+ = V_i$$

$$V_- = V_+ = V_i$$

$$V_- = V_o = V_i$$

FVP

Use VF in FVP

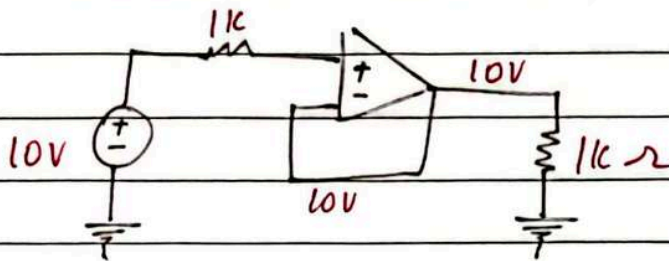

Date

$$V_+ - V_- = 0$$


$$V_+ = V_-$$

$$V_+ = V_i$$

$$V_- = V_+ = V_i$$


$$V_- = V_o = V_i$$

Use VF in FVP

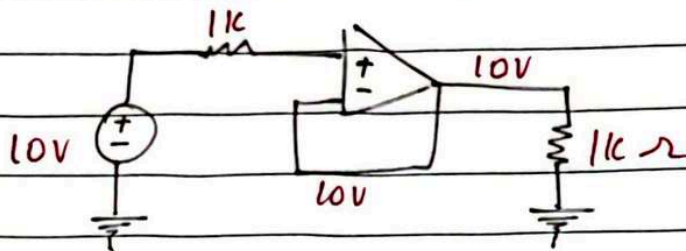

DAY - 8

A special case of Inv. Amp. :-

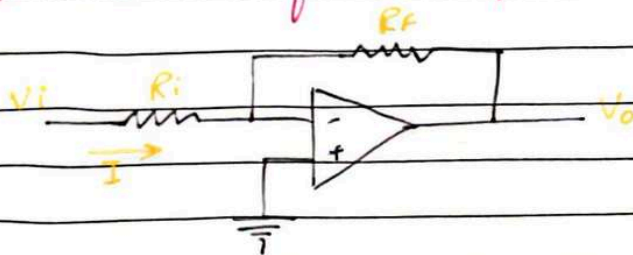


$$G = \frac{V_o}{V_i} = - \frac{R_F}{R_i} = -100$$

Objective :- I want my R_i to be large. I also want my G to be large and I also want my R_F to be practically possible -

sol.

$$G = -1000$$

Date

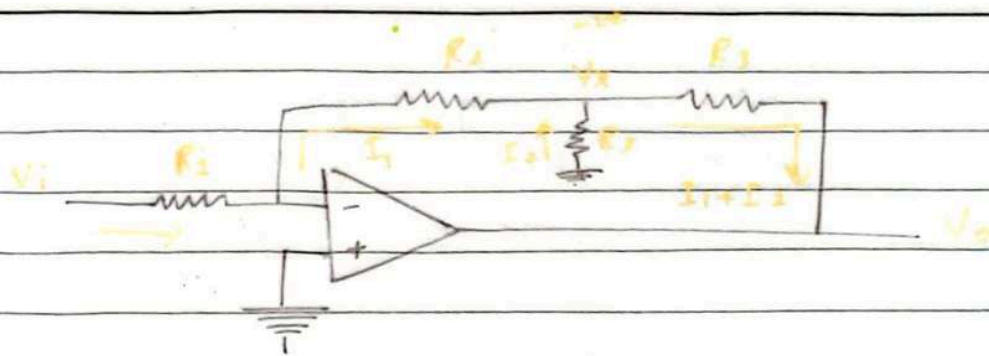

$$I_1 = \frac{V_i}{R_1} \quad \text{--- (1)}$$

$$0 - V_x = I_1 R_2$$

$$V_x = -I_1 R_2 \quad \text{--- (2)}$$

$$0 - V_x = I_2 R_3 \Rightarrow V_x = -I_2 R_3 \quad \text{--- (3)}$$

$$V_x - V_o = (I_1 + I_2) R_4 \quad \text{--- (4)}$$

From (1) & (2)

$$V_x = -I_1 R_2 = -\left(\frac{R_2}{R_1}\right) V_i$$

From (3)

$$V_x = -I_2 R_3$$

$$I_2 = -\frac{V_x}{R_3} = \left(\frac{R_2}{R_1 R_3}\right) V_i$$

$$V_x - V_o = (I_1 + I_2) R_4$$

$$-\left(\frac{R_2}{R_1}\right) V_i - V_o = \left(\frac{V_i}{R_1} + \left(\frac{R_2}{R_1 R_3}\right) V_i\right) R_4$$

$$-V_o = \left(\frac{R_2}{R_1}\right) V_i + \left(\frac{R_4}{R_1}\right) V_i + \left(\frac{R_2 R_4}{R_1 R_3}\right) V_i$$



$$-V_o = \left[\frac{R_2}{R_1} + \frac{R_4}{R_1} + \frac{R_2 R_4}{R_1 R_3} \right] V_i$$

$$\frac{V_o}{V_i} = - \left[\frac{R_2}{R_1} + \frac{R_4}{R_1} + \frac{R_2 R_4}{R_1 R_3} \right]$$

Date

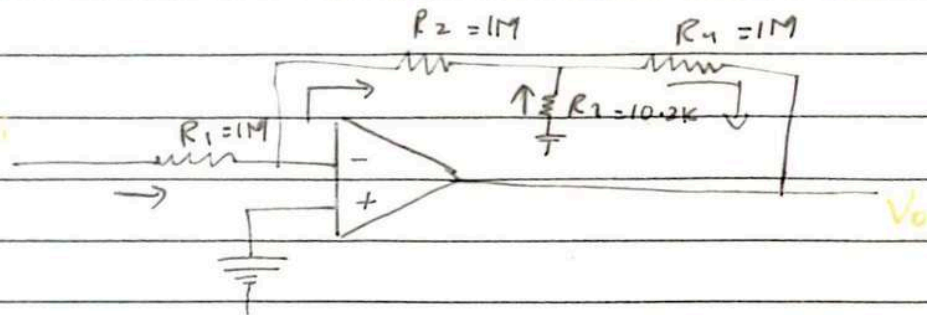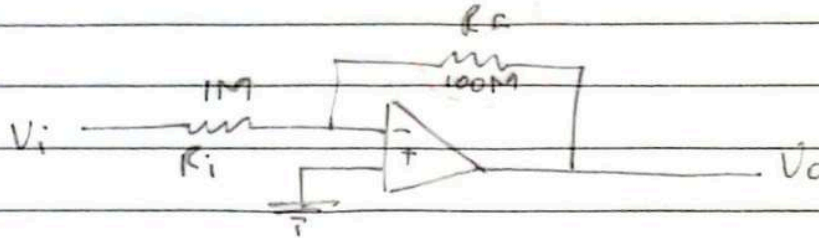QUESTION:-

Design a normal inverting amp. of gain = 1000. The input resistance should be exactly $1\text{M}\Omega$. Design an improved T network amp. . All the resistances should be less than or equal to $1\text{M}\Omega$.



putting in the formula

$$+1000 = 1 + \left(\frac{1\text{M}}{1\text{M}} + \frac{1\text{M}}{1\text{M}} + \frac{1\text{M} \times 1\text{M}}{1\text{M} \times R_3} \right)$$

$$1000 = 1 + 1 + \frac{1\text{M}}{R_3}$$

$$\frac{1\text{M}}{R_3} = 998$$


$$R_3 = \frac{1\text{M}}{998} = 1.02\text{K}\Omega$$

QUESTION:-

$$V_o = +6V_1 + 4V_2 - 3V_3$$

Date

(Make up lecture)

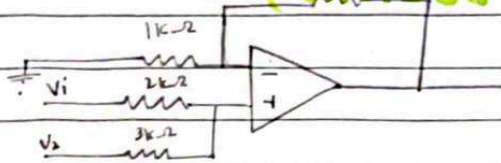

Assume $V_+ = V_-$ in every question

$$V_+ = V_- = V_x$$

$$\frac{V_x - V_1}{2k} + \frac{V_x - V_2}{3k} = 0 \quad (\text{node voltage on non-inverting terminal})$$

$$3V_x - 3V_1 + 2V_x - 2V_2 = 0$$

$$5V_x = 3V_1 + 2V_2 \rightarrow \textcircled{1}$$

$$\frac{V_x - 0}{1k} + \frac{V_x - V_o}{9k} = 0 \quad (\text{N.V on inverting terminal})$$

$$9V_x + V_x - V_o = 0$$

$$V_o = 10V_x \rightarrow \textcircled{2}$$

put $\textcircled{1}$ in $\textcircled{2}$

$$V_o = 10 \left(\frac{3V_1 + 2V_2}{5} \right)$$

$$V_o = 6V_1 + 4V_2$$

$$\frac{V_x - V_3}{1k} + \frac{V_x - V_o}{9k} = 0$$

$$9V_x - 9V_3 + V_x - V_o = 0$$

$$V_o = 10V_x - 9V_3 \rightarrow \textcircled{3}$$


$$V_o = -9V_3 + 10 \left(\frac{3V_1 + 2V_2}{5} \right)$$

$$V_o = 6V_1 + 4V_2 - 9V_3$$

Date

(Make Up LECTURE)

Single op-amp Difference Amp:-

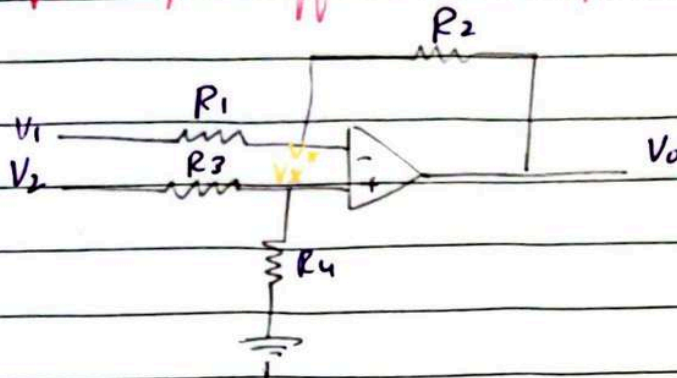

$$V_+ = V_- = V_X$$

$$\frac{V_X - V_2}{R_3} + \frac{V_X - 0}{R_4} = 0$$

(N.V on non-inverting ter.)

$$\frac{V_X}{R_3} - \frac{V_2}{R_3} + \frac{V_X}{R_4} = 0$$

$$V_X \left(\frac{1}{R_3} + \frac{1}{R_4} \right) = \frac{V_2}{R_3}$$

$$V_X = \left(\frac{R_4}{R_3 + R_4} \right) V_2 \rightarrow \textcircled{1}$$

$$\frac{V_X - V_1}{R_1} + \frac{V_X - V_0}{R_2} = 0 \quad (\text{N.V on inverting term.})$$

$$\frac{V_X}{R_1} - \frac{V_1}{R_1} + \frac{V_X}{R_2} - \frac{V_0}{R_2} = 0$$

$$\frac{V_0}{R_2} = V_X \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_1}{R_1}$$

$$\frac{V_0}{R_2} = \left(\frac{R_1 + R_2}{R_1 R_2} \right) V_X - \frac{V_1}{R_1}$$

$$V_0 = \left(\frac{R_1 + R_2}{R_1} \right) V_X - \left(\frac{R_2}{R_1} \right) V_1$$

Date

$$V_0 = \left(1 + \frac{R_2}{R_1} \right) V_1 - \left(\frac{R_2}{R_1} \right) V_2$$

put ① in ②

$$V_0 = + \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_2 - \left(\frac{R_2}{R_1} \right) V_1$$

Present:-

$$V_0 = 3 V_2 - 1 V_2$$

Expect:-

$$\beta (V_2 - V_1)$$

solution :-

$$\delta = \beta$$

$$\left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) = \frac{R_2}{R_1}$$

$$\frac{R_4}{R_4 + R_3} + \frac{R_2}{R_1} \left(\frac{R_4}{R_4 + R_3} \right) = \frac{R_2}{R_1}$$

$$\frac{R_4}{R_4 + R_3} = \frac{R_2}{R_1} - \frac{R_2}{R_1} \left(\frac{R_4}{R_4 + R_3} \right)$$

$$= \frac{R_2}{R_1} \left(1 - \frac{R_4}{R_4 + R_3} \right)$$

$$\frac{R_4}{R_4 + R_3} = \frac{R_2}{R_1} \left(\frac{R_3}{R_4 + R_3} \right)$$

$$\boxed{\frac{R_4}{R_3} = \frac{R_2}{R_1}}$$

Apply : $\frac{R_4}{R_3} = \frac{R_2}{R_1}$

$$V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

Date

SINGLE OP-AMP DIFFERENCE AMP:

Problems::


at the same ratio

Very difficult to change R_1 and R_2 and so it becomes frustrating -

And the same problem as before -

1st stage

2nd stage

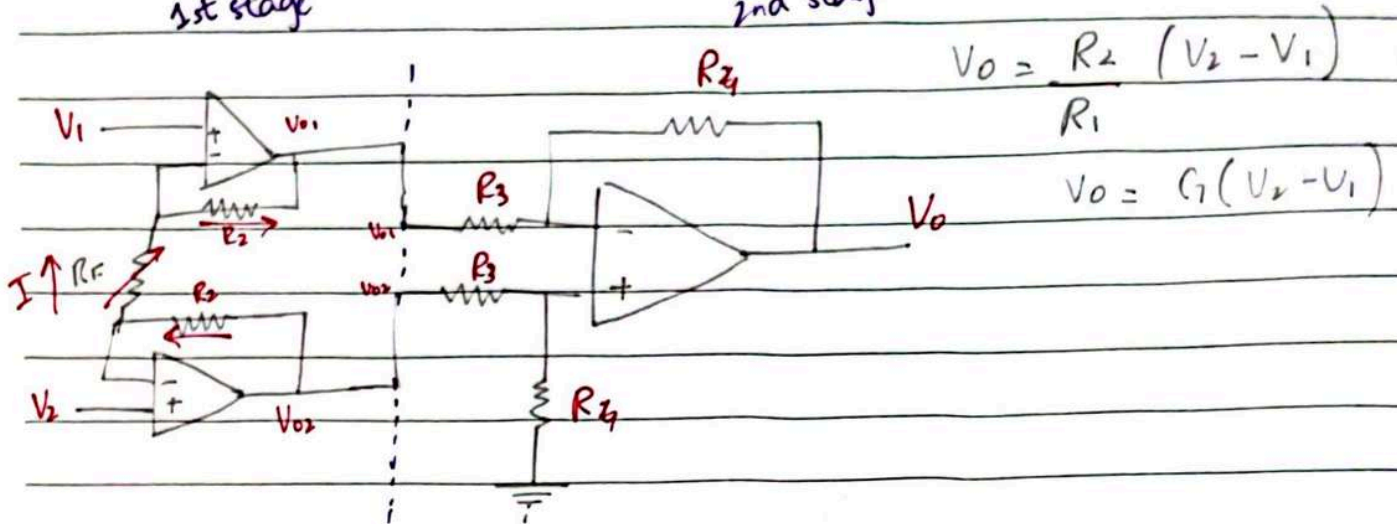

(Instrumentation Amplifier)

$$V_{02} = \left(1 + \frac{R_2}{R_1}\right) V_2$$

$$V_{01} = \left(1 + \frac{R_2}{R_1}\right) V_1$$

$$I = \frac{V_2 - V_1}{2R_1}$$

$$V_{02} - V_{01} = I(R_2) + I(2R_1) + I(R_2)$$

$$= I(2R_2 + 2R_1)$$

$$= \left(\frac{V_2 - V_1}{2R_1}\right)(2R_2 + 2R_1)$$

$$= \left(1 + \frac{2R_2}{2R_1}\right)(V_2 - V_1)$$

$$V_0 = \frac{R_4}{R_3}(V_{02} - V_{01})$$

Date

$$V_0 = \left(\frac{R_4}{R_3} \right) \left(1 + \frac{2 R_2}{R_F} \right) (V_2 - V_1)$$



Date

$$V_o = \left(\frac{R_4}{R_3} \right) \left(1 + \frac{2 R_2}{R_F} \right) (V_2 - V_1)$$

DAY-9

Frequency Dependence of Open-loop Op-Amp gain :-

(acts like a low pass filter)

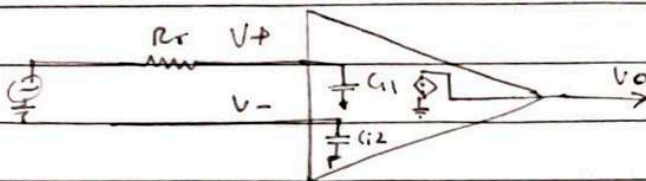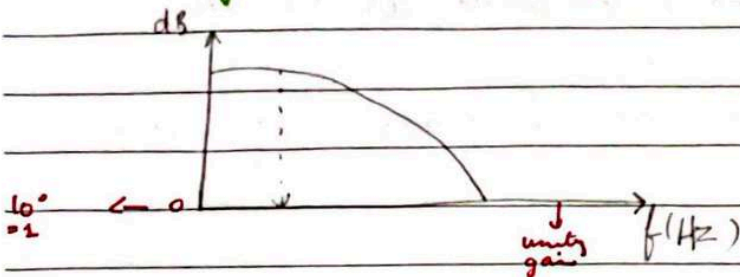

ideal = $A(s) = A_o$ (constant gain throughout)

$$\text{real} = A(s) = \left(\frac{1}{1 + s/\omega_b} \right) A_o$$

$$= \frac{A_o}{1 + s/\omega_b}$$

$$s = j\omega$$

$$A(\omega) = \frac{A_o}{1 + j(\omega/\omega_b)}$$

for large frequencies $\Rightarrow$ at large values of ' ω '
 $1 \ll \frac{\omega}{\omega_b}$

LPF

$$T(s) = \frac{\omega_b}{s + \omega_b}$$

$$= \frac{1}{1 + s/\omega_b}$$

Date

$$A(\omega) = \frac{A_0}{j(\omega/\omega_b)}$$

$$A(\omega) = \frac{A_0 \omega_b}{j\omega}$$

P-YAO

$$|A(\omega)| = \frac{A_0 \omega_b}{\omega}$$

↓
magnitude of
amplified gain at
open loop

at any frequency ω can be evaluated as shown.

Q. What is the amp open loop gain at unity gain frequency?
 $|A(\omega)| = 1$


Q. What is the unity gain frequency?

max. gain value ← $1 = \frac{A_0 \omega_b}{\omega_T} \Rightarrow \boxed{\omega_T = A_0 \omega_b}$

$$\begin{aligned} f_T &= A_0 f_b \\ &= 10^5 \times 10^1 \\ &= 10^6 \text{ Hz} \end{aligned}$$

Frequency Dependence of Closed loop Op-Amp:-

Inverting Amplifier :-

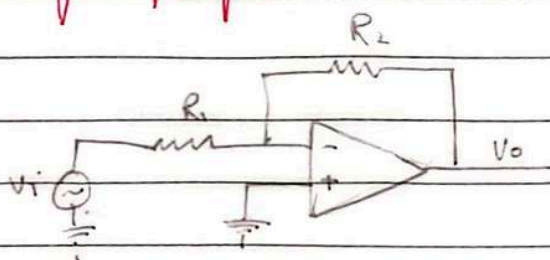

$$G = \frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + 1/A(1 + R_2/R_1)}$$

Inv AM Gain

$$\begin{aligned} A \rightarrow \infty \quad A \rightarrow \infty \\ \frac{-R_2/R_1}{1 + 1/A(1 + R_2/R_1)} &\quad \frac{-R_2/R_1}{1 + 1/A(1 + R_2/R_1)} \\ &\quad \frac{-R_2/R_1}{1 + 1/A(1 + R_2/R_1)} \quad \frac{-R_2/R_1}{1 + 1/A(1 + R_2/R_1)} \end{aligned}$$

Date

$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + \left[\frac{1 + R_2/R_1}{A} \cdot \frac{1}{1 + s/\omega_b} \right]}$$

$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + \left(\frac{1 + R_2/R_1}{A} \right) \left(\frac{1 + s/\omega_b}{A_o} \right)}$$

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{-R_2/R_1}{1 + \left(1 + R_2/R_1 \right) + \frac{s}{A_o \omega_b} \left(1 + R_2/R_1 \right)} \\ &= \frac{-R_2/R_1}{1 + \frac{1}{A_o} \left(1 + R_2/R_1 \right) + \frac{s}{A_o \omega_b} \left(1 + R_2/R_1 \right)} \end{aligned}$$

$A_o = 10^5$ (very large)

$$\frac{V_o(s)}{V_i(s)} = \frac{-R_2/R_1}{1 + \frac{s}{A_o \omega_b} \left(1 + R_2/R_1 \right)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-R_2/R_1}{1 + \frac{s}{A_o \omega_b} \left(1 + R_2/R_1 \right)}$$

Open-loop Op-amp:-

$$A(s) = \frac{A_o}{1 + s/\omega_b}$$

$$\omega_T = A_o \omega_b$$

(unity gain freq.)

$$|A(\omega)| = \frac{A_o \omega_b}{\omega}$$

ω_b = cut off freq.

Closed loop Op-amp:-

$$G(s) = \frac{-R_2/R_1}{1 + \frac{s}{A_o \omega_b} \left(1 + R_2/R_1 \right)}$$

$$\omega_D' = \frac{A_o \omega_b}{1 + R_2/R_1}$$

$$|G(\omega)| = \frac{(R_2/R_1) (A_o \omega_b / (1 + R_2/R_1))}{\omega}$$

Makeup. Lecture

$$G(s) = \frac{-R_2/R_1}{1 + \frac{s}{A_o \omega_b} \left(1 + R_2/R_1 \right)} = \frac{G_o}{1 + s/\omega_D} \Leftrightarrow \frac{A_o}{1 + s/\omega_b}$$

$$\frac{-R_2}{R_1} = G_o$$

Date

$$\omega_c = \frac{A_0 \omega_0}{1 + R_2/R_1}$$

$$G(s) = \frac{G_0}{1 + s/\omega_c}$$

$$s = j\omega$$

$$G(j\omega) = \frac{G_0}{1 + j(\omega/\omega_c)}$$

$$|G(j\omega)| = \frac{G_0}{\sqrt{1 + (\omega/\omega_c)^2}}$$

$$|G(j\omega)| = G_0/\omega/\omega_c$$

$$|G(j\omega)| = \frac{G_0 \omega_0}{\omega}$$

$$|G(j\omega)| = 1$$

$$G_0 \omega_0 = \omega_c$$

$$\omega_c = G_0 \omega_0$$

Main Formulas:-

$$\omega_T = A_0 \omega_b$$

unity gain freq
of open loop

$$\omega_c = \left(\frac{R_2}{R_1} \right) \left(\frac{A_0 \omega_b}{1 + R_2/R_1} \right)$$

cut-off
freq.

$$\omega_c = \frac{A_0 \omega_b}{1 + R_2/R_1}$$

Closed-loop Op-Amp (Non-inverting) :-

$$G(s) = \frac{1 + R_2/R_1}{1 + s/(A_0 \omega_b / (1 + R_2/R_1))} \Rightarrow \frac{G_0}{1 + s/\omega_c}$$

$$G_0 = 1 + R_2/R_1$$

$$\omega_c = \frac{A_0 \omega_b}{1 + R_2/R_1}$$

$$|G(j\omega)| = \frac{G_0 \omega_c}{\omega} = \frac{(1 + R_2/R_1) (A_0 \omega_b / (1 + R_2/R_1))}{\omega}$$

Date


cut off freq.

$$\omega_k = \frac{A_0 \omega_b}{1 + R_2/R_1}$$

unity gain freq. $\omega_y = G_0 \omega_k = \left(\frac{1 + R_2/R_1}{R_1} \right) \left(\frac{A_0 \omega_b}{1 + R_2/R_1} \right)$

DC imperfections of op-amps:-

1) O/p voltage saturation:-

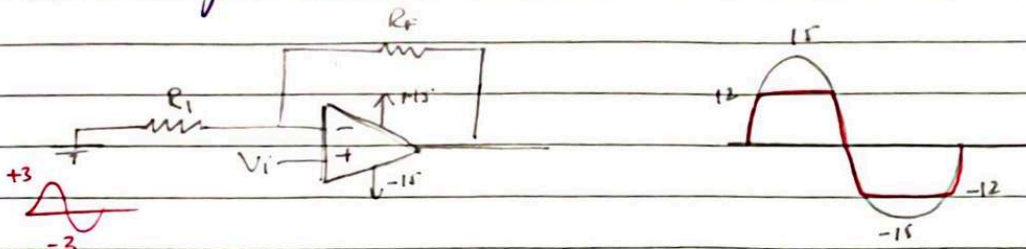


2) O/p current limit:-

→ Max. o/p current limited to $\pm 20\text{mA}$

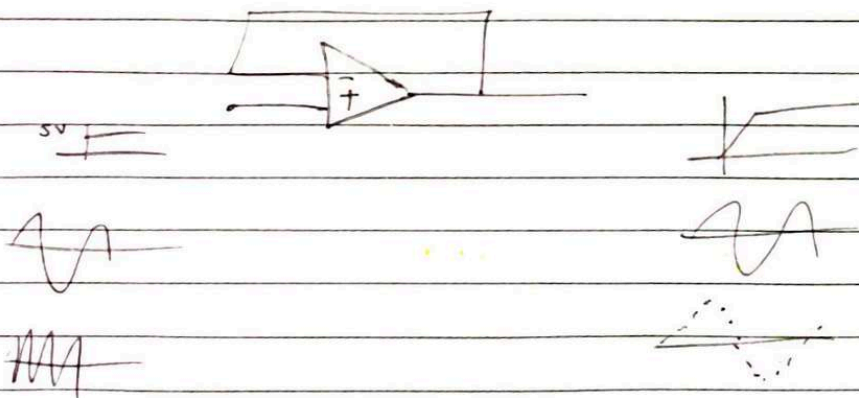3) SLEW Rate:-

If the input signal applied is changing / varying faster than the value of SR, the OP-AMP will not comply.



Date

$$v_i = V_I \sin(\omega t)$$

$$\frac{dv_i}{dt} = V_I \omega \cos(\omega t)$$

dt

$$\left. \frac{dv_i}{dt} \right|_{\max} = V_I \omega$$

$$SR \geq \left. \frac{dv_i}{dt} \right|_{\max}$$

$$\text{or } SR \geq \omega V_I$$

(safe)

$$SR < \omega V_I$$

(unsafe)

$$SR = \omega_{\max} \cdot V_{I, \max}$$

$$SR = 2\pi f_{\max} \cdot V_{I, \max}$$

$$f_{\max} = \frac{SR}{2\pi(V_{I, \max})}$$

$$V_{I, \max} = \frac{SR}{2\pi(f_{\max})}$$

Date

$$v_i = V_I \sin(\omega t)$$

$$\frac{dv_i}{dt} = V_I \omega \cos(\omega t)$$

$$\left. \frac{dv_i}{dt} \right|_{\max} = V_I \omega$$

$$SR \geq \left. \frac{dv_i}{dt} \right|_{\max}$$

$$\text{or } SR \geq \omega V_I$$

(safe)

$$SR < \omega V_I$$

(unsafe)

$$SR = \omega_{\max} \cdot V_{I, \max}$$

$$SR = 2\pi f_{\max} \cdot V_{I, \max}$$

$$f_{\max} = \frac{SR}{2\pi(V_{I, \max})}$$


$$V_{I, \max} = \frac{SR}{2\pi(f_{\max})}$$

DAV-10 (After Mid 1)

The output voltage is across R_L and output current is i through R_L .

Dependant Current & Voltage Sources:-

1) VC-VS

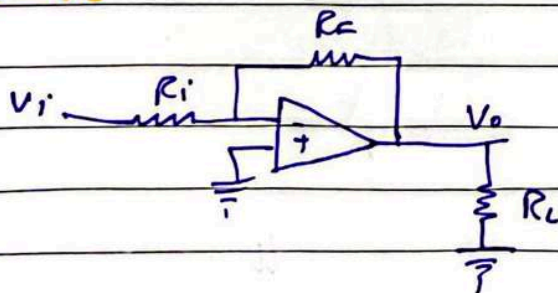


$$V_o = K V_i$$

Shere

Date

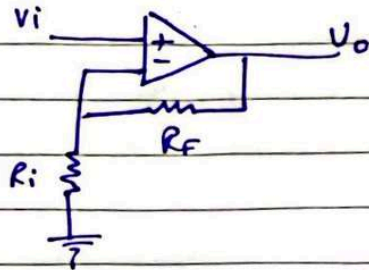
$$V_o = \left(-\frac{R_F}{R_i} \right) V_i$$



$$V_o = \left(1 + \frac{R_F}{R_i} \right) V_i$$

2) VC - CS

$$I_o = K V_i$$

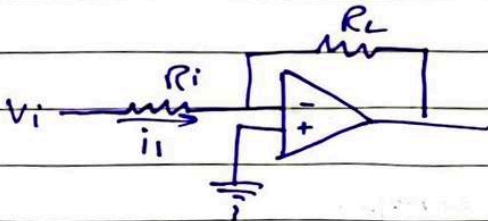


$$i_1 = \frac{V_i}{R_i}$$

$$i_o = \frac{V_i}{R_i}$$

$$i_o = \left(\frac{1}{R_i} \right) V_i$$

3) CC - VS


$$V_o = K i_i$$

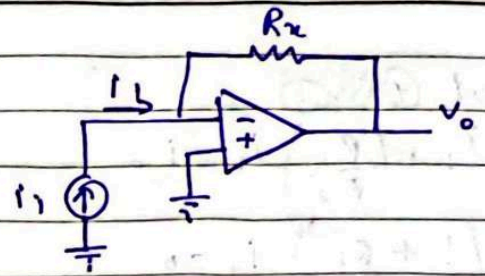

$$0 - V_o = R_F i_i$$

$$V_o = (-R_F) i_i$$

II - VAG) CC - CS

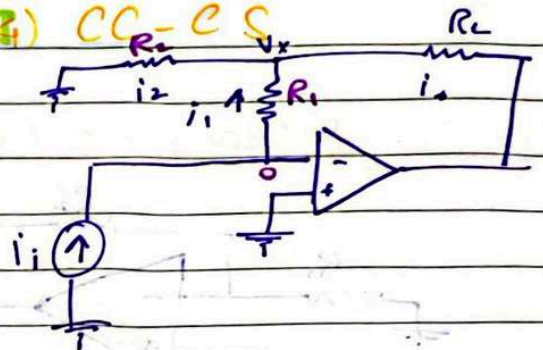

$$i_o = K i_i$$

$$0 - V_x = i_1 R_1$$

$$V_x = -i_1 R_1 \rightarrow (1)$$

$$i_1 = \frac{-V_x}{R_1}$$

$$0 - V_x = i_2 R_2$$

$$V_x = -i_2 R_2 \rightarrow (2)$$

$$i_1 + i_2 = i_o \rightarrow (3)$$

put (1) in (2)

$$i_1 R_1 = i_2 R_2$$

$$i_2 = \left(\frac{R_1}{R_2} \right) i_1 \rightarrow (4)$$

Date

put (4) in (3)


$$i_1 + \left(\frac{R_1}{R_2}\right) i_1 = i_o$$

$$\left(1 + \frac{R_1}{R_2}\right) i_1 = i_o$$

$$i_o = \left(1 + \frac{R_1}{R_2}\right) i_1$$

DAY-11

DC imperfections (Offset Voltage) ::

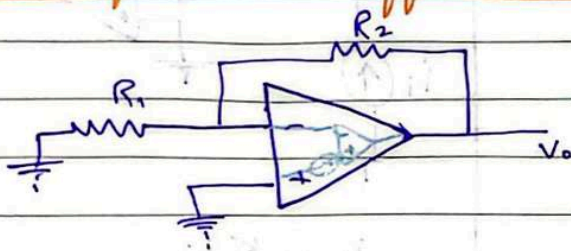

($\therefore$ ideally V_o has to be 0)

Now, as it is a non-inverting op-amp.

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$


$$V_i = V_{os}$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{os}$$

Now applying V_i on non-inverting terminal

$$V_o = \left(1 + \frac{R_2}{R_1}\right) (V_i + V_{os})$$
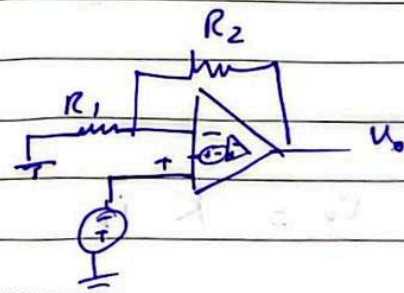
$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i + \underbrace{\left(1 + \frac{R_2}{R_1}\right) V_{os}}_{\text{parasitic}}$$




Date

Body

Now applying V_i on inverting terminal



Using principle of superposition
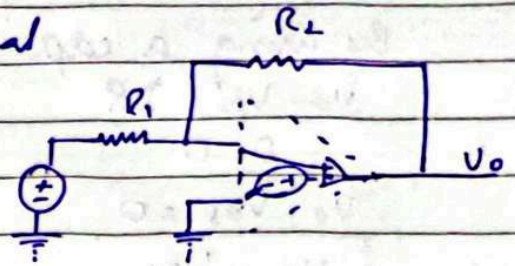
$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{os} - \left(\frac{R_2}{R_1}\right) V_i$$



∴ in POS, we take one source and ground the other and vice versa and after finding all, we sum all the o/p voltages.

solution to this imperfection

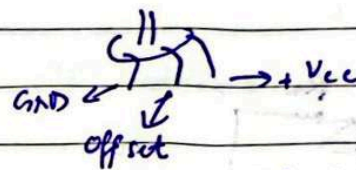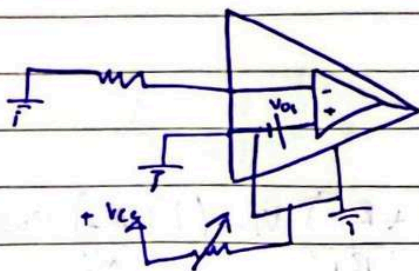


We use variable resistor and check the V_o and keep on rotating until $V_o = 0$. It indicates the V_{os} has been cancelled out.

(V_{os} is a DC signal)

1st Remedy:-

Use a potentiometer at 'offset' pin of op-amp to introduce an equal but opposite voltage in series with V_{os} .

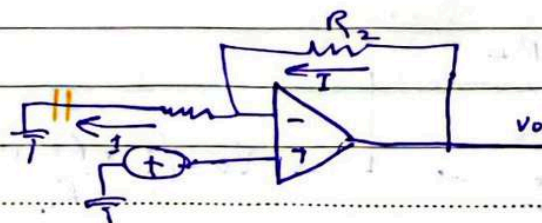2nd Remedy:- (Partial Remedy) (cost effective)



Date

non-polar

By using a capacitor, $I = 0$

$$V_o - V_{os} = IR$$


$$I = 0$$

$$V_o - V_{os} = 0$$

$$V_o = V_{os}$$


(ONLY WORK IF V_i IS AC)

inv. with V_{os} :-

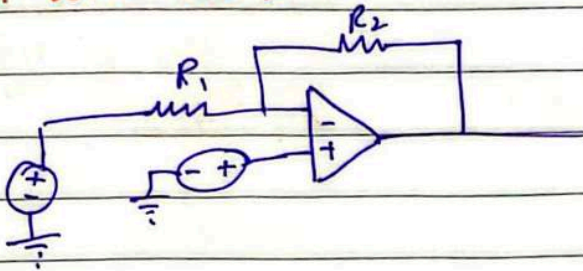

$$V_o = -\left(\frac{R_2}{R_1}\right) V_i + \left(1 + \frac{R_2}{R_1}\right) V_{os}$$


noninv. with V_{os} :-

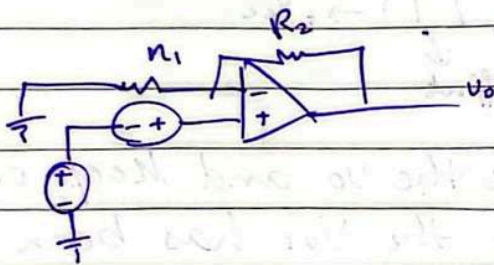

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i + \left(1 + \frac{R_2}{R_1}\right) V_{os}$$


$$= \left(1 + \frac{R_2}{R_1}\right) (V_i + V_{os})$$

inv. with V_{os} & partial remedy :-

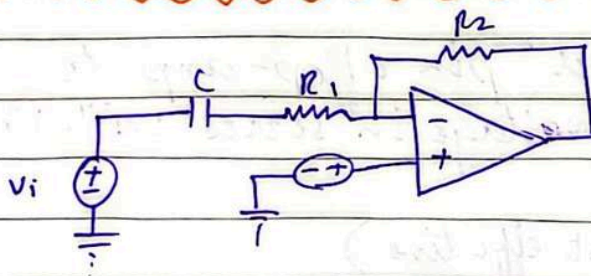

$$V_o = -\left(\frac{R_2}{R_1}\right) V_i + V_{os}$$


non-inv. with V_{os} & partial remedy :-

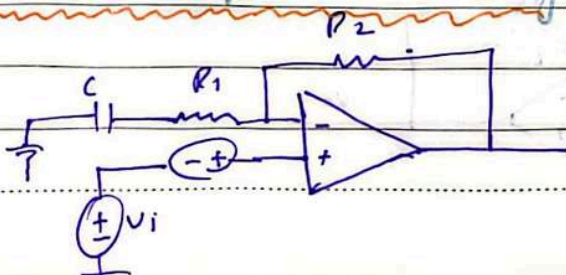

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i + V_{os}$$

Date

DC imperfection (Input Bias Current) :-

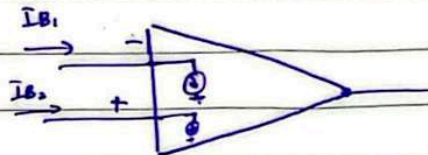


$\therefore$ In real op-amp, some non-zero current I_{B1} & I_{B2} tends to flow in op-amp terminals.

average input Bias current $\Rightarrow I_B = \frac{I_{B1} + I_{B2}}{2} \approx 100 \mu A$

Input offset current $\Rightarrow I_{os} = |I_{B1} - I_{B2}| \approx 1 \mu A (\approx 0)$


PROBLEM:-

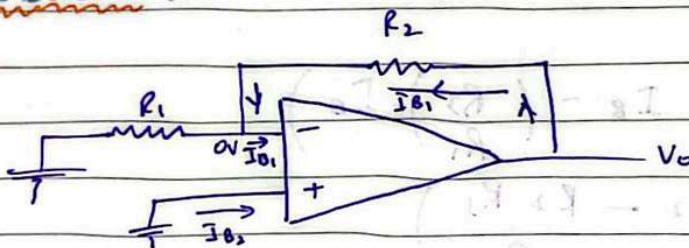

$$V_o - 0 = I_{B1} R_2$$

$$V_o = I_{B1} R_2 \neq 0$$

SOLUTION:-

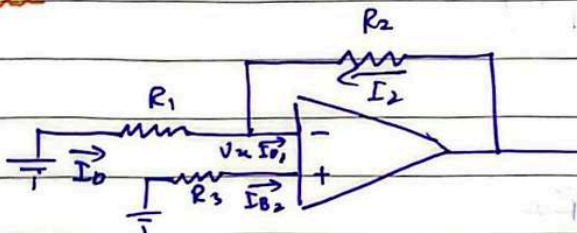

For simplicity $\therefore I_{B1} = I_{B2} = I_B$

$$0 - V_n = I_B R_3$$

$$V_n = -I_B R_3$$

Date

$$I_1 = \frac{0 - V_n}{R_1} = I_B \left(\frac{R_3}{R_1} \right)$$

By applying KCL,

$$I_1 + I_2 = I_B$$

$$I_2 = I_B - I_1$$

$$I_2 = I_B - \left(\frac{R_3}{R_1} \right) I_B$$

$$V_o - V_n = I_2 R_2$$

$$V_o = V_n + I_2 R_2$$

putting values

$$= -I_B R_B + R_2 \left(I_B - \left(\frac{R_3}{R_1} \right) I_B \right)$$

$$V_o = I_B \left(-R_3 + R_2 - \frac{R_2 R_3}{R_1} \right)$$

$$V_o = I_B \left(R_2 - R_3 \left(1 + \frac{R_2}{R_1} \right) \right)$$

lets put $V_o = 0$

$$0 = I_B \left(R_2 - R_3 \left(1 + \frac{R_2}{R_1} \right) \right)$$

$$R_2 - R_3 \left(1 + \frac{R_2}{R_1} \right) = 0$$

$$R_3 \left(1 + \frac{R_2}{R_1} \right) = R_2$$

$$R_3 \left(\frac{R_1 + R_2}{R_1} \right) = R_2$$


$$R_3 = \frac{R_1 R_2}{R_1 + R_2}$$

$$\Rightarrow R_3 = R_1 \parallel R_2$$


Date _____

DAY-12

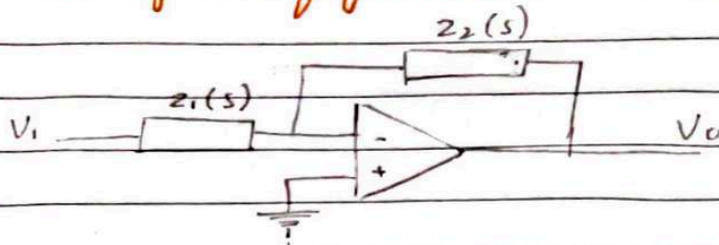Inverting Configuration with General Impedances



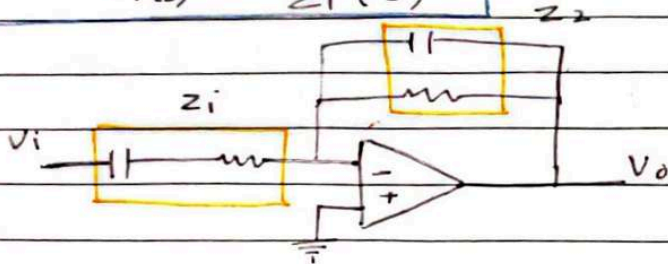
$$G(s) = \frac{V_o(s)}{V_i(s)} = - \frac{Z_2(s)}{Z_1(s)}$$



$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= \frac{Z_2(s)}{Z_1(s)} = - \frac{R_2 \parallel 1/C_2 s}{R_1 + 1/C_1 s} \\ &= - \frac{R_2 (1/C_2 s)}{R_1 + 1/C_1 s} \\ &= - \frac{R_2 / C_2 s}{(R_1 + 1/C_1 s)(R_2 + 1/C_2 s)} \end{aligned}$$

Inverting 'Integrator'

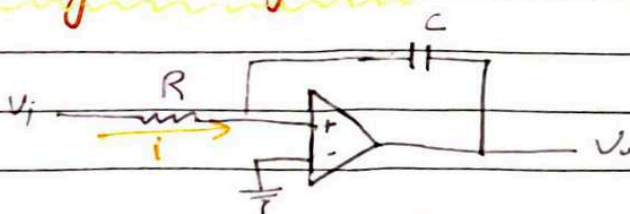

$$i(t) = \frac{V_i(t)}{R}$$

Date

SI-YAD

$$i(t) = C \frac{dv(t)}{dt}$$

$$\int \frac{dv}{dt} = \int \frac{i(t)}{C}$$

$$V_c(t) = \frac{1}{C} \int i(t) dt + V_c(0)$$

$$V_c(0) = 0$$

$$V_c(t) = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{C} \int \frac{V_i(t)}{R} dt$$

$$V_c(t) = \frac{1}{RC} \int V_i(t) dt$$

$$0 - V_o(t) = V_c(t)$$

$$V_o(t) = -V_c(t)$$

$$V_o(t) = -\frac{1}{RC} \int V_i(t) dt$$

Another Method:

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)} = -\frac{V_c s}{R}$$
$$= -\frac{1}{RCs}$$

$$V_o(s) = -\frac{1}{RCs} \left(\frac{V_i(s)}{s} \right)$$

L^{-1} on both sides

$$V_o(t) = -\frac{1}{RC} \int V_i(t) dt$$

Date

Acts as a low Pass Filter :-

$$\frac{V_o(s)}{V_i(s)} = \frac{-1}{RCs}$$

$$G(s) = \frac{-1}{RCs}$$

$$s = j\omega$$

$$G(j\omega) = -\frac{1}{RCj\omega}$$

$$= \frac{j}{RC\omega}$$


$$G(\omega) = 0 + j\left(\frac{1}{RC\omega}\right)$$

$$|G| = \sqrt{0^2 + \left(\frac{1}{RC\omega}\right)^2} = \frac{1}{RC\omega}$$


$$\angle G = \tan^{-1}\left(\frac{1/RC\omega}{0}\right)$$

$$= 90^\circ$$
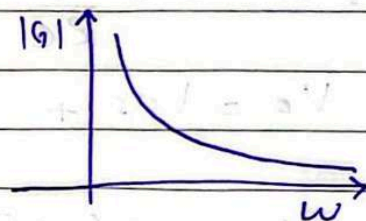
$$G = \frac{1}{RC\omega} \angle 90^\circ$$



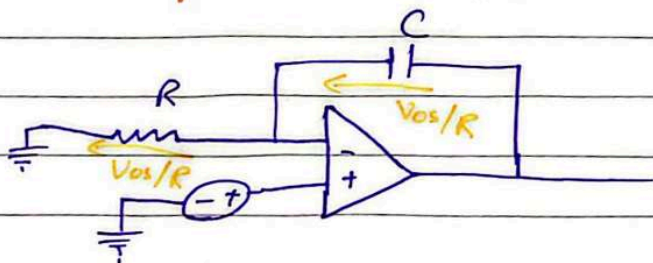Impact Of V_{os} on Integrator's behaviour :-



$$i = C \frac{dv}{dt}$$

Date

$$V_c = \frac{1}{C} \int i(t) dt$$

$$V_c = \frac{1}{C} \int \frac{V_{os}}{R} dt$$

$$V_c = \frac{1}{RC} \int_0^t V_{os} dt$$

$$V_o - V_{os} = V_c$$


$$V_o = V_{os} + V_c$$

$$V_o = V_{os} + \frac{1}{RC} \int_0^t V_{os} dt$$


$$V_o = V_{os} + \frac{1}{RC} (V_{os} \cdot t)$$

$$V_o = V_{os} + \left(\frac{V_{os}}{RC} \right) t$$

$$y = mt + c$$

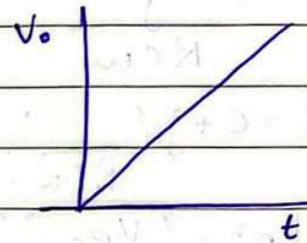

Impact of I_B on integrator's behaviour

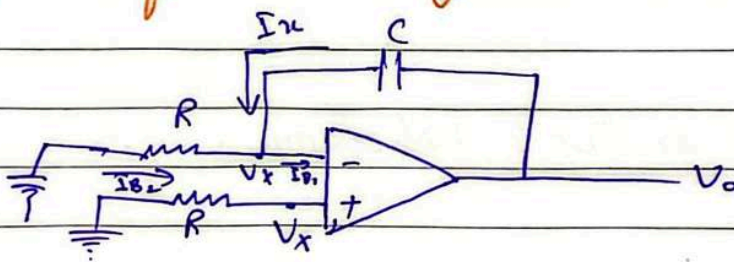

$$0 - V_x = I_{B2} R$$

$$V_x = -R I_{B2}$$

$$i = \frac{0 - (-R I_{B2})}{R}$$

$$i = I_{B2}$$

Date

$$i_x + I_{B2} = I_{B1}$$

$$i_x = I_{B1} - I_{B2}$$

$$V_c = \frac{1}{C} \int_0^t i_x(t) dt$$



$$= \frac{1}{C} \int_0^t I_{B1} - I_{B2} dt$$

$$V_c = \left(\frac{I_{B1} - I_{B2}}{C} \right) t$$

$$V_c = V_o - V_x$$

$$V_o = V_c + V_x$$
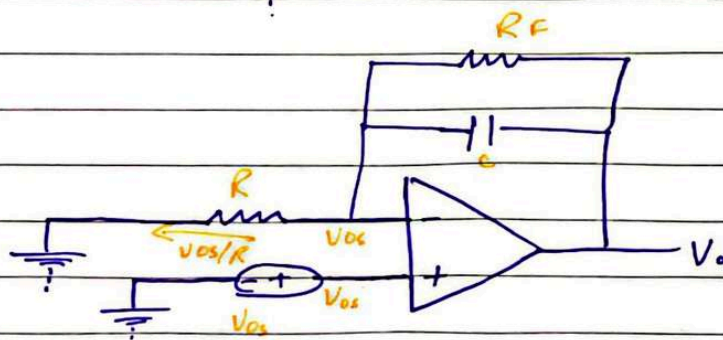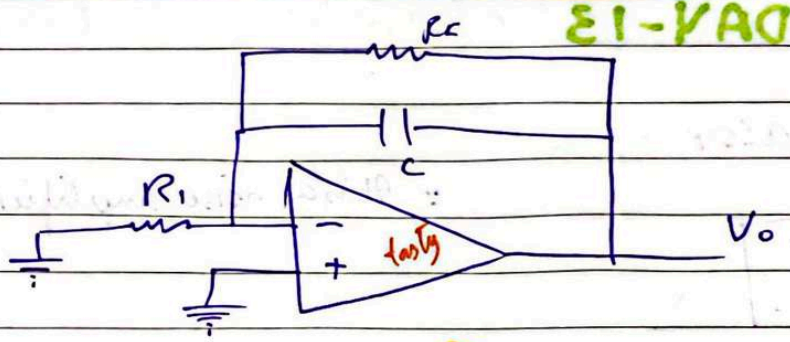
$$V_o = -I_{B2} R + \left(\frac{I_{B1} - I_{B2}}{C} \right) t$$



Current will also choose resistor over capacitor.

$$V_o = V_{os} + \left(\frac{V_{os}}{R} \right) R_f$$


$$V_o = \left(1 + \frac{R_f}{R} \right) V_{os}$$

Date


$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$
$$= -\frac{1/s \parallel R_F}{R_1}$$

$$G(s) = \frac{-R_F/R_1}{1+s(R_F C)}$$

$$G(s) = -\frac{1}{(RC)s}$$

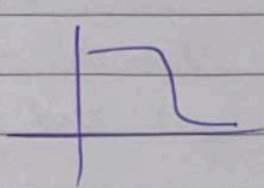


(low pass filter)

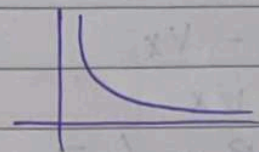

DAY-13

OP-AMP Differentiator :-

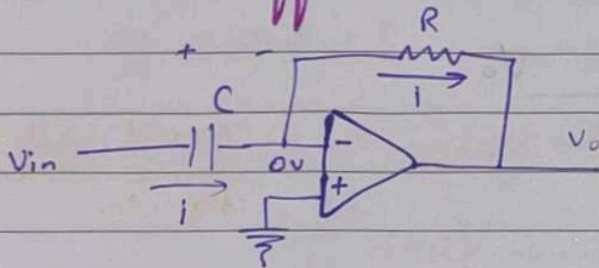

∴ It is a noise amplifier

$$i = C \frac{dV_c}{dt}$$

$$i = C \frac{dV_{in}}{dt} \quad \text{--- ①}$$

$$0 - V_o = iR$$


$$V_o = -iR \rightarrow \text{put in ①}$$

$$V_o = -RC \frac{dV_{in}}{dt}$$

Date

$$RC = 1$$

$$V_o = - \frac{dV_i}{dt}$$

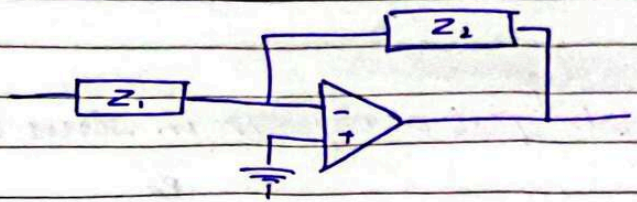

$$\frac{V_o(s)}{V_i(s)} = - \frac{Z_2}{Z_1}$$

$$\frac{V_o}{V_i} = - \frac{R}{1/sC}$$

$$\frac{V_o}{V_i} = -RCs$$

$$V_o(s) = -RC(V_i(s)s)$$

$$\int V_i(t) dt \xrightarrow{L} \frac{V(s)}{s}$$

$$\frac{dV(t)}{dt} \xrightarrow{L} sV(s)$$

Taking L^{-1}

$$V_o(t) = -RC \left(\frac{dV_i}{dt} \right)$$


$$\frac{V_o(s)}{V_i(s)} = -RCs$$

$$s = j\omega$$

$$G(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = -RC(j\omega) = 0 - j(RC\omega)$$

$$|G(\omega)| = RC\omega$$

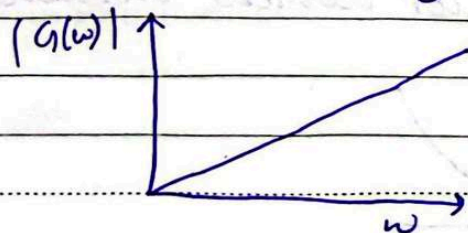
$$\angle G(\omega) = \tan^{-1} \left(\frac{-RC\omega}{0} \right) = -90^\circ$$



Date

Remedy:-

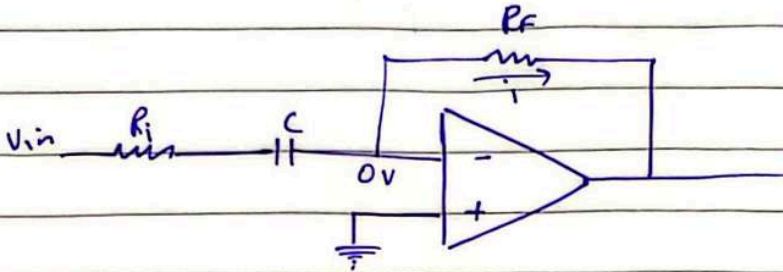We put a resistor in series with a capacitor




(high pass filter)

$$\frac{V_o}{V_i} = - \frac{R}{R_i + 1/Cs}$$


$$\frac{V_o}{V_i} = - \frac{R/R_i}{1 + 1/RCs}$$

Non-linear Operation Of Op-AMP :-

Logarithmic Amp:-

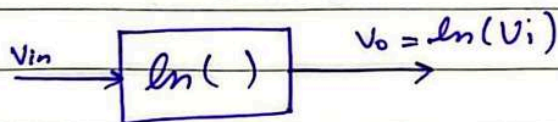

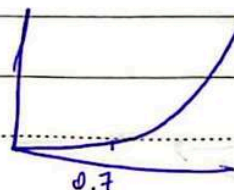All the PN Junction / semiconductor devices exhibit an exp. behaviour




Date

log amp. is an inverting amp. The feedback resistor is replaced with any PN Junction device (Diode)

Log Amplifier:

$$V_o \propto \ln(V_i)$$

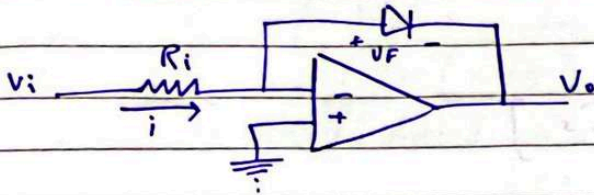

$$i = \frac{V_i}{R_i}$$

Diode I-V eq.:

$$I = I_s \left(e^{V_F/nV_T} - 1 \right)$$

$$n = \begin{cases} 1 & \text{for silicon} \\ 2 & \text{for germanium} \end{cases}$$

V_T = thermal voltage

I = forward current.

I_s = Reverse sat. current

V_F = Voltage across diode

$$\text{Assume } V_F > nV_T \rightarrow e^{V_F/nV_T} \gg 1$$

neglecting 1

$$\therefore I = I_s e^{V_F/nV_T}$$

Taking $\ln()$ on both sides of eq

$$\ln(I) = \ln(I_s e^{V_F/nV_T})$$

$$\ln I = \ln I_s + \ln e^{V_F/nV_T}$$

$$\ln I = \ln I_s + \frac{V_F}{nV_T}$$

$$\ln I = \ln I_s + \frac{V_F}{nV_T}$$

$$V_F = \eta V_T (\ln I - \ln I_s)$$

$$V_F = \eta V_T \left(\ln \left(\frac{V_i}{R} \right) - \ln I_s \right)$$

$$0 - V_o = V_F$$

$$V_o = -V_F$$

$$V_o = -\eta V_T \left[\ln \left(\frac{V_i}{R} \right) - \ln I_s \right]$$


Problems:-

1) $\ln(I_s)$ needs to be removed.

put similar diode in opposite direction

2) $V_o \propto \eta V_T$

Solutions:-

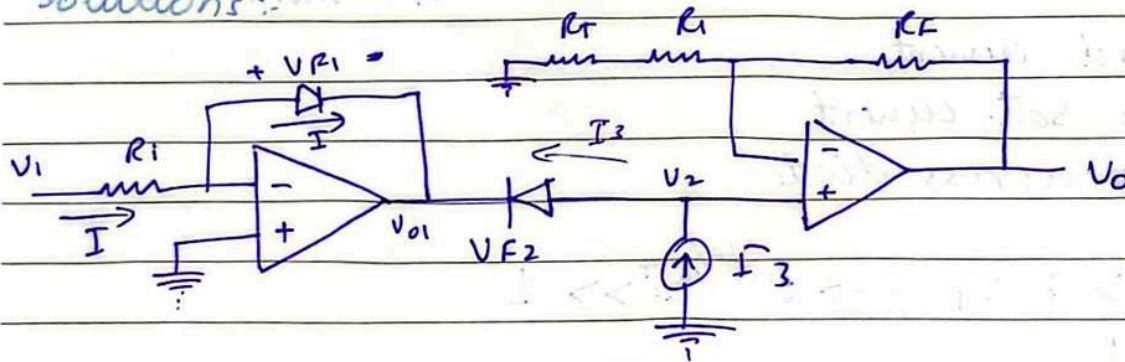

(Modified Log. Amp)

$$V_{o1} = -\eta V_T \left(\ln \left(\frac{V_i}{R} \right) - \ln(I_s) \right)$$

$$V_{F2} = +\eta V_T (\ln I_3 - \ln(I_s))$$

$$\therefore V_{F2} = V_2 - V_{o1}$$

Date

1/10/21

$$V_2 = V_{F2} + V_{D1}$$

$$V_2 = \eta V_T [\ln(I_3) - \ln(I_s)] - \eta V_T [\ln(V_i/R) - \ln I_s]$$

$$= \eta V_T \ln I_3 - \cancel{\eta V_T \ln(I_s)} - \eta V_T \ln(V_i/R) + \cancel{\eta V_T \ln I_s}$$

$$V_2 = \eta V_T (\ln I_3 - \ln(V_i/R))$$

$$V_2 = -\eta V_T (\ln(V_i/R) - \ln(I_3))$$

$$V_2 = -\eta V_T \left(\ln \left(\frac{V_i}{I_3 R} \right) \right) \quad (\text{1st prob. solved})$$


$$V_o = \left(1 + \frac{R_F}{R_1 + R_T} \right) V_2 \quad (\text{as sec amp is non-inverting})$$

$$V_o = - \left(1 + \frac{R_F}{R_1 + R_T} \right) \left(\eta V_T \ln \left(\frac{V_i}{I_3 R} \right) \right)$$

↓
const.

DAY-14

Anti-Log AMP :

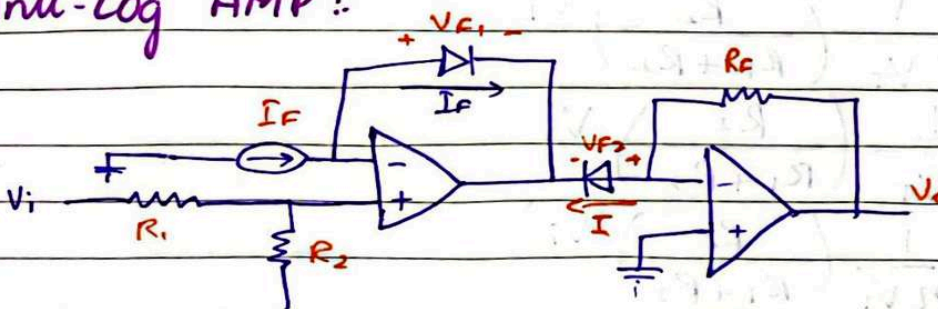

$$I = \frac{V_o}{R}$$

$$V_x = \left(\frac{R_2}{R_1 + R_2} \right) V_i$$

$$V_{F1} = +\eta V_T (\ln I_F - \ln I_s)$$

Date

$$V_X - V_{O1} = V_{F1}$$

$$V_{O1} = V_X - V_{F1}$$

$$V_{O1} = \left(\frac{R_2}{R_1 + R_2} \right) V_i - \eta V_T (\ln \bar{I}_F - \ln \bar{I}_S) \rightarrow \textcircled{1}$$

$$0 - V_{O1} = V_{F2}$$

$$V_{O1} = -V_{F2} \rightarrow \textcircled{2}$$

$$V_{F2} = + \eta V_T (\ln \bar{I} - \ln \bar{I}_S)$$

substitute $\textcircled{1}$ in $\textcircled{2}$

$$-V_{F2} = V_X - V_{F1}$$

$$- \eta V_T (\ln \bar{I} - \ln \bar{I}_S) = \left(\frac{R_2}{R_1 + R_2} \right) V_i - \eta V_T (\ln \bar{I}_F - \ln \bar{I}_S)$$

$$- \eta V_T \ln \bar{I} + \eta V_T \cancel{\ln \bar{I}_S} + \eta V_T \ln \bar{I}_F - \eta V_T \cancel{\ln \bar{I}_S} = \left(\frac{R_2}{R_1 + R_2} \right) V_i$$

$$- \eta V_T (\ln \bar{I} - \bar{I}_F) = \left(\frac{R_2}{R_1 + R_2} \right) V_i$$

$$\left(\frac{R_2}{R_1 + R_2} \right) V_i = \eta V_T (\ln \bar{I}_F - \ln \bar{I})$$

$$\ln \left(\frac{\bar{I}_F}{\bar{I}} \right) = \frac{1}{\eta V_T} \left(\frac{R_2}{R_1 + R_2} \right) V_i$$

$$\ln \left(\frac{\bar{I}}{\bar{I}_F} \right) = - \frac{1}{\eta V_T} \left(\frac{R_2}{R_1 + R_2} \right) V_i$$

$$\frac{\bar{I}}{\bar{I}_F} = \ln^{-1} \left(- \frac{1}{\eta V_T} \left(\frac{R_2}{R_1 + R_2} \right) V_i \right)$$

$$\bar{I} = \bar{I}_F \ln^{-1} \left(- \frac{1}{\eta V_T} \left(\frac{R_2}{R_1 + R_2} \right) V_i \right)$$

$$\frac{V_O}{R_F} = \bar{I}_F \ln^{-1} \left(- \frac{1}{\eta V_T} \left(\frac{R_2}{R_1 + R_2} \right) V_i \right)$$

Date

$$V_o = I_F R_F \ln^{-1} \left(- \frac{1}{\eta V_T} \left(\frac{R_2}{R_1 + R_2} \right) V_i \right)$$

We replace R_2 with R_T

$$V_o = I_F R_F \ln^{-1} \left(- \frac{V_i}{R_{T1}} \right)$$



$$R_2 = R_T$$

$$\frac{1}{\eta V_T} \left(\frac{R_T}{R_1 + R_T} \right)$$


$$R_1 \gg R_T$$

$$\frac{1}{\eta V_T} \left(\frac{R_T}{R_1} \right)$$
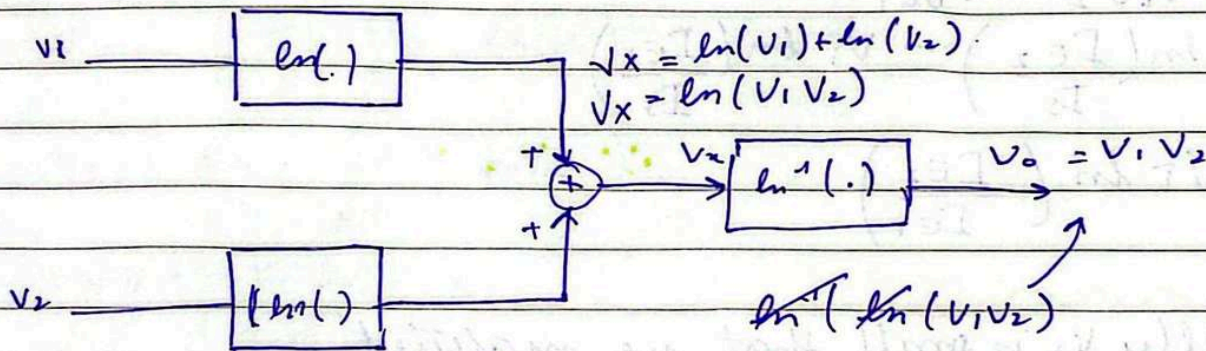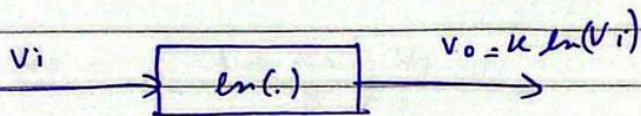
$$\frac{1}{\eta R_1} \left(\frac{R_T}{V_T} \right)$$



Modified 'log' AMP

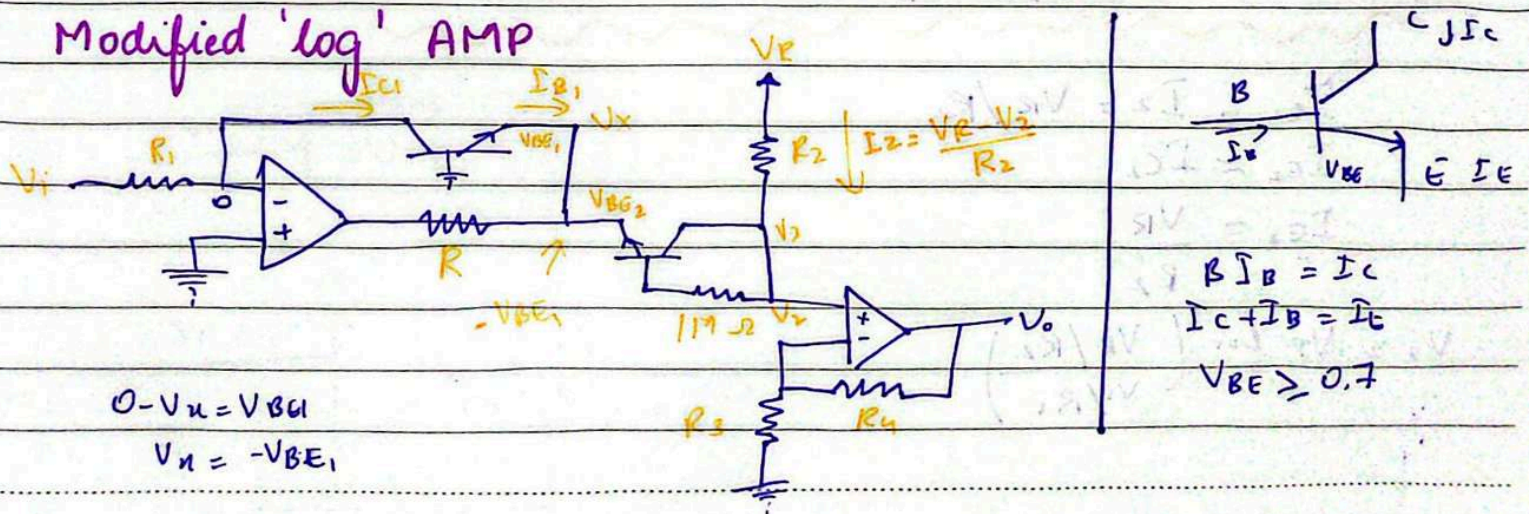

Date

BJT x-tics:

$$I_E = I_S e^{V_{BE}/V_T}$$

$$V_{BE} = V_T \ln\left(\frac{I_E}{I_S}\right)$$

$$I_{C1} = \frac{V_i}{R_1} \approx I_{E1}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{E1}}{I_S}\right)$$

$$V_{BE2} = V_T \ln\left(\frac{I_{E2}}{I_S}\right)$$

$$V_2 - (-V_{BE1}) = V_{BE2}$$

$$V_2 + V_{BE1} = V_{BE2}$$

$$V_2 = V_{BE2} - V_{BE1}$$

$$V_2 = V_T \ln\left(\frac{I_{E2}}{I_S}\right) - V_T \ln\left(\frac{I_{E1}}{I_S}\right)$$

$$V_2 = V_T \ln\left(\frac{I_{E2}}{I_{E1}}\right)$$

generally V_2 is small that we neglected
 $V_2 \ll V_R$

$$I_{C2} = I_2 = V_R / R_2$$

$$I_{E2} \approx I_{C2}$$

$$I_{E2} = \frac{V_R}{R_2}$$

$$V_2 = V_T \ln\left(\frac{V_R / R_2}{V_i / R_1}\right)$$

Date

$$V_2 = V_T \ln \left(\frac{V_R R_1}{V_i R_2} \right)$$

$$V_2 = -V_T \ln \left(\frac{V_i R_2}{R_1 V_R} \right)$$

$$V_2 = V_T \ln(V_i)$$

suppose
 $V_R = 10V$, $R_1 = 10K$
 $R_2 = 100K$

From the last amp

$$V_o = \left(1 + \frac{R_4}{R_3} \right) V_2$$

$$V_o = - \left(1 + \frac{R_4}{R_3} \right) V_T \ln(V_i)$$



$$\frac{R_4}{R_3} \gg 1$$

$$V_o = - \left(\frac{R_4}{R_3} \right) V_T \ln(V_i)$$

$$V_o = - R_4 \left(\frac{V_T}{R_3} \right) \ln(V_i)$$

$$V_o = -K \ln(V_i)$$

Square Root Extractor :



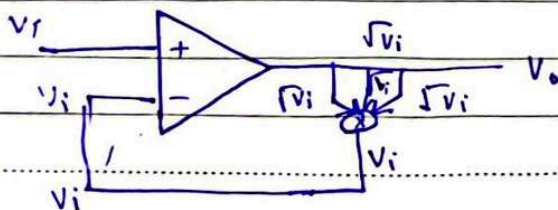
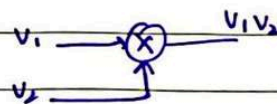


Date

DAY-15


Sine Wave Generator (oscillator)

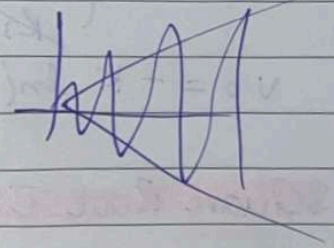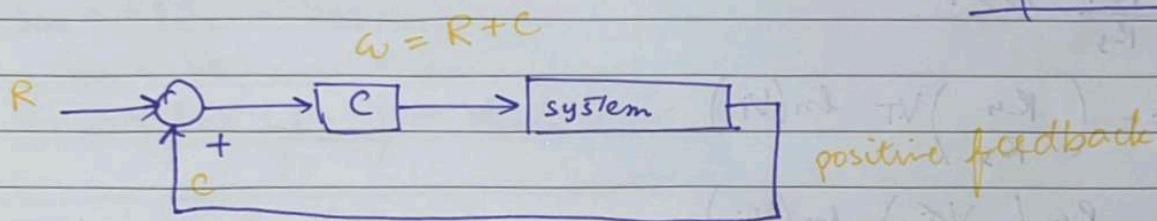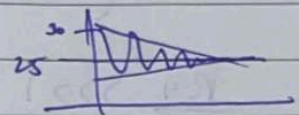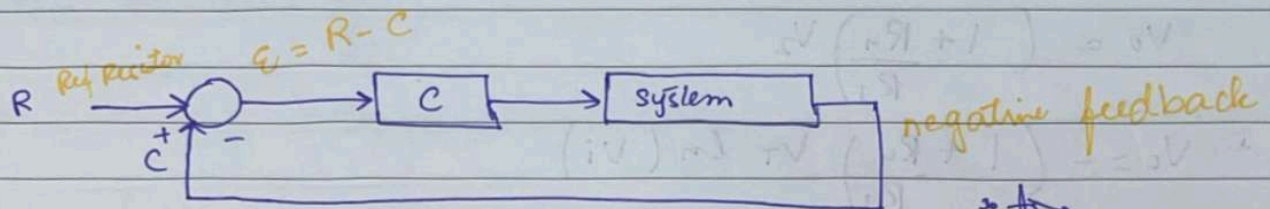Oscillators generate a finite output signal by using an amplifier followed by a frequency selective circuit connected in positive feedback loop with NO input signal.



Negative feedback is preferred because eventually error converges to 0 and the system is stable.

Sinusoidal Oscillator

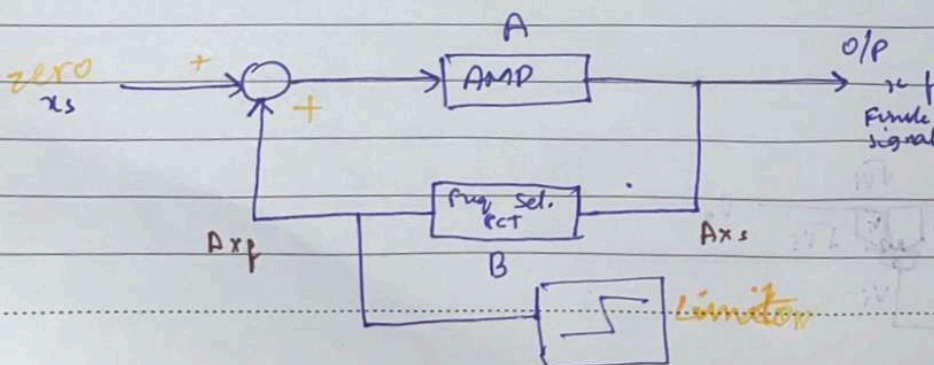

Date

Suppose:

$$V_i = x_s$$

x_s = reservoir of infinite sinusoid frequencies

$$= M_1 \sin(\omega t) + M_2 \sin(2\omega t) + M_3 \sin(3\omega t) - \dots + M_n \sin(n\omega t)$$

Magnitude of $M_1, M_2, M_3 + \dots M_n \rightarrow$ is V.V.V small of the order 10^{-30}

I

$$x_s + 0 \xrightarrow{\text{AMP}} A x_s \xrightarrow{\text{FB}} A \beta x_F$$

II


$$x_s + A \beta x_F \rightarrow A x_s + A^2 \beta^2 x_F \rightarrow A^2 \beta^2 x_F \quad A = 10^5, B = 1$$

III


$$x_s + A^2 \beta^2 x_F \rightarrow A x_s + A^3 \beta^3 x_F \rightarrow A^3 \beta^3 x_F$$

IV
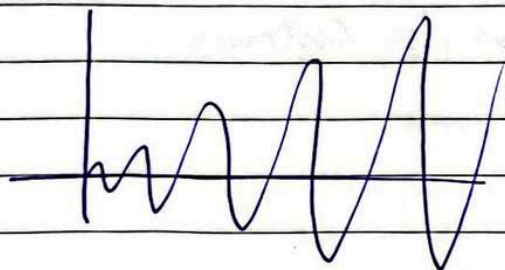
$$x_s + A^3 \beta^3 x_F \rightarrow A x_s + A^4 \beta^4 x_F \rightarrow A^4 \beta^4 x_F$$




Before limiter

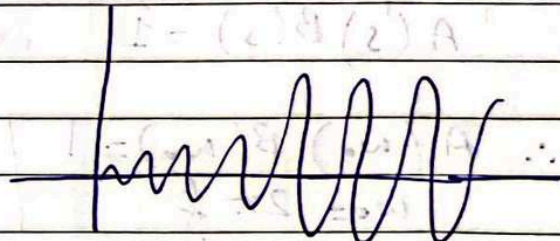


After limiter

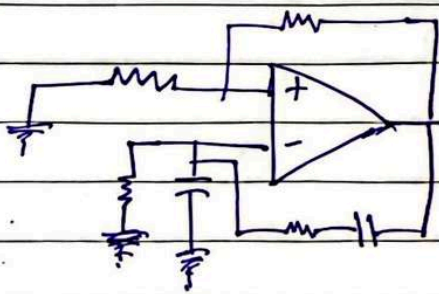Let us use thermal noise of the resistors



(Example)

Date

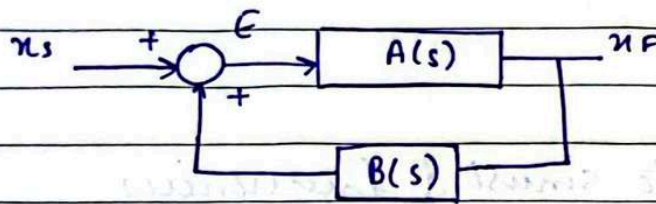

$$E = x_s + \beta(s)x_F \rightarrow \textcircled{1}$$

$$x_F = A(s)E \rightarrow \textcircled{2} \quad (\text{put } \textcircled{1} \text{ in } \textcircled{2})$$

$$x_F = A(s)(x_s + \beta(s)x_F)$$

$$x_F(1 - A(s)\beta(s)) = A(s)x_s$$

$$\frac{x_F}{x_s} = \frac{A(s)}{1 - A(s)\beta(s)}$$

$$\frac{x_F}{x_s} = \frac{x_F}{0} = \infty \quad (\text{Acc. to def.})$$

$$A(s) = \infty$$

$$1 - \beta(s)A(s)$$


$$1 - \beta(s)A(s) = 0$$

$$A(s)\beta(s) = 1 \quad \text{Barkhausen's Criteria}$$

$$\therefore A(\omega_0)\beta(\omega_0) = 1 \rightarrow \textcircled{A}$$

$$\omega_0 = 2\pi f$$

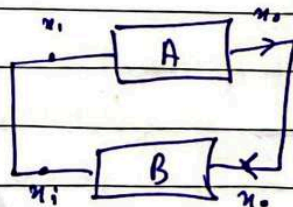If we apply zero input, the output would be a finite signal of frequency f_0 if and only if this condition ^(A) holds at the frequency f_0 .



$$x_i = \beta x_o \rightarrow \textcircled{1}$$

Date


$$x_0 = A x_i \rightarrow \textcircled{2}$$

$$x_0 = A B x_0$$

$$A B = 1$$

DAY-16

Wein - Bridge Oscillator

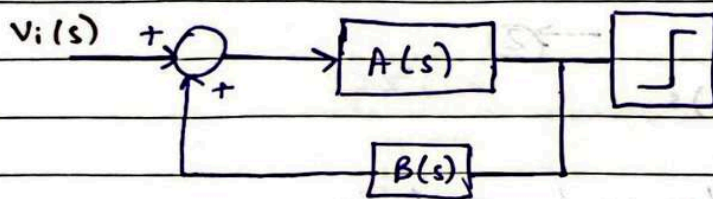


Bark - Housan's Criteria :

To get a finite sine signal at $f = f_0$.

$$A(\omega_0) B(\omega_0) = 1$$

$$\omega_0 = 2 \pi f_0$$

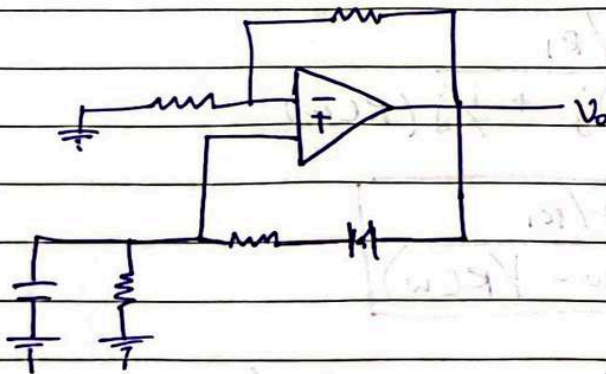

According to the def. of oscillators -

$$V_o(s) = \left(1 + \frac{R_2}{R_1} \right) V_a(s)$$

$$\frac{V_o(s)}{V_a(s)} = 1 + \frac{R_2}{R_1}$$


Date

$$\therefore A(s) = 1 + \frac{R_2}{R_1} \rightarrow \textcircled{1}$$

Using VDR

$$\begin{aligned} \beta(s) &= \frac{Z_2}{Z_1 + Z_2} \\ &= \frac{R \parallel Y_{sc}}{(R + Y_{sc}) + (R \parallel Y_{sc})} \end{aligned}$$
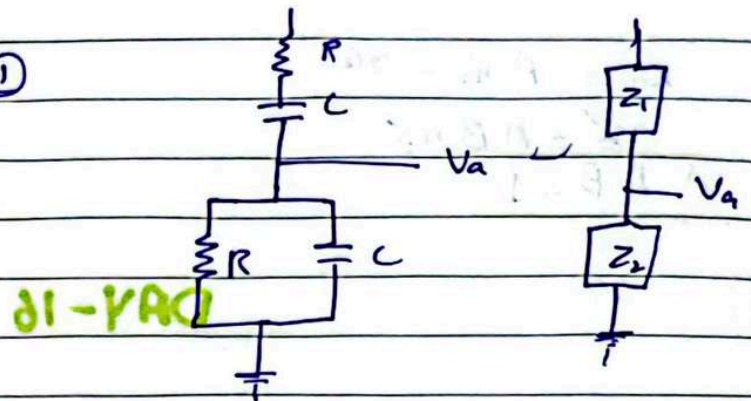
$$B(s) = \frac{1}{3 + (RC)s + 1/(RC)s} \rightarrow \textcircled{2}$$



According to Barkhausen's criteria

$$A(s) \cdot B(s) = 1$$

$$A(s) B(s) = \frac{1 + R_2/R_1}{3 + (RC)s + 1/(RC)s}$$

put $s = j\omega$

$$A(\omega) B(\omega) = \frac{1 + R_2/R_1}{3 + (RC)j + 1/j(RC\omega)}$$

$$A(\omega) B(\omega) = \frac{1 + R_2/R_1}{3 + j(RC\omega - 1/RC\omega)}$$

To get a real finite sine wave of freq. f_0 ,
 $A(\omega_0) B(\omega_0) = 1$ at $f = f_0$

$$A(\omega_0) B(\omega_0) = \frac{1 + R_2/R_1}{3 + j(RC\omega_0 - 1/RC\omega_0)}$$

zero

Date

If we make the imag. part = 0, then this whole thing becomes REAL.

To make the system real:

$$RC\omega_0 - 1 = 0$$

$$RC\omega_0 = 1$$

$$\omega_0^2 = \frac{1}{(RC)^2}$$

$$\omega_0 = \frac{1}{RC}$$

(Filter Design)

$$A(\omega_0) B(\omega_0) = 1$$

$$\frac{1 + R_2/R_1}{3 + j(RC\omega_0 - 1/RC\omega_0)} = 1$$

$$\frac{1 + R_2/R_1}{3} = 1$$

$$1 + \frac{R_2}{R_1} = 3$$

$$\frac{R_2}{R_1} = 2$$

$$\boxed{\frac{R_2}{R_1} \geq 2}$$

Filter:

$$\omega_0 = \frac{1}{RC}$$

given answer $\rightarrow$ we need to find C.


Date

Amp.

$$\frac{R_2}{R_1} \geq 2$$

put R_2 just a little more than twice

Limiter Circuit of Amplitude Control:

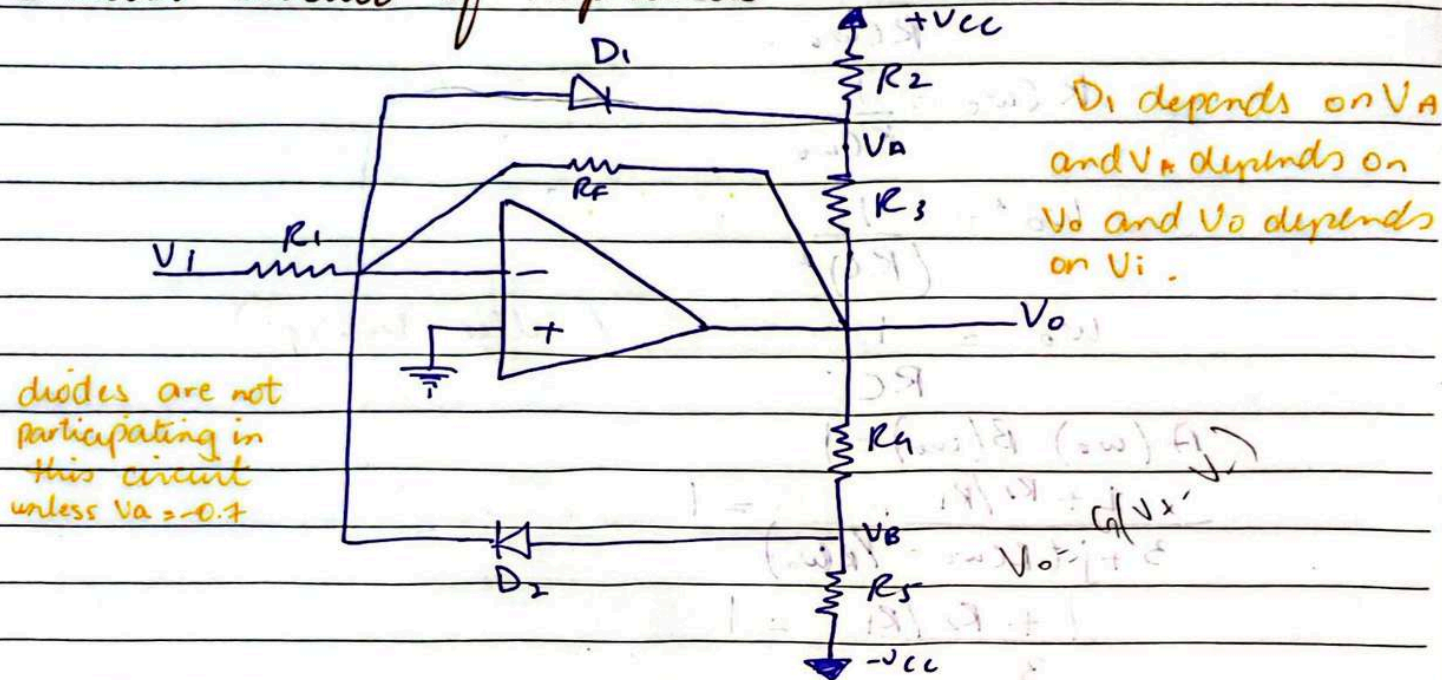

- V_i is very small (close to zero) but +ve
- $V_o = -\left(\frac{R_f}{R_i}\right) V_i$
- V_o is v. small but -ve ≈ -0.01
- V_i will gradually increase (+ve)
- V_o will be more & more (-ve)
- V_A will continue to decrease in magnitude until $V_A = -0.7V$.
At this point D_1 turns on.
- When diode turns on and becomes short circuited, it brings $R_3 \parallel R_f$

Date

$$V_o = - \left(\frac{R_3 \parallel R_F}{R_i} \right) V_i$$

$$\frac{R_F}{R_i} \gg \frac{R_3 \parallel R_F}{R_i}$$

$$G_1 \gg G_2$$


For negative half cycle

V_i is becoming more +ve

V_o is becoming more +ve

V_B is becoming less -ve
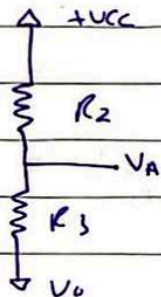
$$V_o = - \left(\frac{R_F \parallel R_4}{R_i} \right) V_i$$




$$V_A = \left(\frac{R_3}{R_3 + R_2} \right) V_{cc} + \left(\frac{R_2}{R_3 + R_2} \right) V_o$$

$$V_A = -V_D$$

$$V_o = L_-$$
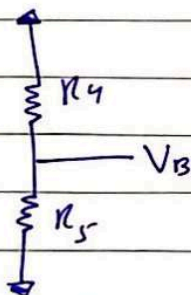
$$L_- = -V_{cc} \left(\frac{R_3}{R_2} \right) - V_D \left(\frac{1 + R_3}{R_2} \right)$$




$$V_B = \left(\frac{R_5}{R_4 + R_5} \right) (-V_{cc}) + \left(\frac{R_4}{R_4 + R_5} \right) V_o$$

$$V_B = +V_D$$

$$V_o = L_+$$

$$L_+ = +V_{cc} \left(\frac{R_4}{R_5} \right) + V_D \left(\frac{1 + R_4}{R_5} \right)$$

Date

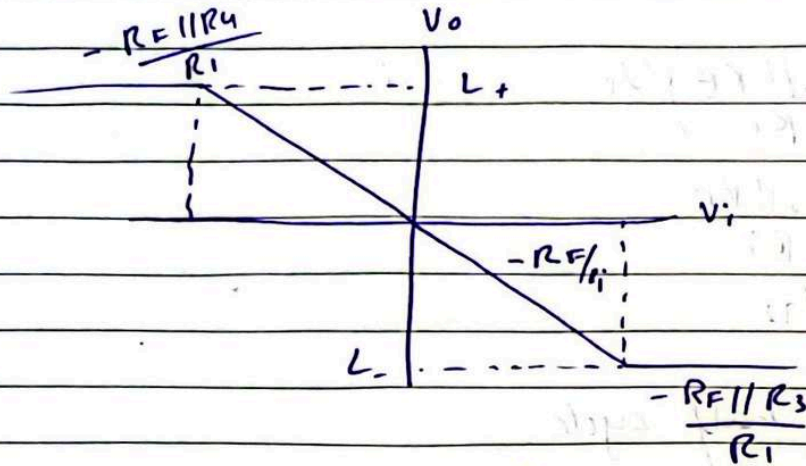

DAY-17

Multi-vibrator cct's for signal generation :-


- 1 BISTABLE MVB (2 stable states)
- 2 MONO STABLE MVB (1 stable state)
- 3 A - stable MVB (No stable state)

BISTABLE MVB

Bistability :: DC Amplifier in +ve feedback loop.

Open loop gain : $A \beta > 1$

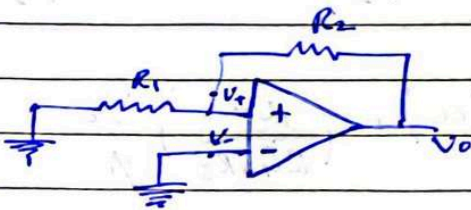Feedback contain a voltage divider of R_1 & R_2



$V_- \rightarrow 0V$

No ext. input voltage

Electrical noise in ckt introduces a small +ve voltage at

V_+

Date



Hence , $V_o' = A(V_+ - V_-)$

$\Rightarrow V_o' > 0$

Output is fed back at $V_+ = \left(\frac{R_1}{R_1 + R_2} \right) V_o'$

$V_o = \beta V_o'$

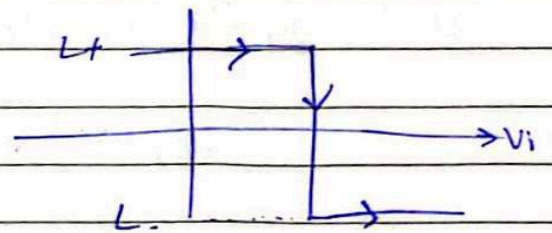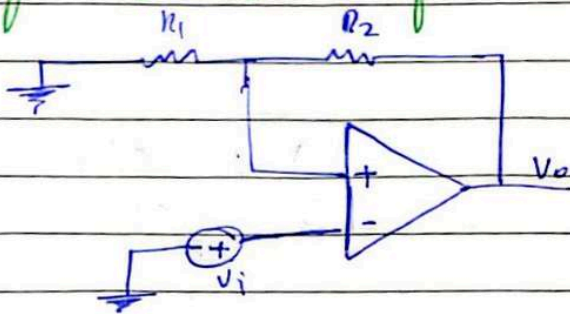
Transfer Characteristics of Bistable MVB :-



Suppose $V_o = L+$; $V_+ = \left(\frac{R_1}{R_1 + R_2} \right) L+ = \beta L+$

- $V_+ = \beta L+$
- $V_- = V_i$
- Amp ; $V_o = A(V_+ - V_-)$
- initially , $V_- = 0V$
- We start increasing V_i gradually

Now

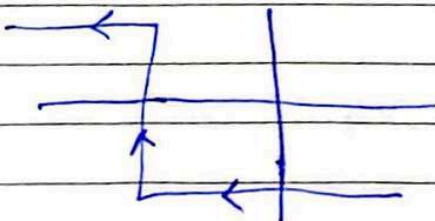

Date

Suppose $V_o = L_-$, $V_+ = \left(\frac{R_1}{R_1 + R_2} \right) L_- = \beta L_-$

$$V_+ = \beta L_- = -5V$$


$$V_- = V_i = 0_{-V}$$

$$Amp = V_o = A(V_+ - V_-)$$

initially $V_- = 0$

We start decreasing V_i gradually

Combining the two graphs

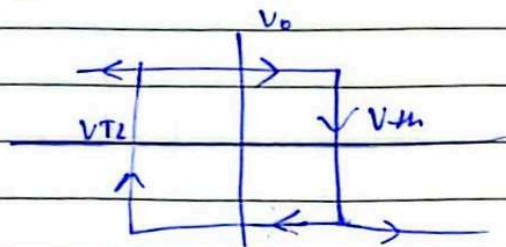


$$V_{TH} = \beta L_+$$

$$V_{TL} = \beta L_-$$

Hysteresis Comparator or Inverting Bistable MVB

If trigger $(V_i) > \beta L_+$ } V_o goes from L_+ to L_-

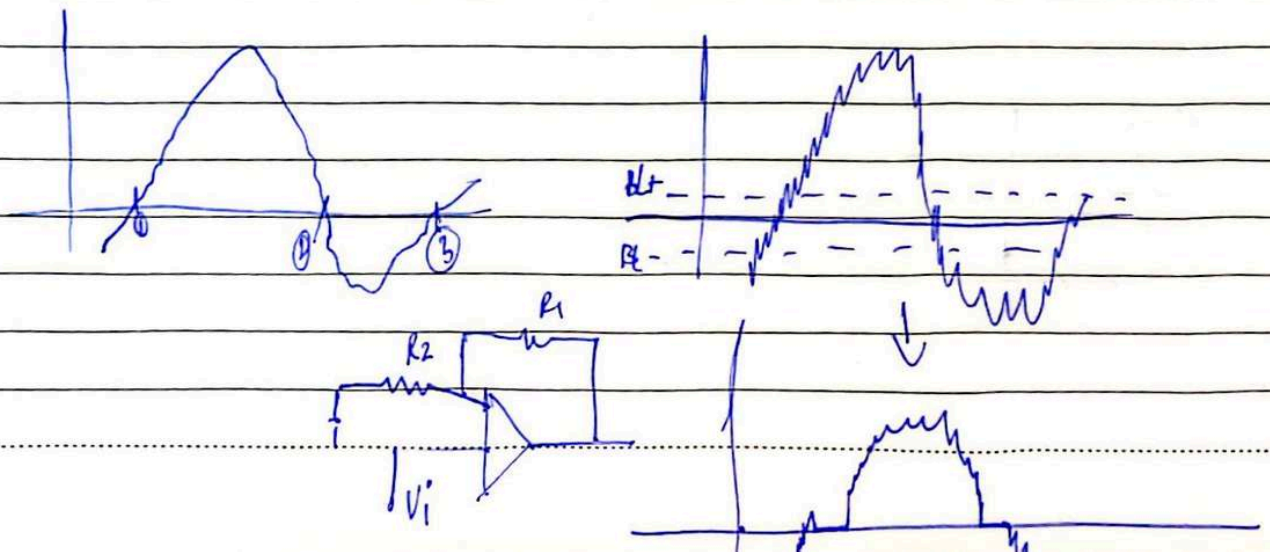If trigger $(V_i) < \beta L_-$ } V_o goes from L_- to L_+





Date

When you have a hysteresis comparator, it helps to eliminate the ripple near zero crossing of signal waveform.

DAY-18

Inverting Bistable MVB :

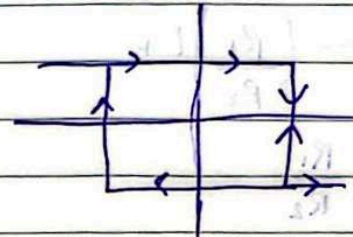
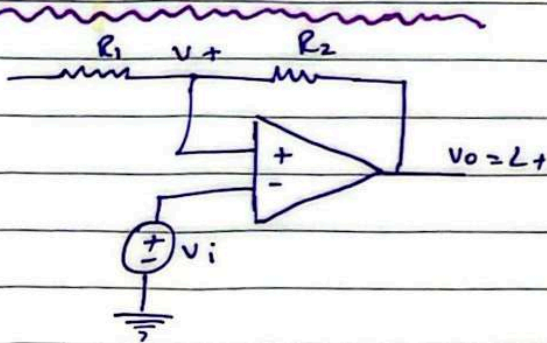


$$V_{th} = \beta L+$$

$$V_{TL} = \beta L-$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

Non-inverting Bistable MVB :

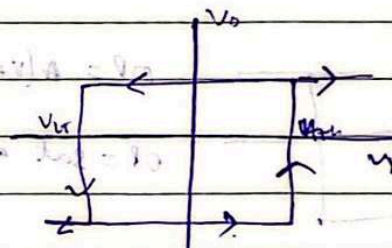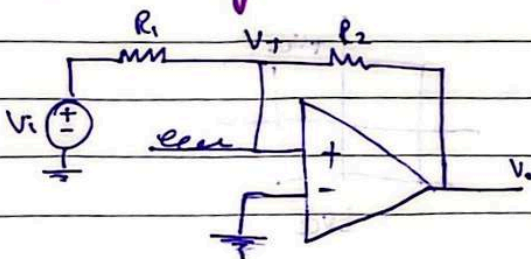


Date

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V_0$$

$$V_1 = \left(\frac{R_2}{R_1 + R_2} \right) V_i$$

$$V_+ = \left(\frac{R_1}{R_1 + R_2} \right) V_0 + \left(\frac{R_2}{R_1 + R_2} \right) V_i$$

81-YAD



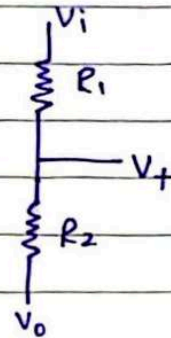


$$V_{th} = - \left(\frac{R_1}{R_2} \right) -$$

$$V_{th} = - \left(\frac{R_1}{R_2} \right) L +$$


$$\beta = \frac{R_1}{R_2}$$

Question :-

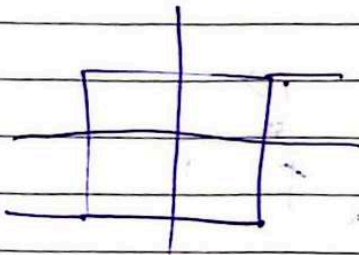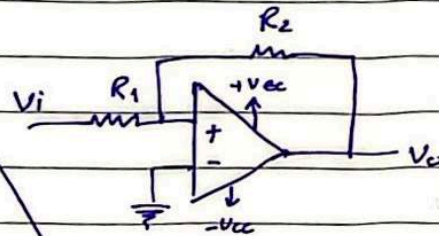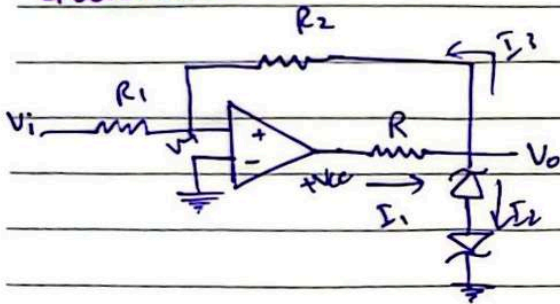

$$OP = A(V_+ - V_-)$$

$$OP = \text{sat at } +V_{cc}$$

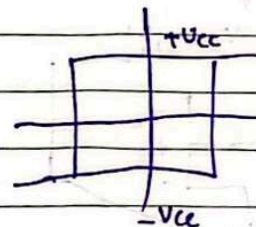

Date

PI-VAD

$$V_2 = 6.8V$$

$$V_D = 0.7V$$

$$V_o = V_2 + V_D$$

$$V_o = 7.5V$$

$$\text{If } V_+ < 0, \\ V_o = -7.5V$$


$$I_1 = \frac{V_{cc} - 7.5}{7.5k} = 10mA$$

$$I_2 = 7.5 - 0 = 0.5mA$$

$$I_2 = \frac{12 + 3k}{I_1 - I_2} \\ = 0.5mA$$

$$V_+ - 0 = (0.5m)(3k)$$

$$V_+ = 1.5V$$


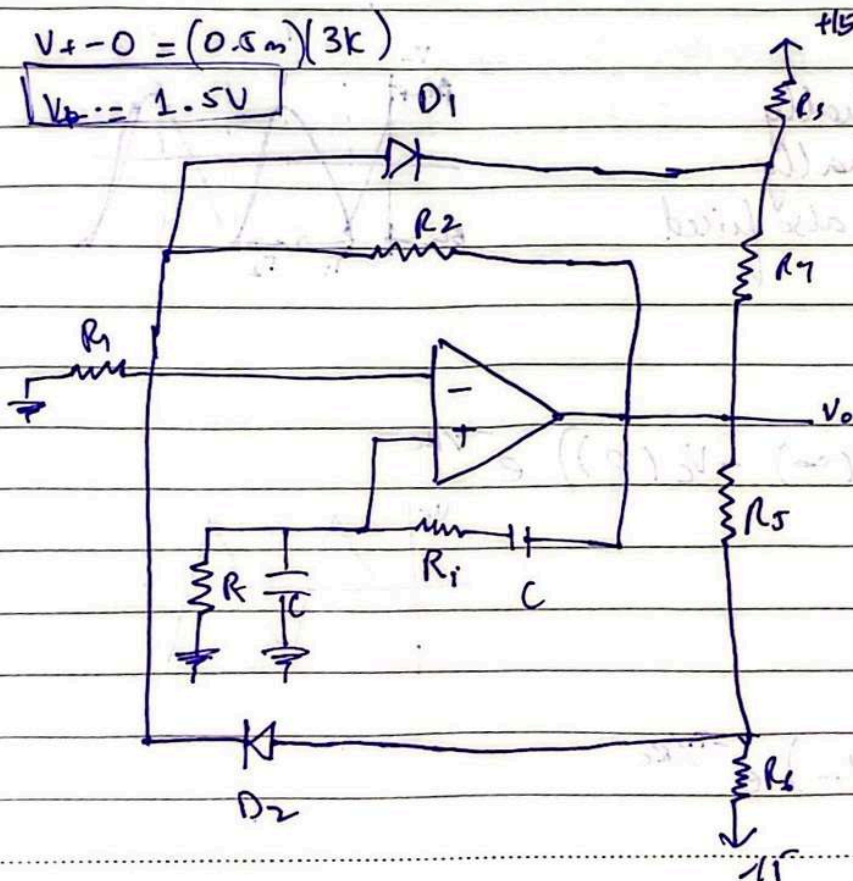


Date

DAY-19

ASTABLE MVB (using inv. bistable config.) :-

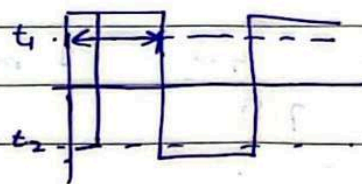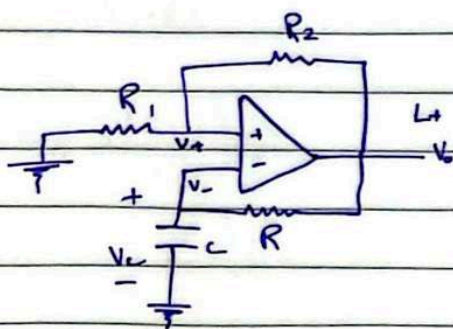- No stable state
- keeps toggling b/w $L+$ & $L-$.
- Used to generate square waves & rectangular waves.
- Uses BISTABLE MVB ckt. with an RC ckt. in -ve feedback.



$$V_o = A(V_+ - V_-)$$



$$V_- = V_c$$

initially $V_o = L+$, $V_+ = \beta L+$

V_c will start rising exponentially

V_- will start rising exponentially

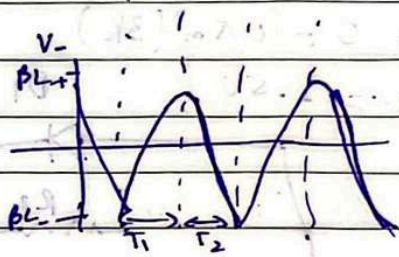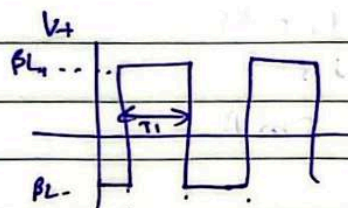Because $V_o = L+$ is fixed, V_+ is also fixed



Time Period :-

$T_1 =$

$$V_c(t) = V_c(\infty) - (V_c(\infty) - V_c(0)) e^{-t/RC}$$


$$V_c(0) = \beta L-$$

$$V_c(\infty) = L+$$

$$t = T_1$$

at $t = T_1$, $V_c(t) = \beta L+$
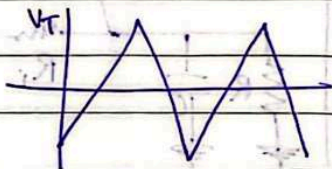
$$\beta L+ = L+ - (L+ - \beta L-) e^{-T_1/RC}$$



Date

$$T_1 = RC \ln \left(\frac{1 - B(L_-/L_+)}{1 - B} \right)$$

For sym. power supplies; $L_+ = -L_-$

$$T_2 = RC \ln \left(\frac{1 + B}{1 - B} \right)$$

Now for T_2 :

T_2

$$V_c(0) = BL_+$$

$$V_c(\infty) = L_-$$


$$t = T_2$$

$$\text{at } t = T_2, V_c(t) = BL_- \quad \text{OC-VAO}$$

$$T_2 = RC \ln \left(\frac{1 + B}{1 - B} \right)$$

having $T_1 = T_2$ because of having sym. power supplies, we will have perfect square wave.

Improvement:

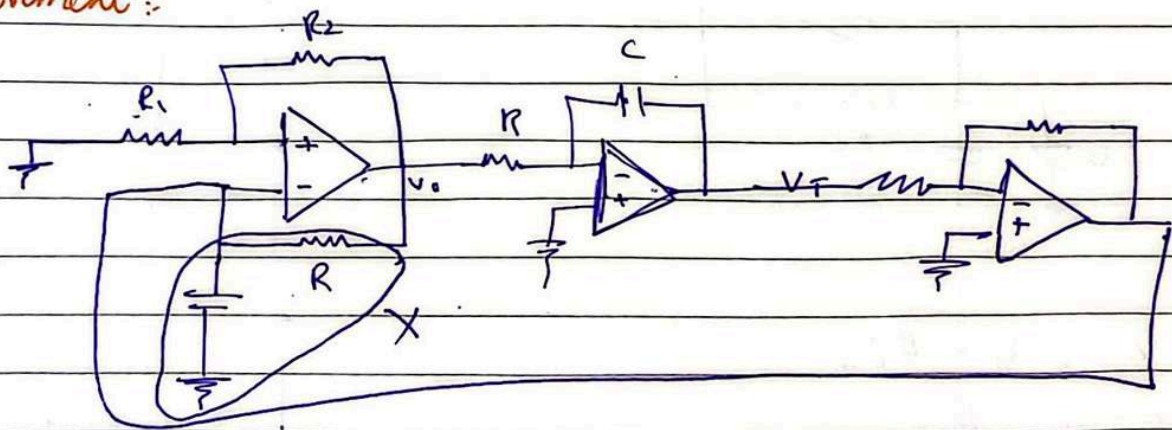

$$V_T = -\frac{1}{RC} \int V_0 dt$$

$$B = \frac{R_1 + R_2}{R_1 + R_2}$$

$$T = T_1 + T_2$$

Date

$$= -\frac{1}{RC} \int 10 \, dt$$

$$RC = 1$$

$$T_1 = RC \left(\frac{V_{TH} - V_{TL}}{L_+} \right)$$



$$T_2 = RC \left(\frac{V_{TH} - V_{TL}}{-L_-} \right)$$

$$V_{TH} = \beta L_+$$

$$V_{TL} = \beta L_-$$

DAY-20

Monostable MVB (Pulse Generator) :

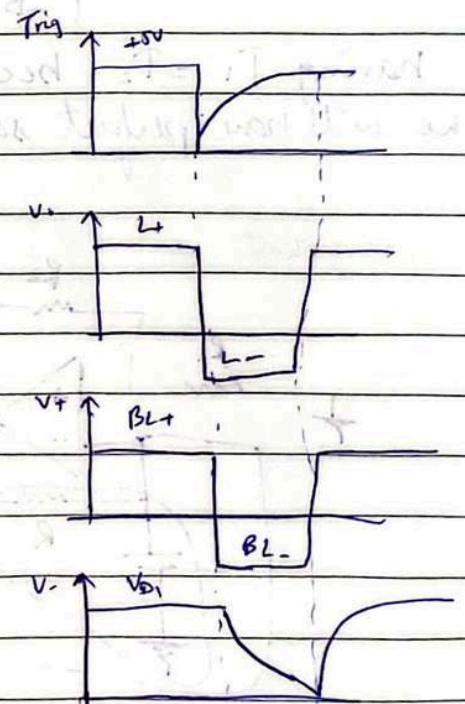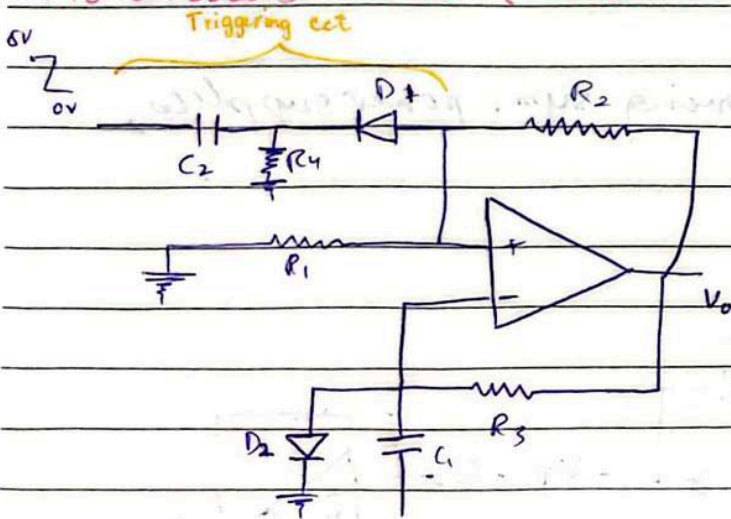

- $V_0 = L_+$, $V_+ = \beta L_+$
- Because $V_+ > \beta L_+$
- D₁ is reversed biased.
- D₁ is open

Date

- For I_n flow, D_2 is forward biased
- D_2 is short ckt.

Low pass filter acts as an integrator
High pass filter acts as a differentiator

- $$V_o = A(V_+ - V_-)$$
$$= A(0.7 - 0.7)$$

- When I apply a trigger; $V_k = 0V$
- D_1 becomes forward biased (short ckt)
- D_1 is short ckt, $0V$ at V_k will travel ahead & flow itself at V_+ .

- $$V_o = A(V_+ - V_-)$$
$$= A(0 - 0.7)$$

- In this ~~dist~~ duration, V_k becomes +ve again. D_1 is open again.

$$V_o = A(V_+ - V_-)$$
$$= A(0.7 - 0.7)$$
$$= 0 - (-12.00V)$$

Mathematical Derivation :-

$$V_c(t) = V_c(\infty) - (V_c(\infty) - V_c(0))e^{-t/R_1C_1}$$

$$V_c(0) = V_{D1}$$

$$V_c(\infty) = L_-$$

at $t = T$; $V_c(T) = BL_-$

$$BL_- = L_- - (L_- - V_{D1})e^{-T/R_1C_1}$$

Date

solving

$$T = R_3 C_1 \ln \left(\frac{V_{O1} - L_-}{B L_- - L_-} \right)$$


Date

solving

$$T = R_3 C_1 \ln \left(\frac{V_{D1} - L_-}{B L_- - L_-} \right)$$

DAY-21 (After Mid 2)


555 Timer Circuit:

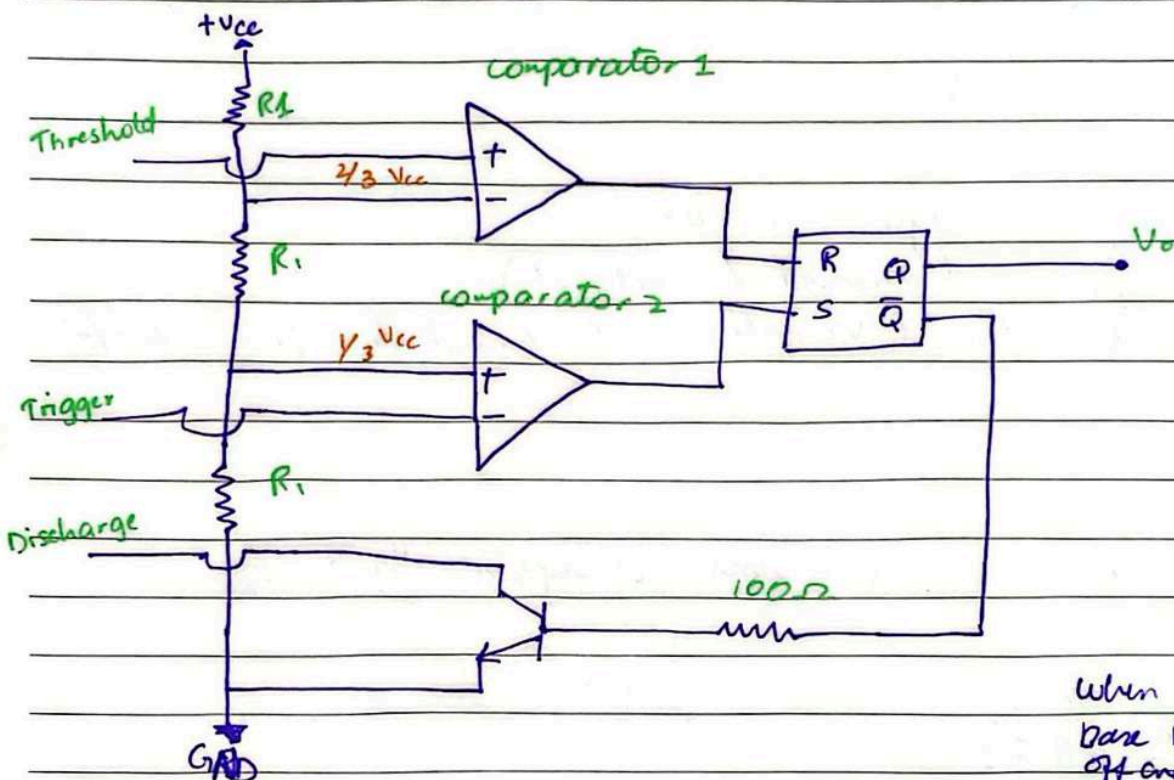

R	S	Q	Q̄
0	0	Pre-state	
0	1	1	0
1	0	0	1
1	1	undefined	

when we apply 0 at base NPN transistor turns off and become open circuit

General Concept:-

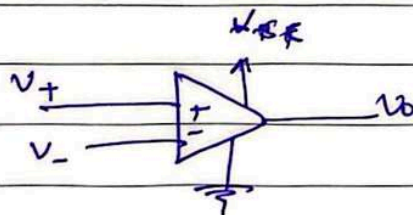

Date

$$V_+ > V_-$$

$$V_o \approx V_{cc}$$


(1)

$$V_+ < V_-$$

$$V_o = \text{GND or } V_{cc}$$

'0'

555 Timer Circuit as a monostable MVB:



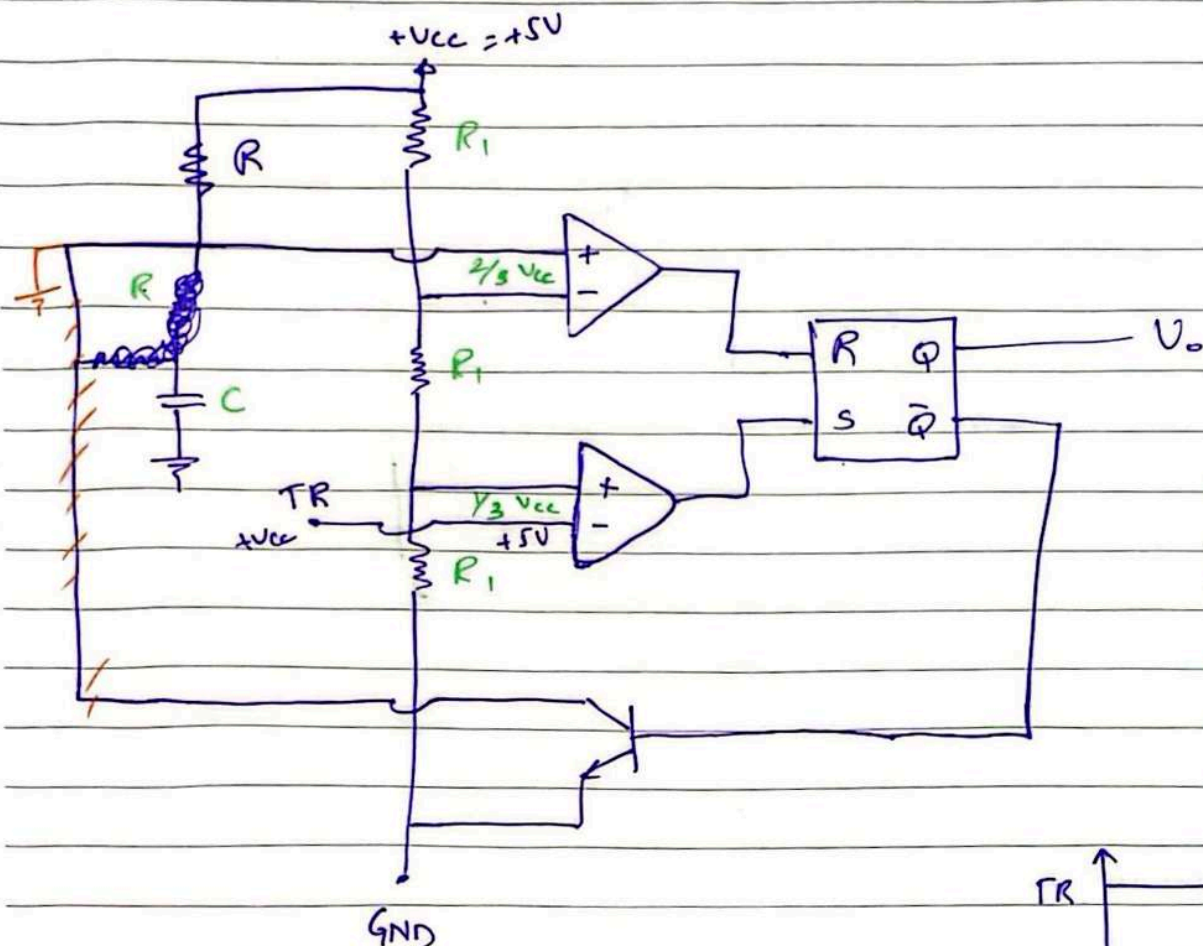


R	S	Q
0	0	prev.
0	1	1
1	0	0
1	1	0


- Suppose, we are in reset mode

$$T = (\ln 3) RC$$

$$T \approx 1.1 RC$$

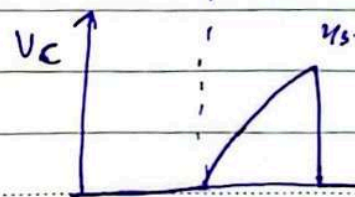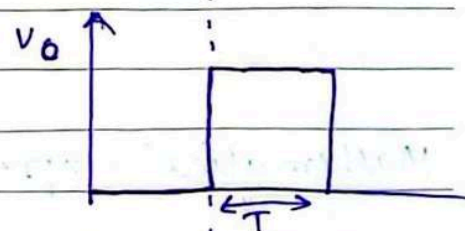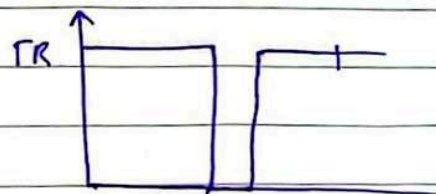


$\therefore$ At 1, transistor turns on (short open circuit)

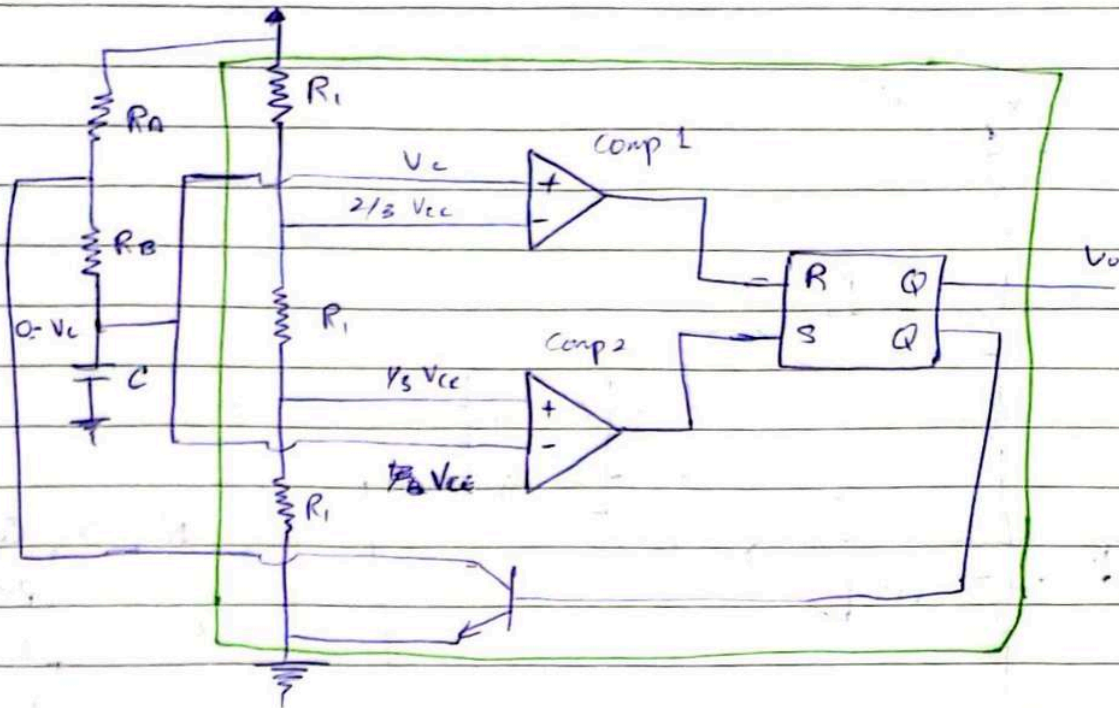A STABLE MVB using 555 Timer :-

R	S	Q
0	0	Prev
0	1	1
1	0	0
1	1	∞


Initially $V_C = 0$

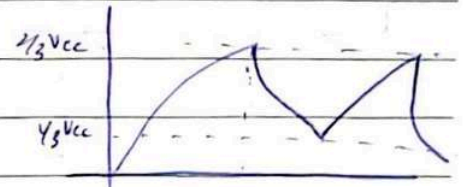

When capacitor is charging, it is through R_A & R_B . So $\tau = (R_A + R_B)C$

When capacitor is discharging, it is through R_B only. So $\tau = (R_B)C$

So T_H is larger than T_L

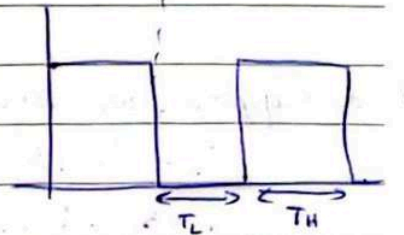Mathematical Expression:-


$$V_C(t) = V(\infty) - (V(\infty) - V(0))e^{-t/\tau}$$

$$V(\infty) = V_{CC}$$

$$V(0) = \frac{1}{3}V_{CC}$$

Date
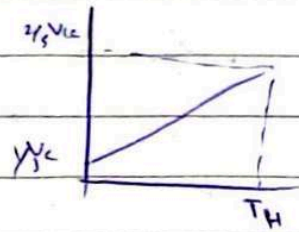
$$\text{at } t = T_H, V_C = \frac{2}{3} V_{CC}$$



$$\frac{2}{3} V_{CC} = V_{CC} - \left(V_{CC} - \frac{1}{3} V_{CC} \right) e^{-\frac{T_H}{(R_A + R_B)C}}$$

$$T_H = \ln 2 (R_A + R_B) C \rightarrow \text{imp formula}$$

For discharging

$$V_C(t) = V(\infty) - (V(\infty) - V(0)) e^{-t/R_C}$$

$$V(\infty) = 0$$

$$V(0) = \frac{2}{3} V_{CC}$$

$$\text{at } t = T_L, V_C = \frac{1}{3} V_{CC}$$

$$-\frac{1}{3} V_{CC} = 0 - \left(0 - \frac{2}{3} V_{CC} \right) e^{-\frac{T_L}{R_B C}}$$

$$T_L = \ln 2 (R_B C) \rightarrow \text{imp formula}$$

$$T = T_H + T_L$$

EC-VAD

$$T = (\ln 2) (R_A + 2R_B) C$$

Duty cycle:-

"The percentage of the total time period for which the signal is logic high or logic 1."

$$D = \frac{T_H}{T_H + T_L} \times 100$$
$$D = \frac{R_A + R_B}{R_A + 2R_B}$$

} IMP. FORMULAS

Date

One of the limitations of this circuit is that T_H is never equal to T_L in current setting of the circuit and therefore you can never achieve a 50% duty cycle and you can never achieve a square wave.

For 50% Duty cycle :-

$$T_H = (\ln 2)(R_A)C$$

$$T_L = (\ln 2)(R_B)C$$

$$T = T_H + T_L$$

$$= (\ln 2)(R_A + R_B)C$$

$$D = \frac{T_H}{T_H + T_L}$$

$$= \frac{R_A}{R_A + R_B}$$

$$R_A = R_B$$

DAY-23

555 Timer Circuit :-

For duty cycle > 50%

$$T_1 = (\ln 2)(R_A + R_B)C$$

$$T_2 = (\ln 2)(R_B)C$$

$$T = T_1 + T_2$$

$$= (\ln 2)(R_A + 2R_B)C$$

$$f = \frac{1}{T}$$

$$D = \frac{R_A + R_B}{R_A + 2R_B}$$

Date

For duty cycle $\leq 50\%$

$$T_1 = (\ln 2)(R_A)C$$

$$T_2 = (\ln 2)(R_B)C$$

$$T = (\ln 2)(R_A + R_B)C$$

$$f = \frac{1}{T}$$

$$D = \frac{R_A}{R_A + R_B}$$

Question :-

Use a 1nF capacitor in a 555 timer circuit, find the value of R to generate a pulse of 10 μ s.

Sol

$$T = (\ln 3)RC$$


$$10\mu s = (\ln 3) \times R \times 10^{-9}$$

$$R =$$

Question :-

Design and generate 2 circuit diagram that generate a 50% (square cycle) MVB that can generate perfect square wave signal.

Sol

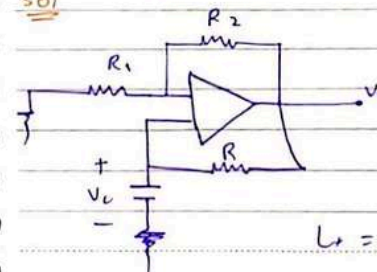

second circuit is a Astable MVB using 555 ckt.

$$T = RC \ln \left(\frac{1+B}{1-B} \right)$$

$$L_+ = -L_-$$

Date

NOTE:

- If we are talking about generating pulse, we are gonna draw MVB monostable diagram)
- If we talking about generating a signal or wave we gonna draw Astable MVB

Question ::

Use a 680pF capacitor, design a circuit with 555 timer that generate a rect. signal of 75% duty cycle & 50kHz frequency.

Sol

$$\frac{R_A + R_B}{R_A + 2R_B} = 0.75 = \frac{3}{4}$$

$$4R_A + 4R_B + 3R_A + 6R_B$$

$$R_A = 2R_B$$

$$f = 50\text{K} = \frac{1}{T} = 20\mu\text{s} = T$$

$$T = (\ln 2) (R_A + 2R_B) C$$

$$20\mu\text{s} = (\ln 2) (R_A + 2R_B) (680\text{p})$$

$$R_A + 2R_B = 42.432\text{K}$$

$$R_B = 10.5\text{K}\Omega$$


$$R_A = 21\text{K}\Omega$$

Cons :


This circuit does not provide any amplification for signal.

~~Defective by charging~~

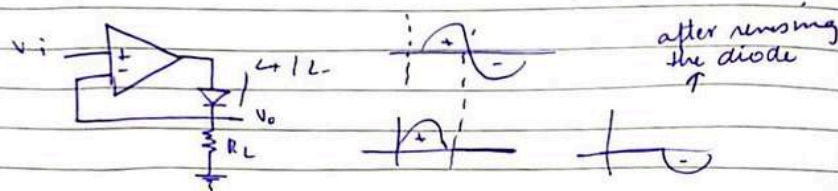Inflexible - it does not offer the feature as to which half cycle need to be passed.




Improved circuit:

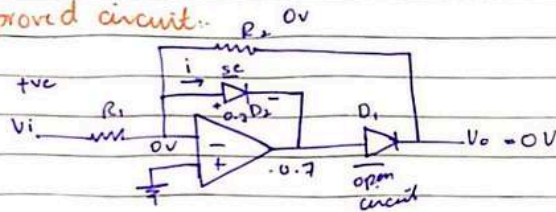

For +ve half cycle (⊕)

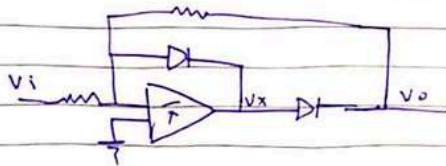- D_2 is forward biased $\rightarrow$ short circuit
- 'i' passes through D_2
- D_1 will be reverse biased $\rightarrow$ open circuit



For -ve half cycle


D_2 is reverse biased $\rightarrow$ OC

D_1 is forward biased $\rightarrow$ SC

It becomes an inverting OP-amp

$$V_o = -\left(\frac{R_2}{R_1}\right) V_i$$

AC Voltmeter: (V.V.V. IMP)

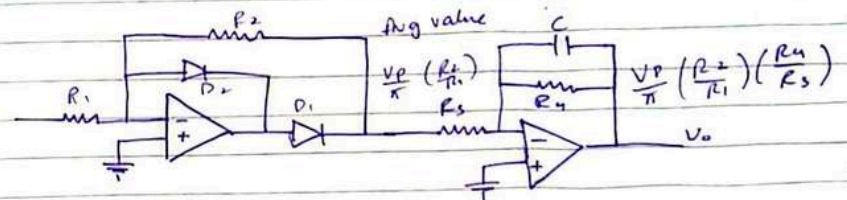

Precision Rectifier
DC gain = R_2/R_1

Low Pass Filter
DC gain = R_4/R_3

$$\text{Avg Value} = \frac{V_p}{\pi}$$

filter design
cutoff freq

$$\omega = \frac{1}{CR_4}$$

$$f = \frac{1}{2\pi CR_4}$$

$$V_o, \text{ avg} = \frac{V_p}{\pi} \left(\frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3}\right)$$

Date

$$W_c = \frac{1}{C R_u}$$

Question:

Design an AC voltmeter for a 10Hz input signal. It is calibrated for sine wave signal to provide +10V o/p for i/p of 1.0 V_{rms}. The R_{in} must as high as possible. Keep the gain of AC rectifier part to unity. The largest resistor available is 1.0 MΩ.

sol.

$$\frac{R_2}{R_1} = 1.0$$

Set R₁ & R₂ = 1MΩ

Convert RMS to peak

$$V_{RMS} = \frac{V_p}{\sqrt{2}}$$

putting in formula

$$V_o = \frac{V_p}{\pi} \left(\frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3} \right)$$

let R₄ = 1MΩR₃ = 45KΩ

$$W = \frac{1}{C R_u}$$




$$f = \frac{1}{2\pi C R_u}$$

$$C = 15.9 \text{ nF}$$

Date





DAY-25

Precision Full Wave Rectifier:

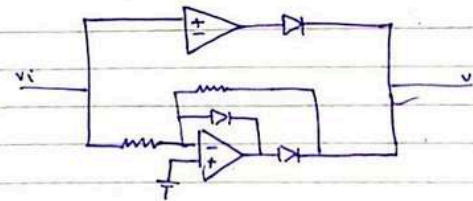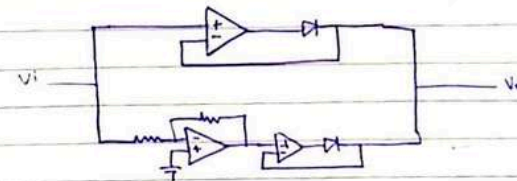
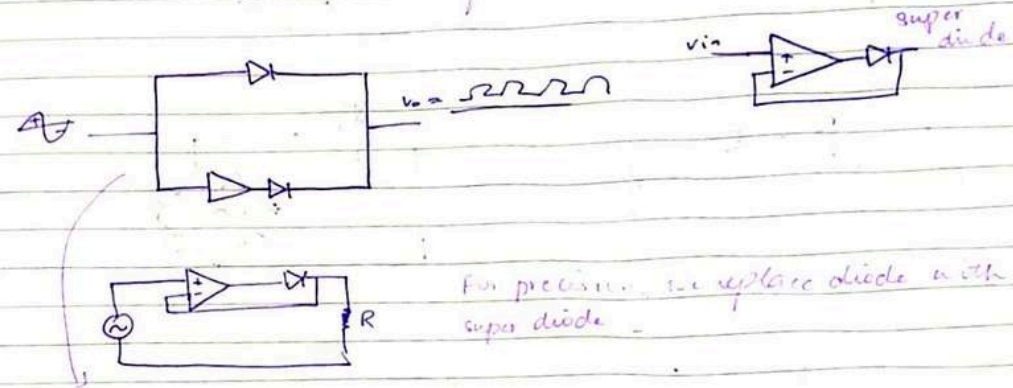


Date


DAY-20

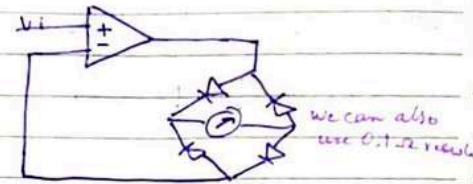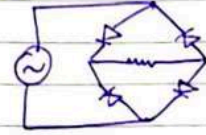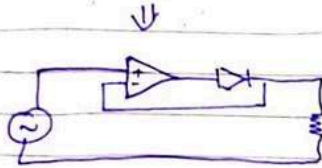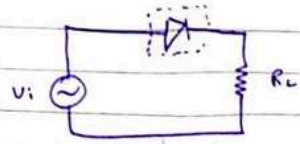


Peak Rectifier:

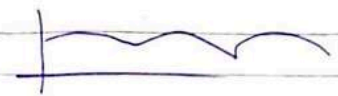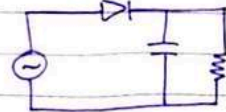

Precision Peak Rectifier:






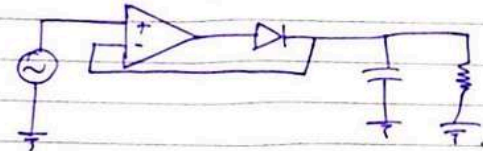


Buffered Precision Rectifier

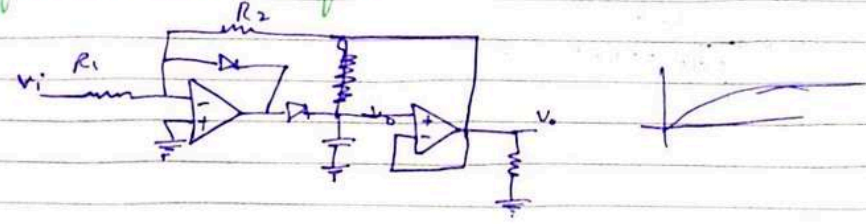

Date


CLAMPER:-

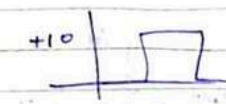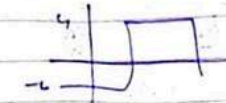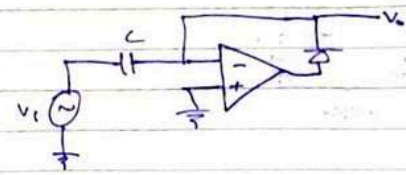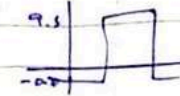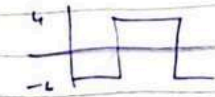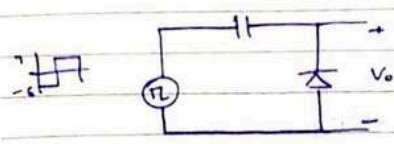

DAY-20

Digital logic Inverter:

Function of inverter:

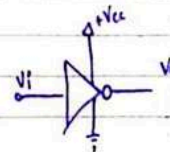


$[0.1 - 2.0V] \rightarrow '0'$
 $[3.5 - 5.0V] \rightarrow '1'$
 $[2.0 - 3.5V] \rightarrow$

$'1' \rightarrow V_{OH} = 5.0V$
 $'0' \rightarrow V_{OL} = 0.1V$
 $V = 2.2V$ (Undefined)


Date

Voltage transfer xtics:

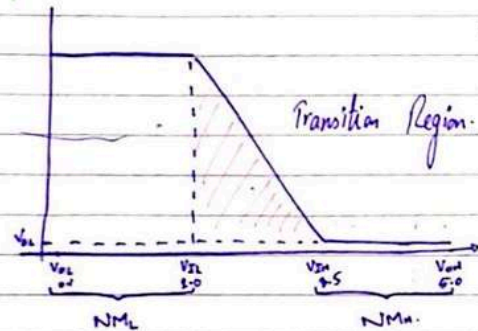


Noise Margin s:-

for NM_L

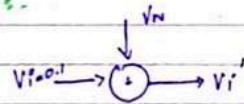


for NM_H

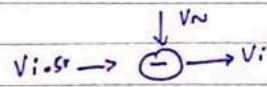

SS-VAG

ideal noise margin graph can be like

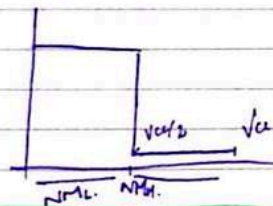

$$NM_H = NM_L = \frac{V_{CC}}{2}$$

$$V_{iL} = V_{iH} = \frac{V_{CC}}{2}$$

when $V_{oL} < V_i' < V_{iL}$; $V_o = V_{oH}$
 when $V_{iH} < V_i' < V_{oH}$; $V_o = V_{oL}$

$V_{iL} \rightarrow$ Max. V_i of an inverter that can be interpreted as logic low (0).



Date

$V_H \Rightarrow$ Min V_i of an inverter that can be interpreted as logic high (1).

$$NM_L = V_{iL} - V_{oL}$$

$$NM_H = V_{oH} - V_{iH}$$

Inverter Implementation:

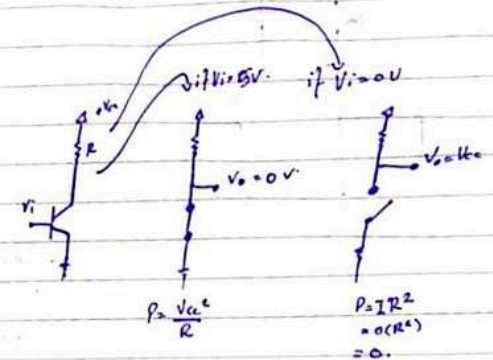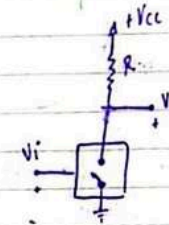


Using Complementary switches.

n-type:


logic 1 $\rightarrow$ SW close.
 logic 0 $\rightarrow$ SW open.

p-type:

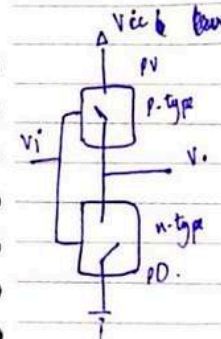
logic 1 $\rightarrow$ SW open.
 logic 0 $\rightarrow$ SW close.




V_i is low

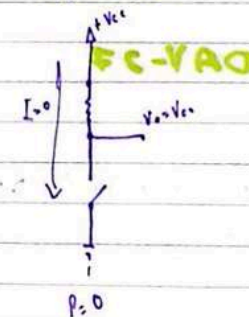

V_i is high.

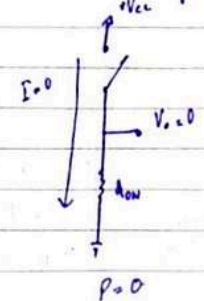

Dynamic Power Dissipation

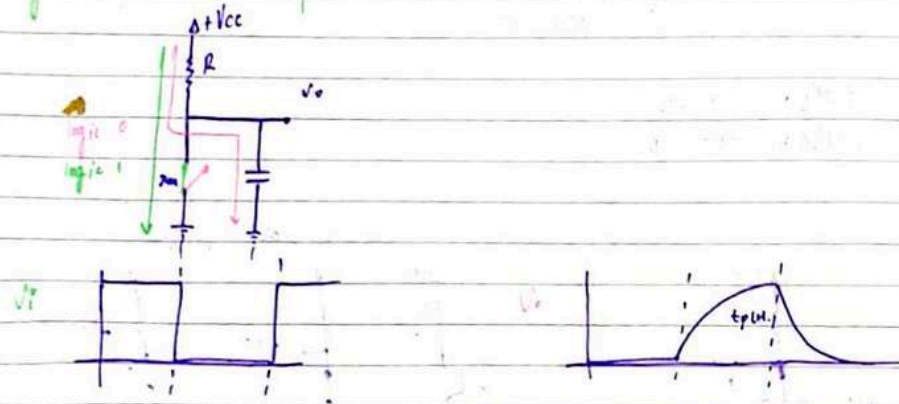

- Once the capacitor fully charged up current will stop flowing.
- Capacitor will discharge through short to resistor.

So charging & discharging power dissipation will be formed.


$$P_{dynamic} = f C V_{cc}^2$$

This topic was about CMOS. b'coz of its low power dissipation.

DAY-23

CMOS Logic Gate Circuits

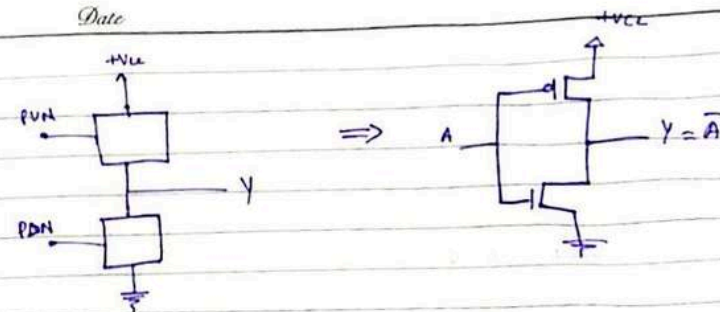1. Logic-level Inverter contain a PUN & PDN.
2. NMOS transistor $\rightarrow$ PDN
PMOS transistor $\rightarrow$ PUN



- Operated in complementary function
- $A = '1'$. NMOS is ON, PMOS is off. $Y = '0'$
- $A = '0'$. PMOS is ON, NMOS is off. $Y = '1'$

For other logic gates:

- PDN contain NMOS transistor only — conducts when gate input is high
- PUN contain PMOS transistor only — conducts when gate input is low

Two NMOS transistors in PDN or


Two PMOS transistors in PUN

- 1) Perform OR function when connected in parallel.
Perform AND function when connected in series

PDN is exact opposite of PUN.

i.e. two series NMOS transistors PDN can interpreted as two parallel PMOS "PUN".

PMOS is not gate followed by NMOS.

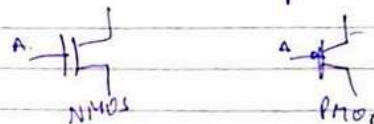

Date

Two i/p NOR Gate:

$$Y = \overline{A+B}$$

PUN : $Y = \overline{A+B}$

$$Y = \overline{A+B}$$

$$Y = A+B$$


} complement of PUN

implement PUN first!


Complement PUN to get PUN!

Two i/p NAND Gate:

$$Y = \overline{AB}$$


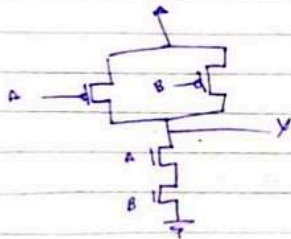


$$Y = \overline{A(B+CD)}$$

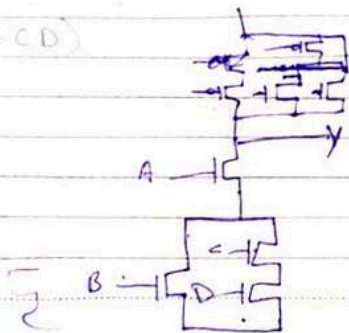


Date

$$Y = \overline{(A+B)(C+D)}$$

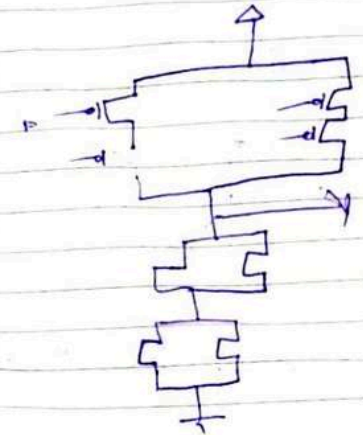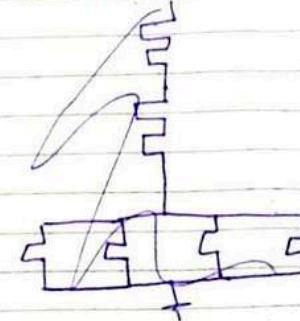

$$F = \overline{AB+CD}$$

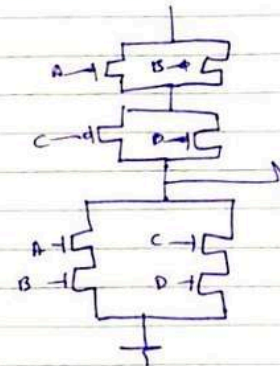


This was the first method of CMOS implementation

Date

2nd Method of CMOS implementation


$$Y = AB$$
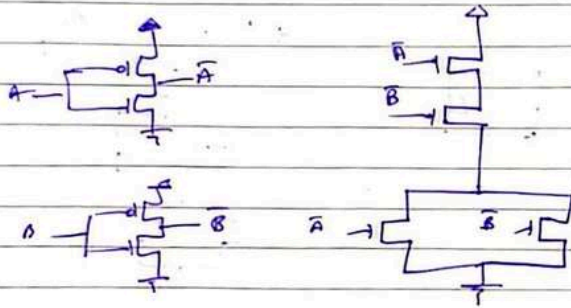
$$\bar{Y} = \overline{AB} = \bar{A} + \bar{B} \Rightarrow \text{PDN}$$



$$Y = A + BC$$
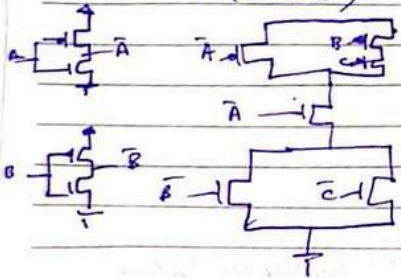
$$\bar{Y} = \overline{A + BC} = \bar{A} (\bar{B} + \bar{C})$$




3rd Method of CMOS implementation: (Post Inversion)


$$Y = AB$$

Date

$$F = \bar{A}\bar{B}$$

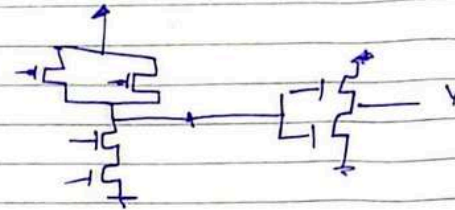

$$Y = A + B + C + D$$

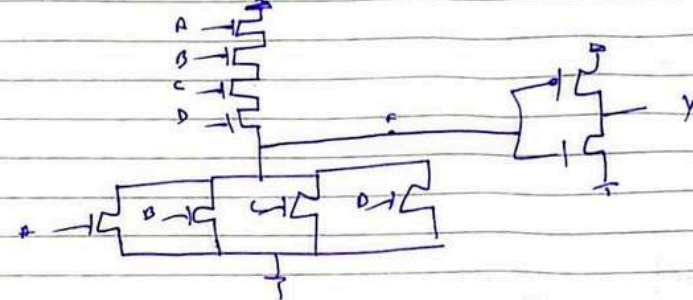

POST INVERSION

In first method, the equation is PUN. In second, we invert and have PUN. In third, we need a probe.

DAY-28


2nd Method

$$Y = AB$$

$$\text{PUN} = Y = AB$$

Date
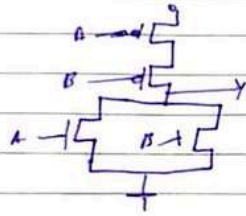
$$PDN = \overline{AB} = \overline{A} + \overline{B}$$



3rd Method


$$Y = AB$$



$$Y = \overline{F}$$

$$PDN = F = \overline{AB}$$

$$PDN = \overline{F} = AB$$

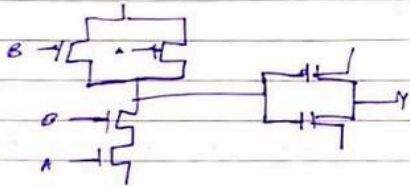



4th Method

$$Y = \overline{AB}$$

$$Y = \overline{A+B}$$

85-VAKI



NOR

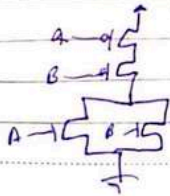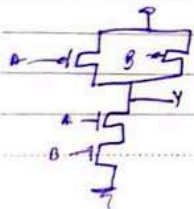

Date



$$Y = AB + CD$$

Make the CMOS circuit using gates only

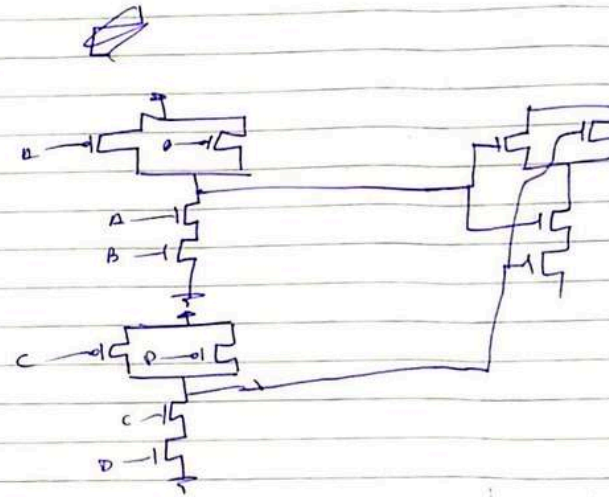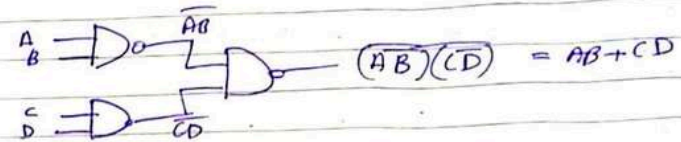


Date

$$Y = ABCD$$

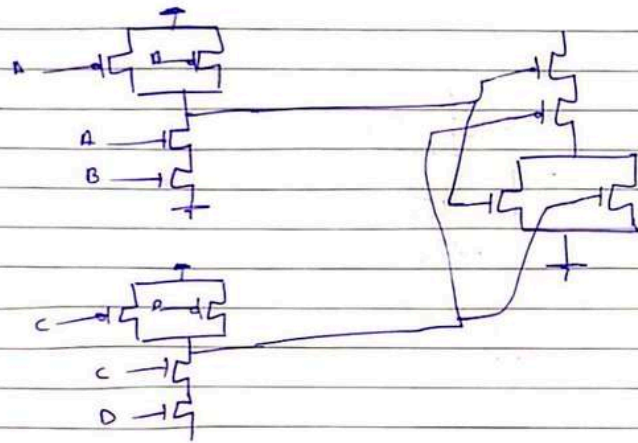
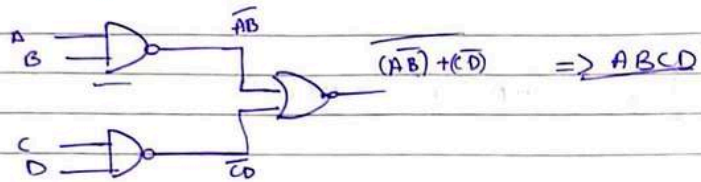


$$Y = (A+B)(C+D)$$

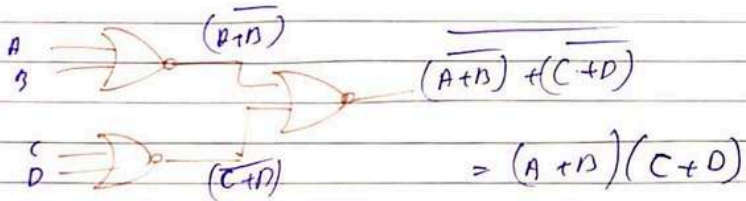

Date

$$A+B+C+D$$

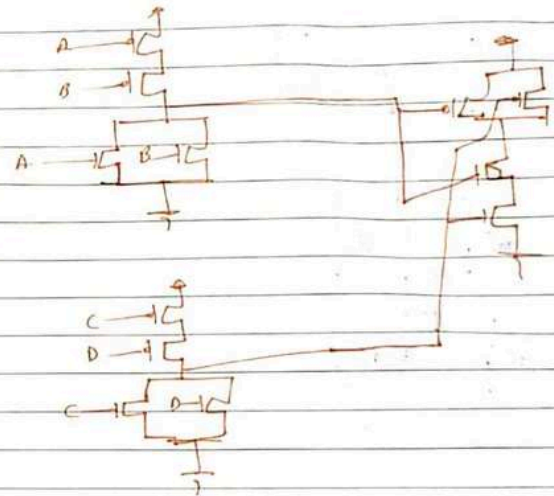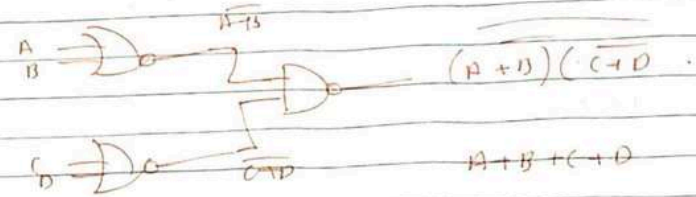

$$Y = AB + C + D$$






$$Y = AB(C+D)$$

Date

XOR Gate

PUN $Y = AB + \bar{A}\bar{B}$

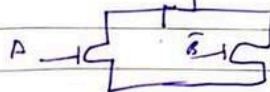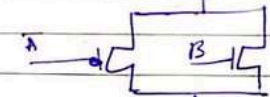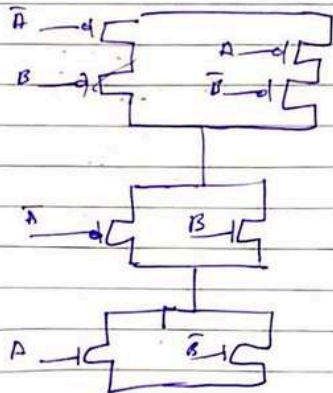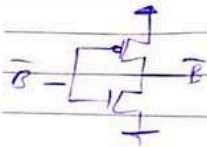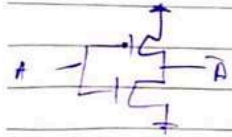PDN $\bar{Y} = A\bar{B} + \bar{A}B$
 $= (A+B)(\bar{A}+\bar{B})$



(2)

PUN $Y = AB + \bar{A}\bar{B}$

PDN $\bar{Y} = A\bar{B} + \bar{A}B$

Date

