

5th Oct 2022

Wednesday

TRANSISTOR

(Bipolar Junction Transistor)

BJT

MOSFET

NPN

PNP

P-channel

N-channel

→ Three terminal non-linear device

★ BJT → Emitter, Base, Collector



★ MOSFET → Source, Gate, Drain

Applications

amplifier

Switch

★ BJT

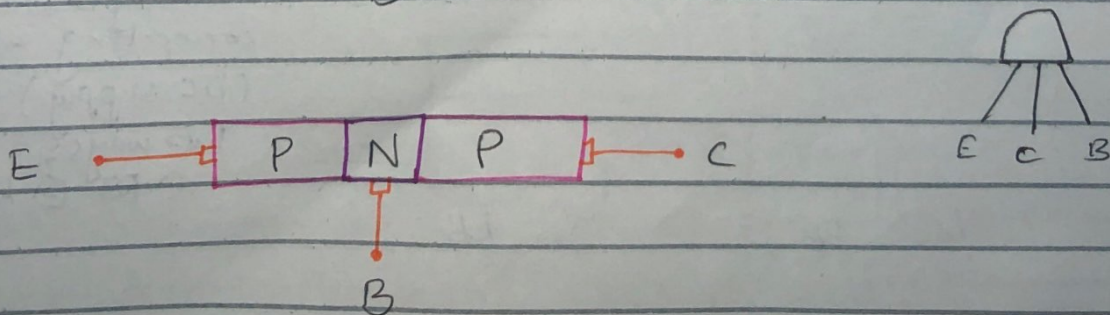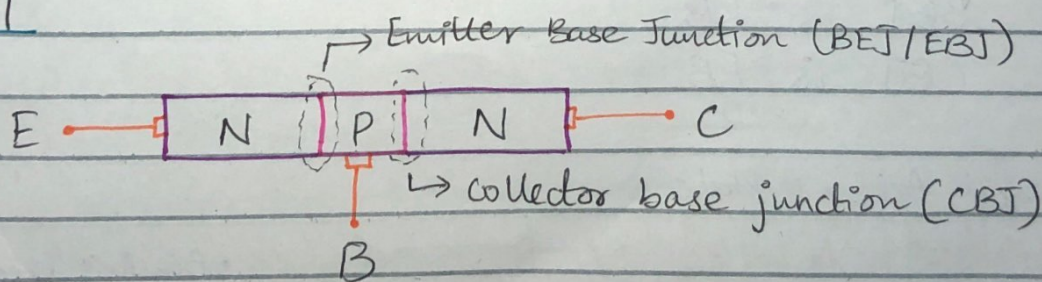

Modes of Operation: (depend on biasing)

① Forward Active / Amplification Mode

(Amplifier)

↓
BJT used as

EBJ / BEJ is FB
CBJ is RB

② Saturation Mode (ON Switch)

Both BEJ and CBJ are FB.

③ Cut off Mode (OFF Switch)


Both EBJ and CBJ are RB

④ Reverse Active / Inverse Mode

BEJ is RB

CBJ is FB


Forward Active Mode

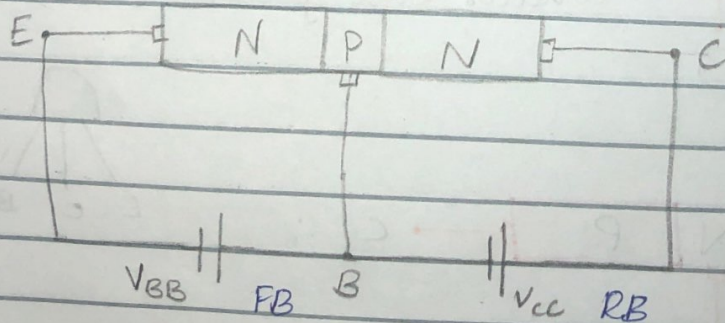


• Biasing means connecting a source (DC supply)

Two ways:

① FB ② RB

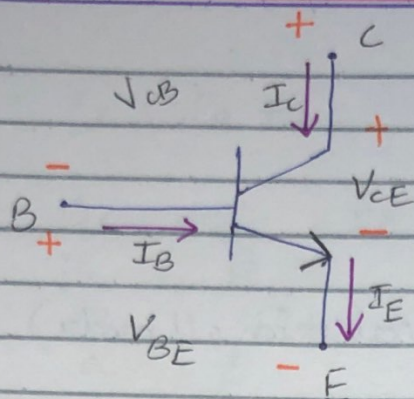

NPN

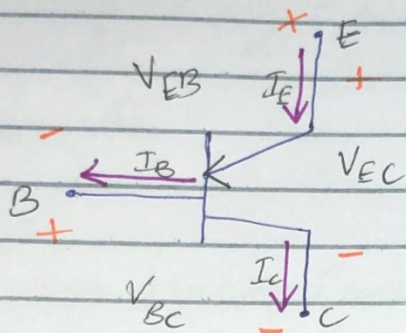

PNP

★ $I_E = I_B + I_C$ (saturation/active)

NPN

• $V_{BE} = V_B - V_E$
(red) (black)

• $V_{CE} = V_C - V_E$

• $V_{CB} = V_C - V_B$

PNP

• $V_{EB} = V_E - V_B$
(red) (black)

• $V_{BC} = V_B - V_C$

• $V_{EC} = V_E - V_C$

Parameters

(mainly for forward active mode)

① $\beta = \frac{I_C}{I_B}$, $\beta \approx 50-250$

② $\alpha = \frac{I_C}{I_E}$, $\alpha \approx 1$

Equations:

$$\bullet I_C = \beta I_B \quad \bullet I_C = \alpha I_E$$

$$\star I_E = I_B + I_C \quad (\text{applicable for all modes})$$

$$I_E = I_B + \beta I_B$$

$$\star I_E = I_B (1 + \beta)$$

$$I_E = I_B + I_C$$

$$\bullet I_B = \frac{I_C}{\beta} \quad I_E = \frac{I_C}{\beta} + I_C$$

$$\star I_E = I_C \left(\frac{1}{\beta} + 1 \right)$$

$$\bullet \frac{I_E}{I_C} = \beta$$

$$\frac{I_E}{I_C} = \frac{1}{\alpha}$$

$$\frac{I_E}{\beta I_B} = \frac{1}{\alpha}$$

$$\frac{1}{\alpha} = \frac{1 + \beta}{\beta}$$

$$\star \alpha = \frac{\beta}{1 + \beta}$$

$$\frac{I_C}{I_E} = \frac{1}{\alpha} = \frac{1 + \beta}{\beta}$$

$$I_E = I_B + I_C$$

$$\frac{I_C}{\alpha} = \frac{I_C}{\beta} + I_C$$

$$\frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\frac{1}{\beta} = \frac{1}{\alpha} - 1$$

$$\star \beta = \frac{\alpha}{1 - \alpha}$$

- Common Emitter Configuration (iskay ref say measurement)

Base $\rightarrow$ Input terminal - I_B, V_{BE}

Collector $\rightarrow$ Output terminal - I_C, V_{CE}

- Common Base Configuration

Emitter $\rightarrow$ Input terminal - I_E, V_{BE}

Collector $\rightarrow$ Output terminal - I_C, V_{CB}

• Base can never be output terminal (always input)

• Collector can never be input terminal (always output)

- Common Collector Configuration

Base $\rightarrow$ Input terminal - I_B, V_{CB}

Emitter $\rightarrow$ Output terminal - I_E, V_{CE}

- Voltages taken w.r.t NPN/PNP

Monday

10th Oct 2022


Input Characteristics:

A graph between input voltage & input current for constant output voltage


Output Characteristics:

A graph between output voltage & output current for constant input current.


① Common Base (CB)

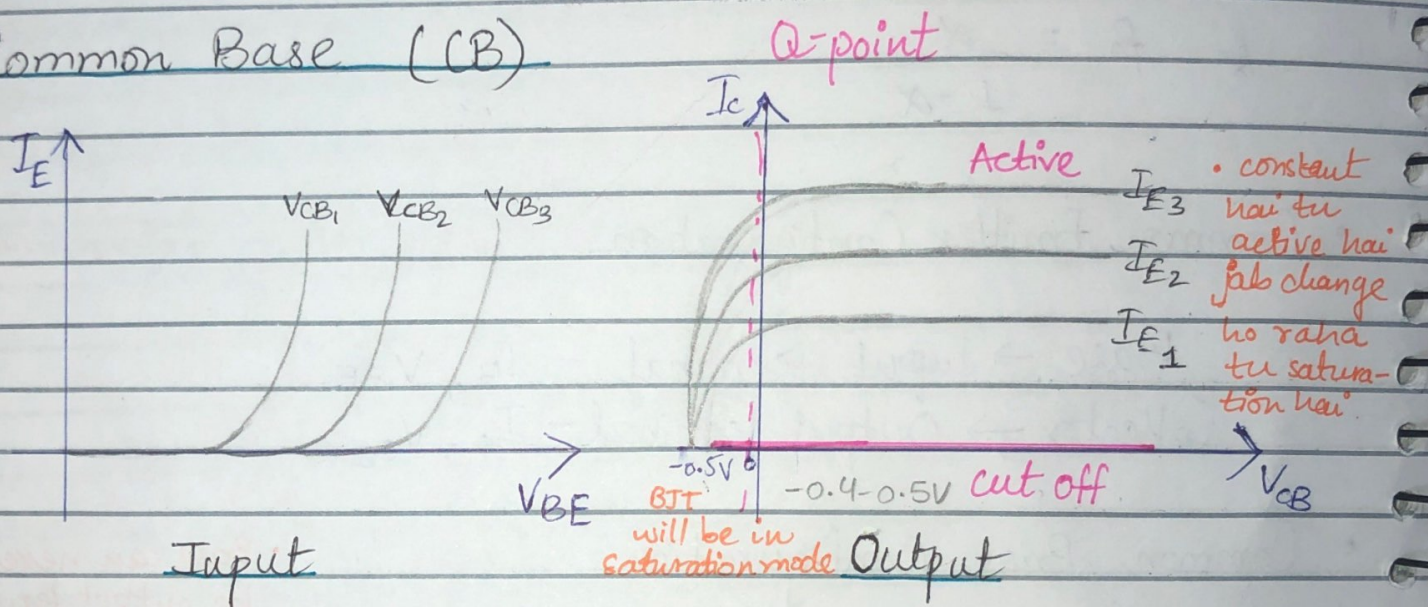


② Common Emitter (CE)

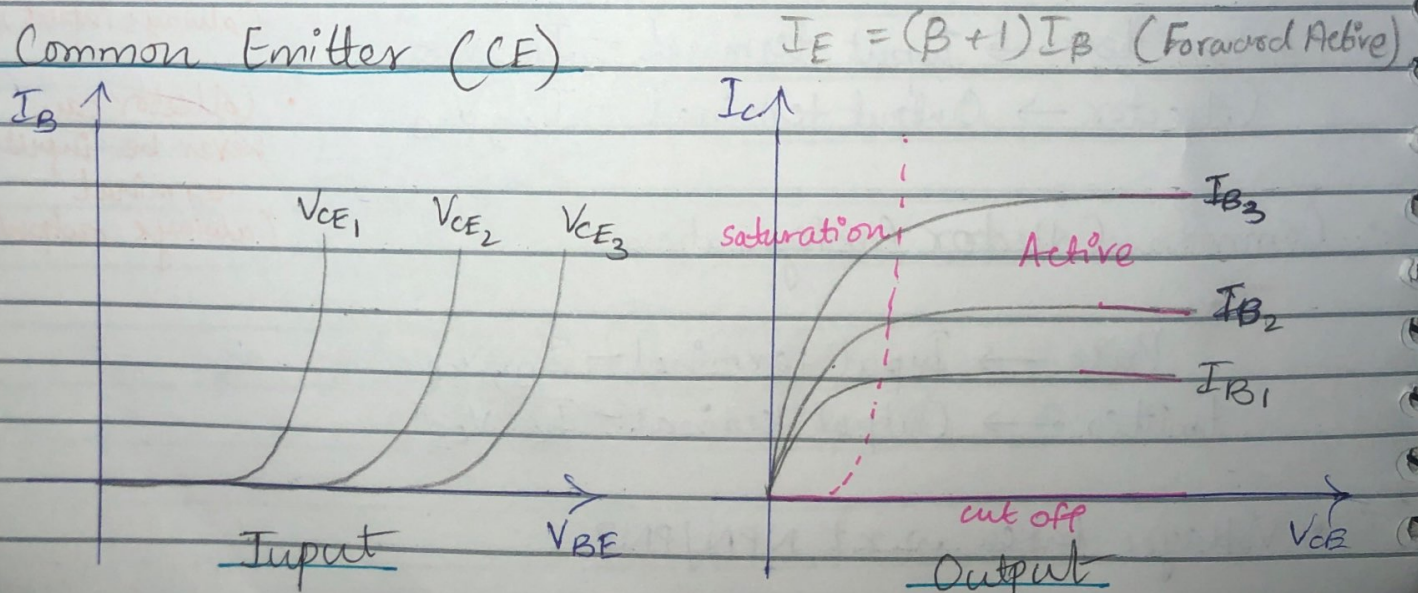

③ Common Collector

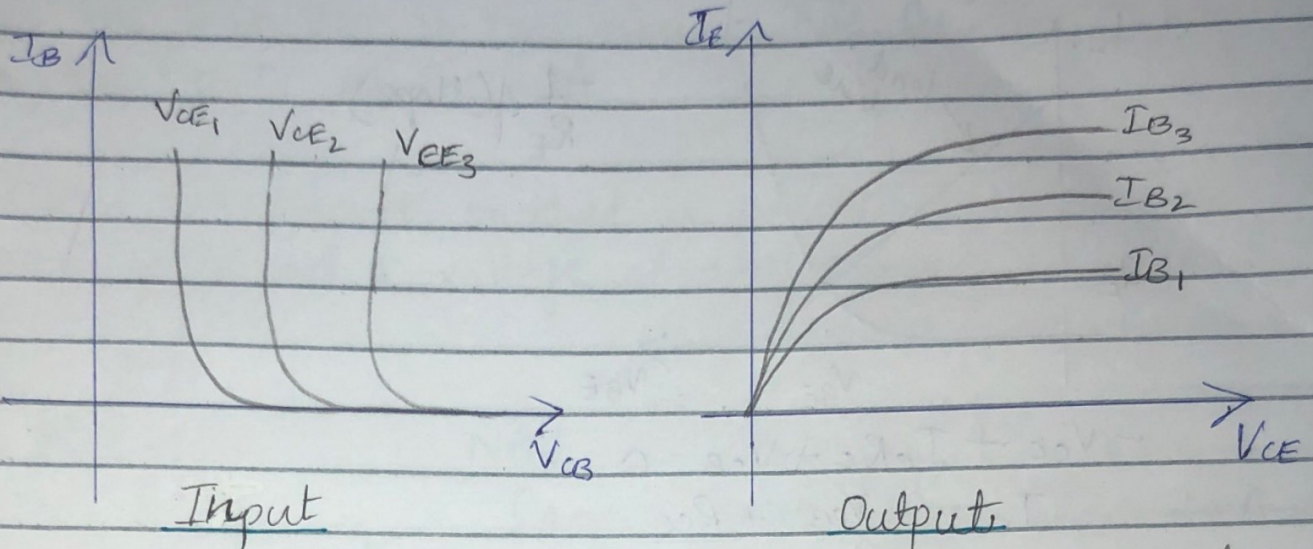

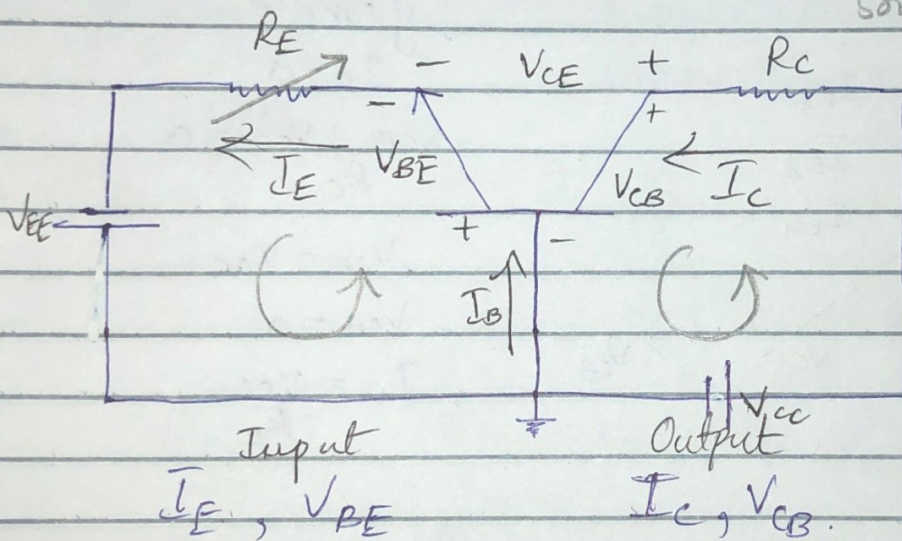$I_C < I_E$ • BJT acts as a constant current source in active mode.



NPN
Common Base
Configuration

Input: $-V_{EE} + V_{BE} + I_E R_E = 0$


Output: $-V_{CC} + V_{CB} + I_C R_C = 0$

$$I_E = \frac{-V_{BE}}{R_E} + \frac{V_{EE}}{R_E}$$

$$y = m x + c$$


$\downarrow$ $\downarrow$
 $-\frac{1}{R_E}$ $\frac{V_{EE}}{R_E}$

Graphical Analysis

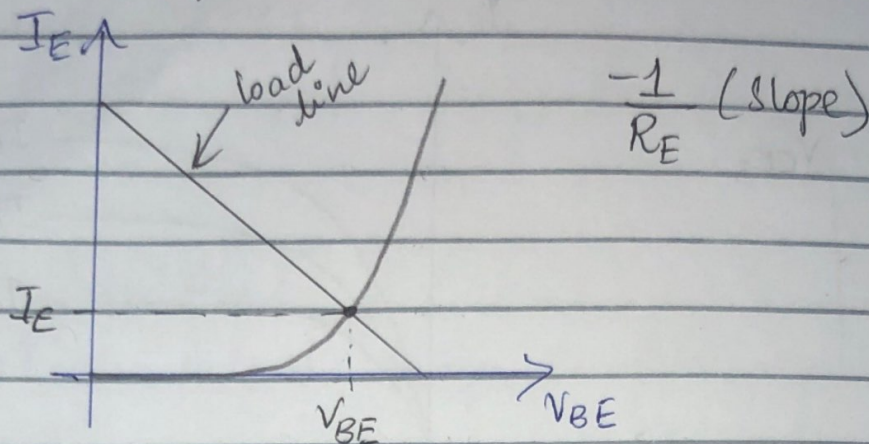

$$-V_{CC} + I_C R_C + V_{CB} = 0$$

$$I_C = \frac{-V_{CB} + V_{CC}}{R_C}$$

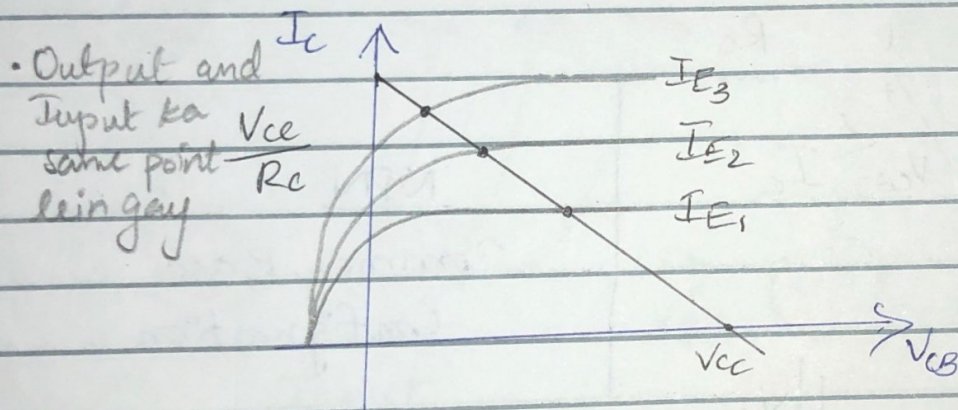

$$y = mx + c$$

$$I_C = 0$$

$$\frac{-V_{CB} + V_{CC}}{R_C} = 0$$

$$V_{CB} = V_{CC}$$

$$V_{CB} = 0$$

$$I_C = \frac{V_{CC}}{R_C}$$

Mathematical Analysis

Input

Assume $V_{BE} = 0.7V$

Output


we need α and β

Wednesday

12th Oct 2022

Q: The transistor in the circuit has $\beta = 100$ and exhibits a $V_{BE} = 0.7V$ at $I_C = 1mA$

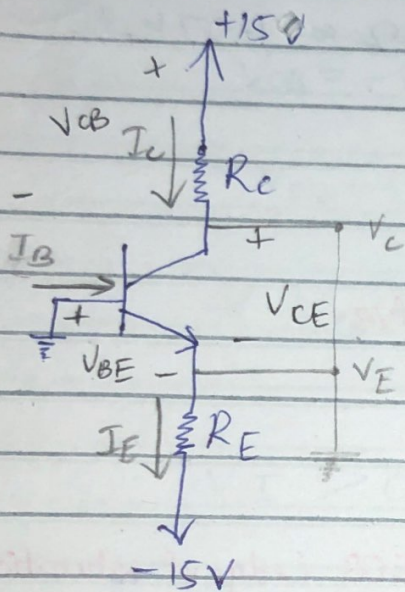Design the circuit so that a current of $2mA$ flows through the collector and a voltage of $+5V$ appears at collector.



NPN

Common Base

$$I_C = 2mA$$

$$V_C = 5V$$

$$V_B = 0V$$

Input: I_E, V_{BE}

Output: I_C, V_{CB}

$$I_E = \frac{I_C}{\alpha}$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{100}{101} = 0.99$$

$$I_E = \frac{2mA}{0.99} = 2.02mA$$

$$R_C = ?$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{15 - 5}{2mA} = 5k\Omega$$

$$R_E = ?$$

$$R_E = \frac{V_E - (-15)}{I_E}$$

$$I_C = I_S e^{V_{BE}/V_T}$$

$n=1$ always in BJT

$$V_{BE_2} = V_{BE_1} + 2.3nV_T \log \frac{I_2}{I_1}$$

$$V_{BE} = 0.7 + 2.3(1)(25m) \log \frac{2mA}{1mA} = 0.717V$$



$$V_{BE} = V_B - V_E$$

$$0.717 = 0 - V_E$$

$$V_E = -0.717V$$

$$R_E = \frac{-0.717 + 15}{2.02m} = 7070.80 \Omega \approx 7.07k\Omega$$

Large Signal Analysis

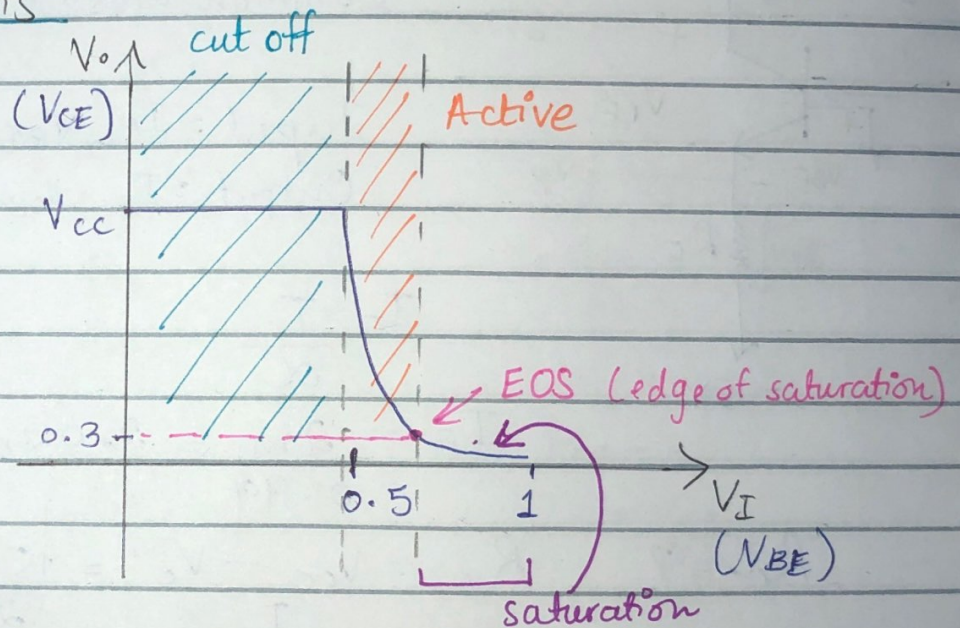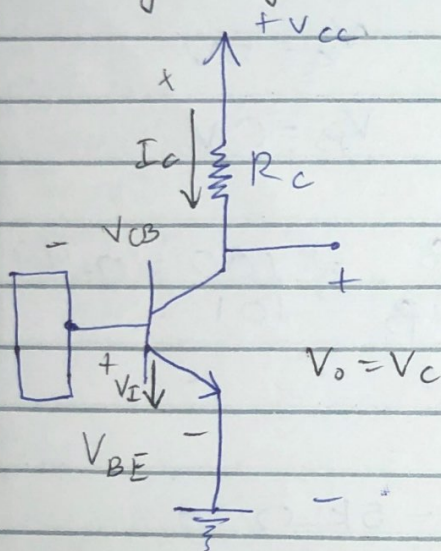

$$* V_C = V_{CE} = V_O = V_{CC} - I_C R_C$$

- ① $V_I < 0.5V$ (it starts conduction according to our assumption)

BEJ is reverse biased

$$\text{cut off } i_B = 0 \Rightarrow i_C$$

- ② $V_I > 0.5V$

$$I_c = \beta I_B \quad I_c = I_{se}^{V_{BE}/V_T}$$

V_{BE} = forward biased.

The transistor is going from cutoff to Active mode.

$V_{CB} = -V_E$ = forward biased.

$V_{CB} = V_C - V_B$ (If base will be at higher potential P higher than N)

* $V_{CB} < -0.4$ (saturation)
 $\downarrow$
 active mode

$$V_I > 0.5V$$

$$V_o = V_{cc} - \overbrace{I_{se}^{V_{BE}/V_T}}^{I_c} R_c$$

$$V_o = V_{cc} - I_c R_c$$

$$V_{BE} > 0.4V$$

$$V_{CB} = -0.4V \text{ (edge of saturation)}$$



is the last point of active mode
 after which transistor enters saturation mode.

* $V_{CB} = V_{CE} - V_{BE}$

$$V_{CB} = V_{CE} - V_{BE}$$

$$= V_C - \cancel{V_E} - [V_B - \cancel{V_E}]$$

$$= V_C - V_B$$

$$-0.4 = V_{CE} - 0.7$$

$$\boxed{V_{CE} = 0.3V} \text{ (EOS)}$$

Edge of Saturation:


$$V_{CE} = 0.3, I_C \text{ (EOS)}$$

For Saturation:

$$V_{CE(sat)} = 0.2V \text{ (less than } 0.3), I_C(sat).$$

Monday

17th Oct 2022

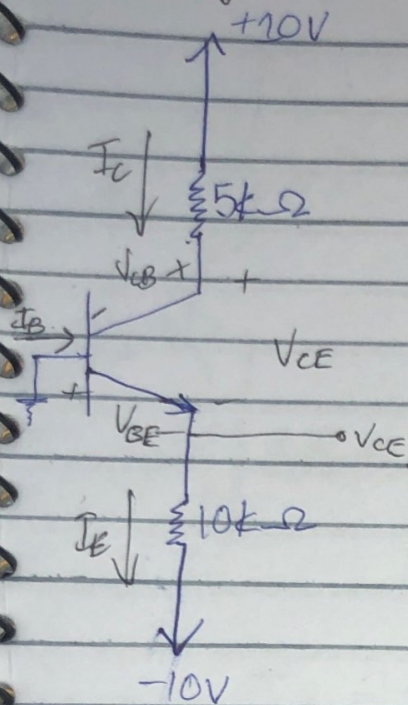

$$\rightarrow \beta = 50$$

$\rightarrow$ Analyze the circuit.

$$\text{find } I_C, I_B, I_E = ?$$

$$V_C, V_B, V_E = ?$$

Operating Mode = ?

Assume Active mode

$$V_{BE} = 0.7V$$

$$V_{CB} = V_C - V_B$$

$$V_{BE} = V_B - V_E$$

$$I_E = I_B + I_C$$

$$0.7 = 0 - V_E$$

$$V_E = -0.7$$

$$I_E = \frac{-0.7 - (-10)}{10 \times 10^3} = 9.3 \times 10^{-4}$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{50}{51} \approx 0.9804$$

$$I_C = I_E \alpha = (9.3 \times 10^{-4})(0.9804) = 9.118 \times 10^{-4} = 0.912 \text{ mA}$$


$$I_B = \frac{I_C}{\beta} = \frac{0.912 \text{ mA}}{50} = 18.24 \mu\text{A}$$

$$V_C = 10 - I_C R_C$$

$$V_C = 10 - (0.912 \times 10^{-3})(5 \times 10^3) = 5.44 \text{ V}$$

$$V_{CB} = V_C - V_B = 5.44 - 0 = 5.44$$

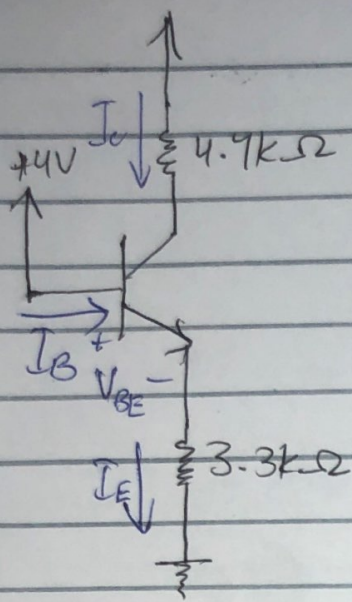(not less than -0.4 V , so assumption is correct and BJT is operating in active mode).



$$\beta = 100$$

$$\alpha = \frac{100}{1+100} = 0.99$$

Assume active mode

$$V_{BE} = 0.7V$$

$$V_{BE} = V_B - V_E$$

$$V_B = 4$$

$$0.7 = 4 - V_E$$

$$V_E = 3.3$$

$$I_E = \frac{3.3}{3.3 \times 10^3} = 1mA$$


$$I_C = \alpha I_E = 0.99 \times 1 \times 10^{-3} = 990 \mu A$$

$$I_B = \frac{I_C}{\beta} = \frac{990 \times 10^{-6}}{100} = 9.9 \mu A$$

$$V_C = 10 - I_C R_C = 10 - (990 \mu)(4.7k) = 5.36V$$

$$V_{CB} = V_C - V_B = 5.36 - 4 > -0.4V$$

$$= 1.36 > -0.4V$$

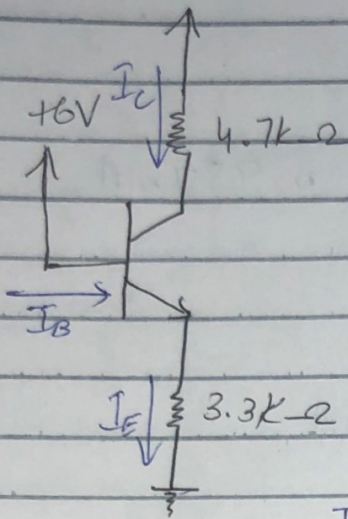

$$\beta = 100$$

$$\alpha = 0.99$$

$$V_{BE} = 0.7$$

$$V_{BE} - V_B = -V_E$$

$$0.7 - 6 = -V_E$$

$$V_E = 5.3$$

$$I_E = \frac{V_E - 0}{R_E} = \frac{-5.3}{3.3k} = 1.61 \text{ mA}$$

$$I_C = 1.59 \text{ mA}$$

$$I_B = 15.9 \mu\text{A}$$

$$V_C = 2.53 \text{ V}$$

$$V_{CB} = 2.53 - 6 < -0.4$$

$$= -3.47 < 0.4$$

(saturation mode)

So, Beta won't be constant.

For Saturation Mode:

$$\beta_{\text{forced}} = \beta_f = \frac{I_C (\text{sat})}{I_B}$$

$$V_{CE} (\text{sat}) = 0.2 \text{ V}$$

$$V_{CE} (\text{sat}) = V_C (\text{sat}) - V_E$$

$$0.2 = V_C (\text{sat}) - 5.3$$

$$V_c(\text{sat}) = 5.5V$$

$$I_c = \frac{10 - V_c(\text{sat})}{R_c} = \frac{10 - 5.5}{4.7k} = 0.957 \text{mA}$$

$$I_B = I_E - I_c$$

$$= 1.61 - 0.957 = 0.653 \text{mA}$$

$$V_{CB} = V_c - V_B$$


$$= 5.5 - 6$$

$$= -0.5 < -0.4V$$

BJT is in Saturation Mode.

$$I_c = \beta I_B$$
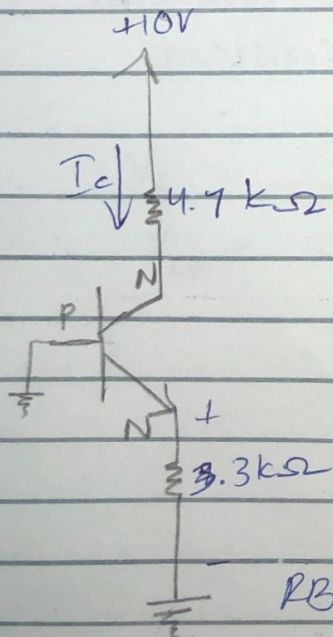
$$\beta_f = \frac{I_c}{I_B} = \frac{0.957}{0.653} = 1.49.$$



BET RB

that means $I_B = I_c = I_E = 0$


$$V_E = V_B = 0$$

$$V_{CC} = V_c = 10$$

RB (Collector Base Junction)

19 Oct 2022

Wednesday

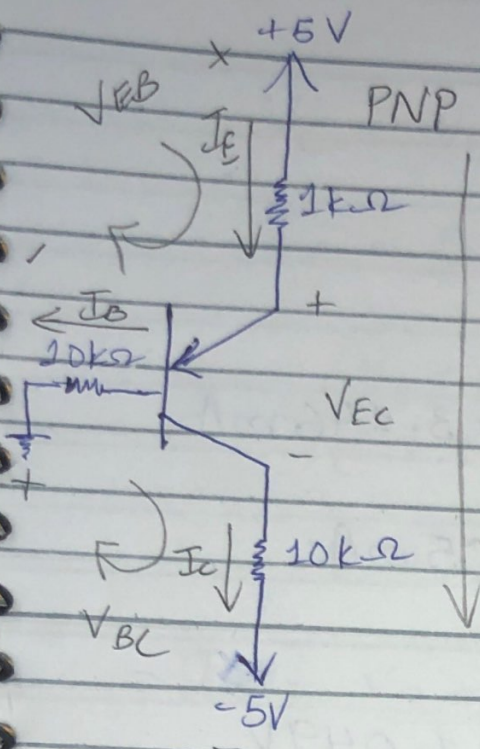

$$\beta = 30$$

Analyze the circuit

Assume active mode

$$V_{EB} = 0.7$$

$$V_B - V_C < -0.4V$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{30}{31} = 0.968$$

$$I_E = I_B + I_C$$

$$V_{EB} = V_E - V_B$$

$$V_B = I_B R_B = (10k)(I_B)$$

$$-5 + I_E R_E + V_{EB} + I_B R_B = 0$$

$$I_E R_E + I_B R_B = 4.3$$

$$I_E = (\beta + 1) I_B$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$I_E R_E + \left(\frac{I_E}{31} \right) R_B = 4.3$$

$$I_E \left(\frac{R_E + R_B}{31} \right) = 4.3$$

$$I_E = \frac{4.3}{\frac{(1k) + (10k)}{31}} = 3.25 \text{ mA}$$

$$I_C = \alpha I_E$$

$$I_C = (0.968)(3.25 \times 10^{-3}) = 3.146 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{3.146 \text{ mA}}{30} = 0.105 \text{ mA}$$

$$V_B = I_B R_B = (0.105)(10k) = 1.049 \text{ V}$$

$$V_E = 1.04 + 0.7 = 1.74 \text{ V}$$

$$V_C = I_C R_C - 5 = (3.14 \text{ mA})(10k) - 5$$

$$= 31.4 - 5 = 26.4 \text{ V}$$

BJT is in saturation mode.

$$V_B - V_C = 1.04 - 26.4 = -25.36$$

$$I_E = I_B + I_C$$

$$V_{EB} = 0.7 \text{ V} = V_E - V_B$$

$$V_{EC}(\text{sat}) = 0.2 \text{ V} = V_E - V_C$$

$$I_E = \frac{5 - V_E}{R_E} \quad I_C = \frac{V_C - (-5)}{R_C}$$

$$V_E = V_B + 0.7$$

$$I_E = \frac{5 - (V_B + 0.7)}{R_B} = \frac{4.3 - V_B}{R_E}$$

$$V_C = V_E - 0.2$$

$$V_C = V_B + 0.7 - 0.2$$

$$V_C = V_B + 0.5$$

$$I_C = \frac{V_B + 0.5 + 5}{R_C} = \frac{V_B + 5.5}{R_C}$$

$$\frac{4.3 - V_B}{R_E} = \frac{V_B}{R_B} + \frac{V_B + 5.5}{R_C}$$

$$\frac{4.3 - V_B}{1k} = \frac{V_B}{10k} + \frac{V_B + 5.5}{10k}$$

$$10k(4.3 - V_B) = 1k(2V_B + 5.5)$$

$$43k - 10kV_B = 2kV_B + 5.5k$$

$$37.5k = 12kV_B$$

$$V_B = 3.125$$

$$V_C = 3.625V$$

$$V_E = 3.825V$$

$$I_B = 0.313mA$$

$$I_C = 0.863mA$$

$$\beta_f = \frac{I_c}{I_b} = \frac{0.863}{0.312} = 2.8$$

$$I_E = 1.175 \text{ mA}$$

$$V_B - V_C = 3.125 - 3.625 = -0.5$$

$$V_B - V_C < -0.4 \text{ V}$$

So, BJT is in saturation mode.


★ Overdrive factor

How deep BJT is in saturation mode.

$$\frac{\beta}{\beta_f} = \frac{I_B}{I_B(\text{EOS})} = \frac{30}{2.8} = 10.7$$

$$\frac{0.104 \text{ m}}{0.372 \text{ m}} = 0.333$$

- Min value of overdrive factor < 1

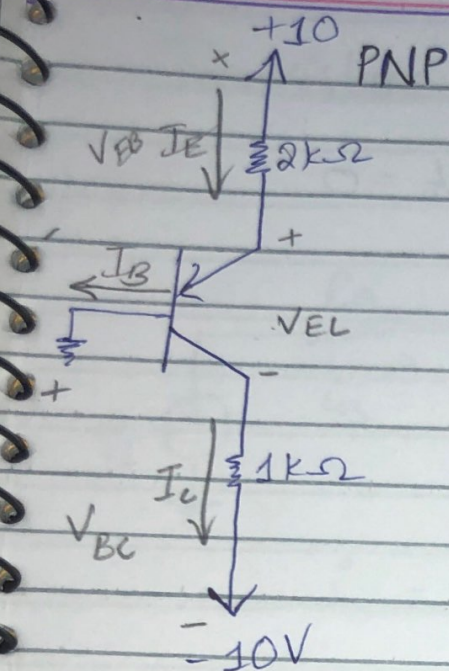

$$\beta = 100$$

$$\alpha = 0.99$$

Active mode

$$V_{EB} = 0.7$$

$$V_{EB} = V_E - V_B$$

$$0.7 = V_E - 0$$

$$V_E = 0.7$$

$$I_E = \frac{10 - 0.7}{2 \times 10^3} = 4.65 \text{ mA}$$

$$I_C = \alpha I_E = 0.99 \times 4.65 \text{ mA} = 4.604 \text{ mA}$$


$$\checkmark I_E = I_B + I_C \quad \text{or} \quad I_B = \frac{I_C}{\beta} = 46 \mu\text{A}$$

$$V_C = -5.4 \text{ V}$$

$$V_B - V_C$$

$$0 - (-5.4) > -0.4 \text{ V}$$

So, BJT in active mode.

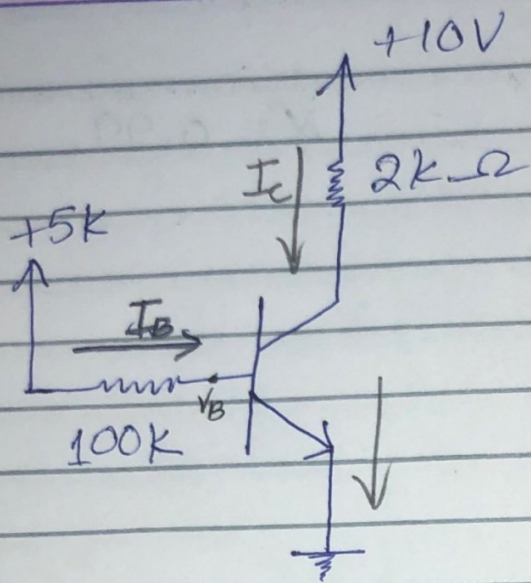

$$\beta = 100$$

$$V_{BE} = 0.7V \quad V_E = 0$$

$$V_{BE} = V_B - V_E$$

$$0.7 = V_B - 0$$

$$V_B = 0.7V$$

$$-5 + I_B R_B + V_{BE} = 0$$

$$I_B = \frac{5 - 0.7}{100K} = \frac{4.3m}{100} = 43\mu A$$

$$I_C = \beta I_B = 4.3mA$$

$$V_C = V_{CC} - I_C R_C = 10 - (4.3)(2) = 1.4V$$


$$V_{CB} = V_C - V_B = 1.4 - 0.7 = 0.7V$$

So, BJT is in active mode.

β dependent design..

β is temperature dependant. So, this circuit is highly dependent on temperature as it is highly dependent on β .

Transistor as a Switch

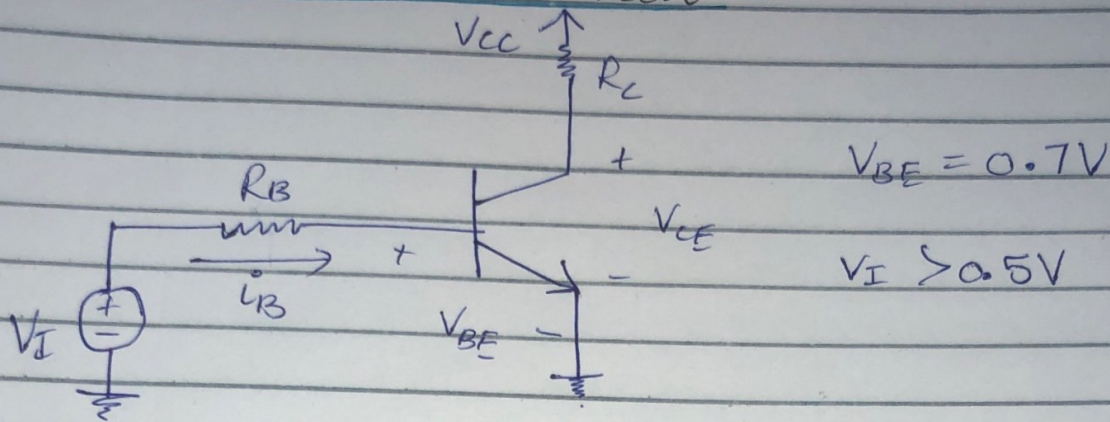

$$I_B = \frac{V_I - V_{BE}}{R_B} \quad I_C = \beta I_B$$

$$I_C(EOS) = \frac{V_{CC} - V_{CE(EOS)}}{R_C} = \frac{V_{CC} - 0.3}{R_C}$$

$$I_C(EOS) = \beta I_B(EOS)$$

$$V_I(EOS) = I_B(EOS) R_B + V_{BE}$$

$$\beta_f = \frac{I_{C(sat)}}{I_B}$$

$$\text{Overdrive} = \frac{\beta}{\beta_f} = \frac{I_B}{I_B(EOS)}$$

$$V_{CE(sat)} = 0.2V$$

$$I_{C(sat)} = \frac{V_{CC} - 0.2}{R_C}$$