


National University of Computer and Emerging Sciences, Lahore Campus



Course:	Instrumentation and Measurement	Course Code:	EE220
Program:	BS(Electrical Engineering)	Semester:	Fall 2018
Duration:	60 Minutes	Total Marks:	30
Paper Date:	03-Oct-2018	Weight	15%
Section:	ALL	Page(s):	1
Exam:	Midterm-I	Questions	3

- Q1** The voltage (V_1) at one ends of $500 \Omega \pm 5\%$ resistor (R) is measured as $V_1 = 10 \pm 0.5$ V. The current through the resistor is $I = 10\text{mA} \pm 5\%$. Find the magnitude and relative accuracy of the voltage V_2 .

[10]
CLO
01

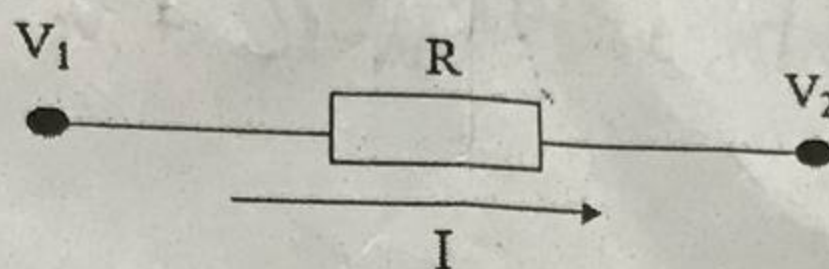

- Q2** A rectifier ammeter is to indicate full scale for a 1 V RMS primary current. The PMMC instrument used has $500 \mu\text{A}$ FSD and the coil resistance $R_M = 1200 \Omega$. The current transformer turns are $N_S = 7000$ and $N_P = 10$. Silicon diodes are used and the meter series resistance is $R_S = 150 \text{k}\Omega$.

[10]
CLO
02

- Draw the circuit diagram.
- Determine the required secondary shunt resistance (R_L) value.

- Q3** A series ohmmeter indicates 80% ohmmeter deflection when measuring a resistance of 100 k Ω . The PMMC instrument used has 1.0 mA FSD and the coil resistance $R_M = 500 \Omega$.

[10]
CLO
02

- Draw the circuit diagram.
- Determine the values of series-resistance (R_S) and the battery-voltage (V_B).

$$20.1 = 0.2 / 500 \times$$

0.2

0.2mA

$$V = IR_M + IR_S + IR_X$$

$$V = I(R_M + R_S + R_X)$$

$$\frac{N_S}{N_P} = \frac{V_S}{V_P}$$

$$\frac{N_S}{N_P} = \frac{I_P}{I_S}$$

$$\frac{N_P}{N_S} \propto I_P = I_S$$

$$V = 700 \text{ V}$$