

National University of Computer and Emerging Sciences, Lahore Campus

	Course Name:	Power Electronics	Course Code:	EE3032
	Program:	BS Electrical Engineering	Semester:	Spring 2025
	Assignment Submission Date:	12-Feb 2025	Total Marks:	50
	Section:	BEE-6A	Weight:	2
	Exam Type:	Assignment- 1	Page(s):	2
			CLO #	1


Student Name: _____ Roll No. _____ Section: _____

- Instructions:**
1. Use A4-sized sheets for this assignment.
 2. Avoid cutting and overwriting.
 3. Secure the pages with staple, clip, or binding. Do not submit loose pages.
 4. Assignment must be submitted on or before deadline during office hours only.
 5. Late submission will incur a penalty of 20% per day. After 2 days, assignment will no longer be accepted.

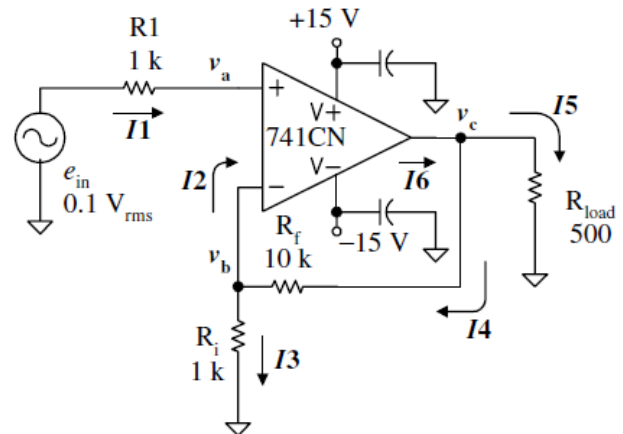Question No. 1 (CLO No. 1)

Marks: 10


Analyze the op-amp circuit shown below and briefly explain its working. Also calculate all the indicated currents and voltages in the figure.



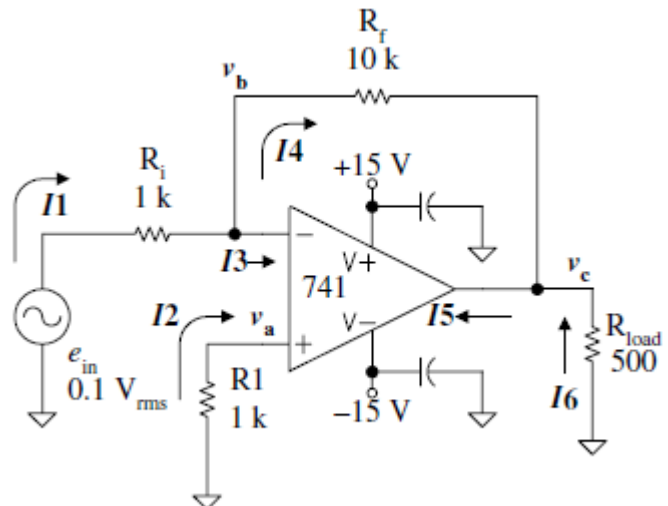Question No. 2 (CLO No. 1)


Marks: 10

Analyze the op-amp circuit shown below and briefly explain its working. Also calculate all the indicated currents and voltages in the figure.




Question No. 3 (CLO No. 1)**Marks: 10**

Analyze the op-amp application shown in the circuit below using Universal Analysis Technique.

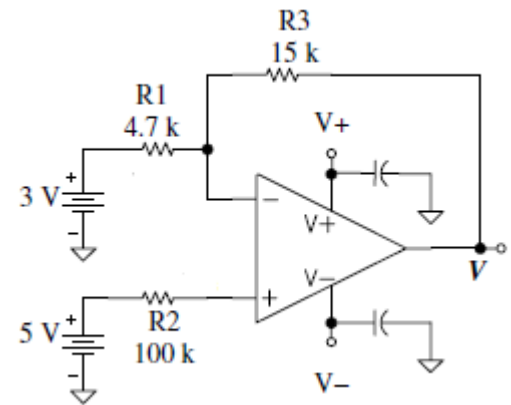**Question No. 4 (CLO No. 1)****Marks: 10**

Analyze the op-amp application shown in the circuit below using Universal Analysis Technique. Assume $e_{in} = 4.5\text{ V}$ and a gain of 100 from the suspended supply amplifier.

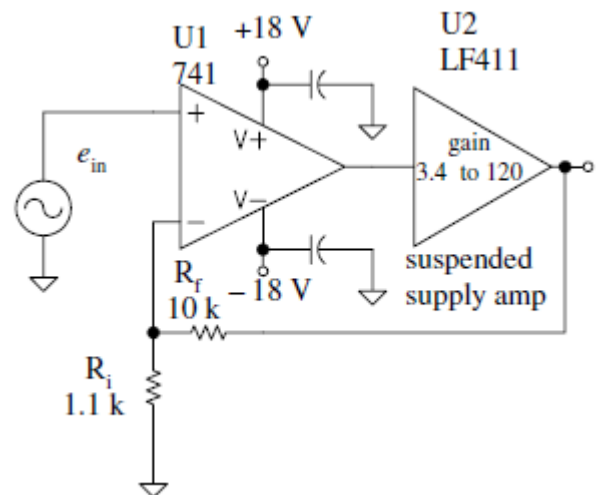**Question No. 5 (CLO No. 1)****Marks: 10**

Analyze the op-amp application shown in the circuit below and calculate the output voltage V_{out} . Consider $V_{in1} = 5\text{ mV}$ and $V_{in2} = 10\text{ mV}$.

