

Date: 24/3



Mo Tu We Th Fr Sa Su

CH # 7 SWITCHING POWER SUPPLIES

(DC to DC)


CASE - I:

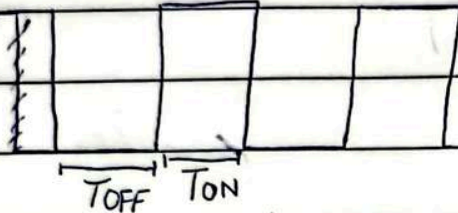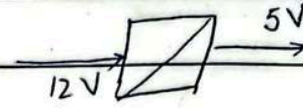- $V_{in} \rightarrow \text{Constant}$
 $V_{out} \rightarrow \text{Constant}$ } fixed, & also D - fixed
5V




CASE - II:

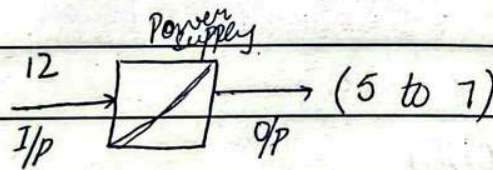- $V_{in} \rightarrow \text{Constant / fixed}$
 $V_{out} \rightarrow \text{Variable}$
 $\Rightarrow D \rightarrow \text{Variable}$



CASE - III:

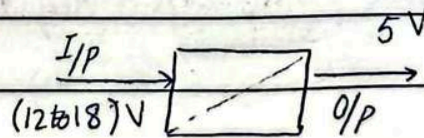- $V_{in} \rightarrow \text{variable}$
 $V_{out} \rightarrow \text{fixed}$
 $D \rightarrow \text{variable}$



CASE - IV

- $V_{in} \rightarrow \text{variable}$
 $V_{out} \rightarrow \text{variable}$

Date: _____


Mo Tu We Th Fr Sa Su

BUCK REGULATORS / CONVERTERS

($V_{in} > V_o$)

- Input is high, o/p is low


eg#

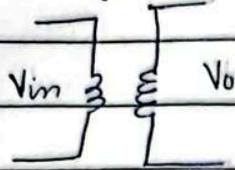

Step down transformer

* $V_{out} = D \times V_{in}$

- ideally $D = 1$

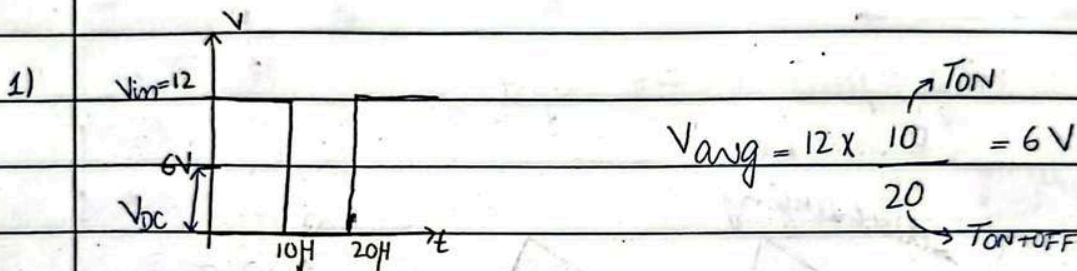

2) $V_{avg} = 12 \times \frac{5}{20} = 3V$

3) $V_{in} = 7V$

$V_{out} = 6V$

$D = \frac{V_{out}}{V_{in}} = \frac{6}{7} = 0.85$

- Switch driver is used to control switch.
- Schottky diode in parallel with switch - used to prevent switch. (Zener)
- O/p of switch is rectangle, filter required.


26/3

PWM




Date: _____

Mo Tu We Th Fr Sa Su /

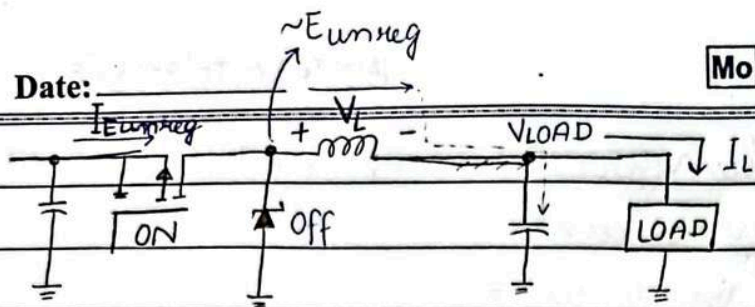


charging part of the cycle

Buck
regulator
operation

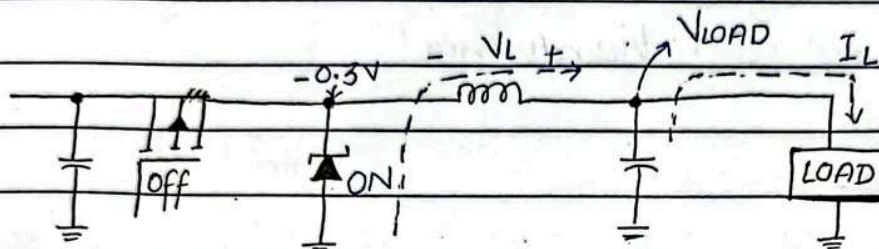

Discharge part of the cycle

* V_L & V_{LOAD}
are different

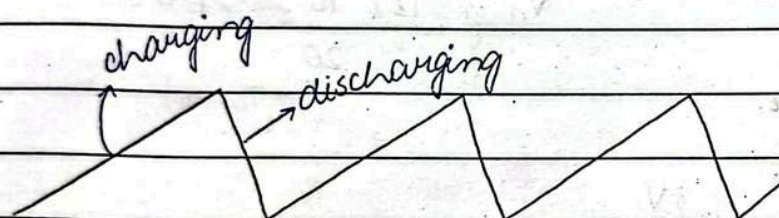

o/p graph

*
current rating $> 1.3 I_{DC, LOAD}$
PIV rating $> 1.3 E_{unreg, max}$

$$V_L = L \frac{\Delta i}{\Delta t}$$

* inductor - opposes
change in current

$$\begin{aligned} V_L &= E_{unreg} - V_{LOAD} \\ &= V_i - V_o \\ &= V_i - DV_i \\ &= (1 - D)V_i \end{aligned}$$

*
Analysis $\rightarrow$ calculate Δi
Design $\rightarrow$ calculate L

Δi - AC current capacitor
will entertain.

AZHAR BOOK

AZHAR BOOK

* ripple current - depends on inductor

Date: _____

Mo Tu We Th Fr Sa Su

$$\Delta t = t_{ON} = DT \quad \left(\begin{array}{l} \text{duty cycle is set by the relationship of i/p to o/p} \\ \Rightarrow D = V_{LOAD} / E_{unreg} \end{array} \right)$$

* Select $\Delta i = 0.25 I_{DC}$ to $0.7 I_{DC}$ (Ripple current)


→ * Load current will be smooth current.

* [→ At or below 200mA DC, allow longer ripple current.

→ Above 1A DC, restrict ripple current to 25%.

→ In analysis, ripple current is set by inductor.

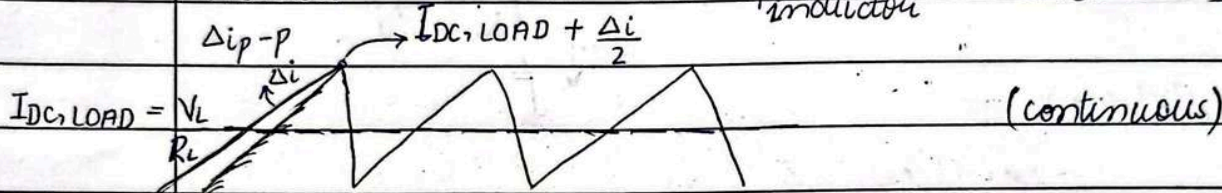* Inductor max current = $i_{P_{inductor}} = I_{DC, LOAD} + \frac{\Delta i}{2}$



EXAMPLE #7.2

$$V_{in} = E_{unreg} = 12V, \quad f = 100kHz \Rightarrow T = 1/100k = 0.01ms$$

$$V_{LOAD} = V_o = 5V, \quad L = 220 \mu H$$

$$R_L = 10 \Omega$$

i) Duty cycle = $D = ?$, ii) on time = $\Delta t = ?$

iii) ripple current = $\Delta i = ?$, iv) avg. Inductor Current = $I_{DC, LOAD} = ?$

v) Peak inductor current = $I_{L, Peak} = ?$

↑ voltage across inductor

$$\begin{aligned} V_L &= E_{unreg} - V_{LOAD} \\ &= 12 - 5 = 7V \end{aligned}$$

$$i) \quad D = \frac{V_{LOAD}}{E_{unreg}} = \frac{V_o}{V_{in}} = \frac{5}{12} = 42\%$$

$$\begin{aligned} ii) \quad \Delta t &= D \times T = 0.42 (0.01ms) \\ &= 4.2 \mu s \end{aligned}$$



AZHAR BOOK

Date: 26/3

Mo Tu We Th Fr Sa Su

POWER ELECTRONICS

CHAPTER # 7

EXAMPLE # 7.2 (Remaining)

iii) $\Delta i = ?$ $V_L = 12 - 5$ OR $V_L = (1-D)V_{in}$
 $V_L = L \frac{\Delta i}{\Delta t}$ $V_L = 7V \Rightarrow (1-D)V_{in} = L(\Delta i/\Delta t)$
 $\Delta i = \frac{V_L \Delta t}{L} = \frac{7(4.2\mu)}{220\mu}$ $\Delta i = (1-0.42)(12)(4.2\mu)$
 $\Delta i = 134mA$ 220μ
 $\Delta i = 133mA$

iv) $I_{DC,LOAD} = \frac{V_{LOAD}}{R_L} = \frac{5V_{DC}}{10}$
 $= 500mA_{DC}$

* To verify:

$\Delta i / I_{DC,LOAD} = \frac{134mA_{PP}}{500mA_{DC}}$
 $= 0.27 \Rightarrow 27\%$

$\Rightarrow$ close to 25% $\rightarrow$ (reasonable)

v) $I_{L,peak} = I_{DC,LOAD} + \frac{\Delta i}{2}$
 $= 500mA_{DC} + \frac{134mA_{PP}}{2}$
 $= 567mA$

OR using $\Delta i = 133mA$

$\Rightarrow I_{L,peak} = 500mA + \frac{133mA}{2}$
 $= 565mA$

$\nearrow$ (O/P smaller than I/P)

7.1 * BUCK REGULATORS: (Remaining)

- $\rightarrow$ A key parameter of for C_{in} is its equivalent series resistance.
- $\rightarrow$ Large capacitors, C_{in} & C_{out} may have hundred milliohms of internal resistance.
- $\rightarrow$ Current flowing off and onto these capacitors produces a voltage drop & forces capacitor to dissipate power (producing heat).

AZHAR BOOK

Date: _____

Mo Tu We Th Fr Sa Su /

* $I_{rms} C_{in} > 0.5 I_{DC, LOAD}$ (I/p capacitor ratings)

* $V_{cin} > 1.5 E_{unreg, max}$

→ * Any capacitor & above 100 μF should work.

* $\Delta V_{PP, LOAD} = \Delta i_{pp, inductor} \times ESR_{out}$ (o/p capacitor's specifications)

* $I_{RMS, out} = \frac{\Delta i_{pp, inductor}}{\sqrt{3}}$

* $C \approx \frac{500 \mu F}{A} \times I_{DC, LOAD}$

EXAMPLE # 7.3

$I_{DC, LOAD} = 500 \text{ mA}_{DC}$, $\Delta i_{pp} = 134 \text{ mA}_{pp}$,

$D = 0.42$

i) $I_{RMS} = ?$ (using trapezoid equation)

ii) $I_{RMS} = ?$ (using simple rectangle with $I_p = I_{DC, LOAD}$)

i) For trapezoid:

$$I_{RMS} = \sqrt{\frac{D}{3} (I_p^2 + I_p I_{min} + I_{min}^2)}$$
 (i)

where,

$I_p = I_{DC} + \frac{\Delta i_{pp}}{2}$ & $I_{min} = I_{DC} - \frac{\Delta i_{pp}}{2}$

$= \frac{500 \text{ mA} + 134 \text{ mA}}{2}$ & $= \frac{500 \text{ mA} - 134 \text{ mA}}{2}$

$I_p = 567 \text{ mA}_{p}$ & $I_{min} = 433 \text{ mA}_{p}$

⇒ ii)
$$I_{RMS} = \sqrt{\frac{0.42}{3} [(567 \text{ mA})^2 + (567 \text{ mA})(433 \text{ mA}) + (433 \text{ mA})^2]}$$

$$= 325 \text{ mA}_{rms}$$

Date: _____

Mo Tu We Th Fr Sa Su

ii) For rectangle (with flat top of 500mA_p)

$$I_{RMS} = \sqrt{D \times I_p} = \sqrt{0.42 \times 500 \text{ mA}_p} \\ = 324 \text{ mA}_{RMS}$$

$$\Delta i = \frac{\Delta i_{pp}}{I_{DC, LOAD}} \times 100 = \frac{134}{500} \times 100$$

$$\Delta i = 26.8\% = 27\%$$

7/4

EXAMPLE #

$$I_{DC, LOAD} = 500 \text{ mA}, \quad \Delta i_{pp} = 134 \text{ mA},$$

$$D = 0.42 \quad (R_{ON} = 0.6 \Omega \text{ at } \approx 150^\circ\text{C})$$

i) Power dissipation of IRF9530 = ?

$$P_Q = D \times I_{DC, LOAD}^2 \times R_{ON} \\ = 0.42 \times (500 \text{ mA})^2 \times 0.6 \\ = 63 \text{ mW}$$

ii) Power dissipation by Schottky diode = ?

$$P_{DIODE} = D \times V_{ON} \times I_{DC, LOAD} \\ = 0.42 \times 0.3 \times 500 \text{ mA} \\ = 63 \text{ mW}$$

iii) $P_L = ?$, $R_L = 10 \Omega$

$$P_L = I_{DC, LOAD}^2 \times R_L \\ = (500 \text{ mA})^2 \times (10) \\ = 2.5 \text{ W}$$

(No effect of load)
[$\square$ x  (continuous)]

iv) efficiency = $\eta = ?$


$$\eta = \frac{P_L}{P_T} \times 100 = \frac{2.5}{63 \text{ m} \times 63 \text{ m} \times 2.5} \times 100$$

when I_p is known
 $\Rightarrow \eta = \frac{\text{Input} - \text{losses}}{\text{input}}$

$$\eta = 95.2\%$$

Date: _____

BUCK REGULATOR (LM 2595)

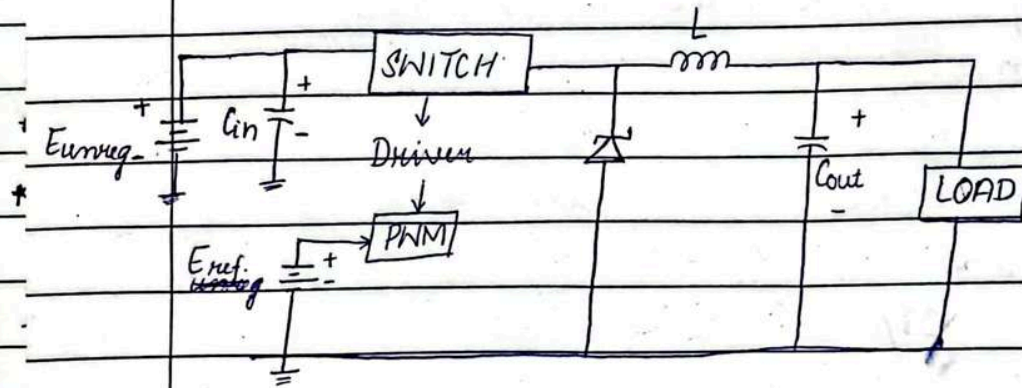

- $P_Q = D \times I_{DC, LOAD} \times V_{sat, max}$
- $P_{IC} = I_{quies} \times E_{unreg}$
- Total Power dissipation = $P_Q + P_{IC}$

EXAMPLE

convert unregulated input voltage of 12V to 5V_{DC}. $R = 10\Omega$, $T_A = 80^\circ C$, $f = 150kHz$, $V_{ref} = 1.23V$ Sol.

Designing Buck regulator.

LM2595 specifications

 $L = ?$ $V_{sat(max)} = 1V_p$

$$V_L = L \frac{\Delta i}{\Delta t}$$

 $\theta_{JC} = 2^\circ C/W$ $\theta_{JA(bare)} = 50^\circ C/W$

$$V_L = 12 - 5 = 7V$$

$$I_{DC, LOAD} = \frac{5}{10} = 0.5A = 500mA$$

Select

$$\Delta i = 0.25 \text{ to } 0.7 I_{DC}$$

$$\Delta i_{pp} = 0.25 \times 500mA = 125mA$$

$$T = \frac{1}{f} = \frac{1}{150k} = 6.7\mu s$$

$$\Delta t = D \times T$$

$$= 0.42 \times 6.7\mu s$$

$$= 2.8\mu s$$

Date: _____

Mo Tu We Th Fr Sa Su

$$V_o = D V_{in} \Rightarrow \frac{5}{12} = D$$

$$\Rightarrow L = 157 \mu H \approx 220 \mu H \quad (V_L = L \Delta i / \Delta t) \quad \text{125m}$$

$$I_{DC, LOAD} = 500 \text{ mA}$$

$$I_p = \frac{500 + 125}{2} = 563 \text{ mA}$$

* $C_{out} = 250 \mu F$

$$C_{in} > 100 \mu F$$

$$I_{Cin} > 0.5 \times I_{DC, LOAD} = 250 \text{ mA}$$

$$V_{Cin} > 1.5 E_{unreg} = 1.5 \times 12 = 18 \text{ V}$$

$$C_{out} \approx 500 \mu F/A \times I_{DC, LOAD}$$

$$P_T = P_Q + P_{IC}$$

$$= (10 \text{ m} \times 12) + (0.42 \times 500 \text{ m} \times 1)$$


$$= 0.33 \text{ W}$$

$$\theta_{SA} = \frac{150 - 80}{0.33} - 2 - 0.2$$

$$= 210 \text{ C/W}$$

* 14/4 BOOST REGULATORS / CONVERTERS

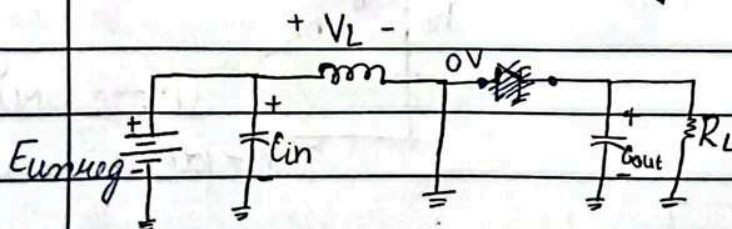- low side instead of high side.
- transistor OFF, diode ON and vice versa.
- Transistor ON: $V_L = E_{unreg} = L \Delta i / \Delta t$ (when changing).



when transistor is ON/
diode is OFF

$$V_L = E_{unreg} - 0$$

$$V_L = E_{unreg} = L \Delta i / \Delta t$$

AZHAR BOOK

current - [inductor - ramp
capacitor - constant.

$$\Delta i_{pp} = \begin{cases} \text{for buck} = 0.25 \times I_{DC, \text{LOAD}} \\ \text{for boost} = 0.25 \times I_{DC, I/P} \end{cases}$$

Date: _____

Mo Tu We Th Fr Sa Su /

• Boost regulators are 90% efficient.

$$* P_{LOAD} = P_{in} \times 0.9 \quad \text{OR} \quad V_{DC, \text{LOAD}} \times I_{DC, \text{LOAD}} = 0.9 E_{unreg} \times I_{DC, I/P} \quad \text{--- (i)}$$

→ When transistor is ON:

ANALYSIS:

$$\Delta i = \frac{E_{unreg}}{L} \Delta t$$

DESIGN:

$$\Delta i = 25\% \text{ of } I_{DC, I/P}$$

$$L = \frac{E_{unreg}}{\Delta i} \Delta t$$

$$\Delta t = D \times T$$

$$I_{L, \text{peak}} = I_L + \frac{\Delta i}{2}$$

inductor

L - inductor

$$V_{LOAD} = E_{unreg} + V_L$$

$$\Rightarrow (i) \quad I_{DC, I/P} = \frac{V_{DC, \text{LOAD}} \times I_{DC, \text{LOAD}}}{0.9 E_{unreg}}$$

$$I_L = \frac{V_{DC, \text{LOAD}} \times I_{DC, \text{LOAD}}}{0.9 E_{unreg}}$$


$$\Rightarrow * \quad I_{DC, I/P} = I_L$$

$$I_{avg, L} = \frac{V_{DC, \text{LOAD}} \times I_{DC, \text{LOAD}}}{0.9 E_{unreg}}$$


$$* I_{DC} = D \times I_L$$

inductor current


when transistor is ON.

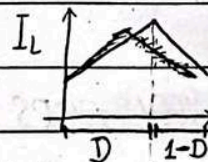

transistor ON

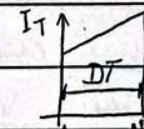


(Transistor current)

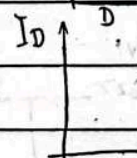

(Diode ON)

(1-D)T (diode current)

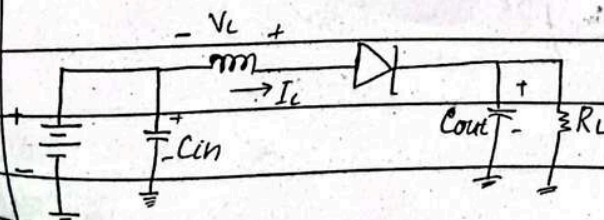

(when transistor -OFF,
diode ON)

$$* \Rightarrow I_{DC, \text{LOAD}} = C_{out} \times \frac{\Delta V_{LOAD}}{\Delta t}$$

AZHAR BOOK

Date: _____

Mo Tu We Th Fr Sa Su

$$\begin{aligned} \bullet \quad I_{avg, Q} &= D \times I_{DC, I/P} \\ \bullet \quad I_{RMS, Q} &= \sqrt{D} \times I_{DC, I/P} \end{aligned} \quad \left. \vphantom{\begin{aligned} I_{avg, Q} &= D \times I_{DC, I/P} \\ I_{RMS, Q} &= \sqrt{D} \times I_{DC, I/P} \end{aligned}} \right\} \text{transistor}$$

$$\bullet \quad I_{avg, D} \xrightarrow{\text{diode}} = (1-D) \times I_{DC, I/P}$$

$$\bullet \quad I_{RMS, D} = \sqrt{(1-D)} \times I_{DC, I/P}$$

• O/p higher than I/p (always)

• when transistor is OFF:

$$-E_{unreg} - V_L + V_{LOAD} = 0$$

$$\star \quad V_{LOAD} = V_L + E_{unreg}$$

• keep $\Delta V_{LOAD} \leq 20\% V_{PP}$ (if ΔV_{PP} is not given)

$$\star \quad V_L = \frac{L \Delta i}{(1-D)T} \quad \text{(i) (discharging)}$$

$$\bullet \quad E_{unreg} = \frac{L \Delta i}{DT} \Rightarrow L = \frac{E_{unreg} \times DT}{\Delta i} \quad \text{(ii)}$$

$$\Rightarrow \text{ii) } V_L = \frac{L \Delta i}{(1-D)T} \Rightarrow \text{(ii) in (i)}$$

$$V_L = E_{unreg} \times \frac{DT}{\Delta i} \times \frac{\Delta i}{(1-D)T}$$

$$V_L = E_{unreg} \times \frac{D}{(1-D)}$$

$$V_{LOAD} = E_{unreg} + V_L$$

$$= E_{unreg} + E_{unreg} \left(\frac{D}{1-D} \right)$$

$$\star \quad V_{LOAD} = E_{unreg} \left(1 + \frac{D}{1-D} \right) = E_{unreg} \left(\frac{1}{1-D} \right) \quad \therefore D < 1$$

$$\downarrow$$

$$\frac{1-D+D}{1-D}$$

AZHAR BOOK

$$D = \begin{cases} \text{for buck regulator} = V_o/V_{in} \\ \text{for boost regulator} = 1 - \frac{V_o}{V_{in}} \end{cases}$$

Date: _____

Mo Tu We Th Fr Sa Su /

$$* C_{OUT} = \frac{I_{DC, LOAD} \times \Delta t}{\Delta V_{LOAD}} = \frac{I_{DC, LOAD} \times DT}{\Delta V_{LOAD}}$$

$$\Delta V_{PP} = \Delta I_{PP, inductor} \times ESR_{Cout}, \quad C_{out} = 1500 \mu F \times \frac{I_{DC, LOAD}}{A}$$

EXAMPLE # 7-6

(Boost regulator $\rightarrow O/P > I_{IP}$)

$$V_{in} = 12 V_{DC}, \quad V_{LOAD} = 22 V_{DC}, \quad 0.7 A_{DC} = I_{LOAD}$$

$$f = 100 kHz \Rightarrow T = 1/100k = 1 \times 10^{-5}$$

$$R_{ON} = 0.4 \Omega, \quad \text{diode drops} = 0.5 V$$

$$i) P_{LOAD} = P_{in} \times 0.9$$

$$= (12 \times 1.425) \times 0.9$$

$$P_{LOAD} = 15.39 W \approx 15.4 W$$

$$I_{DC, I/P} = \frac{22 \times 0.7}{0.9 \times 12} = 1.425$$

$$ii) I_{DC, I/P} = 1.425 A$$

$$iii) \Delta I_{PP} = 0.35 \quad (25\% \text{ of } I_{DC, I/P})$$

$$\therefore 0.25 \times 1.4 = 0.35$$

$$\Delta t = DT$$

$$L = \frac{E_{unreg} \times \Delta t}{\Delta I_{PP}} = \frac{12 \times (0.45)(1 \times 10^{-5})}{0.35}$$

$$* D = 1 - \frac{E_{unreg}}{V_{LOAD}}$$

$$L = 3.08 \times 10^{-4} = 1.54 \times 10^{-4} = 154 \mu H$$

$$= 0.45$$

$$iv) \text{Current rating} = I_{L, P} = \frac{1.4 + 0.35}{2}$$

$$= 1.6 A_p$$

$$v) P_Q = D \times I_L^2 \times R_{ON}$$

$$= 0.45 \times 1.4^2 \times 0.4$$

$$= 353 mW$$

* Buck $\rightarrow I/p > o/p$
 Boost $\rightarrow I/p < o/p$

* for Cout, use 20m if ΔV_{pp} is not given

Date: _____

Mo Tu We Th Fr Sa Su

vii) $P_{DIODE} = (1-D) \times I_L \times V_D = (1-0.45) \times 1.4 \times 0.5$
 $= 390 \text{ mW}$

viii) $C_{out} = \frac{0.7 \times 0.45 \times 1 \times 10^{-5}}{20 \text{ m} \rightarrow V_L < 20 \text{ m}}$
 $= 1.575 \times 10^{-9} = 158 \text{ pF}$

16/8 BOOST REGULATOR LM2585 ($o/p > i/p$)
 $V_{DC, LOAD} = 1.23 V_{DC} \left(\frac{1 + R_f}{R_i} \right)$, $1 \text{ k}\Omega < R_i < 5 \text{ k}\Omega$

$P_Q = I_{RMS, Q}^2 \times R_{ON, Q}$; $I_{RMS, Q} = \sqrt{D} I_{DC, LOAD}$, $R_{ON, Q} = 0.15$

$P_{IC} = \frac{1}{50} \times D \times I_{DC, pp} \times E_{unreg}$

Total power = $P_Q + P_{IC}$

EXAMPLE # 7.7

$E_{unreg} = 12 V_{DC}$, $V_{LOAD} = V_O = 22 V_{DC}$, $I_{LOAD} = 0.7 A_{DC}$
 $T_A = 80^\circ \text{C}$

i) $V_{DC, LOAD} = (1.23 V_{DC}) \left(\frac{1 + R_f}{R_i} \right)$

$\frac{R_f}{R_i} = \frac{22}{1.23 V_{DC}} - 1$

$\frac{R_f}{R_i} = 16.9$ (i)

Assume, $R_i = 1.3 \text{ k}\Omega$

$\Rightarrow$ (i) $R_f = 16.9 \times 1.3 \text{ k} = 21.9 \text{ k}\Omega \approx 22 \text{ k}\Omega$

AZHAR BOOK

EXAMPLE #2 (PRACTICE PROBLEM)

BOOST REGULATOR

$$E_{unreg} = 22 V_{DC}, I_{DC, I/P} = 0.7 A_{DC}$$

$$V_o = V_{LOAD} = 56 V_{DC}$$

$$f = 100 \text{ KHz} \Rightarrow T = 1 \times 10^{-5} \text{ s}$$

$$R_{ON} = 0.4 \Omega, V_D = 0.5 \text{ V}$$

$$\begin{aligned} \text{i) } P_{LOAD} &= P_{in} \times 0.9 = V_{in} \times I_{DC, I/P} \times 0.9 \\ &= 22 \times 0.7 \times 0.9 \\ &= 13.86 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{ii) } \Delta i_{pp} &= 0.25 \times 0.7 \\ &= 0.175 \text{ A} \end{aligned}$$

$$\begin{aligned} \Delta t &= DT & \therefore D &= 1 - \frac{V_{in}}{V_{out}} \\ &= 6.07 \mu\text{s} & &= 0.607 \end{aligned}$$

$$L = \frac{V_{in} \times \Delta t}{\Delta i_{pp}} = \frac{22 \times 6.07 \mu}{0.175}$$

$$L = 763 \mu\text{H}$$

$$\text{Current ratings} = I_{L, \text{PEAK}}$$

$$= I_{I/P} + \frac{\Delta I_{PP}}{2}$$

$$= 0.7 + \frac{0.175}{2} = 0.7875$$

$$x, I_{I/P} = I_L$$

$$P = D \times I_L^2 \times R_{ON} = 0.607 \times (0.7)^2 \times 0.4$$

$$= 119 \text{ mW}$$

$$P_D = (1-D) \times I_L \times V_D$$

$$= (1-0.607) \times (0.7) \times (0.5)$$

$$= 137.5 \text{ mW}$$

$$C_{out} = \frac{I_{DC, \text{LOAD}} \times \Delta t}{\Delta V_{\text{LOAD}}} \quad (i)$$

$$I_{DC, \text{LOAD}} = \frac{P_{\text{LOAD}}}{V_{\text{LOAD}}} = \frac{13.86}{56} = 0.2475$$

$$C_{out} = \frac{0.2475 \times 6.07 \mu}{20 \text{ m}}$$

$$= 75.1 \mu\text{F}$$

Date: _____

Mo Tu We Th Fr Sa Su /

$$P_{in} = (12 \times 1.425) \\ = 17.1 \text{ W}$$

$$I_{DC}, I_{PP} = 1.425 \text{ A}$$

$$P_R = (\sqrt{D} I_{DC,TP})^2 \times R_{ON,Q} \\ = (0.45 \times 1.4)^2 (0.15) \\ = 0.1323 \text{ W} = 132 \text{ mW}$$

$$P_{TC} = \frac{1}{50} \times 0.45 \times 1.4 \times 12 \\ = 0.1512 = 151 \text{ mW}$$

$$P_T = 132 \text{ m} + 151 \text{ m} \\ = 283 \text{ mW}$$

$$T_J = 80 + (0.283)(65^\circ) \quad \theta_{JA} \\ = 98.4^\circ \text{C} < 110^\circ \text{C} \quad (\text{no heat sink})$$


$$V_o = D \times V_{in} \quad V_o = \frac{1}{1-D} \times V_{in}$$

BUCK-BOOST CONVERTER:

$$V_o = \frac{D}{1-D} \times V_{in}$$

$$D > 0.5 \quad (50\%) \quad (\text{Boost converter})$$
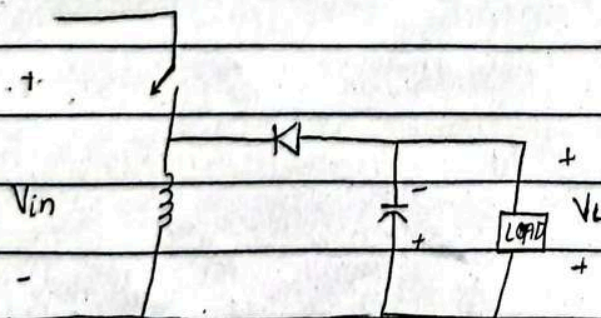
$$D < 0.5 \quad (\text{Buck converter})$$



$$V_L = V_{in} DT - V_o(1-D)T$$

Date: _____

Mo	Tu	We	Th	Fr	Sa	Su
----	----	----	----	----	----	----

EXAMPLE #4

(PROBLEM #7.3)

(Buck regulator)

$$E_{inreg} = 9V_{DC}, \quad V_{LOAD} = 5V_{DC}, \quad I_{DC, LOAD} = 0.8A,$$

$$f = 150 \text{ kHz}, \quad \Delta V_{PP} = 0.1V$$

$$\Rightarrow T = 6.667 \mu s$$

$$D = \frac{5}{9} = 0.56$$

$$\Delta t = D \times T = (0.56)(6.667 \mu s) = 3.73 \mu s$$

$$\Delta i_{PP} = \cancel{0.4938A} \left(\frac{I_{DC, LOAD}}{V_L} \right) = 0.2 \quad \text{OR } (0.8)(0.25) = 0.2$$

$$I_{DC, I/P} = \frac{5 \times 0.8}{0.9 \times 9} = 0.4938 = 493.8 \text{ m}$$

$$\cancel{L = 9 \times 3.73 \mu H} \quad V_L = L \frac{\Delta i}{\Delta t}$$

$$V_L = 9 - 5 = 4$$

$$L = \frac{V_L \times \Delta t}{\Delta i_{PP}} = \frac{4(3.73 \mu s)}{(0.8/4)} = 74.6 \mu H$$

$$C_{out} = 500 \mu F \times 0.8 = 400 \mu F$$

$$ESR_{out} = \frac{\Delta V_{PP}}{\Delta i_{PP}} = \frac{0.1}{0.2} = 0.5$$

$$P_{inreg} = P_{in} = 9 \times 0.49 = 4.41W$$

Date: _____

Mo Tu We Th Fr Sa Su /

EXAMPLE #5

(PROBLEM # 7.11)

(Boost regulator)

$$f = 100 \text{ kHz}, E_{\text{in reg}} = 5 \text{ V}_{\text{DC}}, V_{\text{LOAD}} = 9 \text{ V}_{\text{DC}}, I_{\text{DC, LOAD}} = 0.8 \text{ A}_{\text{DC}}, T = 1 \times 10^{-5} \text{ s}, \Delta V_{\text{PP}} = 0.1 \text{ V}$$

$$\Delta t = 0.44 \times 1 \times 10^{-5} \\ = 4.4 \mu\text{s}$$

$$D = \frac{1-5}{9} = 0.44$$

$$\Delta i_{\text{PP}} = 0.25 \times I_{\text{DC, I/P}} \\ = 1.6 \times 0.25 \\ = 0.4$$

$$I_{\text{DC, I/P}} = \frac{9 \times 0.8}{0.9 \times 5} = 1.6$$

$$L = \frac{E_{\text{in reg}} \times \Delta t}{\Delta i_{\text{PP}}} = \frac{5 \times 4.4 \mu}{0.4} \\ L = 55 \mu\text{H}$$

$$C_{\text{out}} = \frac{0.8 \times 4.4 \mu}{\Delta V_{\text{PP}}} = 36 \mu\text{F}$$

$$P_{\text{in reg}} = P_{\text{in}} = 5 \times 1.6 \\ = 8 \text{ W}$$

* Diode do not conduct in +ve.

Date: 21/4

Mo Tu We Th Fr Sa Su



CHAPTER #10

(~~By~~ from power electronic converters by Hameed Rashid)

UNCONTROLLED RECTIFIERS:



Anode more +ve - diode ON.

SINGLE-PHASE HALF WAVE RECTIFIER:

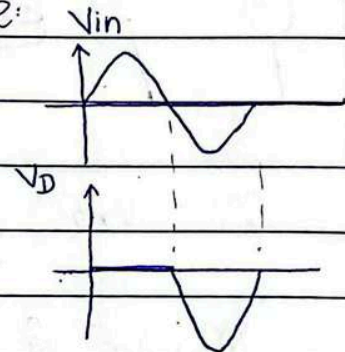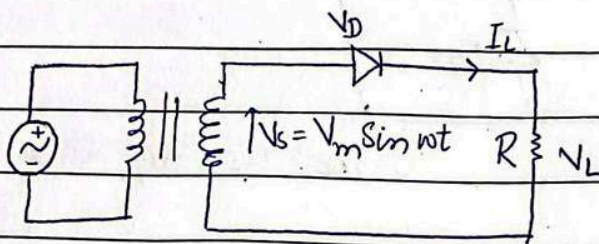


Peak inverse Voltage = PIV = V_m


FULL-WAVE

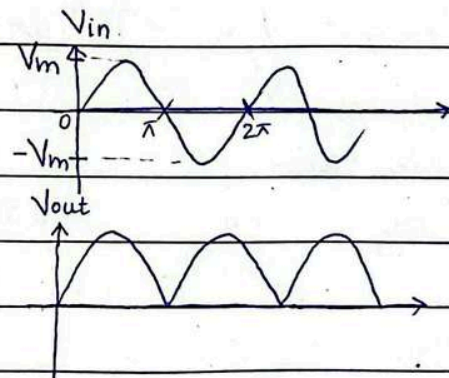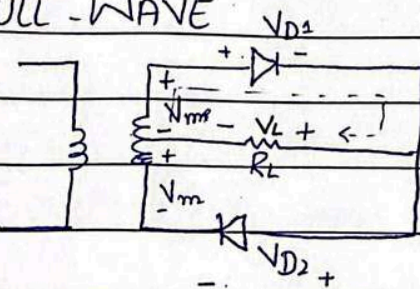

$$V_m + V_m = 2V_m \quad V_{D1} + V_L$$

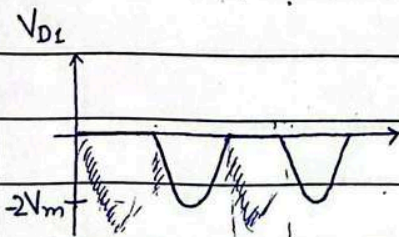


$$* PIV = 2V_m \quad (V_m + V_m)$$

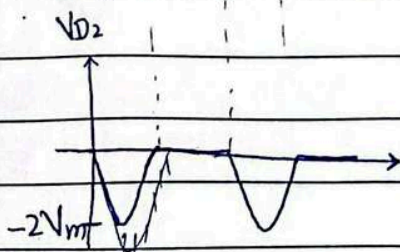

$$V_{D1} + V_L + V_m = 0$$

⇒

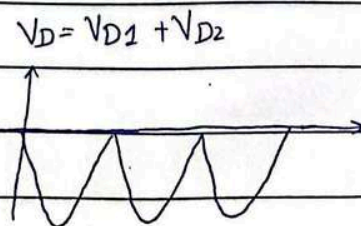


AZHAR BOOK

Date: _____

Mo Tu We Th Fr Sa Su

SINGLE-PHASE BRIDGE RECTIFIER

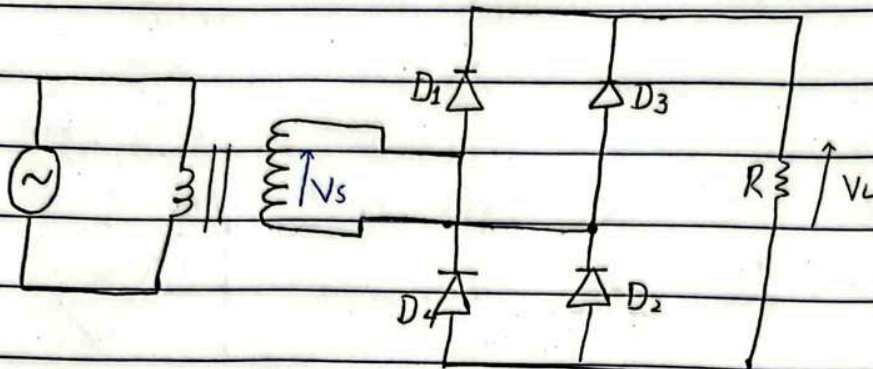

* $PIV = V_m$ (same as half wave)

VOLTAGE RELATIONSHIPS

$$* V_{DC} = \frac{1}{T} \int_0^T v(t) dt$$

→ AVERAGE VALUE:

• Half wave:

$$V_{DC} = V_{avg} = \frac{V_m}{\pi} = 0.318 V_m$$

• full wave:

$$V_{DC} = V_{avg} = \frac{2V_m}{\pi} = 0.636 V_m$$

→ RMS VALUE:

• ~~V_r~~ Half wave:

$$V_{rms} = \frac{V_m}{2} = 0.5 V_m$$

• Full wave:

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

Date: _____

Mo Tu We Th Fr Sa Su

CURRENT RELATIONSHIPS

- $I_{DC} = \frac{V_{DC}}{R}$ (Half wave = Full wave)

- $I_{RMS} = \frac{V_{RMS}}{R}$ (Half wave = Full wave)

OUTPUT DC POWER:

- $P_{DC} = V_{DC} \times I_{DC}$

OUTPUT AC POWER

- $P_{AC} = V_{RMS} \times I_{RMS}$

RECTIFICATION RATIO (CONVERSION EFFICIENCY)

- $\eta = \frac{P_{DC}}{P_{AC}} = \frac{V_{DC} \times I_{DC}}{V_{RMS} \times I_{RMS}}$

* HALF WAVE:

$$\begin{aligned} \eta &= \frac{V_{DC} \times (V_{DC}/R)}{V_{RMS} \times (V_{RMS}/R)} = \frac{V_{DC}^2}{V_{RMS}^2} = \frac{(V_m/\pi)^2}{(2V_m/\pi)^2} \\ &= \frac{V_m^2}{\pi^2} \times \frac{4}{V_m^2} = \frac{4}{\pi^2} = 0.405 = 40.5\% \end{aligned}$$

* FULL WAVE:

$$\begin{aligned} \eta &= \frac{V_{DC}^2}{V_{RMS}^2} = \frac{(2V_m/\pi)^2}{(V_m/\sqrt{2})^2} = \frac{4V_m^2}{\pi^2} \times \frac{2}{V_m^2} \\ &= \frac{8}{\pi^2} = 0.81 = 81\% \end{aligned}$$

Date: _____

Mo Tu We Th Fr Sa Su /

FORM FACTOR (FF)

$$FF = \frac{V_{RMS}}{V_{DC}}$$

• HALF WAVE:

$$FF = \frac{V_m/2}{V_m/\pi} = \frac{\pi}{2} = 1.57$$

• FULL WAVE:

$$FF = \frac{V_m/\sqrt{2}}{2V_m/\pi} = 1.11$$

RIPPLE FACTOR:

$$* \quad RF = \frac{V_{AC}}{V_{DC}} \quad (i)$$

$$\therefore V_{AC} = \sqrt{V_{RMS}^2 - V_{DC}^2}$$

$$\Rightarrow (i) \quad RF = \frac{\sqrt{V_{RMS}^2 - V_{DC}^2}}{\sqrt{V_{DC}^2}} = \sqrt{\frac{V_{RMS}^2}{V_{DC}^2} - 1}$$

$$= \sqrt{FF^2 - 1}$$

• TRANSFORMER UTILIZATION FACTOR:

$$TUF = \frac{P_{DC}}{V_s I_s} = \frac{V_{DC} \times I_{DC}}{V_s \times I_s}$$

$$* \quad \therefore V_s = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

Date: _____

Mo Tu We Th Fr Sa Su

$$* I_s = I_L$$

$$\Rightarrow I_s = 0.5 \frac{V_m}{R} \quad , \quad I_s = 0.707 \frac{V_m}{R}$$

H.W F.W

• HALF-WAVE:

$$TUF = \frac{(V_m/\pi)(V_{DC}/R)}{(0.707 V_m)(0.5 V_m/R)}$$

$V_{DC} = V_m/\pi$
H.W

$$= \frac{V_m^2/\pi^2}{0.3535 V_m^2} = \frac{1}{0.3535 \pi^2}$$

$$TUF = 0.286$$

• FULL-WAVE:

for center tapped;
Full wave $V_s I_s$ is $\leftarrow 2 \times V_s \times I_s$
double of half wave-
rectifiers or 2 half
wave rectifiers are
operating together.

$$TUF = P_{DC} = \frac{(2V_m/\pi)(2V_m/\pi R)}{2 \times (V_m/\sqrt{2})(0.5 V_m/R)}$$

$$= \frac{4V_m^2/\pi^2 R}{2 \times (0.5 V_m^2)/\sqrt{2} R}$$

$$= \frac{4}{\pi^2} \times \frac{\sqrt{2}}{0.5} \times \frac{1}{2} = 0.572$$

• BRIDGE RECTIFIER:

$$TUF = P_{DC} = \frac{V_{DC} \times I_{DC}}{V_s \times I_s}$$

$$= \frac{(2V_m/\pi)(2V_m/\pi R)}{(0.707 V_m)(0.707 V_m/R)} = \frac{4/\pi^2}{(0.707)^2}$$

$$TUF = 0.81$$

Date: _____

Mo Tu We Th Fr Sa Su /

POWER FACTOR:

$$PF = \frac{P_{AC}}{V_s \times I_s}$$

CREST FACTOR:

(measure of peak I/P current compared to RMS of I_L).

$$CF = \frac{I_s (\text{PEAK})}{I_s}$$

EXAMPLE # 1

Full wave transformer - center tapped:

$$\begin{aligned} \text{i) Efficiency} = \sigma &= \frac{P_{DC}}{P_{AC}} = \frac{V_{DC} \times I_{DC}}{V_{RMS} \times I_{RMS}} \\ &= \frac{(2V_m/\pi)(2V_m/\pi R)}{(0.707V_m)(0.707V_m/R)} \\ &= \frac{4/\pi^2}{(0.707)^2} \end{aligned}$$

$$\sigma = 0.81$$

$$\begin{aligned} \text{ii) Form Factor} = FF &= \frac{V_{RMS}}{V_{DC}} = \frac{V_m/\sqrt{2}}{2V_m/\pi} \\ &= \frac{V_m}{\sqrt{2}} \times \frac{\pi}{2V_m} \end{aligned}$$

$$FF = 1.11$$

$$\begin{aligned} \text{iii) Ripple factor} = RF &= \sqrt{FF^2 - 1} \\ &= \sqrt{(1.11)^2 - 1} \\ &= 0.48 \end{aligned}$$

Date: _____

Mo Tu We Th Fr Sa Su

iv) $TUF = 0.572$

v) $PIV_{D1} = 2V_m$

(PIV is same on both diodes $\Rightarrow 2V_m$)

$\therefore PIV_{F.W} = 2V_m$

vi) $CF = \frac{I_{S(PEAK)}}{I_S}$

$RMS = \frac{PEAK}{\sqrt{2}}$

$$\frac{I_{S(PEAK)}}{(PEAK)} = \frac{\sqrt{2} \times 0.707 V_m}{R} \quad \therefore \frac{I_S}{F.W} = \frac{0.707 V_m}{R}$$

$$\frac{I_{S(PEAK)}}{R} = 0.999 V_m$$

$$\Rightarrow CF = \frac{0.999 V_m / R}{0.707 V_m / R} = 1.414$$

vii) $PF = \frac{P_{AC}}{V_s \times I_s} = \frac{V_{RMS} \times I_{RMS}}{V_s \times I_s}$

$$= \frac{(V_m / \sqrt{2}) (V_m / \sqrt{2} R)}{(0.707 V_m) (0.707 V_m / R)}$$

$$= \frac{1/(\sqrt{2})^2}{(0.707)^2}$$

$$PF = 1$$

23/4 EXAMPLE # 2

Single phase bridge rectifier

$TUF = 1$


$I_{S1} = 0.9 I_a$

$I_s = I_a$

$\phi = 0^\circ \Rightarrow \cos 0^\circ = 1$

$HF = ?$, $PF = ?$

$HF = T^* HD$

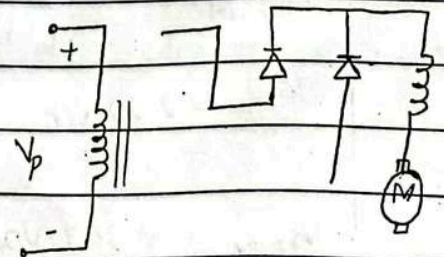

Date: _____

Mo Tu We Th Fr Sa Su /

$$* \quad \text{H.F} = \left(\frac{I_s^2 - I_{s1}^2}{I_{s1}^2} \right)^{1/2} = \left[\left(\frac{I_s}{I_{s1}} \right)^2 - 1 \right]^{1/2}$$

$$= \sqrt{\left(\frac{I_a}{0.9 I_a} \right)^2 - 1} = 0.484$$

$$* \quad \text{PF} = \frac{I_{s1} \cos \phi}{I_s} = \frac{0.9 I_a (\cos 0^\circ)}{I_a}$$

$$= 0.9 \quad (\text{lagging})$$

* [→ inductive load — lagging
→ capacitive load — leading

DESIGN CONSIDERATIONS:

If, $V_{DC} = 10 \text{ V}$

For Half wave:

$$i) \quad V_s: \quad \left. \begin{array}{l} V_{DC} = 0.318 V_m \\ V_{RMS} = 0.5 \cancel{18} V_m \end{array} \right] \text{ o/p} \quad \Rightarrow V_m = V_{DC} / 0.318$$

$$* \quad V_{s, \text{I/p secondary voltage}} = V_s = 0.707 V_m$$

$$V_{s, \text{H.W}} = 0.707 \frac{V_{DC}}{0.318}$$

$$= 2.22 V_{DC}$$

$$V_{s, F.W} = 0.707 V_{DC} \quad 0.636$$

$$V_{DC, F.W} = 0.636 V_m$$

$$= 1.11$$

AZHAR BOOK

Date: _____

Mo Tu We Th Fr Sa Su

ii) PIV: $\rightarrow$ Peak repetitive reverse voltage

$\rightarrow$ Half wave: $V_{RRM} = V_m = \frac{V_{DC}}{0.318} = 3.14 V_{DC}$

$\therefore PIV_{H.W} = V_m$

$\rightarrow$ Full wave: $2V_m$

$\bullet$ Center tapped $= V_{RRM} = \frac{V_{DC}}{0.636} \times 2 = 3.14 V_{DC}$

$PIV_{FW} = 2V_m$
(center tapped)

$\bullet$ Bridge rectifier $= V_{RRM} = V_m = \frac{V_{DC}}{0.636} = 1.57 V_{DC}$

$PIV(\text{bridge rectifier}) = V_m$

iii) Peak repetitive forward current $= I_{FRM} = V_m/R$

$\rightarrow$ Half wave: $I_{DC} = V_{DC}/R \Rightarrow I_{DC} \times R$

$I_{FRM} = \frac{V_{DC}}{0.318} = I_{DC} \times \frac{R}{0.318}$

$= 3.14 I_{DC}$

$\rightarrow$ Full wave:

$I_{FRM} = \frac{V_{DC}}{0.636 R} = 1.57 I_{DC}$

THREE-PHASE UNCONTROLLED RECTIFIER:

- Single phase — used for low to medium power application
- For output higher than 15kW, three phase rectifiers are used.

TYPES:

$\rightarrow$ Star rectifier

$\rightarrow$ Bridge rectifier

* Full wave - conduction angle = 360

Date: _____

Mo Tu We Th Fr Sa Su /


→ STAR RECTIFIERS (Half wave)

• Diode - ON: when voltage on that phase is greater than the other two.


• Diode conduction angle: $2\pi/3$ instead of π .

→ 1 phase → 1 diode ⇒ half wave

→ 2 phase → 2 diode ⇒ full wave.

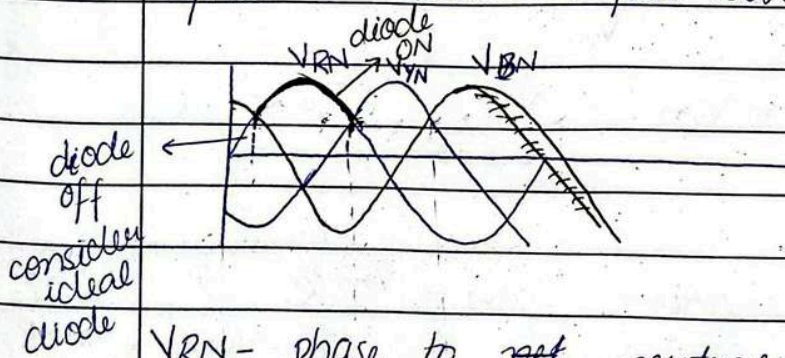

V_{RN} - phase to net neutral

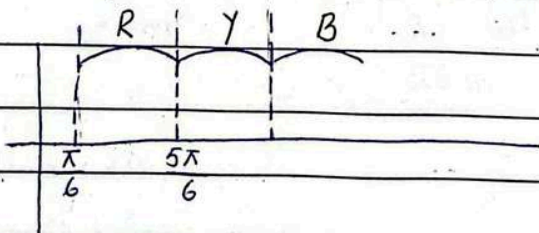

$$V_m \sin \omega t \text{ dwt}$$

$$= V_m \sin \theta d\theta$$

$$T_{ON} = \frac{5\pi}{6} - \frac{\pi}{6} = \frac{2\pi}{3} \text{ rad}$$

Conduction angle = 120° OR $\frac{2\pi}{3}$ rad

$$V_{DC} = \frac{1}{T_{ON}} \int_{\pi/6}^{\frac{5\pi}{6}} V_m \sin \theta d\theta$$

$$= \frac{3}{2\pi} \int_{\pi/6}^{\frac{5\pi}{6}} V_m \sin \theta d\theta$$

Date: _____

Mo Tu We Th Fr Sa Su

$$V_{DC} = 0.8269 V_m$$

$$\approx 0.827 V_m$$

$$V_{RMS} = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m^2 \sin^2 \theta d\theta}$$

$$RMS = \frac{PEAK}{\sqrt{2}}$$

$$V_{RMS} = 0.84 V_m$$

$$I_s = \sqrt{\frac{1}{2\pi} \int_{\pi/6}^{5\pi/6} I_m^2 \sin^2 \theta d\theta}$$

works one time for each winding

$$I_s = 0.485 I_m$$

$$I_s = 0.485 \frac{V_m}{R}$$

EXAMPLE #3

A three ^{phase} star rectifier:

i) Efficiency = $\sigma = \frac{V_{DC} \times I_{DC}}{V_{RMS} \times I_{RMS}}$

$$= \frac{0.827 V_m \times 0.827 V_m / R}{0.84 V_m \times 0.84 / R}$$

$$= 0.969 = 96.9\%$$

$$I_{RMS} = V_{RMS} / R$$

ii) $FF = \frac{V_{RMS}}{V_{DC}} = 1.015$

Date: _____

Mo Tu We Th Fr Sa Su /

$$\text{iii) } RF = \sqrt{FF^2 - 1} = \sqrt{(1.01)^2 - 1} = 0.141$$

$$\text{iv) } TUF = \frac{P_{DC}}{3 \times V_s \times I_s} = \frac{V_{DC} \times I_{DC}}{3 \times V_s \times I_s}$$

$$V_s = 0.707 V_m$$

$$I_s = 0.485 I_m$$

$$TUF = (0.827)^2 / (3 \times 0.707 \times 0.485)$$

$$TUF = 0.66 < 1 \quad \text{*(always less than 1)}$$

$$V_{ab} = V_a - V_b$$

$\downarrow$
 phase to phase voltage
 OR
 line-to-line voltage
 (line voltage)
 V_L

$\downarrow$
 Phase-to-neutral voltage (Phase voltage)
 OR
 line-to-neutral voltage
 V_P

$$* \quad V_L = \sqrt{3} V_P \quad (1 \angle 0 - 1 \angle 120 = \sqrt{3})$$

$$\Rightarrow * \quad PIV = \sqrt{3} V_m$$

$\downarrow$
 line rating

$$\rightarrow \text{v) } PF = \frac{P_{AC}}{3 \times V_s \times I_s} = \frac{0.84^2}{3 \times 0.707 \times 0.485} = 0.685$$

$$\text{vi) } PIV = V_m$$

Date: _____

Mo Tu We Th Fr Sa Su

vii) $I_{DC} = 30 A$ (given) , $V_{DC} = 140 V$ (given)

$$I_{\text{Diode (avg)}} = \frac{30}{3} = 10 \quad (i)$$

$$I_{DC} = 0.827 I_m$$

$$I_{\text{Diode (avg)}} = 0.275 I_m \quad (ii) \therefore 0.827/3$$

Compare eq. (i) & (ii)

$$10 = 0.275 I_m$$

$$I_m = 36.27 A$$

(Peak)

30/4 THREE PHASE BRIDGE RECTIFIERS:

- Conduction angle = $\frac{2\pi}{3}$

- highest possible TUF

→ No. of diode shows how it will ON.

→ At a time, 2 diodes will be ON.

- Line voltage = $\sqrt{3} V_m$

$$V_p = \sqrt{3} V_m = 1.73 V_m$$

- * $V_{DC} = V_{AVG} = \frac{6}{2\pi} \int_{\pi/3}^{2\pi/3} \sqrt{3} V_m \sin \theta d\theta \quad (6 \text{ waves})$

$$= 1.6539$$

$$= 1.654 V_m$$

- * $V_{RMS} = \sqrt{\frac{6}{2\pi} \int_{\pi/3}^{2\pi/3} (\sqrt{3} V_m \sin \theta)^2 d\theta}$

$$= 1.655 V_m$$

$$I_{S(AVG)} = \frac{4}{2\pi} \int_{\pi/3}^{\pi/3} I_m \sin \theta d\theta$$

Date: _____

Mo Tu We Th Fr Sa Su /

$$I_s = \sqrt{\frac{4}{2\pi} \int_{\pi/3}^{\pi/3} I_m^2 \sin^2 \theta d\theta}$$

(in transformer:
current flows only if
related diodes are ON)

$$I_s = 0.78 I_m \quad (\text{each winding - transformer secondary current})$$

$$I_m = \frac{\sqrt{3} V_m}{R}$$

$$\text{Diode current} = \frac{\sqrt{3} V_m}{R} I_{D_{RMS}} = \sqrt{\frac{2}{2\pi} \int_{\pi/3}^{\pi/3} I_m^2 \sin^2 \theta d\theta}$$

$$= 0.552 I_m$$

$$TUF = \frac{(1.654)^2}{3 I_s V_s}$$

$$= \frac{(1.654)^2 (1.654 V_m / R)}{3 \times 0.707 V_m \times 0.78 \times \sqrt{3} V_m / R}$$

$$= 0.954$$

EXAMPLE #4

(from Power electronics 4th Edition
by Hameed Rashid)

$$V_{DC} = 280.7 \text{ V}$$

$$(i) \& (ii) \quad V_{DC} = 1.654 V_m \quad (iii)$$

$$\Rightarrow V_m = 169.71 \text{ V}$$

$$V_m = \frac{280.7}{1.654}$$

$$PIV = \sqrt{3} V_m$$

$$= 293.94$$

* if not given, consider it as RMS value.

Date: _____

Mo Tu We Th Fr Sa Su

EXAMPLE #5 (Line to neutral voltage)


$$I_{DC} = 60A, V_{supply} = 120$$

$$\rightarrow I_D (avg) = \frac{1}{2\pi} \int_{\pi/3}^{\pi} I_{DC} d\theta = 20A$$

$$\rightarrow I_D (RMS) = \sqrt{\frac{1}{2\pi} \int_{\pi/3}^{\pi} 60^2 d\theta}$$

$$= 34.64$$
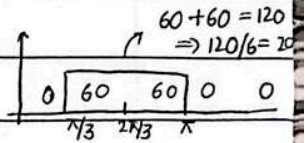
$$OR \frac{I_{DC}}{\sqrt{3}} = \frac{60}{\sqrt{3}} = 34.64$$



$$\rightarrow PIV = \sqrt{3} V_m$$

$$= \sqrt{3} \times 120_{RMS}$$

$$= \sqrt{3} \times \sqrt{2} \times 120$$

$$= 293.93$$

$$V_{RMS} = \frac{V_{peak}}{\sqrt{2}}$$

EXAMPLE #6

$$a) I_{RMS} = ?$$

$$t_1 = 100\mu s, t_2 = 350\mu s, t_3 = 500\mu s,$$

$$f = 250Hz, f_s = 5kHz, I_m = 450A, I_a = 150A$$

$$I_{(AVG)} = \frac{1}{T} \int_0^{t_1} I_m \sin \omega_0 t dt + \frac{1}{T} \int_{t_2}^{t_3} i_2 dt$$

$$\frac{1}{T} = 250$$

$$\frac{250}{\pi} 5000 t$$

$$\therefore \omega_0 = 2\pi f_s = (2\pi 5000)$$


$$= \frac{1}{\pi} 250 \left[\int_0^{100\mu} 450 \sin(2\pi 5000 t) dt + \int_{350\mu}^{500\mu} 150 dt \right]$$

$$= 12.79$$

$$I_{RMS} = 58.09$$

THYRISTORS

(uncontrolled rectifiers)


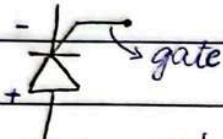


(it will not work until trigger is applied at gate)
(will also work if voltage is increased - No gate pulse applied)

- Delivers 1000's of W to the load of 98% efficiency.

→ SCR (Silicon controlled rectifiers)

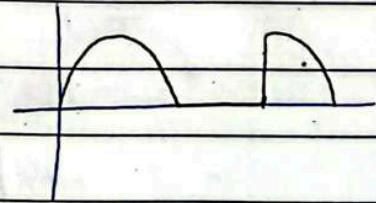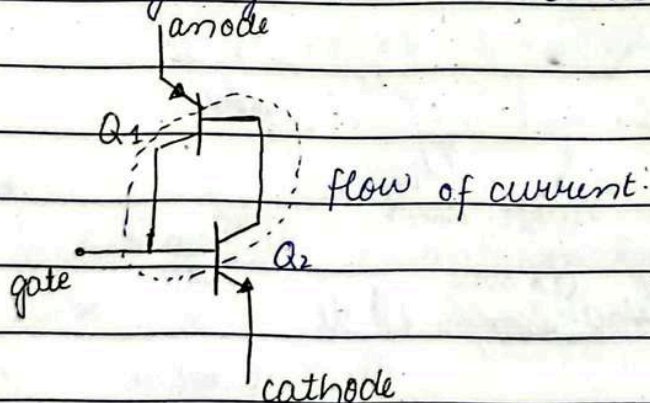- Circuits that protect thyristors and line are called snubbers.
- Q_2 keeps Q_1 ON, Q_1 keeps Q_2 ON.
- Thyristors - 4 layers $\Rightarrow$ PNP
- Inherently they are always OFF.
- To stop working thyristors - reduce its current.





5/5 SILICON CONTROLLED RECTIFIER

- Current above holding current $\Rightarrow$ SCR - ON
 I_H

Date: _____

Mo Tu We Th Fr Sa Su

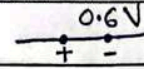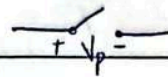- $V_{TM(min)} = 0.6V$
- I_{SM} : Surge current



Thousands of Watts delivers to load.

- $I_{RMS} = I_P/2$

- V_{gt} :

0.7V to forward-bias the gate collector junction.

SNUBBING

- Thyristors turn on in 10 μ s to 100 μ s.
- Voltage across them $\downarrow$ (line peak of 100's to 2V)
- Current increases from 0 to tens to hundreds Ampere.
- $\rightarrow$ to control di/dt place an inductor in series with the thyristors.
- in snubbers: (CRITICAL RATE OF RISE ^{OF} ~~I~~ CURRENT)

*
$$L > \frac{V_{P, LINE (peak)}}{(di/dt)_{(peak) spec.}}$$

EXAMPLE #1

$V_{UNE} = 220V_{RMS}$, $f_{LINE} = 50Hz$

$R_L = 80\Omega$, $di/dt = 50A/\mu s$.

a)
$$L > \frac{220\sqrt{2}}{50/\mu} = 4.4\mu H$$

$$L > 6.22\mu H$$



Date: _____

Mo Tu We Th Fr Sa Su /

b) $Z_L = j\omega L$ (impedance of inductor)
 $= (2\pi (50)) (6.2\mu) \angle 90^\circ$
 $\searrow +j$
 $= 1.95_m \angle 90^\circ$
 $= 0.00195 \angle 90^\circ$

CRITICAL RATE OF RISE OF VOLTAGE:

- Transistor may turn on due to noise (w/o gate pulse) because of parasitic capacitance b/w main terminal & gate.


→ $V_c = V_{p,noise} (1 - e^{-t/(R_L \times C_{snub})})$

→ $\tau = 1/RC \Rightarrow \text{natural response} = V_0 e^{-t/\tau} = V_0 e^{-t/RC}$

→ $\frac{dV_c(snub)}{dt} = \frac{V_{p,noise}}{R_L \times C_{snub}} e^{-t/(R_L \times C_{snub})}$

→ Worst case, $t=0$ capacitor charges quickly.

$\left. \frac{dV_c(snub)}{dt} \right|_{\text{worst case, } t=0} = \frac{V_{p,noise}}{R_L \times C_{snub}}$

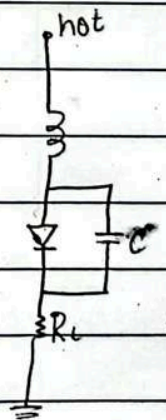

→ $i = C \frac{dV_c}{dt}$

* Use V_{RMS} as $V_{p,noise}$

$C_{snub} > \frac{V_{DRM}}{R_{LOAD} \times (dV/dt)_{spec}}$

$R_{LOAD} \times (dV/dt)_{spec}$

data by manufacturer

Date: _____

Mo Tu We Th Fr Sa Su

EXAMPLE #2

$$V_{LINE} = 220 V_{RMS}, \quad f_{LINE} = 50 Hz, \quad V_{DRM} = 400 V_{(PEAK)}$$

$$R_L = 80 \Omega, \quad dv/dt = 75 / \mu V$$

$$a) \quad C > \frac{V_{RM}}{R_L \times (dv/dt)} = \frac{400}{80(75/\mu)}$$

$$C > 66.7 nF = 0.067 \mu F$$

$$C \approx 0.1 \mu F$$

$$b) \quad i = \frac{C dv}{dt} = (0.067 \mu)(75/\mu)$$

$$Z_{Xc} = \frac{1}{j\omega C}$$

$$*X_c = 1/\omega C \text{ (w/o } j)$$

$$= \frac{1}{(2\pi \times 50)(0.1 \mu F)} \angle -90^\circ$$

$$= 31830.9 \angle -90^\circ$$

$$= 32k \angle -90^\circ$$

$$* I_{Leakage} = I_{LOAD} = \frac{V_{RMS}}{R_{LOAD} + Z_c} = \frac{220}{(80) + (32k \angle -90^\circ)}$$

$$= 6.87_m \angle 89.85^\circ$$

$$= 6.9_m \angle 90^\circ A$$

$$* I_L = I_{RMS}$$

$$V_{LOAD} = (6.9_m \angle 90^\circ)(80)$$

$$= 0.5 V_{RMS} \angle 90^\circ$$

$$P_{LOAD} = I_{LOAD} \times V_{LOAD}$$

$$= 3 mW$$

AZHAR BOOK

LEAKAGE CURRENT:

- Current through capacitor is leakage current.

$$I_{\text{discharge}} = \frac{V_{P, \text{LINE}}}{R_{\text{snubbing}}}$$

Total current at anode becomes.

$$I_{\text{SCR}} = I_{P, \text{LOAD}} + I_{\text{discharge}} < I_{\text{TSM}}$$

$$I_{\text{TSM}} > I_{P, \text{LOAD}} + I_{\text{discharge}}$$

$$\Rightarrow R_{\text{snubbing}} > \frac{V_{P, \text{LINE}}}{I_{\text{TSM}} - I_{P, \text{LOAD}}}$$

EXAMPLE #3

$$V_{\text{LINE}} = 220 \text{ VRMS}, \quad f_{\text{LINE}} = 50 \text{ Hz}$$

$$R_{\text{LOAD}} = 80 \Omega, \quad I_{\text{TSM}} = 46 \text{ A}$$

$$R_{\text{snubbing}} > \frac{220 \sqrt{2}}{46 - \left(\frac{220 \sqrt{2}}{80} \right)}$$

V_{LINE}

R_{LOAD}

$$= 7.38 \Omega$$