

POWER ELECTRONICS

Power Switches

Introduction

- Linear amplifier can deliver hundreds of watt to the load, at low distortion
- Dissipates half of the power provided by the dc supply
- Converts dc voltage into heat
- Can be replaced with a **switch** (distortion about 0.5%)
- When switch is off – no power dissipation
- When switch is on – low voltage drop
- 90% of power delivered to the load
- Much efficient and accurate

Low Side and High Side


- Switch circuit common
 - Allowing load to float
 - Low side switch
- Switch the power on and off
 - High side switch

Objectives

- To get familiar with switching characteristics of diodes and transistors, defining key parameters
- Study diode, Schottky diode, BJT transistor, MOSFET transistor as switch
- Familiar with the design and operation of low side and high side switch

Switching Characteristics, Diode

- Potential barrier, forward bias, reverse bias, Diode 1N4002
- For 60 Hz
- For higher frequencies like 100 kHz
- First problem:
 - Only 9 out of 10 V delivered to the load
 - 10% is dropped by the diode
 - Depending on diode, the drop may be 2 V
 - 2 V out of 160 V_p is insignificant (line powered app)
 - 2 V out of 5 V is too much (logic circuit)
- Second problem:
 - Diode doesn't turn off during negative half
 - Diode conducts in two directions

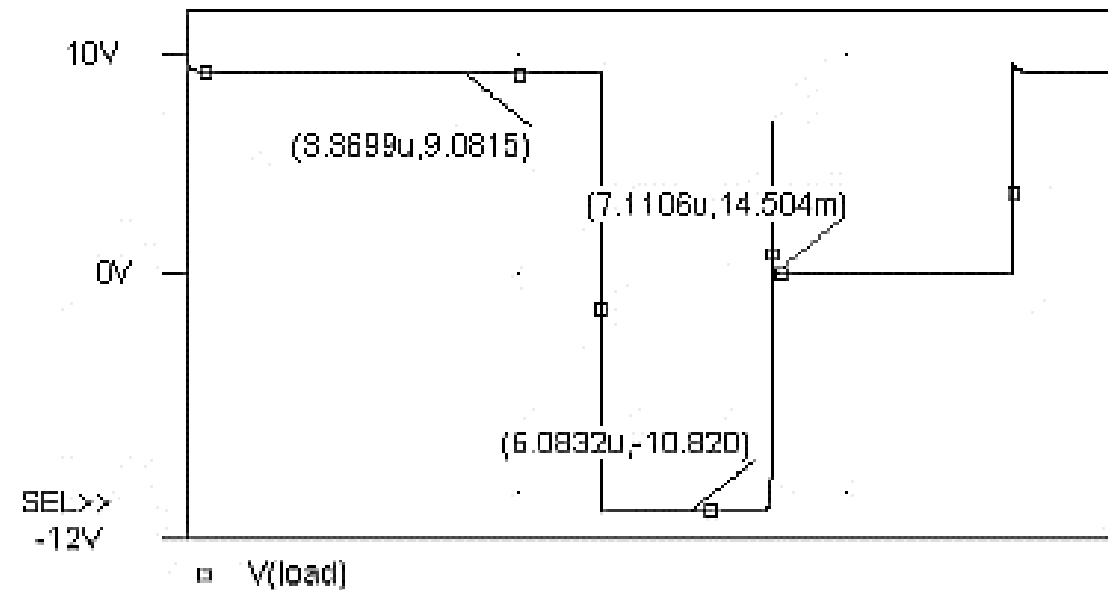

Switching Characteristics, Diode


- Depletion region characteristics
- **Reverse Recovery Time (t_{rr})**
- For 60 Hz this time is a small part of the signal, no effect is observed
- At 100 kHz, significant part of the negative cycle is delivered to the load
- During t_{rr} the diode is not rectifying
- Select a diode whose $t_{rr} \ll t_{signal\ off}$

Schottky Diode


- No traditional pn junction
- Metal contact attached to n – type semiconductor
- No p – type material available
- By eliminating pn junction, both problems of traditional diode are solved
- Negligible voltage drop (on state)
- Negligible reverse recovery time

Schottky Diode

- 0.3 V drop
- Negligible reverse recovery
- **Problem with Schottky Diode:**
- Small **Reverse Voltage Breakdown**
- Usually less than 60 V
- **PIV** ratings

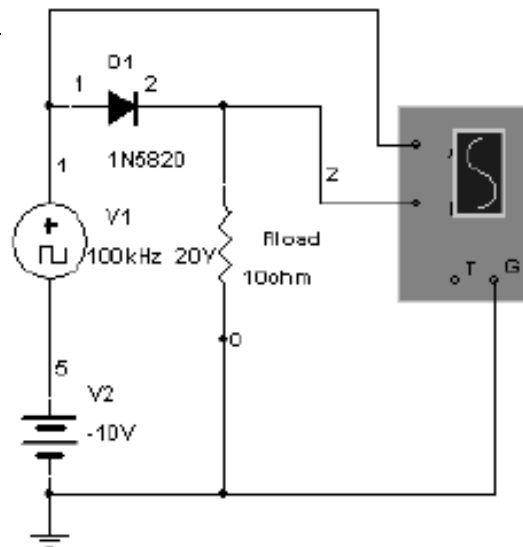


Only 0.3V
dropped across
the diode

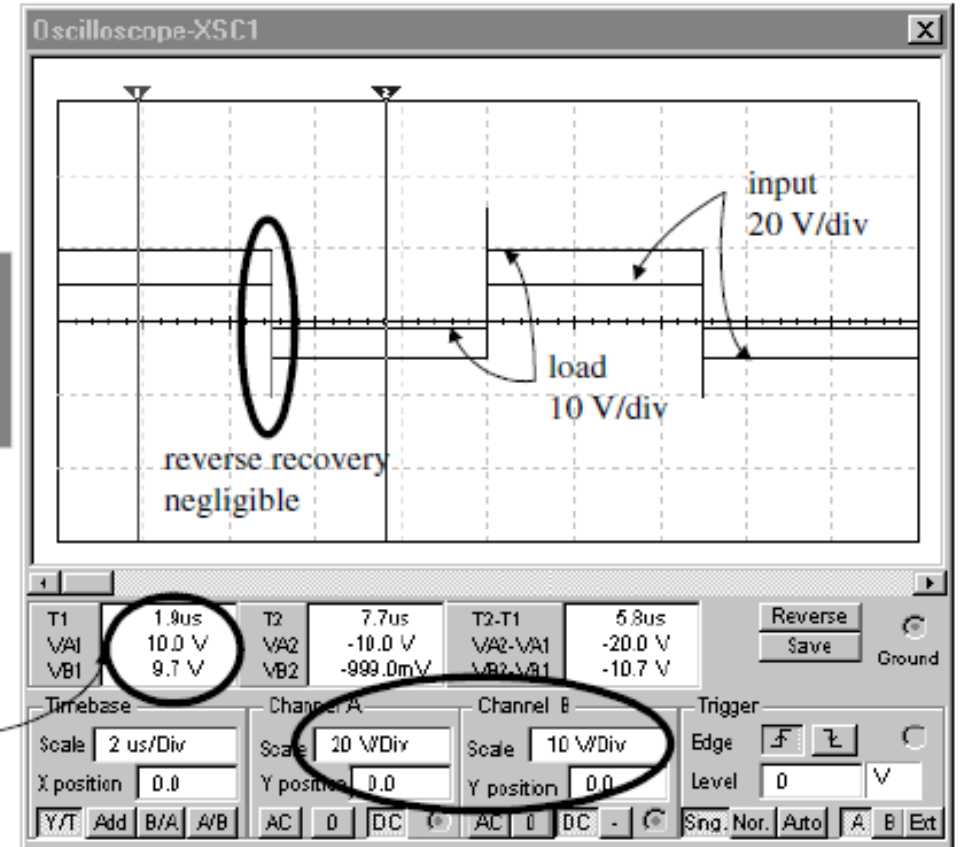

Switching Characteristics, Transistors

- Figure shows npn or pnp transistor?
- The base current depends on positive E_{in}
- $I_{base} = \frac{E_{in} - 0.6}{R_{base}}$
- Collector current depends on base current
- $I_c = \beta I_{base}$
- For power transistor β may be as low as 20
- For switching, transistor must be turned on, passing all current
- $I_c = \frac{E_{supply} - V_{CE(sat)}}{R_{load}}$
- Where $0.2 \text{ V} < V_{CE(sat)} < 1.0 \text{ V}$
- $V_{CE(sat)}$ depends on transistor, I_c and temperature

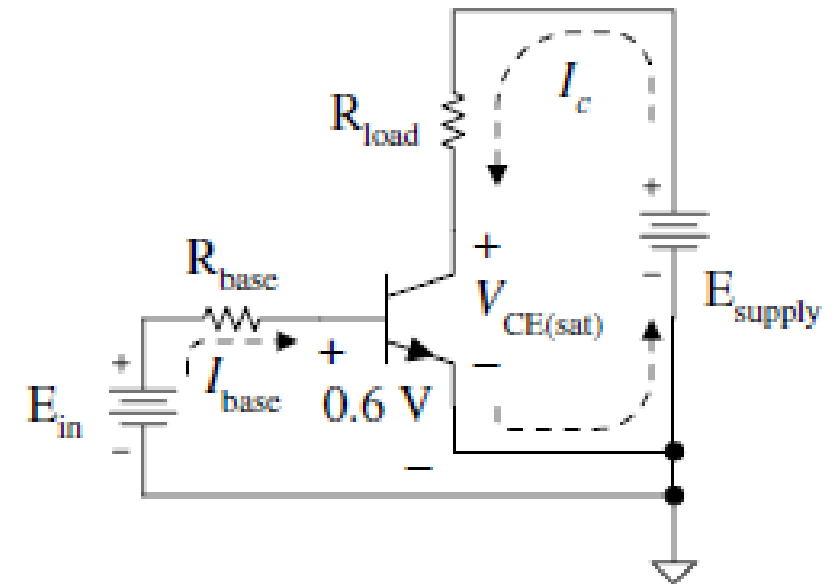

Switching Characteristics, Transistors

- Higher the collector current, larger the voltage across the transistor switch
- To ensure the transistor is on as hard as possible, base current should be higher than the required value
- $I_{base} > \frac{I_c}{\beta}$


Example

- For the circuit shown in figure, $E_{supply} = 28 \text{ V}_{dc}$, $E_{in} = 5 \text{ V}_{dc}$, $R_{load} = 15 \Omega$

$$V_{CE(sat)} = 0.8 \text{ V}, \quad \beta = 20$$


Calculate the following:
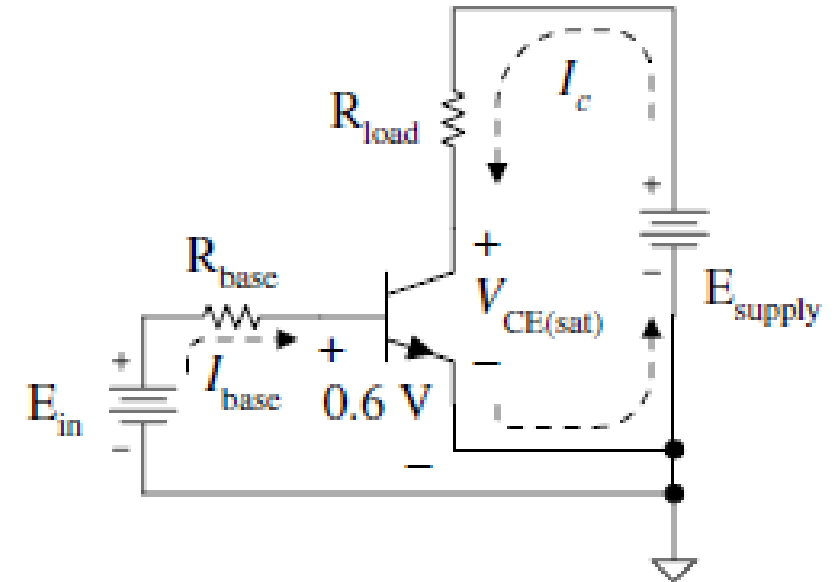
$$I_C, \quad P_{load}, \quad P_Q, \quad I_{base}, \quad R_{base}$$




Key Points in Previous Example

- Almost 50 W is delivered to load while the power dissipation in transistor is only 1.5 W
- Much better than delivering power with push-pull amplifier
- 90 mA base current is so large (because β is small)
- By increasing β , base drive requirements drop
- High β and high collector current is possible with **Darlington Pair** configuration
- Single package with three terminals; base, emitter and collector

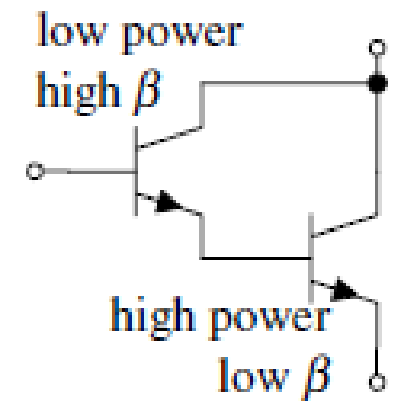

High Frequency Testing

- $E_{supply} = 12\text{ V}$
- 10 kHz, 50% duty cycle, 5 V input
- When on, $V_{col} = 0.849\text{ V}$
- When input goes low, turns off and $V_{col} = 12\text{ V}$
- **Storage Time** (transistor remains on)
 - Middle of input edge to 10% rise point in V_{col}
- **Rise Time** (V_{col} rises from 10% to 90%)
 - Depends on load resistance and capacitance
- **Delay Time** (to turn the transistor on)
 - Middle of rising edge to 90% point in V_{col}
- **Fall Time** (V_{col} falls from 90% to 10%)
 - all capacitors are discharged

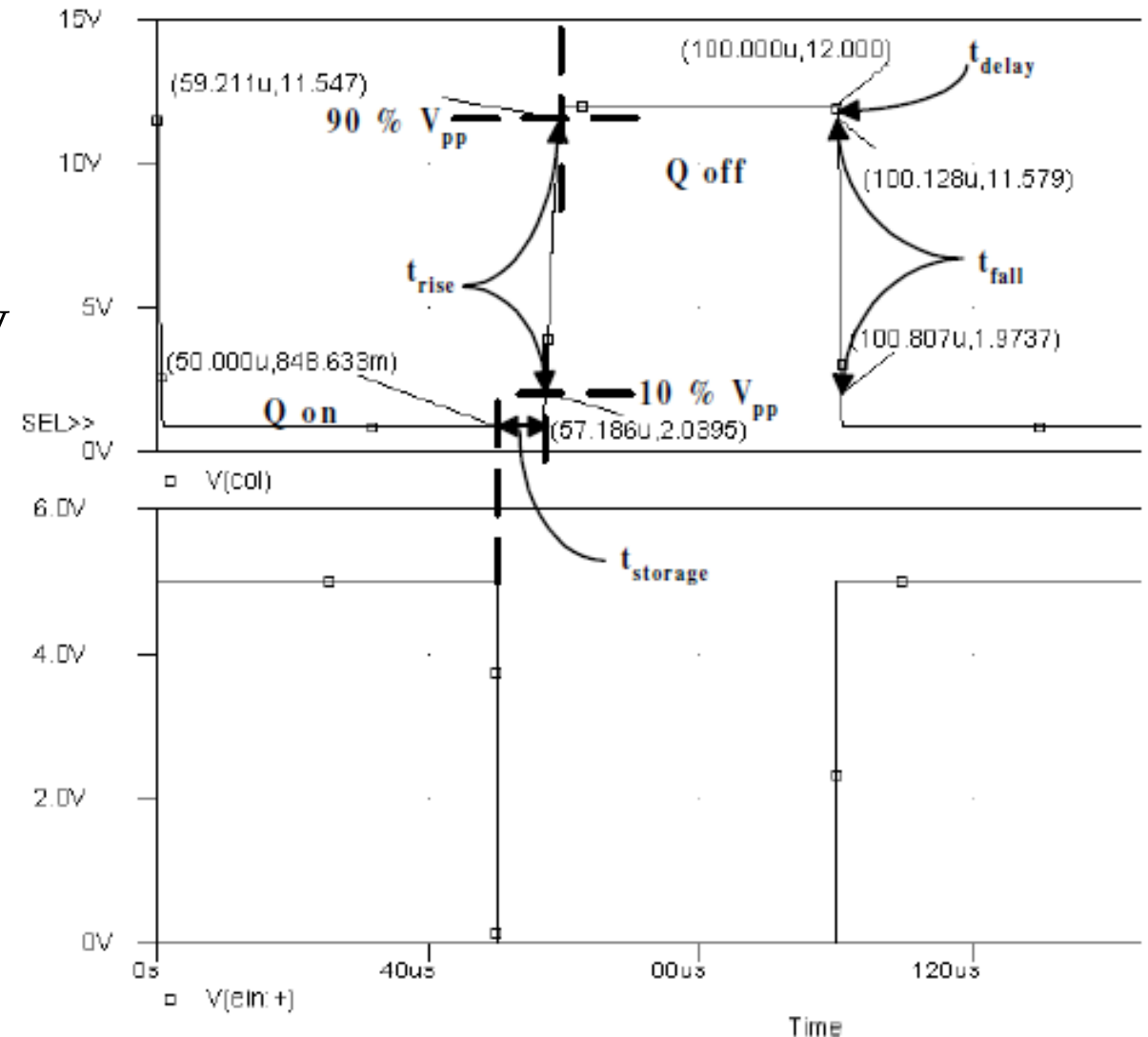

Problems with Darlington Pair

- In previous circuit, the frequency is 10 kHz, produces high pitch whine
- Interference (too much annoying)
- Solution: run the circuit at 100 kHz
 - Storage time becomes greater than pulse width
 - Transistor never goes off
- Conclusion: Darlington Pair can not switch above the audio range


Enhancement Mode MOSFET

- Can be used as switch
- Larger the gate-to-source voltage, larger the channel between the source and drain
- Therefore, lower the channel resistance
- To turn the transistor hard on $10\text{ V} < V_{GS} < 20\text{ V}$

Comparison with Darlington Pair

- Comparable to Darlington pair discussed before but it operates 50 times faster
- 0.17 V instead of 0.89 V in *on* state
- 0.33 W wastes only, four times better
- Little storage time
- Negligible rise and fall time

	Darlington Pair	MOSFET
Storage Time	7.19 μ s	9.2 ns
Rise Time	2.03 μ s	8.0 ns
Delay Time	128 ns	0.9 ns
Fall Time	679 ns	2.6 ns


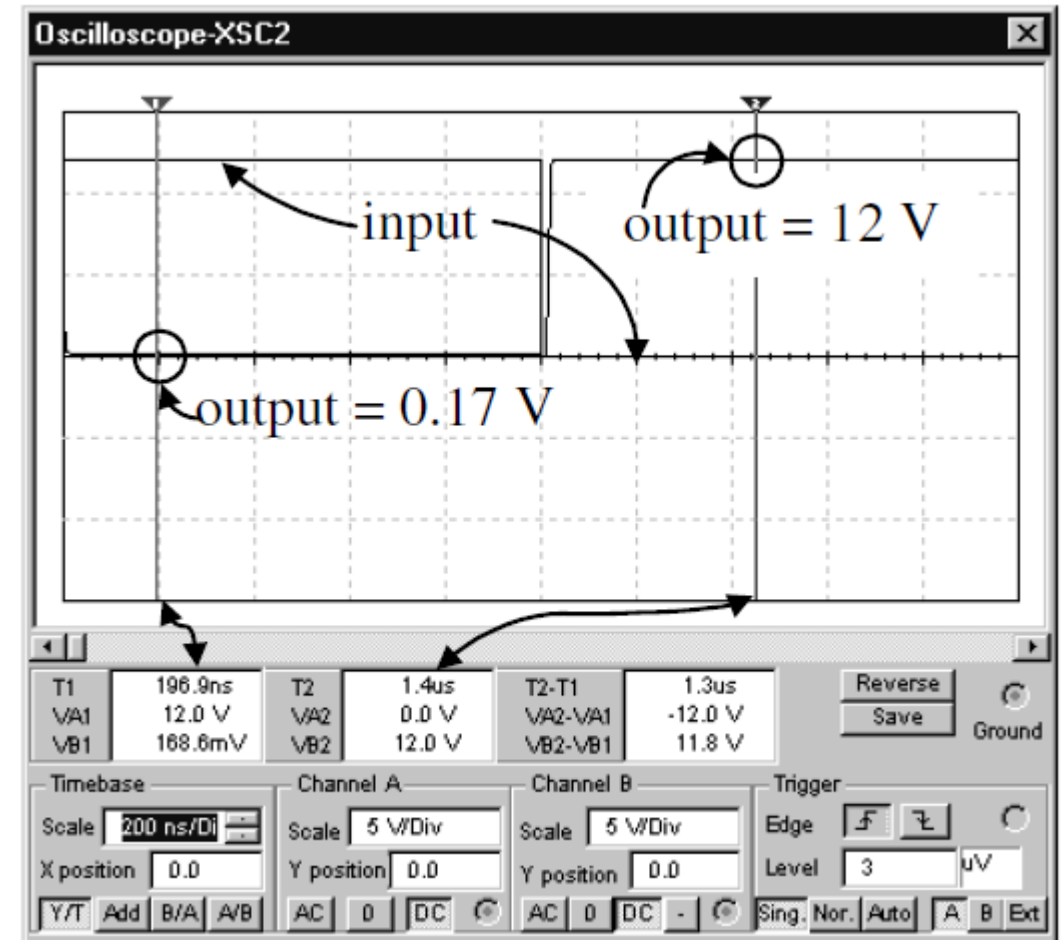


Parallel MOSFET Switches

- Drain to drain to drain..., source to source to source..., gate to gate to gate...
- R_{on} reduces from $0.11\ \Omega$ to $0.014\ \Omega$ in 8 parallel MOSFET
- $0.33\ \text{W}$ reduces to $0.056\ \text{W}$
- Transistor stays cooler
- Less cost as compared to buy a heat sink for single transistor
- Less space required as compared to single transistor with heat sink

Low Side Switches

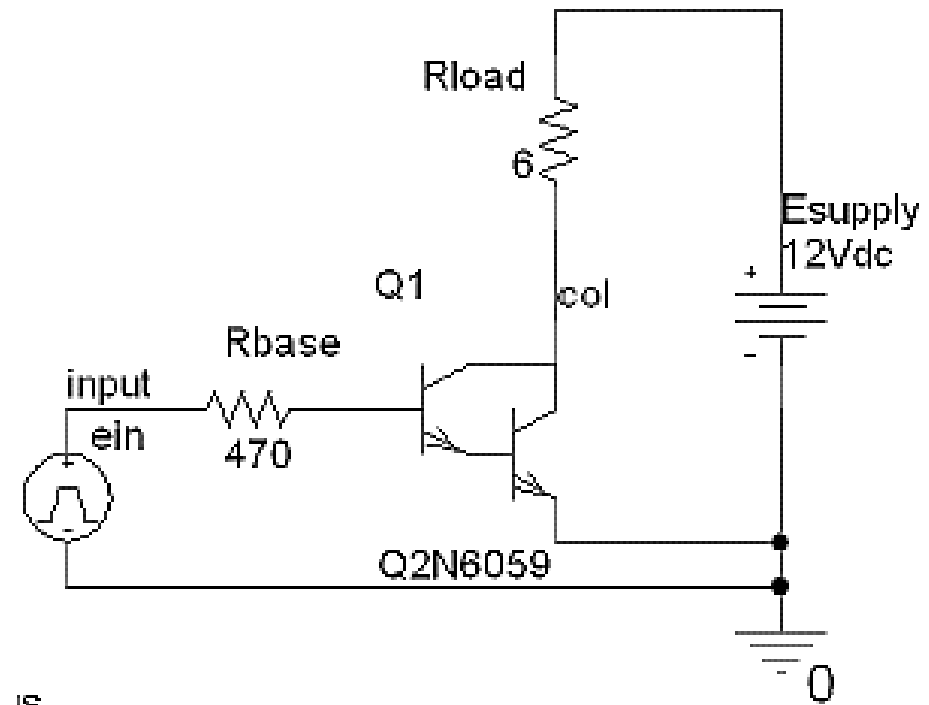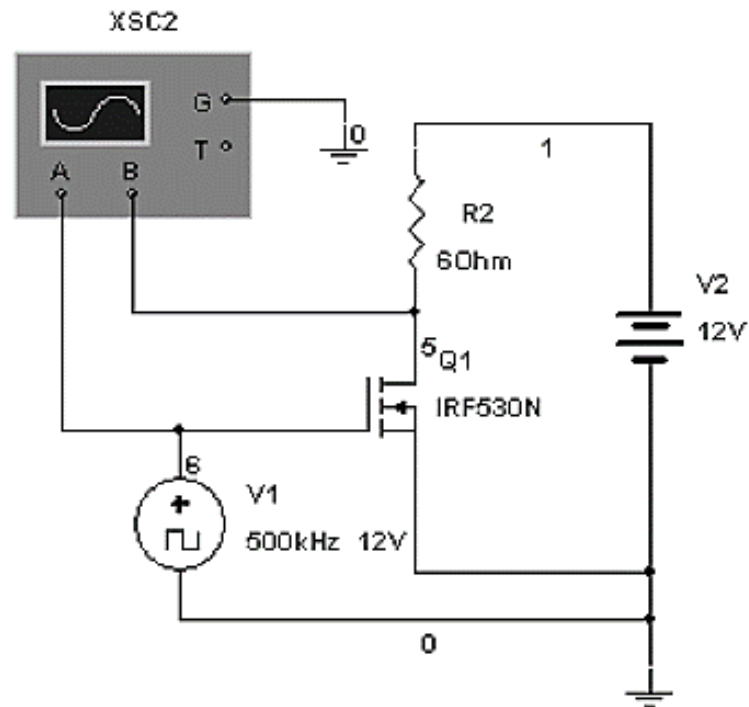- Placed between load and circuit common,
- The other end of the load is pulled up by the supply



BJT as Low Side Switch



- BJT is a poor high speed, high current switch
- For applications that require 100 mA current or less, BJT works well
- Preferable to MOSFET in some cases
- Hard on from a supply voltage of 3.3 V to 5 V
- Smaller and lighter circuit board with BJT as compared to MOSFET
- For hard on BJT, $V_{BE} = 0.9 \text{ V}$, $V_{CE} = 0.3 \text{ V}$ and $I_C = 50 \text{ mA}$

Example

- Design a low side switch using 2N3904, a supply voltage of 28 V dc with a rectangular pulse input of 0 V to 2.4 V, 100 kHz. Set collector current to 50 mA peak. Use the smallest practical load resistance. $\beta = 100$
- Calculate P_{load} and P_Q

Parasitic Capacitance Effect

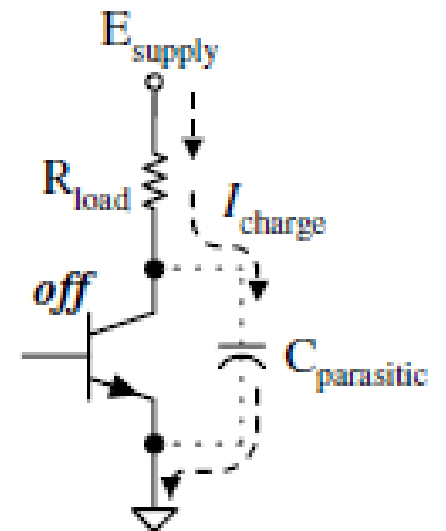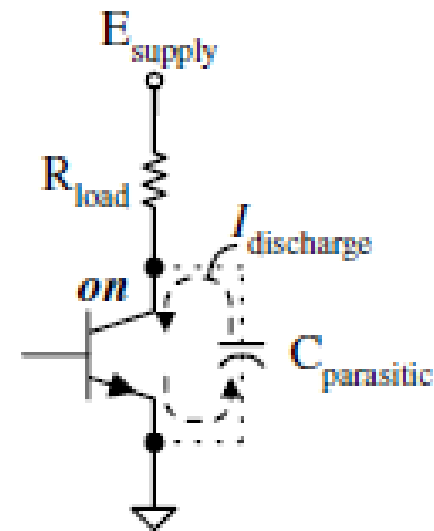- Effect on rise and fall time
- $t_{rise\ RC} = 2.2R_{load}C_{parasitic}$



Example


- Determine the rise time for $C = 640 \text{ pF}$, $R_{load} = 560 \text{ }\Omega$, and for $C = 640 \text{ pF}$ and $R_{load} = 3.3 \text{ k}\Omega$ in the previous example.

MOSFET as Low Side Switch

- Switch several amps of current or more
- For speed less than 100 ns, enhancement mode MOSFET can be used
- *hard on*: $10 V_p \leq V_{GS} \leq 20 V_p$
- Opening resistance less than 0.11Ω at 25°C
- Resistance increases when MOSFET heats up

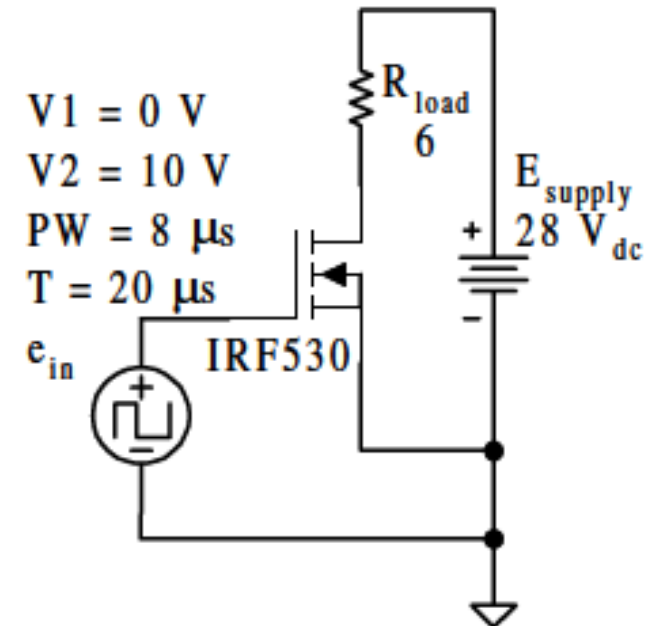
Example

- For the circuit shown in figure, the open resistance at 175 °C is scaled up by the factor of 2.6 over its resistance at 25 °C. Calculate $R_{on\ worstcase}$, $i_{p\ load}$, P_{load} , P_Q , T_J with $T_A = 40^\circ\text{C}$ and no heat sink ($\Theta_{JA} = 62 \frac{^\circ\text{C}}{\text{W}}$)



Improved Circuit

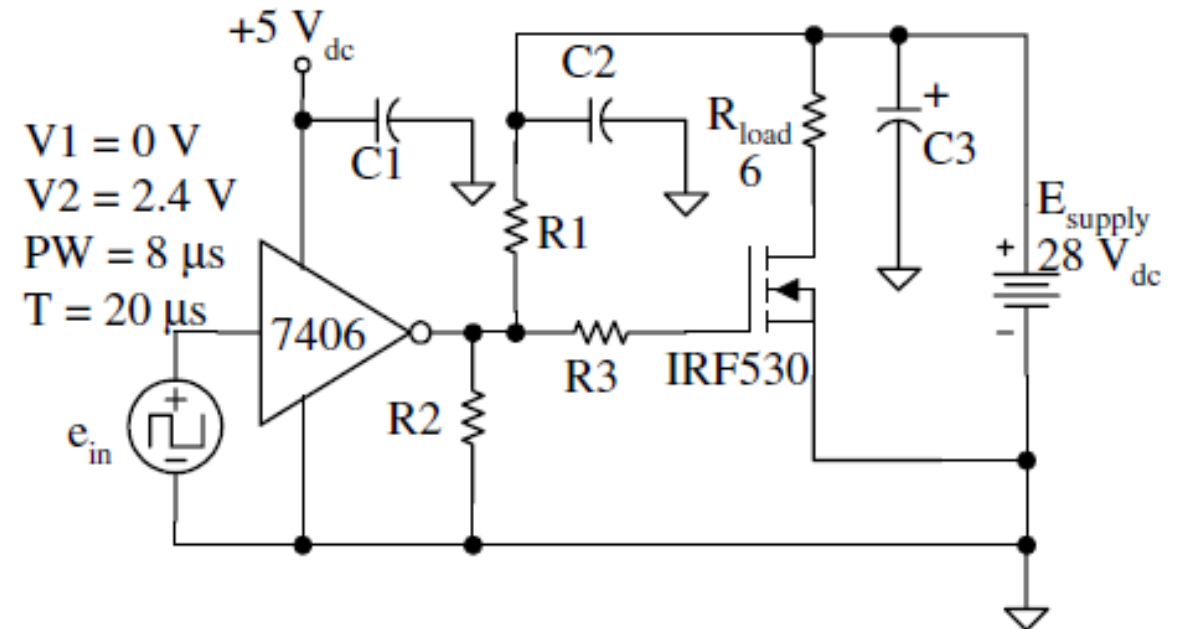- The current 4.45 A_P is far more than 7406 logic gate or the 2N3904 BJT can handle
- Less than half of the maximum of IRF530
- Input logic level comes from logic circuit or microprocessor = 2.4 V only
- 7406 to increase input to 10 to 20 V
- R_1 and R_2 provides voltage divider
- Capacitors are for decoupling the power circuits
- R_3 dampens the parasitic capacitance effect




High Side Switch

- Many loads must be tied to common
- In this case, switch removes the voltage from the supply
- Switch sits on the **high side** of the load
- How to make high side switch? Your thoughts?


n-Channel MOSFET as High Side Switch

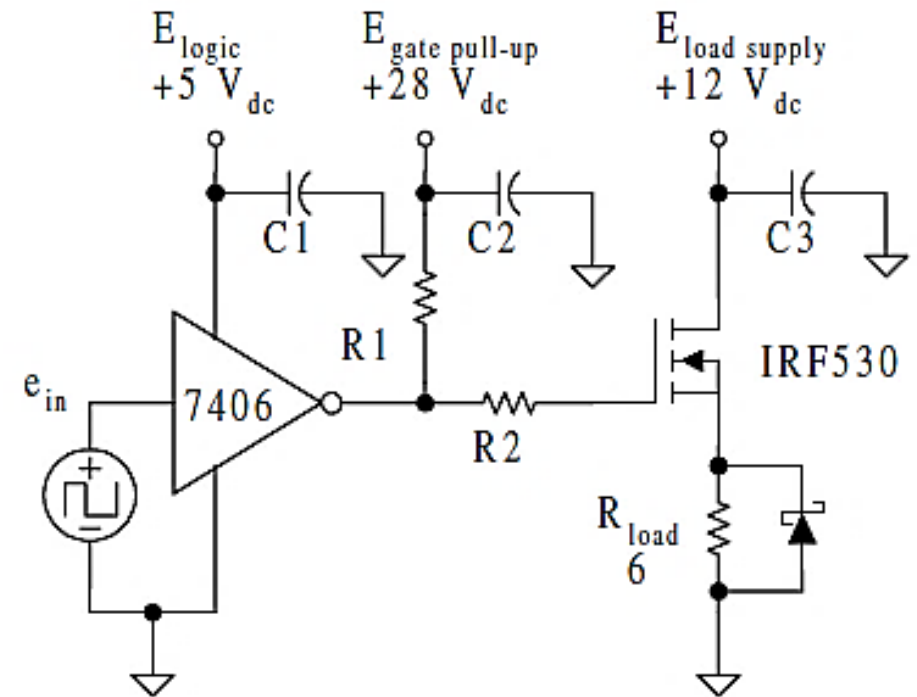- Voltage divider removed from the MOSFET's gate
- When input is high, 7406 outputs a low, turning the switch off
- When input goes low, 7406 output transistor goes on, the gate is pulled up to 28 V dc and the switch turns on
- When MOSFET is on, source voltage increases too
- Gate at +28 V, source at +12 V
- $V_{GS} = 28 - 12 = 16 \text{ V}$




p-Channel MOSFET as High Side Switch

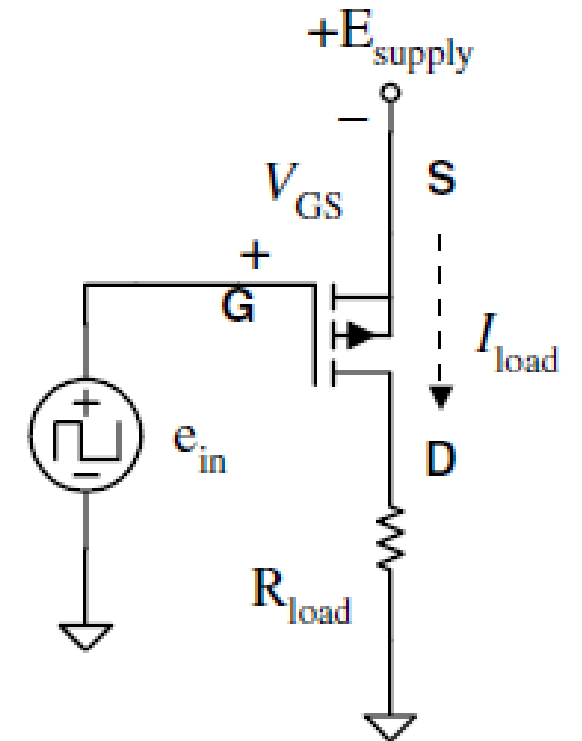- Slower than n-channel MOSFET
- Can be used as high side switch
- $V_{GS} = V_G - V_S$



p-Channel MOSFET as High Side Switch

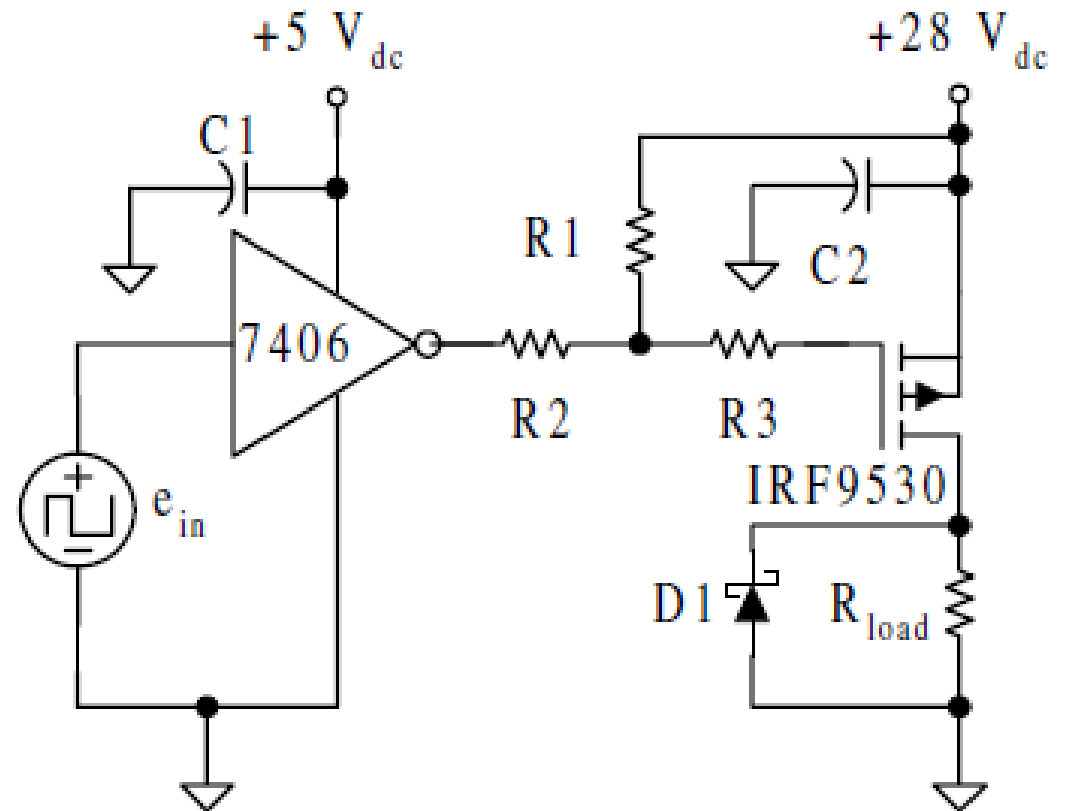- Practical circuit as n-channel low side switch
- R_1 and R_2 should be selected as per current requirements
- 7406 can sinks up to 40 mA_P at output of 0.7 V_P
- $8 \leq V_G \leq 18$




Example

- Design a p-channel high side switch
- For $R_{load} = 12\ \Omega$ determine voltage at each node when $e_{in} = 0.8 V_P$ and when $e_{in} = 2.4 V_P$
- Calculate v_{load} if IRF9530 on resistance is 0.57
- When e_{in} is a 30 kHz, 80% duty cycle, calculate:


P_{load} , P_Q and Θ_{SA} if $T_{Jmax} = 150\ ^\circ\text{C}$ and $T_A = 50\ ^\circ\text{C}$

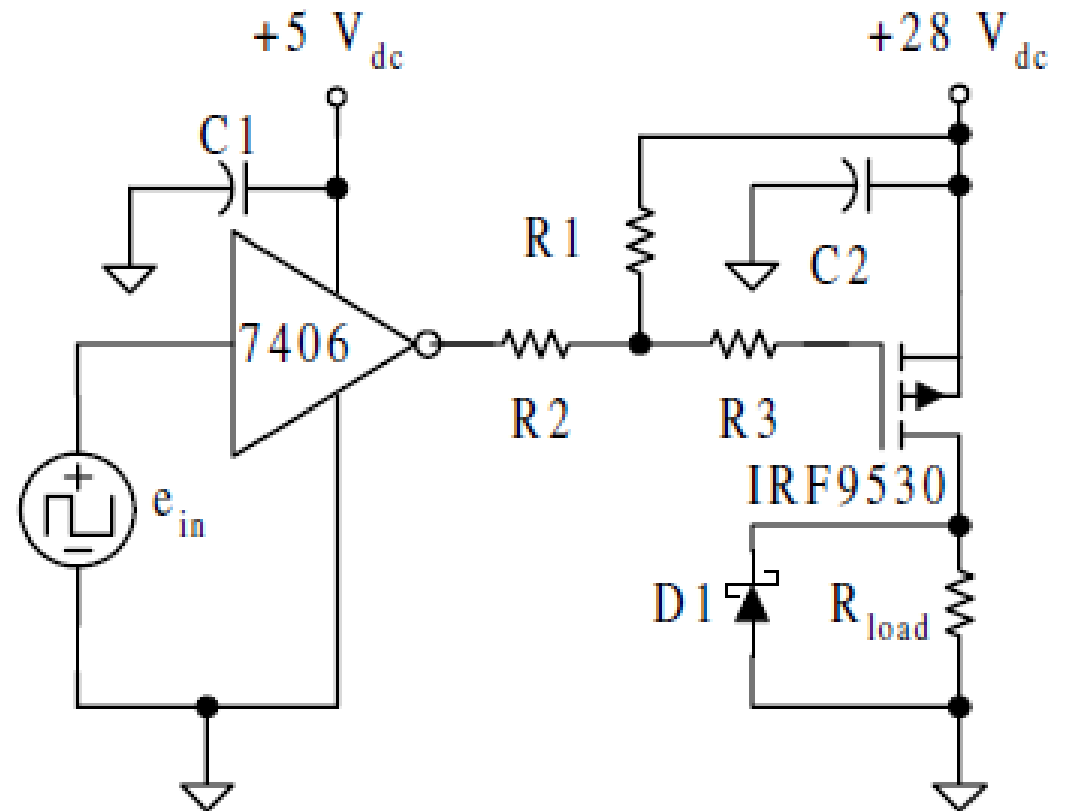$\Theta_{JC} = 1.7\ ^\circ\text{C/W}$ and $\Theta_{CS} = 2\ ^\circ\text{C/W}$ with mica wafer



pnp High Side Switch

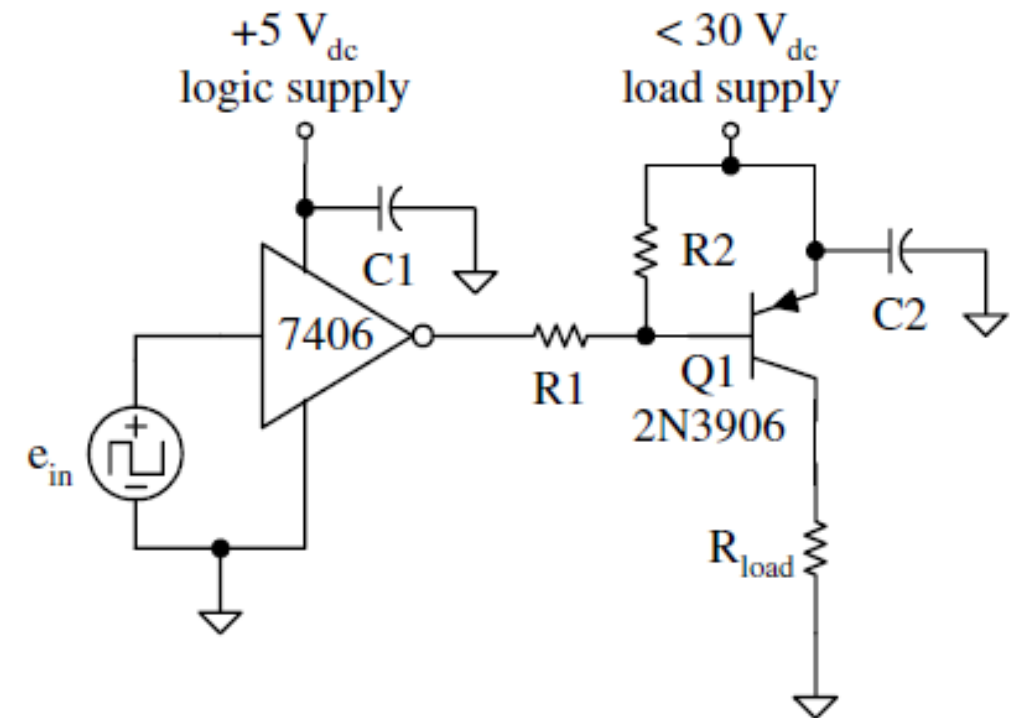- For 100 mA peak of load current, or if switch speed is not critical, pnp BJT or Darlington pair can be used
- $i_{load} = ?$
- $i_{base} = ?$



Reference

Power Electronics, Principles and Applications
J. Michael Jacob

Power Electronics
Ned Mohan