

National University of Computer and Emerging Sciences, Lahore Campus



Course:	Electronics Circuit Design	Course Code:	EE2001
Program:	BS (Electrical Engineering)	Semester:	Fall 2024
Duration:		Total Marks:	20
Submit On:	22 - Oct - 2024	Weight	5
Section:	BEE - 5A	Page(s):	01
Exam:	Assignment - 02	CLO:	02

Question 1:


Design a circuit that implements the following function of PID controller using operational-amplifiers. Initiate your design from the two analog input signals, V_{ref} and V_{sense} , and onwards build the rest of the circuit that yields the following output. Use 50 kΩ resistors in the feedback path.

$$V_o = 12(V_e) + 300 \left(\int V_e dt \right) + 0.5 \left(\frac{dV_e}{dt} \right)$$

such that, $V_e = V_{ref} - V_{sensor}$

Question 2:

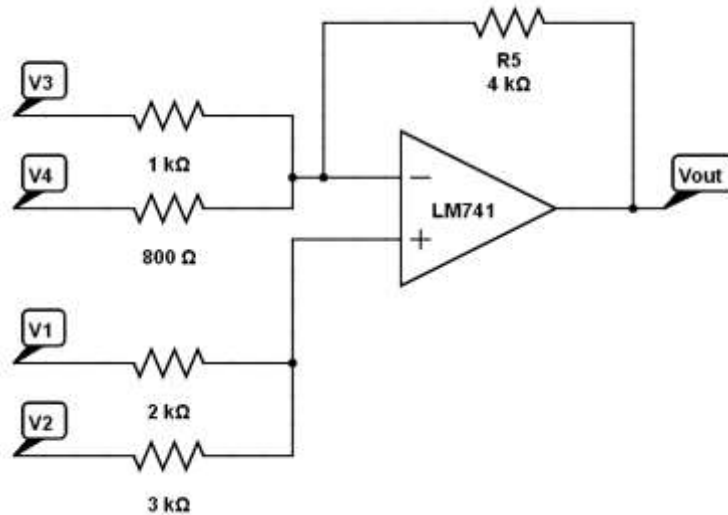a. Analyze the following operational amplifier circuit and find the expression of V_{out} .



b. Implement the function computed in part (a) using the weighted summing amplifier.

ECD

A02

Owais Rao

22L-7638

BEE-SA

Q. No. 1

$$V_o = 12(V_e) + 300 \left(\int V_e dt \right) + 0.5 \left(\frac{dV_e}{dt} \right)$$

$$\Rightarrow V_e = V_{ref} - V_{sensor}$$

$$\Rightarrow R_f = 50 k\Omega$$

Proportional control:-

For non-inverting configuration,

$$V_o = \left(1 + \frac{R_f}{R_i} \right) V_i \Rightarrow V_o = G_p V_e$$

As G_p (gain of Proportional control) = 12


$$\Rightarrow 12 = 1 + \frac{R_f}{R_i}$$

$$12 - 1 = \frac{50k}{R_i}$$

$$R_i = \frac{50k}{11}$$

$$R_i = 4.55 k\Omega$$

Proportional Control Circuit:-

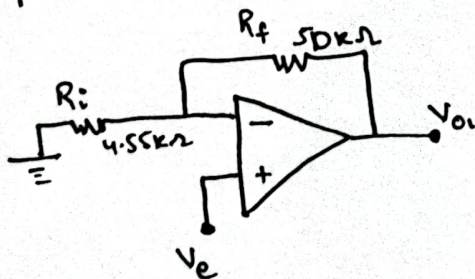

Integral Control:-

The output voltage of an integrator is given by

$$V_o = -\frac{1}{RC} \int V_i dt \Rightarrow V_{o2} = -G_I \int V_e dt$$


As G_I (gain of Integral Control) = 300

$$\Rightarrow 300 = \frac{1}{RC}$$

$$C = \frac{1}{300(50k\Omega)}$$

$$C = 66.67 \text{ nF}$$

Integral Control Circuit:-

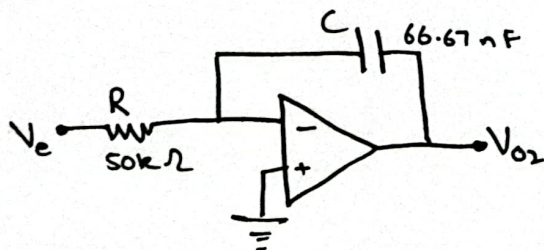

Derivative Control:-

The output voltage of a differentiator is given by

$$V_o = -RC \frac{dV_i}{dt} \Rightarrow V_{o3} = -G_D \frac{dV_e}{dt}$$


As G_D (gain of ~~der~~ derivative control) = 0.5

$$\Rightarrow 0.5 = RC$$

$$C = \frac{0.5}{50k}$$

$$C = 10 \mu\text{F}$$

Derivative Control Circuit:-

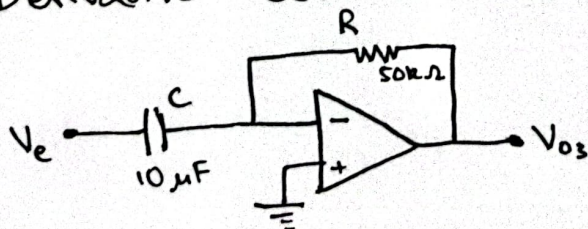

For $V_e = V_{ref} - V_{sensor}$, using a single op-amp difference amplifier


$$V_o = \frac{R_f}{R_i} (V_2 - V_1) \Rightarrow V_e = G (V_{ref} - V_{sensor})$$

As G should be $\Rightarrow 1$


$$\Rightarrow 1 = \frac{R_f}{R_i}$$

$$R_i = \frac{50k}{1}$$

$$R_i = 50k\Omega$$

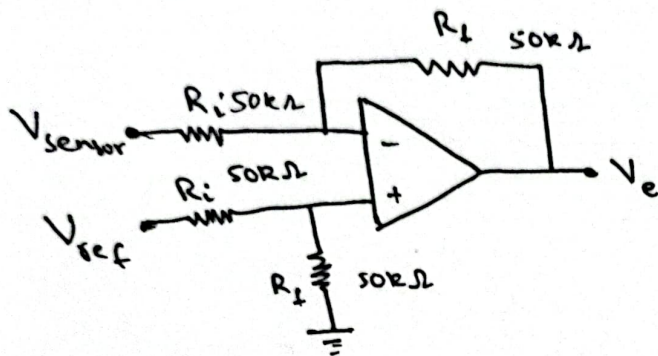

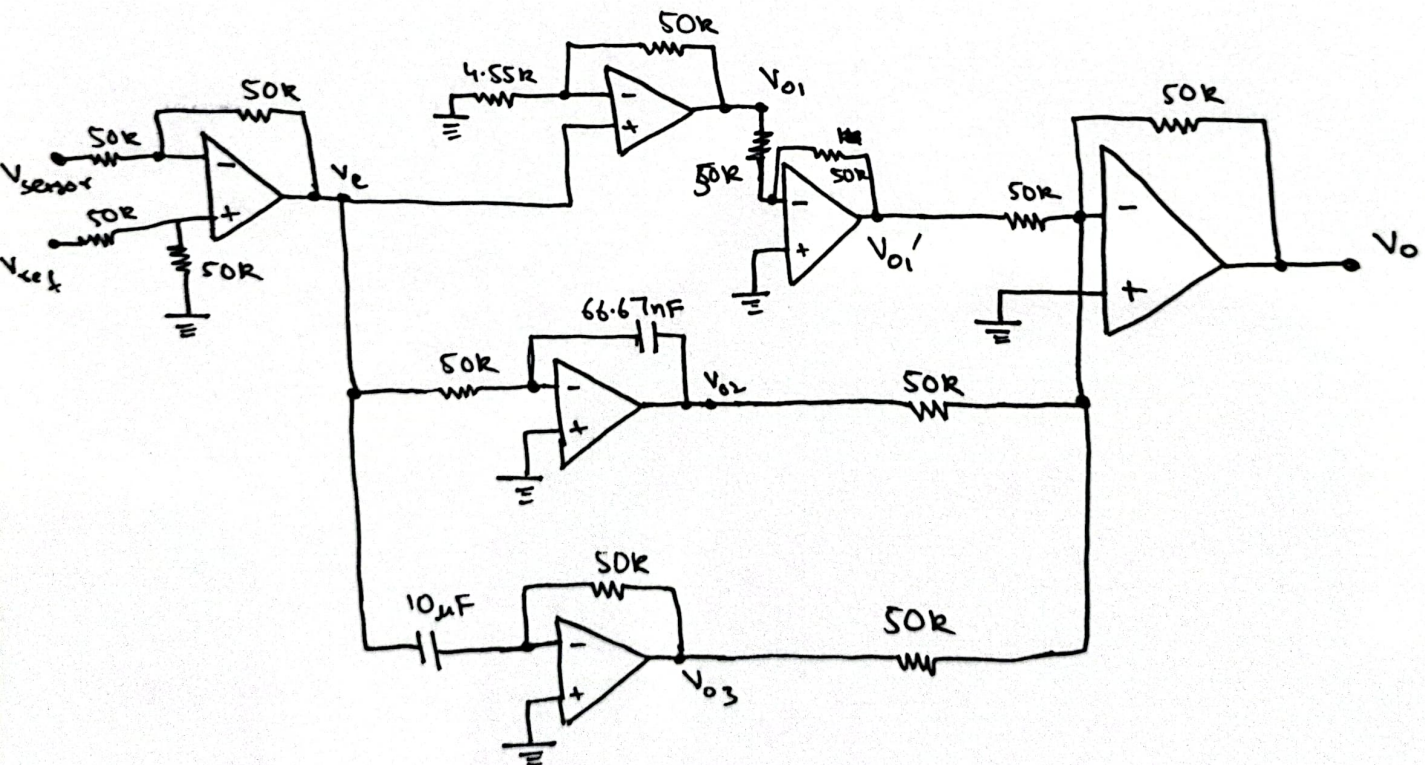Combining outputs of individual op-amps using a summing amplifier of gain $G=1$



Hence, the output voltage is


$$V_o = -V_{o1} + V_{o2} + V_{o3}$$

$$V_o = -(-12V_e) - (-300 \int V_e dt) - (-0.5 \frac{dV_e}{dt})$$

$$= 12V_e + 300 \int V_e dt + 0.5 \frac{dV_e}{dt}$$

$$\underline{0.1 \sim 0.2}$$

(a)

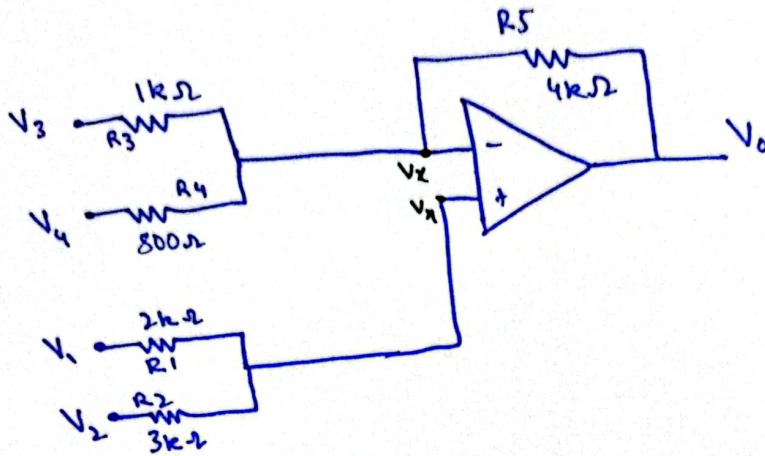

$$\Rightarrow V_+ = V_- = V_x \quad (\text{internal short circuit})$$

$$\Rightarrow \frac{V_x - V_1}{2k} + \frac{V_x - V_2}{3k} = 0$$

$$3kV_x - 3kV_1 + 2kV_x - 2kV_2 = 0$$

$$5kV_x - 3kV_1 - 2kV_2 = 0$$

$$5V_x = (3V_1 + 2V_2)$$

$$5V_x = 3V_1 + 2V_2$$

$$V_x = \frac{1}{5} (3V_1 + 2V_2) \quad \text{--- ①}$$

$$\Rightarrow \frac{V_x - V_3}{1k} + \frac{V_x - V_4}{800} + \frac{V_x - V_0}{4k} = 0$$

$$\frac{V_x}{1k} - \frac{V_3}{1k} + \frac{V_x}{800} - \frac{V_4}{800} + \frac{V_x}{4k} - \frac{V_0}{4k} = 0$$

$$\frac{V_x}{400} = \frac{V_3}{1k} + \frac{V_4}{800} + \frac{V_0}{4k}$$

$$V_x = 0.4V_3 + 0.5V_4 + 0.1V_0 \quad \text{--- ②}$$

From ① & ②


$$\frac{1}{5} (3V_1 + 2V_2) = 0.4V_3 + 0.5V_4 + 0.1V_0$$

$$0.1V_0 = 0.6V_1 + 0.4V_2 - 0.4V_3 - 0.5V_4$$

$$V_0 = 6V_1 + 4V_2 - 4V_3 - 5V_4$$

(b)

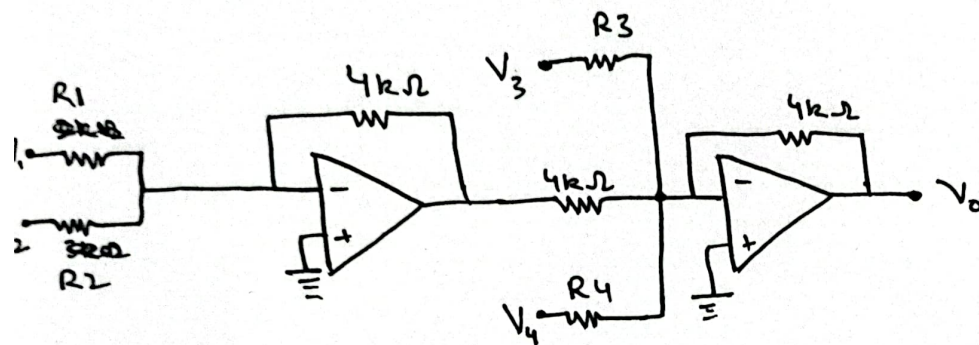Implementing V_0 using a weighted summing amplifier,



For V_1 ,

$$\frac{R_f}{R_1} = 6$$

$$\frac{4k}{6} = R_1$$

$$R_1 = 666.67\Omega$$

For V_2 ,

$$\frac{R_f}{R_2} = 4$$

$$\frac{4k}{4} = R_2$$

$$R_2 = 1k\Omega$$

For V_3 ,

$$\frac{R_f}{R_3} = 4$$

$$\frac{4k}{4} = R_3$$

$$R_3 = 1k\Omega$$

For V_4 ,

$$\frac{R_f}{R_4} = 5$$

$$\frac{4k}{5} = R_4$$

$$R_4 = 800\Omega$$

