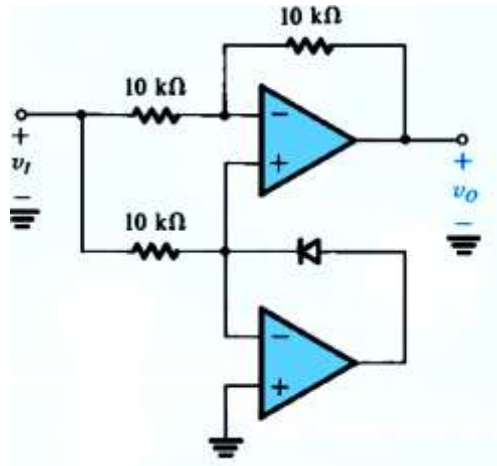


EE2001 –Electronic Circuit Design
Assignment # 3 (Total = 30)
CLO-04

Due Date: 28th Nov, 2024

Question 1

Sketch the transfer characteristics of the following circuit.



Question 2

- For an astable multi-vibrator using 555 timer IC with a $C = 1.0 \text{ nF}$ capacitor, find the values of R_A and R_B that results in an oscillation frequency of 100 kHz and a duty cycle of 75%. Draw the circuit diagram as well.
- What is the duty cycle and oscillation frequency of the circuit designed in part (a), that is R_A , R_B and C are the same as in (a); if the a diode is connected in parallel with R_B to bypass it during the charging phase.


Question 3

A pressure sensor outputs a voltage signal P_s ranging from -2.4 to 1.1 V. For interface to an analog-to-digital converter, this signal is normalized to signal P_m that ranges between 0 to 2.5 V. Find the transfer function equation of P_s to P_m , and hence develop the required signal conversion circuit with high-input impedance.

ECD
A03

Oweis Rao
22L-7638
BEE-SA

Q.1

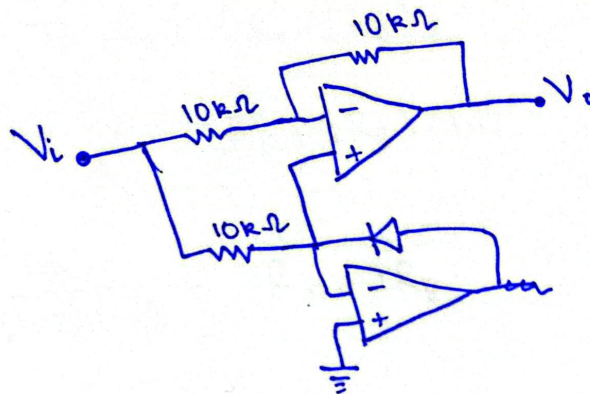


When $V_i < -0.7V$,
Diode is reverse biased

When $-0.7V \leq V_i \leq 0.7V$

The input voltage is less than the diode voltage ($0.7V$), which restricts the output voltage.

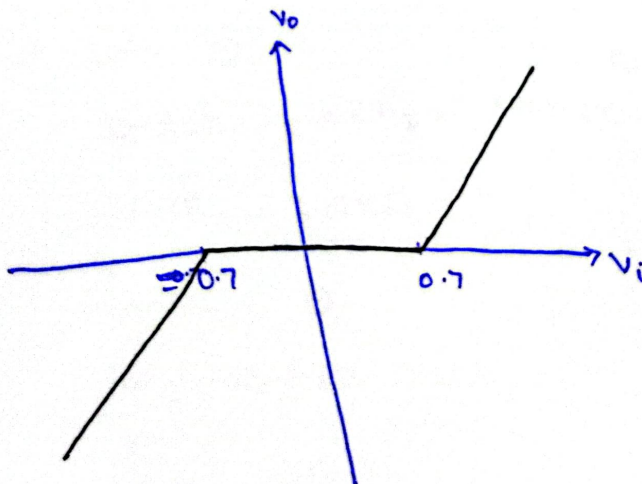When $V_i > 0.7V$,
Diode is forward biased



Q. No. 2

(a)

A-stable MVB using 555 timer

$$C = 1nF, f = 100kHz, D = 75\%$$

$$\Rightarrow T = \frac{1}{f} = \frac{1}{100k} = 10\mu s$$

$$\Rightarrow T = \ln 2 (R_A + 2R_B) C$$

$$\frac{10\mu}{\ln 2} = (R_A + 2R_B) (1n)$$

$$\frac{10\mu}{(\ln 2) (1n)} = R_A + 2R_B$$

$$R_A + 2R_B = 14.43k \quad \text{--- (1)}$$

$$\Rightarrow D = \frac{R_A + R_B}{R_A + 2R_B}$$

$$75\% = \frac{R_A + R_B}{14.43k}$$

$$10.82k = R_A + R_B$$

$$R_A = 10.82k - R_B \quad \text{--- (2)}$$

Put in (1)


$$10.82k - R_B + 2R_B = 14.43k$$

$$R_B = 3.61k\Omega$$

Put in (2)

$$R_A = 10.82k - 3.61k$$

$$R_A = 7.21k\Omega$$

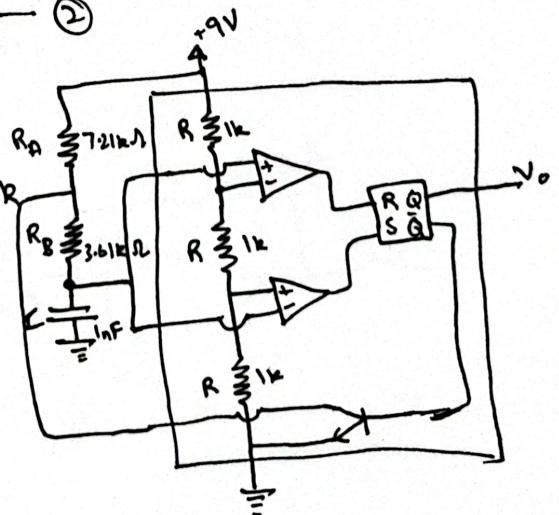

(b)

When a diode is connected parallel to R_B , the charging cycle depends on R_A only while discharging cycle depends on R_B .

$$\Rightarrow D = \frac{T_H}{T} = \frac{T_H}{T_H + T_L} = \frac{R_A}{R_A + R_B}$$

$$= \frac{7.21k}{7.21k + 3.61k}$$


$$D = 66.6\%$$

$$\Rightarrow T = (\ln 2)(R_A + R_B)C$$

$$\frac{1}{f} = (\ln 2)(7.21k + 3.61k)(1\mu)$$

$$\frac{1}{7.499 \times 10^{-6}} = f$$

$$f = 133.35 \text{ kHz}$$

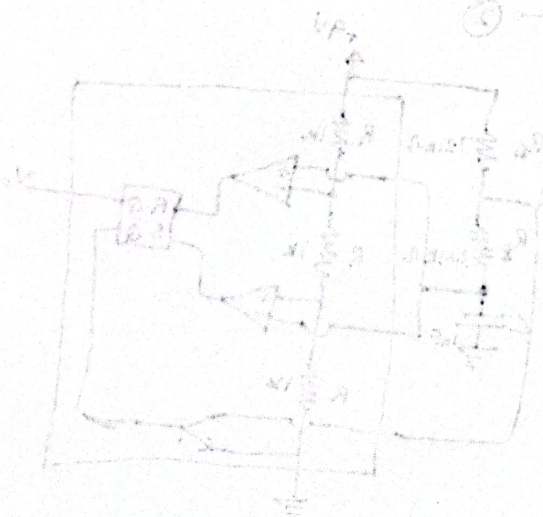

Q.3

$$P_s: -2.4V \text{ to } 1.1V$$

$$P_m: 0V \text{ to } 2.5V$$

$$As \quad y = mx + c$$

$$Put \quad y = P_m \quad (\text{Output})$$

$$\text{and} \quad x = P_s \quad (\text{Input})$$

$$\text{Slope: } m = \frac{\text{Output range}}{\text{Input range}}$$

$$= \frac{2.5 - 0}{1.1 - (-2.4)} = \frac{2.5}{3.5}$$

$$= 0.714$$

$$\Rightarrow P_m = 0.714 P_s + c$$

For c (offset), Put boundary points i.e. $P_m = 0$ & $P_s = -2.4$

$$0 = 0.714(-2.4) + c$$

$$c = 1.7136$$

Hence, the transfer function is

$$P_m = 0.714 P_s + 1.7136$$

$$\text{For } G = 0.714,$$

Using inverting configuration,

$$G = -\frac{R_2}{R_1}$$


$$0.714 = -\frac{R_2}{R_1}$$

$$\text{Let } R_1 = 1k\Omega,$$


$$(0.714)(1k) = R_2$$

$$R_2 = 714\Omega$$

$$R_2 = 0.714k\Omega$$

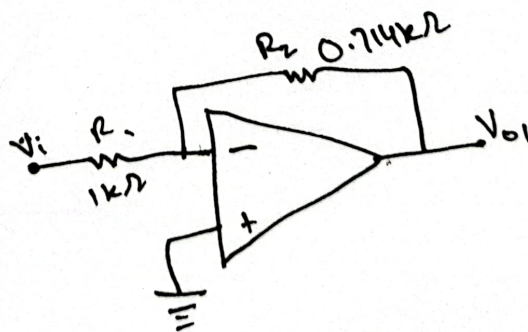

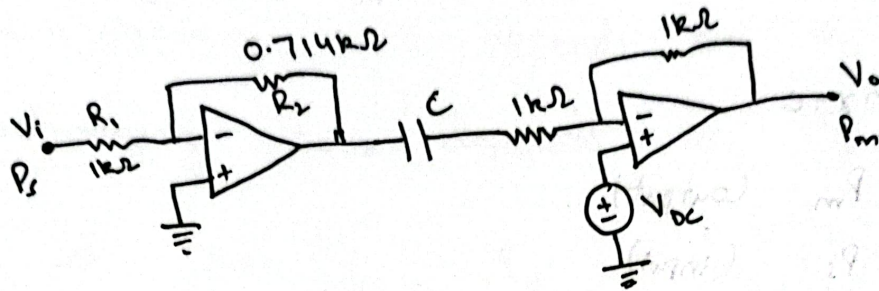To add offset 1.7136, using summing amplifier configuration with a capacitor.



Here $V_i = P_s$, $V_o = P_m$, $V_{DC} = 1.7136V$

$$P_m = 0.714P_s + 1.7136$$